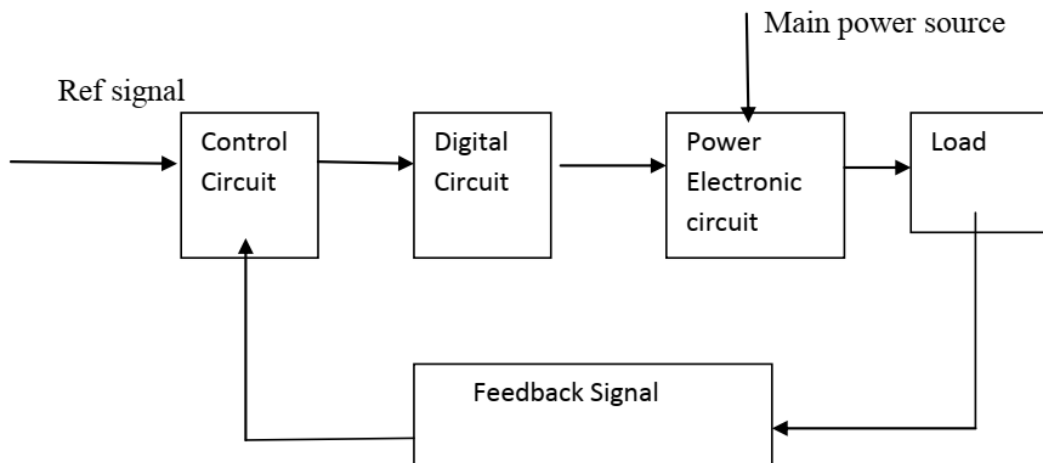


UNIT-1

POWER SWITCHING DEVICES

POWER ELECTRONICS

The control of electric motor drives requires control of electric power. Power electronics have eased the concept of power control. Power electronics signifies the word power electronics and control or we can say the electronic that deal with power equipment for power control.




Power electronics based on the switching of power semiconductor devices. With the development of power semiconductor technology, the power handling capabilities and switching speed of power devices have been improved tremendously.


SCOPE AND APPLICATION

Power electronics systems are known for their reliability and precise controllability. That's why the scope of power electronics is huge. Whether it be Power Systems, Electrical Machines, Signal Processing, or Industrial applications, the role of power electronics is immense.

Power electronics revolutionized the way electrical systems worked and were controlled. One of the major issues that the power electronic-based systems addressed was improved efficiency with higher accuracy in the output of the applications. Earlier, we used to achieve one by sacrificing the other but power electronics changed the situation. Let's understand the working of a power electronics-based system. Let's understand the working of a power electronics-based system.

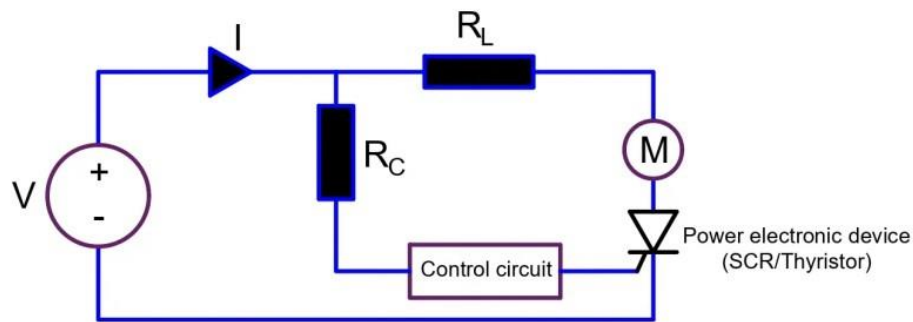

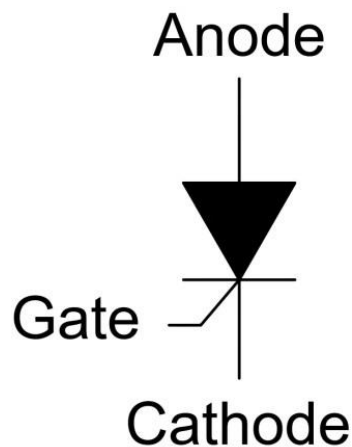The circuit diagram shown above is that of a motor control system using SCR. SCR stands for Silicon Controlled Rectifier and is also known as Thyristor. It has three terminals – Anode, Cathode and Gate. It is similar to that of a diode except that it has an extra terminal called



Just like a Diode, an SCR is forward-biased when the Anode is connected to the positive terminal and the cathode is connected to the negative terminal of a voltage source. However, it can't conduct unless the gate terminal is supplied with a voltage source. Once the gate terminal is active, the switch (SCR) behaves ideally like a short circuit and allows the normal flow of electric current.

Thus, the gate terminal acts like a control terminal for the switching device i.e, the SCR. If the gate terminal voltage is low, the switch acts as an open circuit and stops the current to flow whereas if the gate voltage is high, it allows the normal flow of current through the connected circuit. Thus, instead of cutting off the power source to the [motor](#), we can turn the gate supply ON/OFF to start and stop the motor respectively. voltage drop across the rheostat, the power loss in SCR-controlled speed control is very low.

Application of Power Electronics

- A whole lot of power electronics applications that we use in our daily life, such as a fan regulator, air-conditioning, induction cooking, light dimmer, emergency lights, vacuum cleaners, personal computers, UPS, battery charges, etc., are the major applications of power electronics.
- P over electronics are also extensively used in automotive applications, like hybrid electric

vehicles, trolleys, subways, forklifts, etc. A modern car itself is an example of power electronics that has some components like windshield wiper control, ignition switch, adaptive front lighting, electric power steering, interior lighting, etc. Apart from these, power electronics are widely used in ships and modern traction systems.

- Power electronics are used in industries since the industries have a huge installation of high-power motors that are controlled by power electronic drives, for instance, cement mills, rolling mills, compressor pumps, fans, elevators, textile mills, blowers, elevators, rotary kilns, etc. Some other applications consist of arc furnaces, welding, heating applications, construction machinery, excavators, emergency power systems, etc.

- Power electronics are used in defence and aerospace to supply power to aircraft, advance control in missiles, satellites, unmanned vehicles, space shuttles, and several other equipment of defence.


- Power electronics are used in the generation of renewable energy, such as solar, wind etc., which needs storage systems and conversion systems, and power conditioning systems in order to become usable.

:

TYPES OF POWER CONVERTERS:-


Static Power converters execute power conversion quite efficiently. Power electronic switches have solid-state devices with components like inductors and capacitors. Generally, inductors and capacitors exhibit negligible power loss characteristics in comparison to resistors.

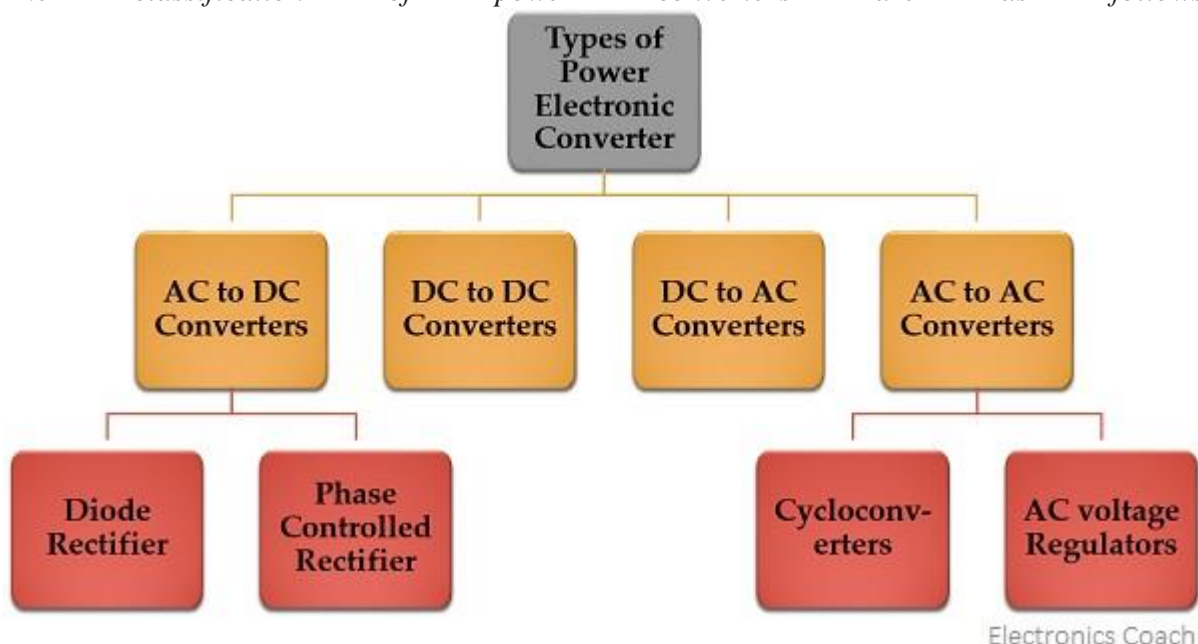The classification of power converters are as follows:



AC to DC Converters

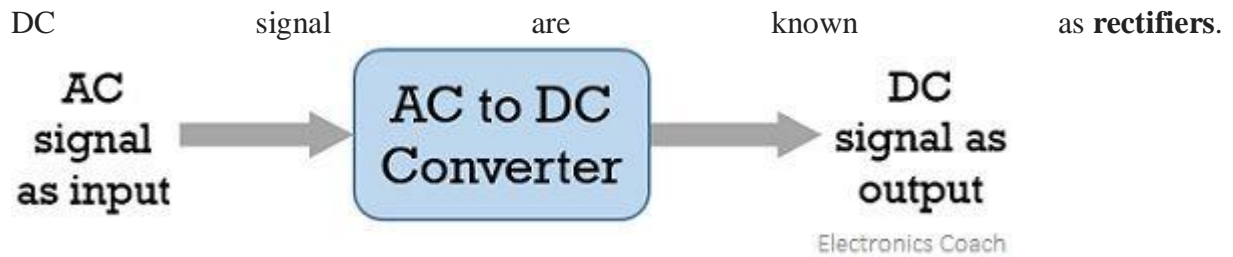A type of converter that changes input AC signal into a DC is known as AC to DC converter. We have already learned in basic electronics that the devices that convert the AC signal into




AC to DC Converter is further classified as:

Diode Rectifiers: This rectifier circuit changes applied ac input voltage into a fixed dc voltage. Either a single-phase or three-phase ac signal is applied at the input. These are mainly used in electric traction and in electrochemical processes like electroplating along with in battery charging and power supply. These are also used in welding and [UPS](#) related services.

Phase Controlled Rectifiers: Unlike diode rectifiers, phase-controlled rectifiers are designed to convert a fixed value of ac signal voltage into a variable dc voltage. Here line voltage operates the rectifier hence these are sometimes known as line commutated ac to dc converters. Similar to diode rectifiers, here also the applied ac signal can be a single-phase or three-phase ac signal. Its major applications are in dc drives, HVDC systems, compensators, metallurgical and chemical industries as well as in excitation systems for synchronous machines.

DC to DC Converters

The converters that convert the dc signal of fixed frequency present at the input into a variable dc signal at the output are also known as **choppers**. Here the achieved output dc voltage may have a different amplitude than the source voltage. Generally, power transistors, MOSFETs, and thyristors are the semiconductor devices used for their fabrication. The output is controlled by a low power signal that controls these semiconductor devices from a control unit.

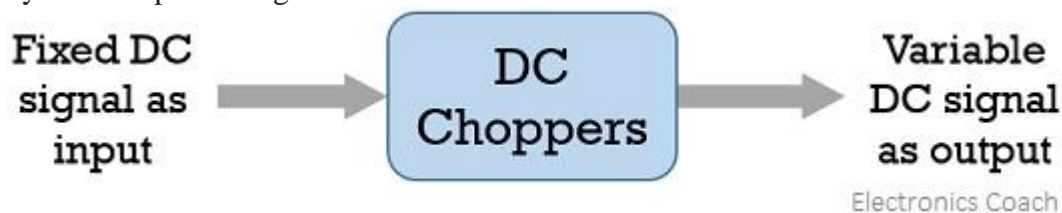


Here forced commutation is required to turn off the semiconductor device. Generally, in low power circuits power transistors are used while in high power circuits thyristors are used.

Choppers are classified on the basis of the type of commutation applied to them and on the basis of the direction of power flow. Some major uses of choppers are in dc drives, SMPS, subway cars, electric traction, trolley trucks, vehicles powered by battery, etc.

DC to AC Converters

The devices that are designed to convert the dc signal into ac signal are known as **inverters**. The applied input is a fixed dc voltage that can be obtained from batteries but the output obtained is variable ac voltage. The voltage and frequency of the signal obtained are of variable nature. Here the semiconductor device i.e., the thyristor is turned off by using either line, load, or forced commutation.

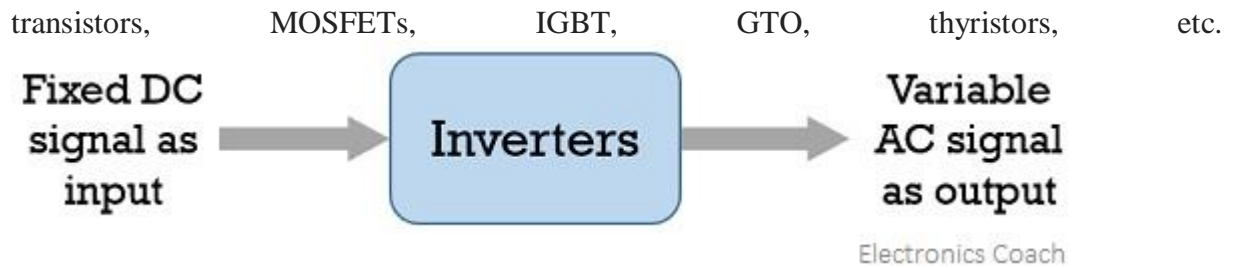Thus, it can be said that by the use of inverters, a fixed dc voltage is changed into an ac voltage of variable frequency. Generally, the semiconductor devices used for its fabrication are power




Inverters mainly find applications in induction motor and synchronous motor drives along with UPS, aircraft, and space power supplies. In high voltage dc transmission system, induction heating supplies as well as low power systems of mobile nature like flashlight discharge system in photography camera to very high power industrial system.

Like choppers, in inverters also conventional thyristors are used in high power applications and power transistors are used in low power applications.

AC to AC Converters

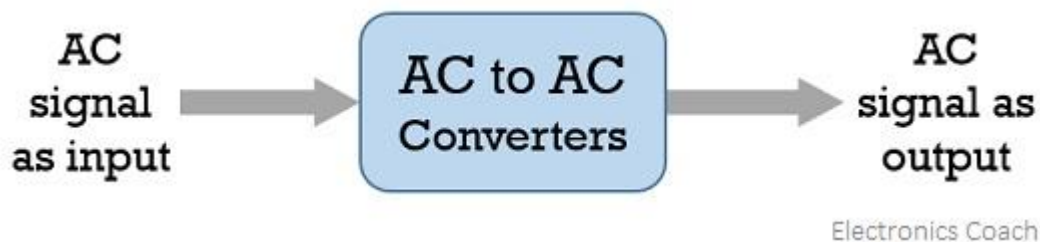An ac to ac converter is designed to change the ac signal of fixed frequency into a variable ac output voltage.



There are two classifications of ac to ac converters which are as follows:

Cycloconverters: A cycloconverter is a device used for changing ac supply of fixed voltage and single frequency into an ac output voltage of variable voltage as well as different frequency. However, here the obtained variable ac signal frequency is lower than the frequency of the applied ac input signal. It adopts single-stage conversion. Generally, line commutation is mostly used in cycloconverters however forced or load commutated cycloconverters are also used in various applications.

These mainly find applications in slow-speed large AC traction drives such as a rotary kiln, multi MW ac motor drives, etc.

AC Voltage Controllers (AC voltage regulators): The converters designed to change the applied ac signal of fixed voltage into a variable ac voltage signal of the same frequency as that of input. For the operation of these controllers, two thyristors in an antiparallel arrangement are used. Line commutation is used for turning off both the devices. It offers the controlling of the output voltage by changing the firing angle delay.

The major applications of ac voltage controllers are in lighting control, electronic tap changers, speed control of large fans and pumps as well.

POWER SEMICONDUCTOR SWITCHES&THEIR V-I CHARACTERISTICS:-

POWER DIODE:-


A power diode is a type of diode that is commonly used in power electronics circuits. Just like a regular diode, a power diode has two-terminals and conducts current in one direction. A power diode varies in construction from a standard diode to enable this higher current rating.

To better understand how a power diode differs from a regular diode, let's revisit how a standard diode works.

Diodes are the simplest semiconductor device having only two layers, two terminals, and one junction.


The ordinary signal diodes have a junction formed by p type semiconductor and n type semiconductor, the lead joining p-type is called the anode and the other side lead joining the n-type is called the cathode.

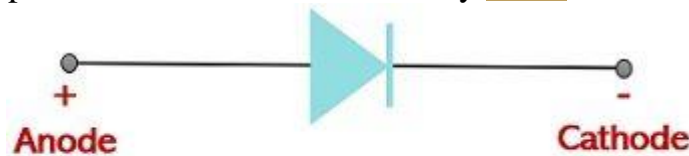The figure below depicts the structure of an ordinary diode and its symbol.



Symbol of Power Diode

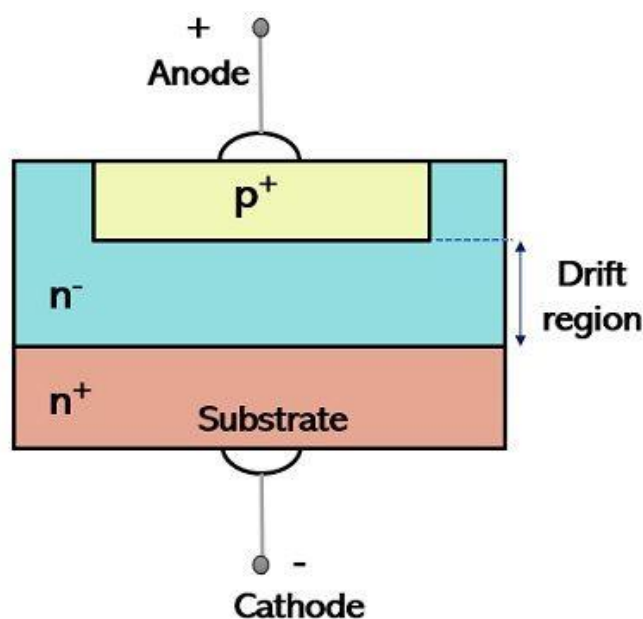
Power diodes are also similar to regular diodes, although they vary slightly in their construction. In regular diodes (also known as “signal diode”), the doping level of both P and N sides is the same and hence we get a PN junction, but in power diodes, we have a junction formed between a heavily doped P⁺ and a lightly doped N⁻ the layer which is epitaxially grown on a heavily doped N⁺ layer.



Structure of Power Diode

V-I Characteristics

Initially with no supply voltage forward current is 0 but as the supply input increases, and reaches the threshold value (of about 0.7 V), a small amount of forward current flows through the device. Once the threshold value is surpassed, a considerable increase in diode current (at 1V) is noticed as it starts conduction. Here linear rise in forward current is noticed when voltage increases beyond the threshold.

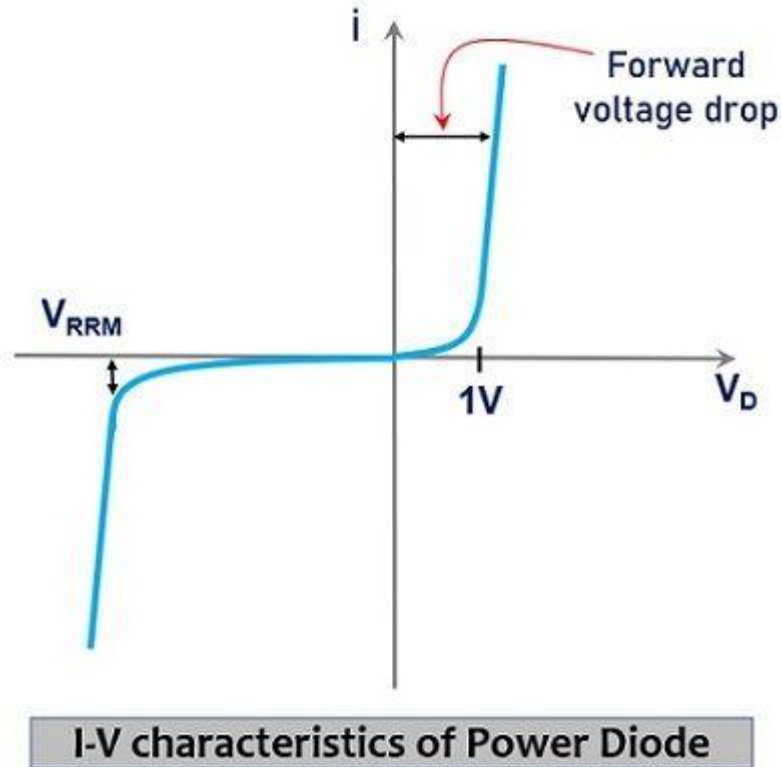

POWER BJT:-

Bipolar Junction Transistor (BJT) is a three terminal, three layer, two junction semiconductor device. Emitter(E), Base(B) and Collector(C) are the three terminals of the device.

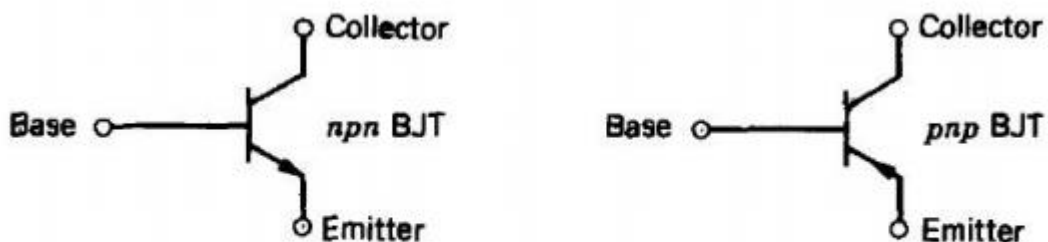


Figure 5.17 Symbol of power BJT

Symbol: The symbol of the Power BJT is same as signal level transistor.

Structure

The construction of the Power Transistor is different from the signal transistor as shown in the following figure. The n- layer is added in the power BJT which is known as drift region.

- A Power BJT has a four layer structure of alternating P and N type doping as shown in above npn transistor.
-
- It has three terminals labeled as Collector, Base, Emitter.
-
- In most of Power Electronic applications, the Power Transistor works in Common Emitter configuration.
-
- ie, Base is the input terminal, the Collector is the output terminal and the Emitter is common between input and output.
-
- In power switches npn transistors are most widely used than pnp transistors.
-
- The thickness of the drift region determines the breakdown voltage of the Power transistor.

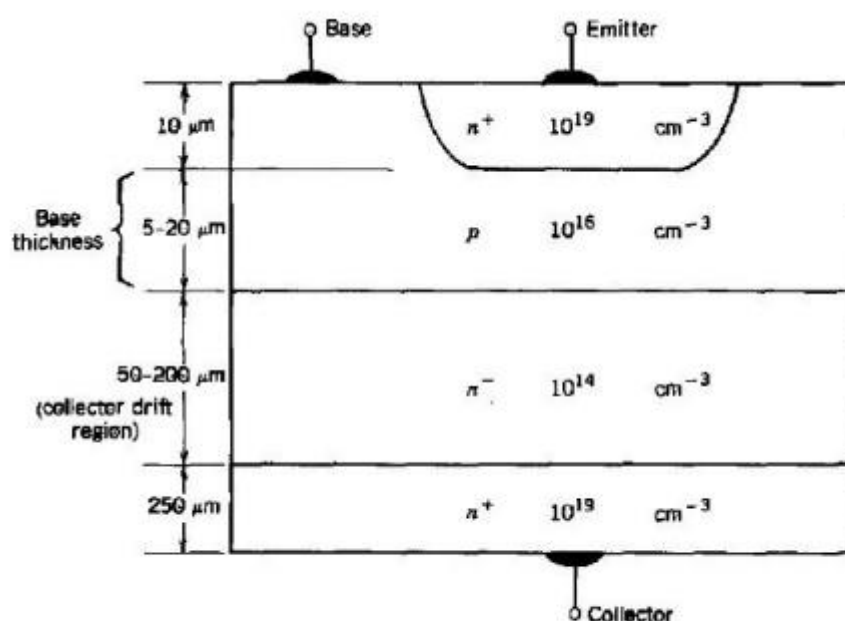


Figure 5.18 Structure of Power BJT

Figure 5.18 Structure of Power BJT

- The characteristics of the device is determined by the doping level in each of the layers and the thickness of the layers.

VI Characteristics

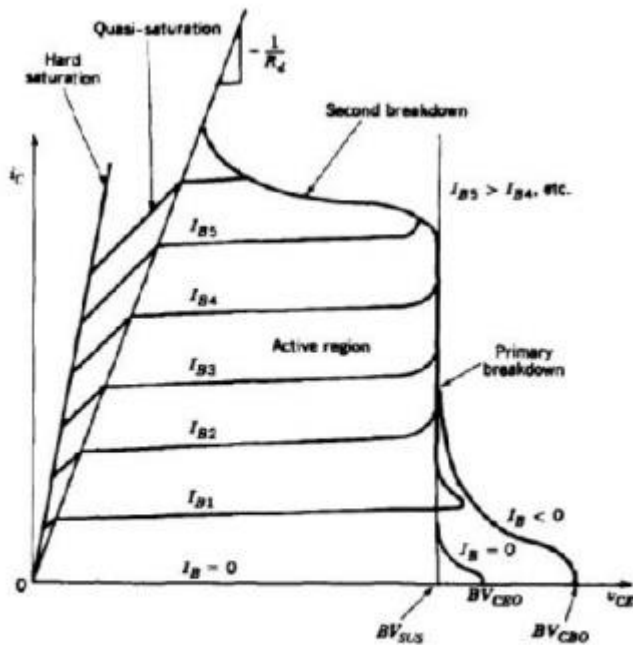


Figure 5.18 VI Characteristics Power BJT

Figure 5.18 VI Characteristics Power BJT


- The VI characteristics of the Power BJT is different from signal level transistor.
-
- The major differences are Quasi saturation region & secondary breakdown region.
-
- The Quasi saturation region is available only in Power transistor characteristic not in signal transistors. It is because of the lightly doped collector drift region present in Power BJT.
-

□ The primary breakdown is similar to the signal transistor's avalanche breakdown

□ Operation of device at primary and secondary breakdown regions should be avoided as it will lead to the catastrophic failure of the device.


Silicon Controlled Rectifier

A Silicon Controlled Rectifier is a 3 terminal and 4 layer semiconductor current controlling device. It is mainly used in the devices for the control of high power. Silicon controlled rectifier is also sometimes referred to as SCR diode, 4-layer diode, 4-layer device, or Thyristor. It is made up of a silicon material which controls high power and converts high AC current into DC current (rectification). Hence, it is named as silicon controlled rectifier.

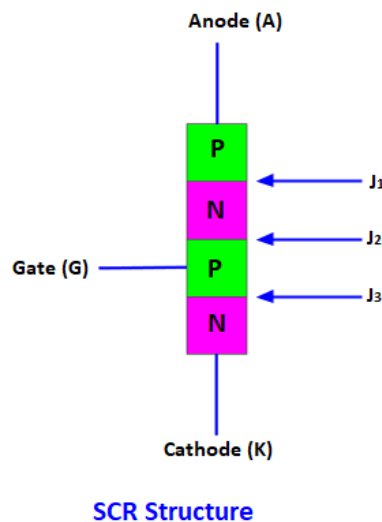

Silicon Controlled Rectifier Symbol

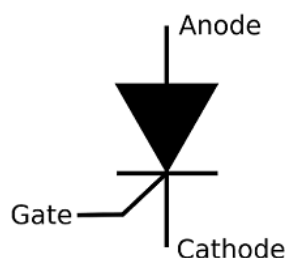The schematic symbol of a silicon controlled rectifier is shown in the below figure. A SCR diode consists of three terminals namely anode (A), cathode (K), Gate (G). The diode arrow represents the direction of [conventional current](#).



Construction of Silicon Controlled Rectifier

A silicon controlled rectifier is made up of 4 semiconductor layers of alternating P and N type materials, which forms NPNP or PNPN structures. It has three P-N junctions namely J₁, J₂, J₃ with three terminals attached to the semiconductors materials namely anode (A), cathode (K), and gate (G). Anode is a positively charged electrode through which the conventional current enters into an electrical device, cathode is a negatively charged electrode through which the conventional current leaves an electrical device, gate is a terminal that controls the flow of current between anode and cathode. The gate terminal is also sometimes referred to as control terminal.

The anode terminal of SCR diode is connected to the first p-type material of a PNPN structure, cathode terminal is connected to the last n-type material, and gate terminal is connected to the second p-type material of a PNPN structure which is nearest to the cathode.

In silicon controlled rectifier, silicon is used as an [intrinsic semiconductor](#). When pentavalent impurities are added to this intrinsic semiconductor, an N-type semiconductor is formed. When trivalent impurities are added to an intrinsic semiconductor, a p-type semiconductor is formed.

When 4 semiconductor layers of alternating P and N type materials are placed one over another, three junctions are formed in PNPN structure. In a PNPN structure, the junction J_1 is formed between the first P-N layer, the junction J_2 is formed between the N-P layer and the junction J_3 is formed between the last P-N layer. The doping of PNPN structure is depends on the application of SCR diode.

V-I Characteristics of SCR


The V-I characteristics of SCR is shown in the below figure. The horizontal line in the below figure represents the amount of voltage applied across the SCR whereas the vertical line represents the amount of current flows in the SCR.

V_A = Anode voltage, I_A = Anode current, $+V_A$ = Forward anode voltage, $+I_A$ = Forward anode current, $-V_A$ = Reverse anode voltage, $-I_A$ = Reverse anode current

The V-I characteristics of SCR is divided into three regions:

- Forward blocking region F
- Forward conduction region F
- Reverse blocking region R
- Reverse conduction region F

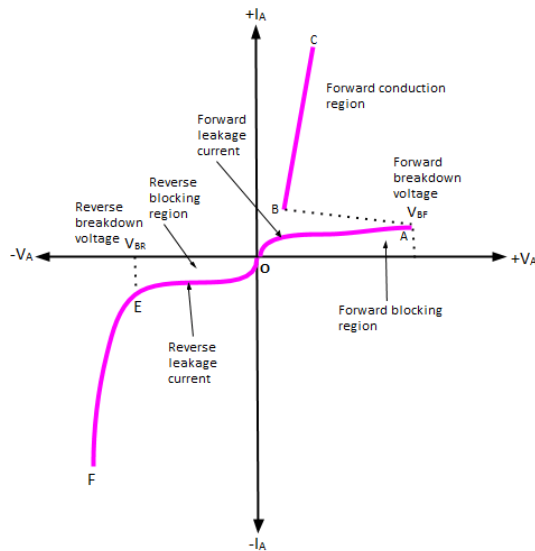In this region, the positive voltage (+) is given to anode (+), negative voltage (-) is given to cathode (-), and gate is open circuited. Due to this the junction J_1 and J_3 become forward biased while J_2 become reverse biased. Therefore, a small leakage current flows from anode to cathode terminals of the SCR. This small leakage current is known as forward leakage current.



V-I Characteristics of SCR

The region OA of V-I characteristics is known as forward blocking region in which the SCR does not conduct electric current.

- Forward Conduction region F

If the forward bias voltage applied between anode and cathode is increased beyond the breakdown voltage, the minority carriers (free electrons in anode and holes in cathode) gain a large amount of energy and are accelerated to greater velocities. This high speed minority carrier collides with other atoms and generates more charge carriers. Likewise, many collisions happen with atoms. Due to this, millions of charge carriers are generated. As a result, depletion region breakdown occurs at junction J_2 and current starts flowing through the SCR. So the SCR will be in On state. The current flow in the SCR increases rapidly after junction breakdown occurs.

The voltage at which the junction J_2 gets broken when the gate is open is called forward breakdown voltage (V_{BF}).

The region BC of the V-I characteristics is called conduction region. In this region, the current flowing from anode to cathode increases rapidly. The region AB indicates that as soon as the device becomes on, the voltage across the SCR drops to some volts.

- Reverse Blocking Region R

In this region, the negative voltage (-) is given to anode (+), positive voltage (+) is given to cathode (-), and gate is open circuited. In this case, the junction J_1 and junction J_3 are reverse biased whereas the junction J_2 becomes forward biased.


As the junctions J_1 and junction J_3 are reverse biased, no current flows through the SCR circuit. But a small leakage current flows due to drift of charge carriers in the forward biased junction J_2 . This small leakage current is called reverse leakage current. This small leakage current is not sufficient to turn on the SCR.

If the reverse bias voltage applied between anode and cathode is increased beyond the reverse breakdown voltage (V_{BR}), an avalanche breakdown occurs. As a result, the current increases rapidly. The region EF is called reverse avalanche region. This rapid increase in current may damage the SCR device.

POWER MOSFET

One kind of MOSFET which handles high levels of power is known as Power MOSFET. As compared to normal MOSFETs in the less voltage range, these MOSFETs work much better by exhibiting high speed of switching. Its operating principle is the same as general MOSFETs.

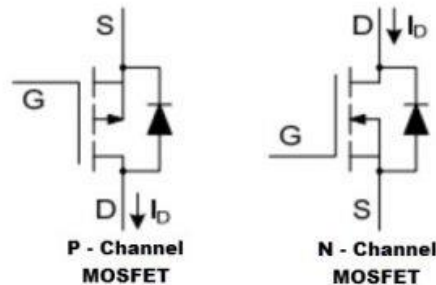The most widely used power MOSFETs are p-channel Enhancement-mode, n-channel Enhancement-mode or n-channel depletion mode & p-channel depletion mode. The power MOSFET frequency is high like up to 100 kiloHertz. The **power MOSFET symbol** is shown below.




These are three-terminal silicon devices that work through applying a signal toward the gate terminal so that it controls current conduction among source & drain terminals. The current conduction capacities are equal to thousands of amperes including breakdown voltage ratings from 10Volts-1000Volts.

Further, power MOSFETs are available in different structures such as VDMOS (Vertical Diffused MOS or DMOS (Double-Diffused MOS), Trench-MOS (UMOS), or VMOS, etc.

In integrated circuits, the power MOSFET used is a lateral device including source, drain & gate terminals on the pinnacle of the device where the current flowing within a lane is parallel as compared to the exterior. The VDMOS (Vertical Double diffused MOSFET) utilizes the substrate of a device like a drain terminal.

Power MOSFET Construction

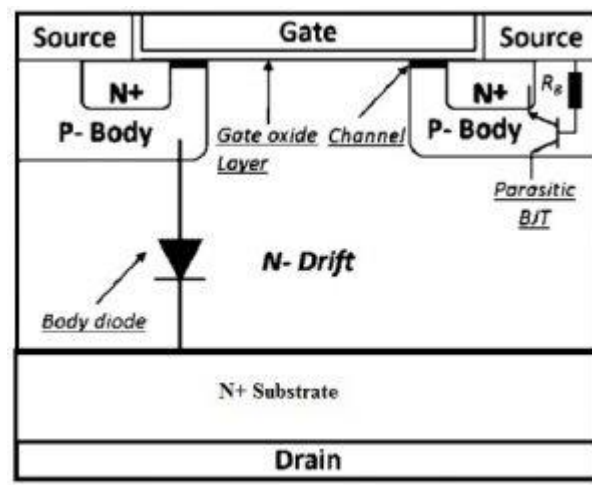Generally, the power MOSFETs are enhancement types. A drift layer is used to enhance the voltage rating for enhancement MOSFET. The structure of the power MOSFET is the vertical shape and it includes four layers. This type of structure is mainly used to decrease the region of the flow of current. So this structure will decrease the on-state resistance & on-state loss.



In the MOSFET structure, the middle layer like p-type is called as body whereas n- layer is called as the drift region. This layer is doped lightly as evaluated to the other layers like source & drain. This drift region will decide the breakdown voltage for this MOSFET. In the power MOSFET construction, both the first & last layers are n+ layers. Here the source layer is the primary layer whereas the drain layer is the last layer.

The structure of n+ p n- n+ is the n channel MOSFET in enhancement mode. But the structure of a p-channel MOSFET includes quite opposite doping shape. In this construction, the gate terminal is not connected directly to p-type as there is an oxide layer in between the metal & semiconductor which works as a dielectric layer.


It forms a metal oxide semiconductor capacitance on the MOSFET's input which is high like above 1000 pF. The oxide layer provides excellent insulating properties by offering the silicon dioxide layer to separate the terminal from the body to the gate.

Power MOSFET Characteristics

In the MOSFET structure, the middle layer like p-type is called as body whereas n- layer is called as the drift region. This layer is doped lightly as evaluated to the other layers like source & drain. This drift region will decide the breakdown voltage for this MOSFET. In the power MOSFET construction, both the first & last layers are n+ layers. Here the source layer is the primary layer whereas the drain layer is the last layer.

The structure of n+ p n- n+ is the n channel MOSFET in enhancement mode. But the structure of a p-channel MOSFET includes quite opposite doping shape. In this construction, the gate terminal is not connected directly to p-type as there is an oxide layer in between the metal & semiconductor which works as a dielectric layer.

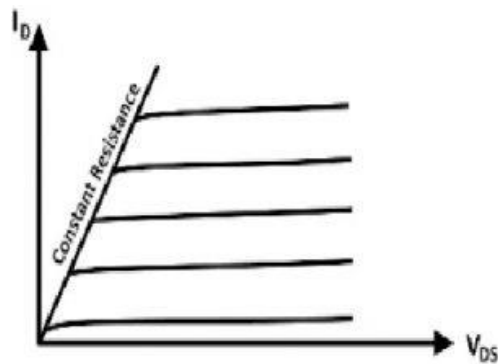It forms a metal oxide semiconductor capacitance on the MOSFET's input which is high like above 1000 pF. The oxide layer provides excellent insulating properties by offering the silicon dioxide layer to separate the terminal from the body to the gate.




Once the voltage of the gate-source is low as compared to the threshold voltage, then power MOSFET will be in the cut-off region. To keep away from a breakdown, the breakdown voltage from the drain to the source must be larger as compared to the voltage applied. So avalanche breakdown will occur.

The power MOSFET moves into the ohmic state then the power dissipation is low in this region. In the saturation state, the drain current is approximately independent of the voltage of drain to source.

It is simply dependent on the voltage of the gate to source terminals. The voltage of the gate terminal is greater as compared to the threshold voltage. The drain current will increase when the voltage from gate to source increases.

POWER IGBT

The **IGBT or Insulated Gate Bipolar Transistor** is the combination of [BJT and MOSFET](#). Its name also implies the fusion between them. “Insulated Gate” refers to the input part of MOSFET having very high input impedance. It does not draw any input current rather it operates on the voltage at its gate terminal. “Bipolar” refers to the output part of the BJT having bipolar nature where the current flow is due to both types of charge carriers. It allows it to handle very large currents and voltages using small voltage signals. This hybrid combination makes the IGBT a voltage-controlled device.

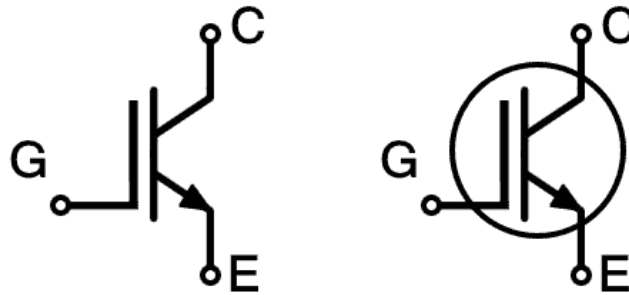


IGBT - Insulated-Gate Bipolar Transistor
Symbol

It is a four-layer PNP device having three PN junctions. It has three terminals Gate (G), Collector(C) and Emitter (E). The terminal's name also implies being taken from both transistors. Gate terminal as it is the input part, taken from MOSFET while the collector and emitter as they are the output, taken from the BJT.

Construction of IGBT

IGBT is made of four layers of semiconductor to form a PNP structure. The collector (C) electrode is attached to P layer while the emitter (E) is attached between the P and N layers. A P+ substrate is used for the construction of IGBT. An N- layer is placed on top of it to form PN junction J1. Two P regions are fabricated on top of N- layer to form PN junction J2. The P region is designed in such a way to leave a path in the middle for the gate (G) electrode. N+ regions are diffused over the P region as shown in the figure.

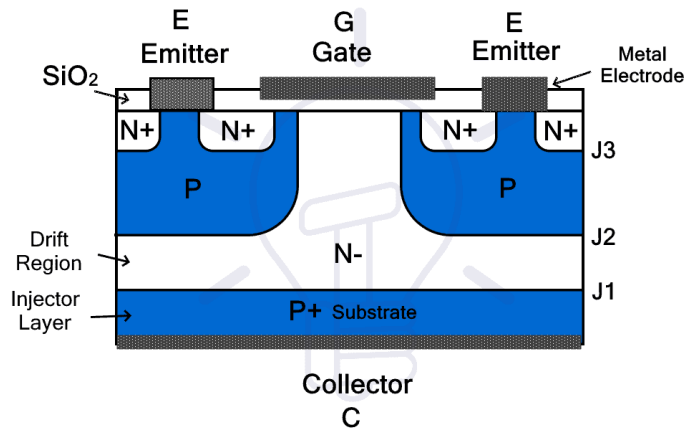

Structure of IGBT


The emitter and gate are metal electrodes. The emitter is directly attached to the N+ region while the gate is insulated using a silicon dioxide layer. The base P+ layer injects holes into the N- layer, that is why it is called an injector layer. While the N- layer is called the drift region. Its thickness is proportional to the voltage blocking capacity. The P layer above is known as the body of the IGBT.

The N- layer is designed to have a path for current flow between the emitter and collector through the channel that is created under the influence of the voltage at the gate electrode.

V-I Characteristics of IGBT

Unlike a BJT, an IGBT is a voltage-controlled device that requires only a small voltage at its gate to control the collector current. However, the gate-emitter voltage V_{GE} needs to be greater than the threshold voltage.

Transfer characteristics of the IGBT show the relation of input voltage V_{GE} to output collector current I_C . When V_{GE} is 0V, there is no I_C and the device remains switched off. When V_{GE} is slightly increased but remains below the threshold voltage V_{GET} , the device remains switched off but there is a leakage current. When V_{GE} exceeds the threshold limit, the I_C starts to increase and the device [switches](#) ON. Since it is a unidirectional device, the current only flows in one direction.

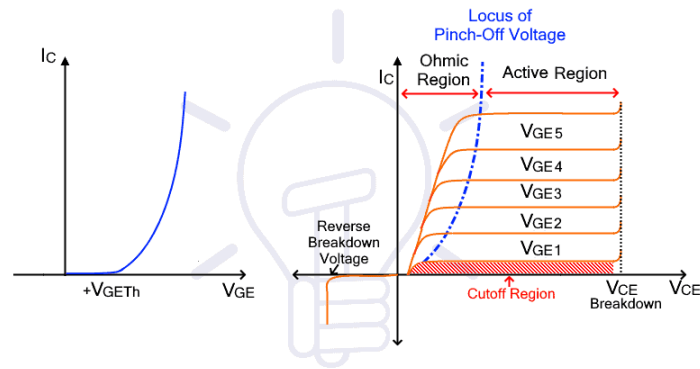

I-V Characteristics of IGBT

The given graph shows the relation between the collector current I_c and collector-emitter voltage V_{ce} at different levels of V_{ge} . At $V_{ge} < V_{GETh}$ the IGBT is in **cutoff mode** and the $I_c = 0$ at any V_{ce} . At $V_{ge} > V_{GETh}$, the IGBT goes into active mode, where the I_c increases with an increase in V_{ce} . Furthermore, for each V_{ge} where $V_{GE1} < V_{GE2} < V_{GE3}$, the I_c is different.

The reverse voltage should not exceed the reverse breakdown limit. So does the forward voltage. If they exceed their respective breakdown limit, uncontrolled current starts passing through it.

THYRISTOR RATINGS AND PROTECTION

Ratings of Thyristor

There are different ratings that are specified by the device manufacturers and they are available in SCR manuals. The designer must make use of this data in order to select a device which has adequate ratings. The specified ratings should not be exceeded in order to operate SCR reliably. In this section some of the important ratings have been discussed.

- **Latching Current (I_L):** Latching current I_L is the minimum anode current required to maintain thyristor in ON state immediately after thyristor has been Turn ON and the gate signal has been removed.
- **Holding Current (I_H):** Minimum anode current below which device stop conducting and return to its off state usually this value is very small in mA.
- **Forward Breakdown Voltage (VBO):** If anode to cathode voltage V_{AK} is increase to sufficient large value, the reverse bias junction J_2 breaks this is known as Avalanche Breakdown and corresponding voltage is called as forward breakdown voltage VBO.
- **Reverse Breakdown Voltage (VBR):** If reverse voltage is increased During reverse blocking if $I_g = 0$ then only reverse saturation current (I_s) flows until the reverse voltage reaches reverse break down voltage (VBR). At this point current starts rising sharply. Large reverse voltage and current generates excessive heat and destroys the device.
- **dv/dt:** dv/dt rating of thyristor indicates maximum rate of rise of anode voltage that will not trigger the device without any gate signal.
- **di/dt:** di/dt rating of thyristor indicates maximum rate of rise of anode to cathode current.
- **Surge Current:** It specifies the maximum allowable non repetitive current the device can withstand. The device is assumed to be operating under rated blocking voltage, forward current and junction temperature before the surge current occurs. Following the surge the device should be disconnected from the circuit and allowed to cool down. Surge currents are assumed

to be sine waves of power frequency with a minimum duration of $\frac{1}{2}$ cycles. Manufacturers provide at least three different surge current ratings for different durations.

- **Gate current to trigger (IGT):** Minimum value of the gate current below which reliable turn on of the thyristor cannot be guaranteed. Usually specified at a given forward break over voltage.

- **Gate voltage to trigger (VGT):** Minimum value of the gate cathode forward voltage below which reliable turn on of the thyristor cannot be guaranteed. It is specified at the same break over voltage as IGT.

THYRISTOR PROTECTION:-

There are different types of **thyristor protection** schemes available for satisfactory operation of the device like

1. Over voltage protection. O
2. Over current protection. O
3. High dv/dt protection. H
4. High di/dt protection. H
5. Thermal protection. T

Over Voltage Protection

It is the most important protection scheme w. r. t. others as thyristors are very sensitive to over voltages. Maximum time thyristor failures happen due to over-voltage transients.

A thyristor may be subjected to internal or external over-voltages.

Internal Over-Voltages : After commutation of a thyristor reverse recovery current decays abruptly with high di/dt which causes a high reverse **voltage** [as, $V = L(di/dt)$ so if di/dt is high then V will be large] that can exceed the rated break-over voltage and the device may be damaged.

External Over-Voltages : These are caused due to various reasons in the supply line like lightning, surge conditions (abnormal voltage spike) etc. External over voltage may cause different types of problem in thyristor operation like increase in leakage current, permanent breakdown of junctions, unwanted turn-on of devices etc. So, we have to suppress the over-voltages.

Protective Measure: The effect of over-voltages can be minimized by using non-linear **resistors** called voltage clamping devices like metal oxide varistors. At the time of normal operation, it offers high impedance and acts as it is not present in the circuit. But when the voltage exceeds the rated voltage then it serves as a low impedance path to protect SCR.

Over Current Protection

Overcurrent mainly occurs due to different types of faults in the circuit. Due to overcurrent i^2R loss will increase and high generation of heat may take place that can exceed the permissible limit and burn the device.

Protective Measure: SCR can be protected from overcurrent by using Circuit Breaker (CB) and fast acting current limiting fuses (FACL). CBs are used for protection of thyristor against continuous overloads or against surge currents of long duration as a CB has long tripping time. But fast-acting fuses is used for protecting SCR against high surge current of very short duration.

High dv/dt Protection

When a thyristor is in forward blocking state then only J_2 junction is reverse biased which acts as a capacitor having constant capacitance value C_j (junction capacitance). As we know that current through capacitor follows the relation

$$i = C \frac{dv}{dt} \Rightarrow i \propto \frac{dv}{dt} \text{ (if } C \text{ constant)}$$

Hence leakage current through the J_2 junction which is nothing but the leakage current through the device will increase with the increase in dv_a/dt i.e. rate of change of applied voltage across the thyristor. This current can turn-on the device even when the gate signal is absent. This is called dv/dt triggering and must be avoided which can be achieved by using Snubber circuit in parallel with the device.

Protective Measure :

Snubber Circuit: It consists of a capacitor connected in series with a resistor which is applied parallel with the thyristor, when S is closed then voltage V_s is applied across the device as well as C_s suddenly. At first Snubber circuit behaves like a short circuit. Therefore voltage across the device is zero. Gradually voltage across C_s builds up at a slow rate. So dv/dt across the thyristor will stay in allowable range.

Before turning on of thyristor C_s is fully charged and after turning on of thyristor it discharges through the SCR. This discharging current can be limited with the help of a resistance (R_s) connected in series with the capacitor (C_s) to keep the value of current and rate of change of current in a safe limit.

High di/dt Protection

When a thyristor is turned on by gate pulse then charge carriers spread through its junction rapidly. But if rate of rise of anode current, i.e. di/dt is greater than the spreading of charge carriers then localized heat generation will take place which is known as local hot spots. This may damage the thyristor.

Protective Measure: To avoid local hot spots we use an inductor in series with the device as it prevents high rate of change of current through it.

High Temperature Protection

With the increase in the temperature of the junction, insulation may get failed. So we have to take proper measures to limit the temperature rise.

Protective Measure: We can achieve this by mounting the thyristor on heat sink which is mainly made by high thermal conductivity metals like aluminum (Al), Copper (Cu) etc. Mainly aluminum (Al) is used due to its low cost. There are several types of mounting techniques for SCR such as – Lead-mounting, stud-mounting, Bolt-down mounting, press-fit mounting, press-pack mounting etc.

Gate Protection of Thyristor

Like a thyristor, Gate circuit should also be protected from overvoltages and overcurrents. Overvoltages in the gate circuit can cause false triggering and overcurrent can cause high

junction temperature.

Protective Measure: Overvoltages **thyristor protection** is achieved by using a zener diode and a resistor can be used to protect the gate circuit from overcurrent. Noise in gate circuit can also cause false triggering which can be avoided by using a resistor and a capacitor in parallel. A diode (D) may be connected in series or in parallel with the gate to protect it from high reverse voltage.

Overall Protection of a Thyristor

Lead mounting: In such mounting technique housing of SCR itself is used as heat radiator. Hence no need of additional heat sink arrangement. Hence, this technique of thyristor Protection is generally used for low current application, normally less than one ampere.

Stud mounting: The anode of the thyristor is in the form of threaded stud which is screwed to a metalling heat sink block.

Bolt-down mounting: Here the device is connected to the heat sink with the help of nut-bolt mechanism. It is mainly used in small and medium rating circuit.

Press fit mounting: This kind of mounting is obtained by inserting the whole SCR into the metallic block. It is used in high rating circuit.

Press-Pack mounting: This kind of mounting for **thyristor protection** is obtained by sandwiching the thyristor between to heat sink with the help of clamps. It is used for very high rating circuit.

METHODS OF SCR COMMUTATION:-

To turn On a Thyristor, there are various triggering methods in which a trigger pulse is applied at its Gate terminal. Similarly, there are various **techniques to turn Off a Thyristor**, these techniques are called **Thyristor Commutation Techniques**. It can be done by bringing the Thyristor back into the forward blocking state from the forward conduction state. To bring the Thyristor into forward blocking state, forward current is reduced below the holding current level. For the purpose of power conditioning and power control a conducting Thyristor must be commutated properly.

There are mainly two techniques for Thyristor Commutation: Natural and Forced. The Forced commutation technique is further divided into five categories which are Class A, B, C, D, and E.

Below is the Classification:


- Natural Commutation N
- Forced Commutation F
 - Class A: Self or Load Commutation
 - Class B: Resonant-Pulse Commutation
 - Class C: Complementary Commutation
 - Class D: Impulse Commutation
 - Class E: External Pulse Commutation

Natural Commutation

Natural Commutation occurs only in AC circuits, and it is named so because it doesn't require any external circuit. When a positive cycle reaches to zero and the anode current is zero,

immediately a reverse voltage (negative cycle) is applied across the Thyristor which causes the Thyristor to turn OFF.

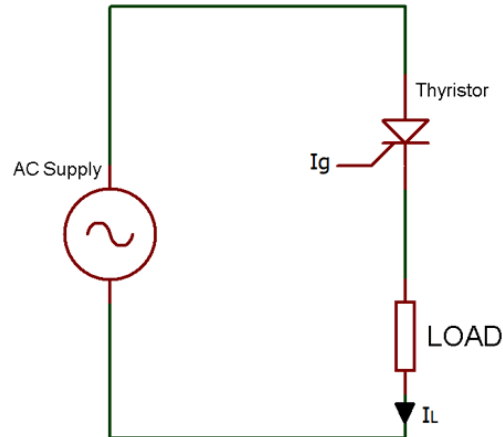A Natural Commutation occurs in AC Voltage Controllers, Cycloconverters, and Phase Controlled Rectifiers.




Forced Commutation

As we know there is no natural zero current in DC Circuits like as natural commutation. So, Forced Commutation is used in DC circuits and it is also called as **DC commutation**. It requires commutating elements like inductance and capacitance to forcefully reduce the anode current of the Thyristor below the holding current value, that's why it is called as **Forced Commutation**. Mainly forced commutation is used in Chopper and Inverters circuits. Forced commutation is divided into six categories, which are explained below:

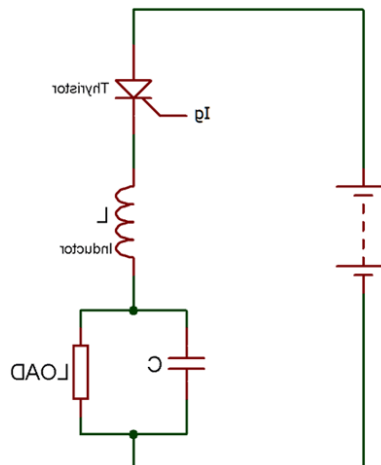1. Class A: Self or Load Commutation


Class A is also called as “Self-Commutation” and it is one of the most used technique among all Thyristor commutation technique. In the below circuit, the inductor, capacitor and resistor form a second order under damp circuit.



When we start supplying the input voltage to the circuit the Thyristor will not turn ON, as it requires a gate pulse to turn ON. Now when the Thyristor turns ON or forward biased, the current will flow through the inductor and charges the capacitor to its peak value or equal to the input voltage. Now, as the capacitor gets fully charged, inductor polarity gets reversed and inductor starts opposing the flow of current. Due to this, the output current starts to decrease and reach to zero. At this moment the current is below the holding current of the Thyristor, so the Thyristor turns OFF.

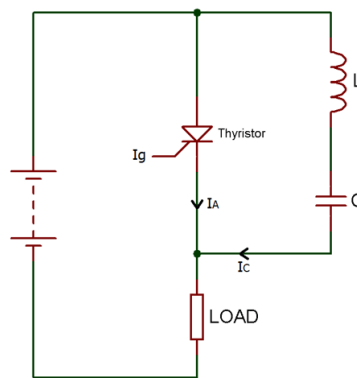2. Class B: Resonant-Pulse Commutation

Class B commutation is also called as Resonant-Pulse Commutation. There is only a small change between Class B and Class A circuit. In class B LC resonant circuit is connected in parallel while in Class A it's in series.




Now, as we apply the input voltage, the capacitor starts charging upto the input voltage (V_s) and Thyristor remains reversed biased until the gate pulse is applied. When we apply the gate pulse, the Thyristor turns ON and now the current start flowing from both the ways. But, then the constant load current flows through the resistance and inductance connected in series, due to its large reactance.

Then a sinusoidal current flow through the LC resonant circuit to charge the capacitor with the reverse polarity. Hence, a reverse voltage appears across the Thyristor, which causes the current I_c (commutating current) to oppose the flow of the anode current I_A . Therefore, due to this opposing commutating current, when the anode current is getting lesser than the holding current, Thyristor turns OFF.

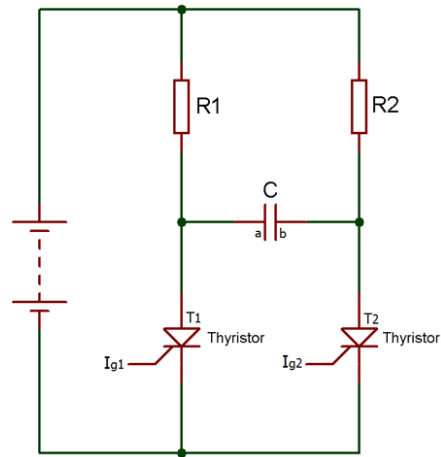3. Class C: Complementary Commutation

Class C commutation is also called as Complementary Commutation. As you can see the circuit below, there are two Thyristor in parallel, one is main and another is auxiliary.




Initially, both the Thyristor are in OFF condition and the voltage across capacitor is also zero. Now, as the gate pulse is applied to the main Thyristor, the current will start flowing from two paths, one is from R1-T1 and second is R2-C-T1. Hence, the capacitor also starts charging to the peak value equal to the input voltage with the polarity of plate B positive and plate A negative.

Now, as the gate pulse is applied to the Thyristor T2, it turns ON and a negative polarity of current appear across the Thyristor T1 which cause T1 to get turn OFF. And, the capacitor starts charging with the reverse polarity. Simply we can say that when T1 turns ON it turns OFF T2 and as T2 turns ON it turns OFF T1.

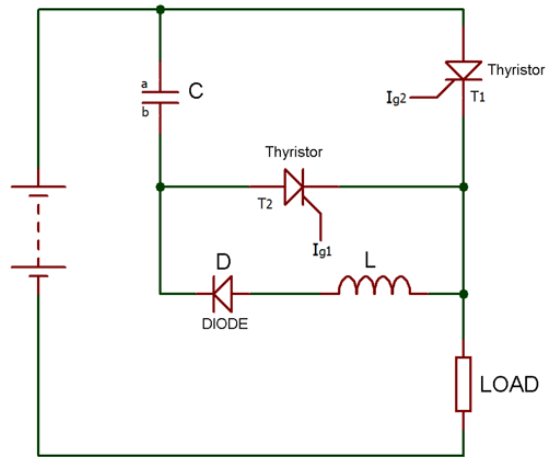4. Class D: Impulse Commutation

Class D commutation is also called as Impulse Commutation or Voltage Commutation. As Class C, Class D commutation circuit also consists of two Thyristor T1 and T2 and they are named as main and auxiliary respectively. Here, diode, inductor, and auxiliary Thyristor form the commutation circuit.




Initially, both the Thyristor are in OFF state and voltage across capacitor C is also zero. Now as we apply the input voltage and trigger the Thyristor T1 the load current starts flowing through it. And, the capacitor starts charging with polarity of plate A negative and plate B positive.

Now, as we trigger the auxiliary Thyristor T2, the main Thyristor T1 turns OFF and the capacitor starts charging with the opposite polarity. When it gets full-charged, it causes the auxiliary Thyristor T2 to turn OFF, because a capacitor does not allow the flow of current through it when it gets fully charged.

Therefore, the output current will also be zero because at this stage because of both the Thyristors are in OFF state.

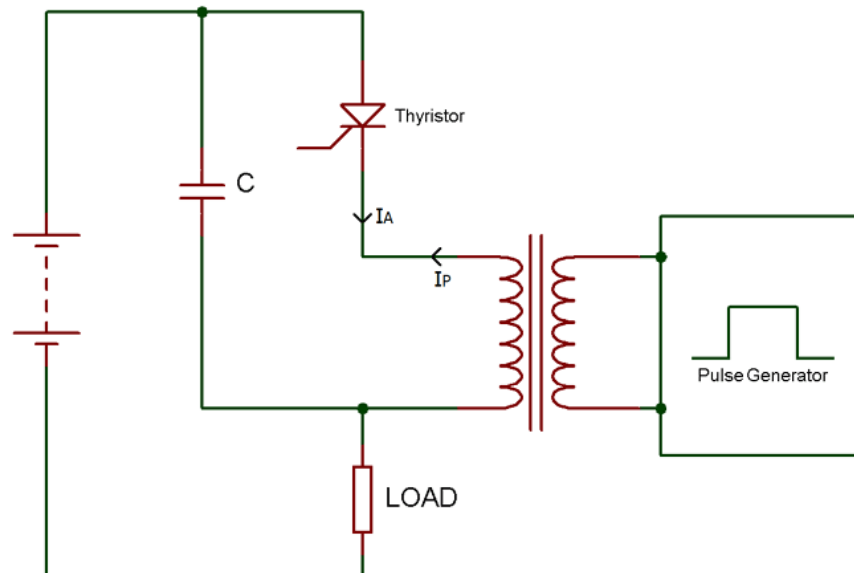5. Class E: External Pulse Commutation

Class E commutation is also called External Pulse Commutation. Now, you can see in the circuit diagram, the Thyristor is already in forward bias. So, as we trigger the Thyristor, the current will appear at the load.



The capacitor in the circuit is used for the dv/dt protection of the Thyristor and the pulse transformer is used to turn OFF the Thyristor.

Now, when we give pulse through the pulse transformer an opposite current will flow in the direction of the cathode. This opposite current oppose the flow of the anode current and if $I_A - I_P < I_H$ Thyristor will turn OFF.


Where I_A is Anode current, I_P is pulse current and I_H is holding current.

starts charging to the peak value equal to the input voltage with the polarity of plate B positive and plate A negative.

Now, as the gate pulse is applied to the Thyristor T2, it turns ON and a negative polarity of current appear across the Thyristor T1 which cause T1 to get turn OFF. And, the capacitor starts charging with the reverse polarity. Simply we can say that when T1 turns ON it turns OFF T2 and as T2 turns ON it turns OFF T1.

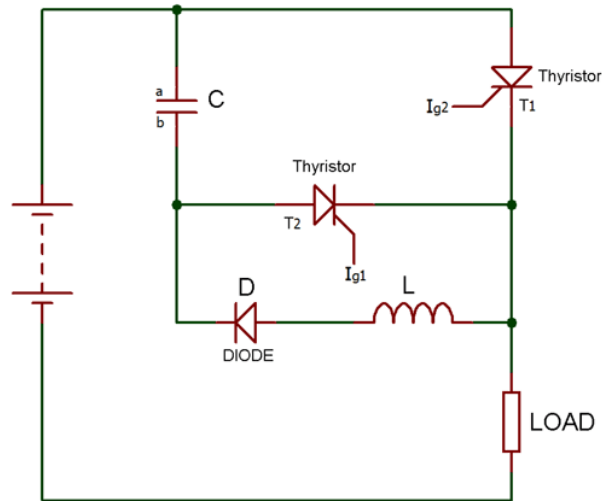4. Class D: Impulse Commutation

Class D commutation is also called as Impulse Commutation or Voltage Commutation. As Class C, Class D commutation circuit also consists of two Thyristor T1 and T2 and they are named as main and auxiliary respectively. Here, diode, inductor, and auxiliary Thyristor form the commutation circuit.




Initially, both the Thyristor are in OFF state and voltage across capacitor C is also zero. Now as we apply the input voltage and trigger the Thyristor T1 the load current starts flowing through it. And, the capacitor starts charging with polarity of plate A negative and plate B positive.

Now, as we trigger the auxiliary Thyristor T2, the main Thyristor T1 turns OFF and the capacitor starts charging with the opposite polarity. When it gets full-charged, it causes the auxiliary Thyristor T2 to turn OFF, because a capacitor does not allow the flow of current through it when it gets fully charged.

Therefore, the output current will also be zero because at this stage because of both the Thyristors are in OFF state.

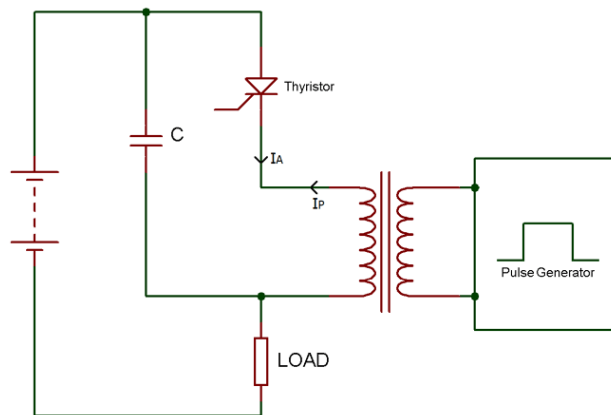5. Class E: External Pulse Commutation

Class E commutation is also called External Pulse Commutation. Now, you can see in the circuit diagram, the Thyristor is already in forward bias. So, as we trigger the Thyristor, the current will appear at the load.



The capacitor in the circuit is used for the dv/dt protection of the Thyristor and the pulse transformer is used to turn OFF the Thyristor.

Now, when we give pulse through the pulse transformer an opposite current will flow in the direction of the cathode. This opposite current oppose the flow of the anode current and if $I_A - I_P < I_H$ Thyristor will turn OFF.

Where I_A is Anode current, I_P is pulse current and I_H is holding current.

UJT AS A TRIGGER SOURCE:-

UJT Triggering of SCR Working Principle – One common application of the unijunction transistor is the triggering of the other devices such as the SCR, triac etc. The basic elements of such a triggering circuit are shown in Fig. 26.91. The resistor R_E is chosen so that the load line determined by R_E passes through the device characteristic in the negative resistance region i.e., to the right of the peak point but to the left of the valley point, as shown in Fig. 26.92. If the load line does not pass to the right of the peak point P, the device cannot turn on.

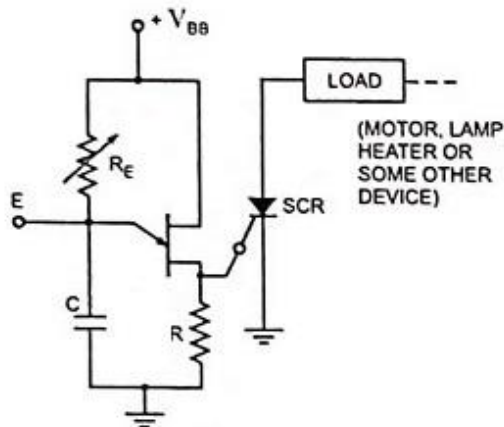


Fig. 26.91 UJT Triggering of An SCR

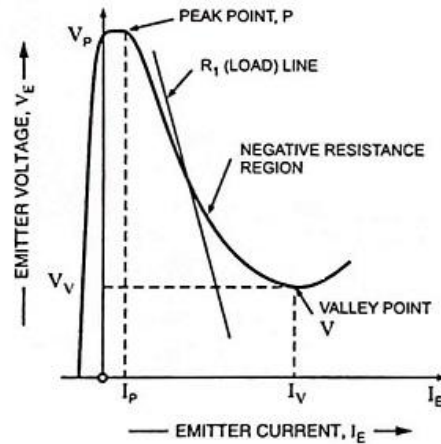


Fig. 26.92

$$R_E < \frac{V_{BB} - V_P}{I_P} \quad \dots(26.37)$$

This can be established as below :

Consider the peak point at which $I_{RE} = I_P$ and $V_E = V_P$ (the equality $I_{RE} = I_P$ is valid because the charging current of capacitor at this instant is zero i.e., the capacitor, at this particular instant, is changing from a charging state to a discharging state). Then $V_E = V_{BB} - I_{RE}R_E$.

So

$$R_{E(max)} = \frac{V_{BB} - V_E}{I_{RE}} = \frac{V_{BB} - V_P}{I_P} \text{ at the peak point.}$$

$$\text{or } R_E < \frac{V_{BB} - V_P}{I_P}$$

At the valley point, V

$I_E = I_V$ and $V_E = V_V$ so that

$$V_E = V_{BB} - I_{RE}R_E$$

So

$$R_{E(min)} = \frac{V_{BB} - V_E}{I_{RE}} = \frac{V_{BB} - V_V}{I_V}$$

or for ensuring turn-off

$$R_E > \frac{V_{BB} - V_V}{I_V} \quad \dots(26.38)$$

So the range of resistor R_E is given as

$$\frac{V_{BB} - V_P}{I_P} > R_E > \frac{V_{BB} - V_V}{I_V}$$

The resistor R is chosen small enough so as to ensure that SCR is not turned on by voltage V_R when emitter terminal E is open or $I_E = 0$ (Fig. 26.93). The Voltage $V_R = RV_{BB}/R + R_{BB}$ for open-emitter terminal.

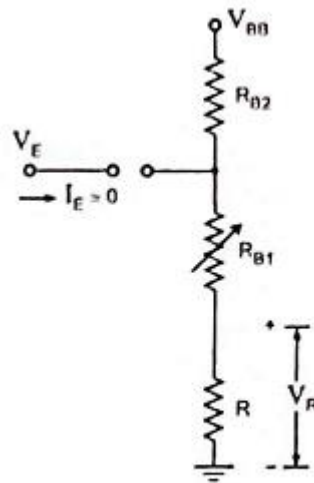



Fig. 26.93

The capacitor C determines the time interval between triggering pulses and the time duration of each pulse.


By varying R_E , we can change the time constant R_EC and alter the point at which the UJT fires. This allows us to control the conduction angle of the SCR, which means the control of [load current](#).

GATE DRIVE CIRCUITS FOR BJT AND MOSFETs

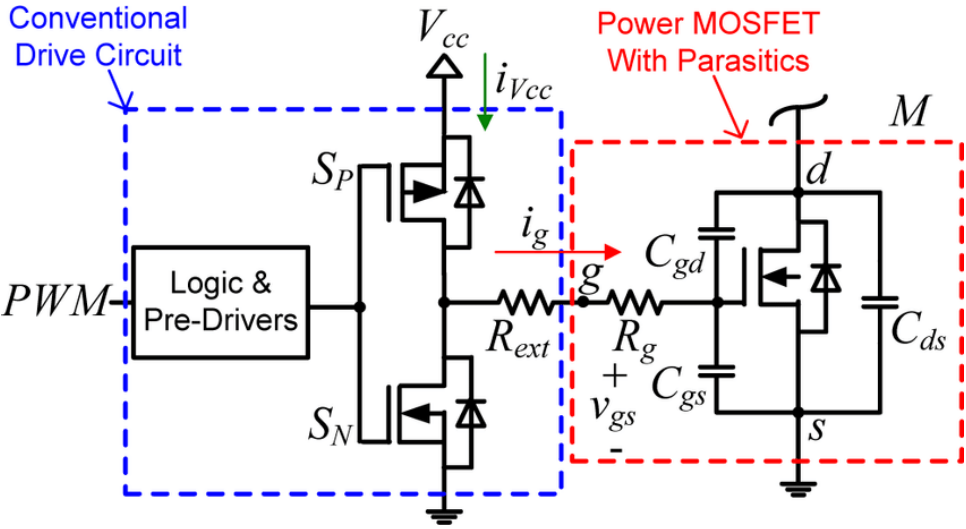A gate driver is a power amplifier that accepts a low-power input from a controller IC and produces a high-current drive input for the gate of a high-power transistor such as a BJT and MOSFET. Gate drivers can be provided either on-chip or as a discrete module.



BJT

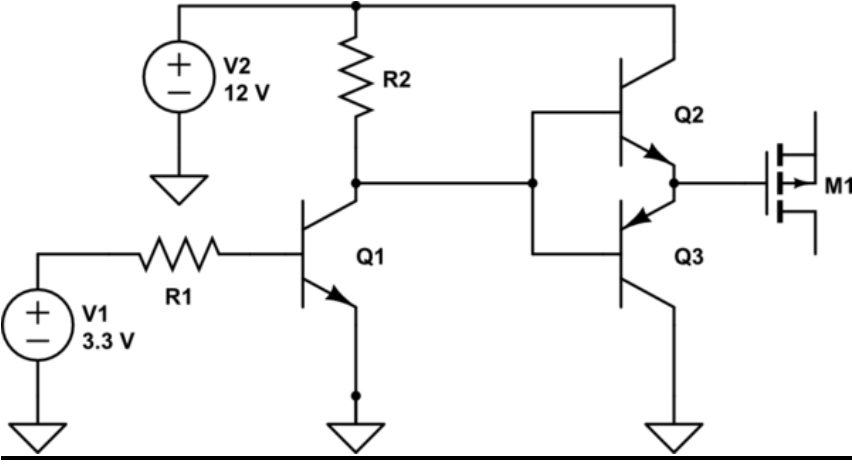

UNIT – II

Single phase and three phase controlled rectifiers

Phase control technique – Single phase Line commutated converters

Unlike diode rectifiers, PCR or phase controlled rectifiers has an advantage of regulating the output voltage. The diode rectifiers are termed as uncontrolled rectifiers. When these diodes are switched with Thyristors, then it becomes phase control rectifier. The o/p voltage can be regulated by changing the firing angle of the Thyristors. The main application of these

rectifiers is involved in speed control of DC motor.

What is a Phase Controlled Rectifier?

The term PCR or Phase controlled rectifier is a one type of rectifier circuit in which the diodes are switched by Thyristors or SCRs (Silicon Controlled Rectifiers). Whereas the diodes offer no control over the o/p voltage, the Thyristors can be used to differ the output voltage by adjusting the firing angle or delay. A phase control Thyristor is activated by applying a short pulse to its gate terminal and it is deactivated due to line commutation or natural. In case of heavy inductive load, it is deactivated by firing another Thyristor of the rectifier during the negative half cycle of i/p voltage.

Types of Phase Controlled Rectifier

The phase controlled rectifier is classified into two types based on the type of i/p power supply. And each kind includes a semi, full and dual converter.

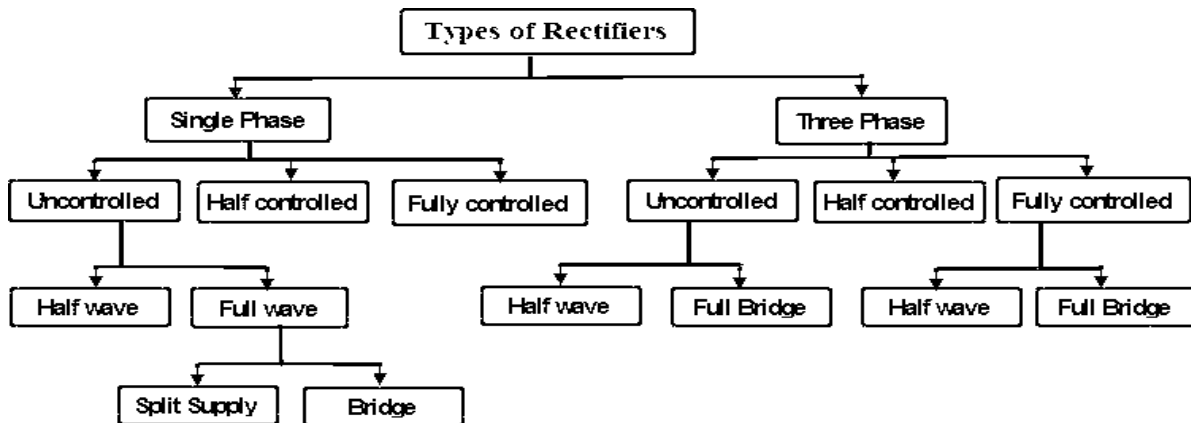


Figure: 2.1. Classification of rectifiers

Single-phase Controlled Rectifier

This type of rectifier which works from single phase AC i/p power supply

Controlled Rectifiers are classified into different types

Half wave Controlled Rectifier: This type of rectifier uses a single Thyristor device to provide o/p control only in one half cycle of input AC supply, and it offers low DC output.

Full wave Controlled Rectifier: This type of rectifier provides higher DC output

- Full wave controlled rectifier with a center tapped transformer requires two Thyristors.
- Full wave bridge controlled rectifiers do not need a center tapped transformer

Three-phase Controlled Rectifier

This type of rectifier which works from three phase AC i/p power supply

- A semi converter is a one quadrant converter that has one polarity of o/p voltage and current.
- A full converter is a two quadrants converter that has polarity of o/p voltage can be either +ve or –ve but, the current can have only one polarity that is either +ve or -ve.
- Dual converter works in four quadrants – both o/p voltage and o/p current can have both the polarities.

Operation of Phase Controlled Rectifier

The basic working principle of a PCR circuit is explained using a single phase half wave PCR circuit with a RL load resistive shown in the following circuit.

A single phase half wave Thyristor converter circuit is used to convert AC to DC power conversion. The i/p AC supply is attained from a transformer to offer the required AC supply voltage to the Thyristor converter based on the o/p DC voltage required. In the above circuit, the primary and secondary AC supply voltages are denoted with V_P and V_S .

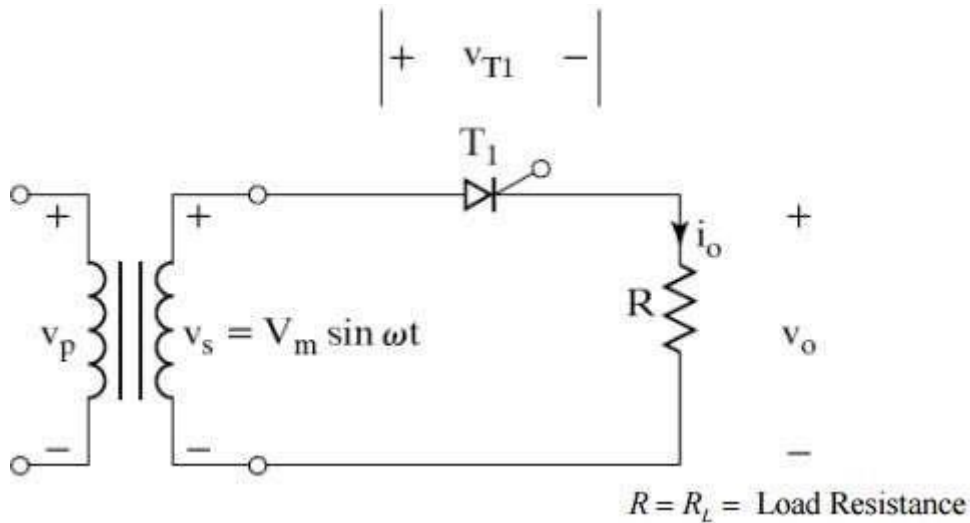


Figure: 2.2. Single phase half wave rectifier circuit

During the +ve half cycle of i/p supply when the upper end of the transformer secondary winding is at a +ve potential with respect to the lower end, the Thyristor is in a forward biased state.

The thyristor is activated at a delay angle of $\omega t = \alpha$, by applying an appropriate gate trigger pulse to the gate terminal of thyristor. When the thyristor is activated at a delay angle of $\omega t = \alpha$, the thyristor behaves and assuming a perfect thyristor. The thyristor acts as a closed switch and the i/p supply voltage acts across the load when it conducts from $\omega t = \alpha$ to π radians. For a purely resistive load, the load current i_o that flows when the thyristor T1 is on, is given by the expression.

$$i_o = \frac{V_m \sin \omega t}{R} \quad \alpha \leq \omega t \leq \pi$$

Applications of Phase Controlled Rectifier

Phase controlled rectifier applications include paper mills, textile mills using DC motor drives and DC motor control in steel mills.

- AC fed traction system using a DC traction motor.
- Electro-metallurgical and Electrochemical processes.
- Reactor controls.

- Magnet power supplies.
- Portable hand instrument drives.

- Flexible speed industrial drives.
- Battery charges.
- High voltage DC transmission.
- UPS (Uninterruptible power supply systems).

Operation of half converter with R and RL loads

Single Phase Half Wave Controlled Rectifier with ‘R’ load:

As shown in figure below primary of transformer is connected to ac mains supply with which SCR becomes forward bias in positive half cycle. T1 is triggered at an angle α , T1 conducts and voltage is applied across R.

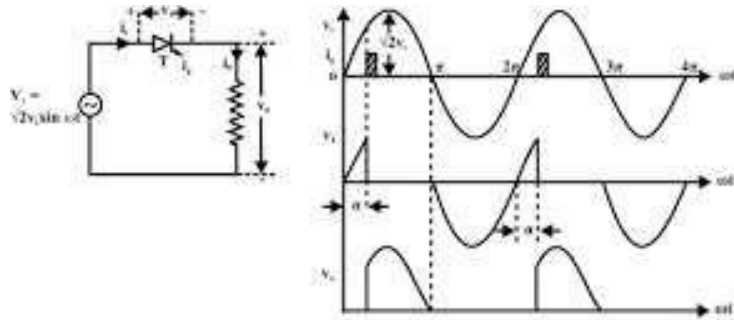


Figure: 2.3 Single phase half wave rectifier with R load with waveforms

The load current i_o flows through ‘R’ the waveforms for voltage & current are as shown above. As load is resistive, Output current is given as,

$$I_o = \frac{V_o}{R}$$

Hence shape of output current is same as output voltage

As T1 conducts only in positive half cycle as it is reversed bias in negative cycle, the ripple frequency of output voltage is-

fripple= 50 Hz (supply frequency) Average output voltage is given as,

$$V_o(Avg) = \frac{1}{T} \int_0^T V_o(\omega t) d\omega t$$

i.e Area under one cycle.

Therefore $T=2\pi$ & $V_o(\omega t) = V_m \sin \omega t$ from α to π & for rest of the period $V_o(\omega t)=0$

$$\begin{aligned} \therefore V_o(Avg) &= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin(\omega t) d\omega t \\ &= \frac{V_m}{2\pi} [-\cos \omega t]_{\alpha}^{\pi} \\ &= \frac{V_m}{2\pi} (1 + \cos \alpha) \end{aligned}$$

Power transferred to load,

$$P_o(Avg) = \frac{V_o^2(Avg)}{R}$$

Thus, power & voltage can be controlled by firing angle.

Single Phase Half Wave Controlled Rectifier with 'RL' load

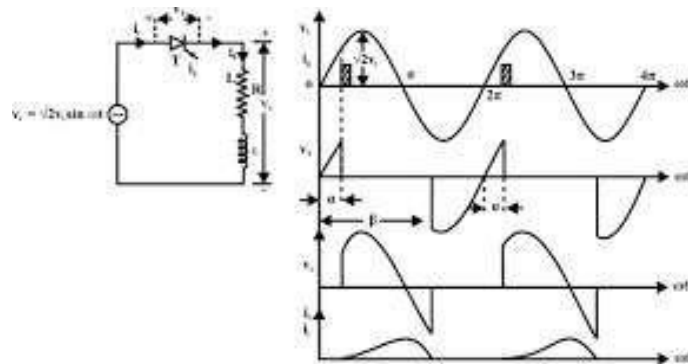


Figure: 2.4 Single phase half wave rectifier with RL load with waveforms

Figure above shows the single phase half wave rectifier with RL Load.

N

ormally motors are inductive loads L= armature of field coil inductance

R= Resistance of coil.

- In positive half cycle, SCR starts conduction at firing angle “ α ”.
- Drop across SCR is small & neglected so output voltage is equal to supply voltage.
- Due to ‘ R_L ’ load, current through SCR increases slowly.
- At ‘ π ’, supply voltage is at zero where load current is at its max value.
- In positive half cycle, inductor stores energy & that generates the voltage.
- In negative half cycle, the voltage developed across inductor, forward biases SCR & maintains its conduction.
- Basically with the property of inductance it opposes change in current.
- Output current & supply current flows in same loop, so all the time $i_o=i_s$.
- After π the energy of inductor is given to mains & there is flow of ‘ i_o ’. The energy reduces as if gets consumed by circuit so current also reduces.
- At ‘ β ’ energy stored in inductance is finished, hence ‘ i_o ’ becomes zero & ‘T1’ turns off.
- ‘ i_o ’ becomes zero from ‘ β ’ to ‘ $2\pi+\alpha$ ’ hence it is discontinuous conduction.

The average output voltage
$$= \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m \sin \omega t \, d(\omega t) = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta)$$

$$I = \frac{V_m}{2\pi R} (\cos \alpha - \cos \beta)$$

RMS output
$$= \frac{1}{\sqrt{2\pi}} \sqrt{\int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t \, d(\omega t)}$$

$$= \frac{V_m}{2\sqrt{\pi}} [(\beta - \alpha) - \frac{1}{2} \{\sin 2\beta - \sin 2\alpha\}]^{1/2}$$

Single phase half controlled converter with RLE load

The diode D2 and D4 conducts for the positive and negative half cycle of the input voltage waveform respectively. On the other hand T1 starts conduction when it is fired in the positive half cycle of the input voltage waveform and continuous conduction till T3 is fired in the negative half cycle. Fig. shows the circuit diagram and the waveforms of a single phase half controlled converter supplying an R – L – E load.

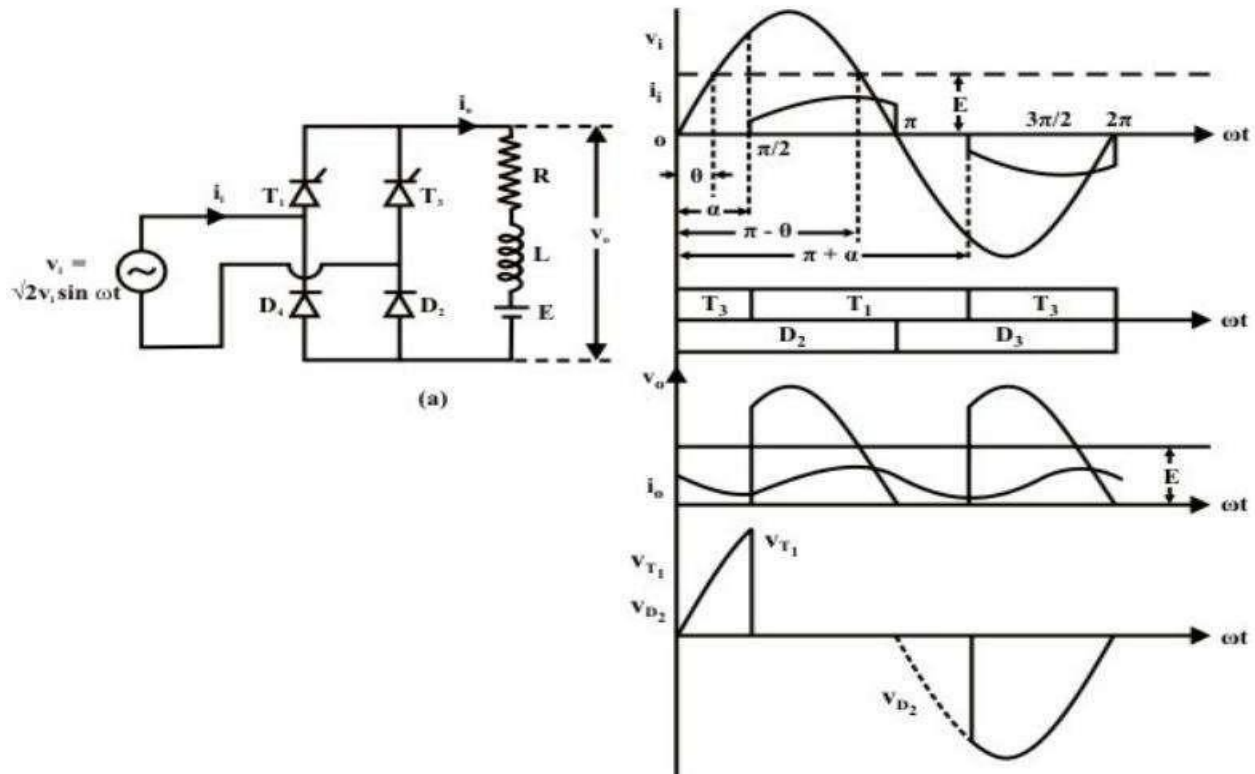


Figure: 2.5 single phase half controlled converter with RLE load

Referring to Fig T1 D2 starts conduction at $\omega t = \alpha$. Output voltage during this period becomes equal to

i. A

At $\omega t = \pi$ as v_i tends to go negative D4 is forward biased and the load current commutates from D2 to D4 and freewheels through D4 and T1. The output voltage remains clamped to zero till T3 is fired at $\omega t = \pi + \alpha$. The T3 D4 conduction mode continues upto $\omega t = 2\pi$. Where upon load current again free wheels through T3 and D2 while the load voltage is clamped to zero. From the discussion in the previous paragraph it can be concluded that the output voltage (hence the output current) is periodic over half the input cycle. Hence

$$V_{oav} = \frac{1}{\pi} \int_0^{\pi} v_o d\omega t = \frac{1}{\pi} \int_{\alpha}^{\pi} \sqrt{2}V_i \sin \omega t d\omega t = \frac{\sqrt{2}V_i}{\pi} (1 + \cos\alpha)$$

$$I_{ov} = \frac{V_{oav} - E}{R} = \frac{\sqrt{2}V_i}{\pi R} (1 + \cos\alpha - \pi \sin\theta)$$

Single phase half controlled converter with RLE load and freewheeling diode

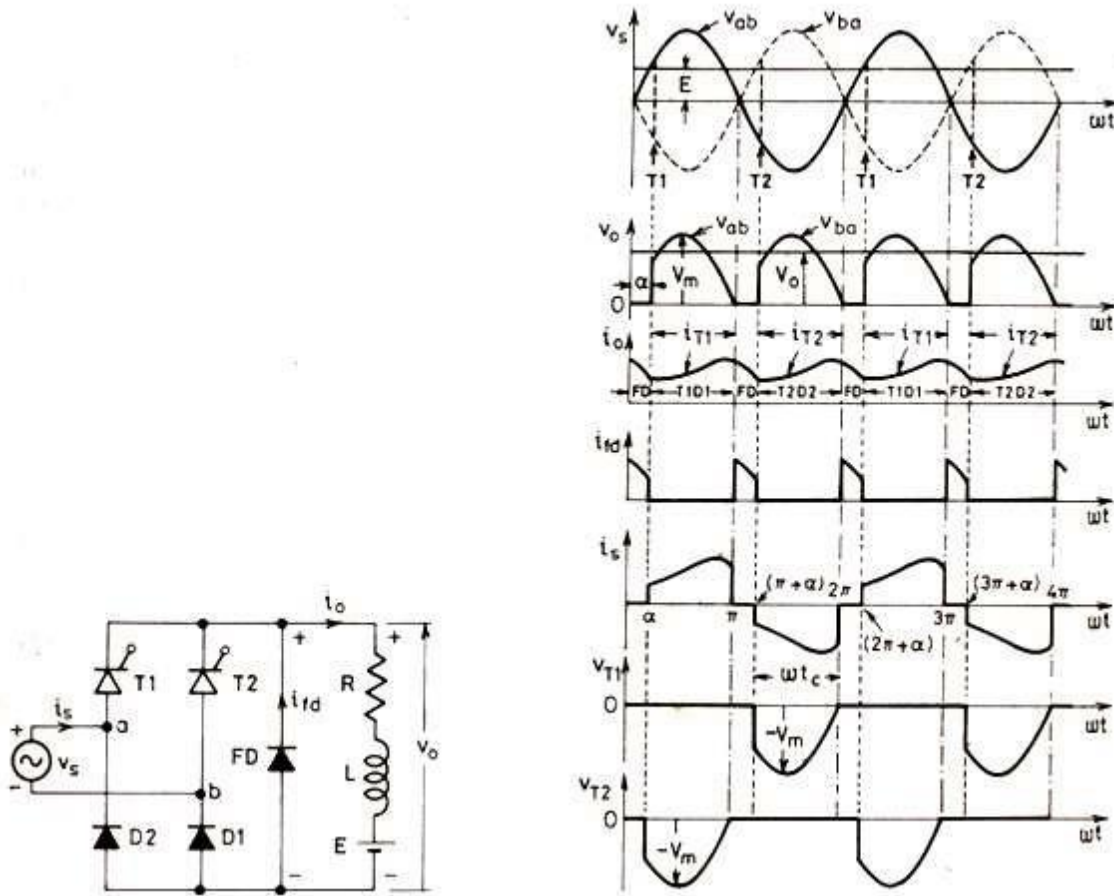


Figure: 2.6 single phase half controlled converter with RLE load and freewheeling diode
Numerical problems

1. A single phase 230V, 1 Kwheter is connected across 1 phase 230V, 50Hz supply through an SCR. For firing angle delay of 45° and 90°, calculate the power absorbed in the heater element.

Solution: Heater resistance $R = 230^2/1000 \Omega$

The rms value of voltage is V_{or}

$$= \frac{2\sqrt{\pi}}$$

$$= \frac{\sqrt{2 \times 230}}{2\sqrt{\pi}}$$

$$= \frac{1}{2\sqrt{\pi}} \left[\sin^2 \alpha + \frac{1}{4} \sin^2 2\alpha \right]$$

$$= \frac{1}{2\sqrt{\pi}} \left[\left(\frac{\pi}{4} \right)^2 + \frac{1}{4} \sin^2 \left(\frac{\pi}{2} \right) \right] = 155.071V$$

Power absorbed by the heater element for $\alpha = 45^\circ$ is

$$P = \frac{V_{or}^2}{R} = \frac{(155.071)^2}{230} \times 1000 = 103457.1W$$

for $\alpha = 90^\circ$ the rms voltage is

$$V_{or} = \frac{1}{2\sqrt{\pi}} \left[\left(\frac{\pi}{2} \right)^2 + \frac{1}{4} \sin^2 \left(\frac{\pi}{2} \right) \right] = 115V$$

Power absorbed by the heater element for $\alpha = 90^\circ$ is

$$V_{or^2} = \left[\frac{115^2}{R} \times 1000 = 250W \text{ — } \frac{230}{230} \right]$$

2. A resistive load of 10Ω is connected through a half-wave controlled rectifier circuit to 220V, 50Hz, single phase source. Calculate the power delivered to the load for a firing angle of 60° . Find also the value of input power factor
3. A single phase semi converter delivers to RLE load with $R=5\Omega$, $L = 10\text{mH}$ and $E = 80\text{V}$. The source voltage is 230V, 50Hz. For continuous conduction, Find the average value of output current for firing angle $= 50^\circ$.

Single phase full wave controlled rectifier

Single Phase Full Wave Controlled Rectifier with 'R' load:

Figure below shows the Single phase Full Wave Controlled Rectifiers with R load


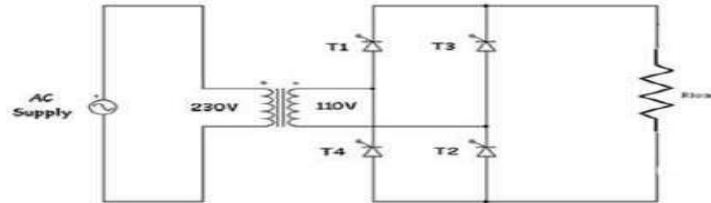


Figure: 2.7 single phase full converter circuit with R load

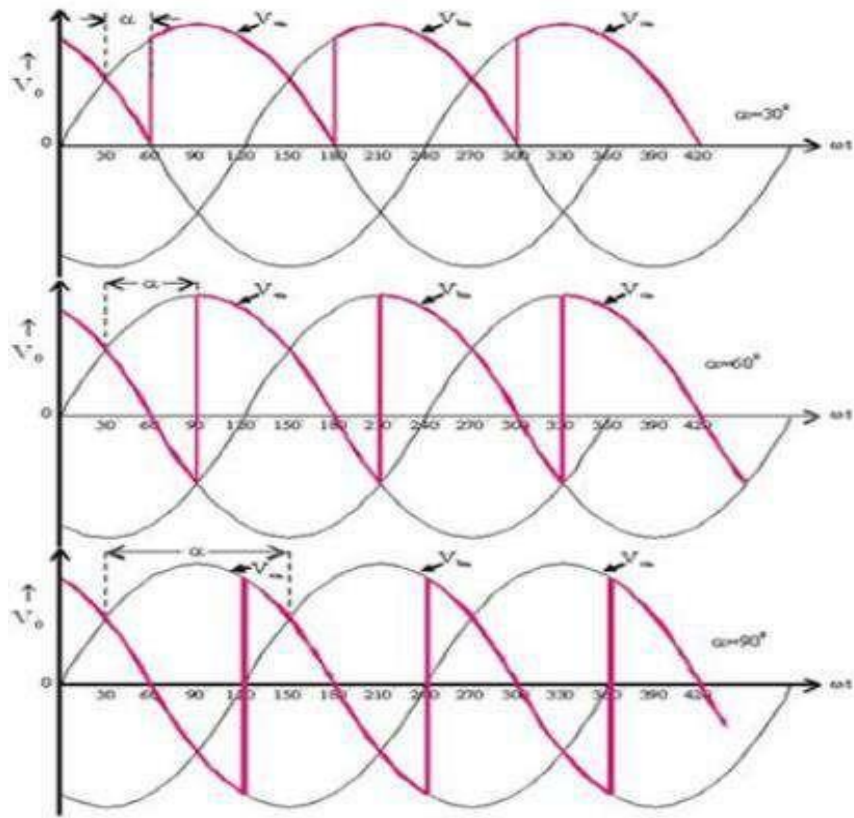

single phase full converter circuit with R load input and output waveforms

The single phase fully controlled rectifier allows conversion of single phase AC into DC. Normally this is used in various applications such as battery charging, speed control of DC motors and front end of UPS(Uninterruptible Power Supply) and SMPS (Switched Mode Power Supply).

•

A

If four devices used are Thyristors. The turn-on instants of these devices are dependent on the firing signals that are given. Turn-off happens when the current through the device reaches zero and it is reversebiased at least for duration equal to the turn-off time of the device specified in the data sheet.

- In positive half cycle Thyristors T1 & T2 are fired at an angle α .

•

W

when T1 & T2 conducts $V_o = V_s$ $I_o = i_s = V_o/R = V_s/R$

- In negative half cycle of input voltage, SCR's T3 & T4 are triggered at an angle of $(\pi + \alpha)$
- Here output current & supply current are in opposite direction

$\therefore i_s = -i_o$

T3 & T4 becomes off at 2π .

$$V = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t \, (\omega t) = \frac{2V_m}{\pi} \cos \alpha$$

single Phase Full Wave Controlled Rectifier with 'RL' load:

Figure below shows Single phase Full Wave Controlled Rectifiers with RL load.

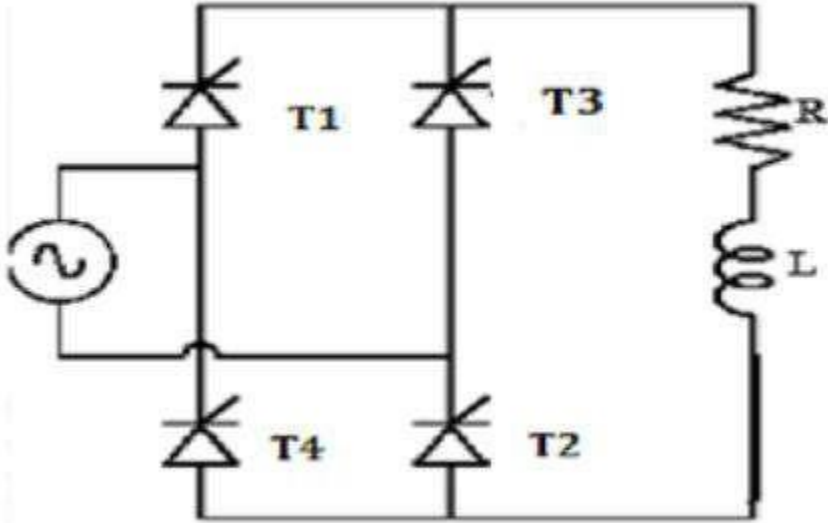


Figure: 2.9 single phase full converter circuit with RL load

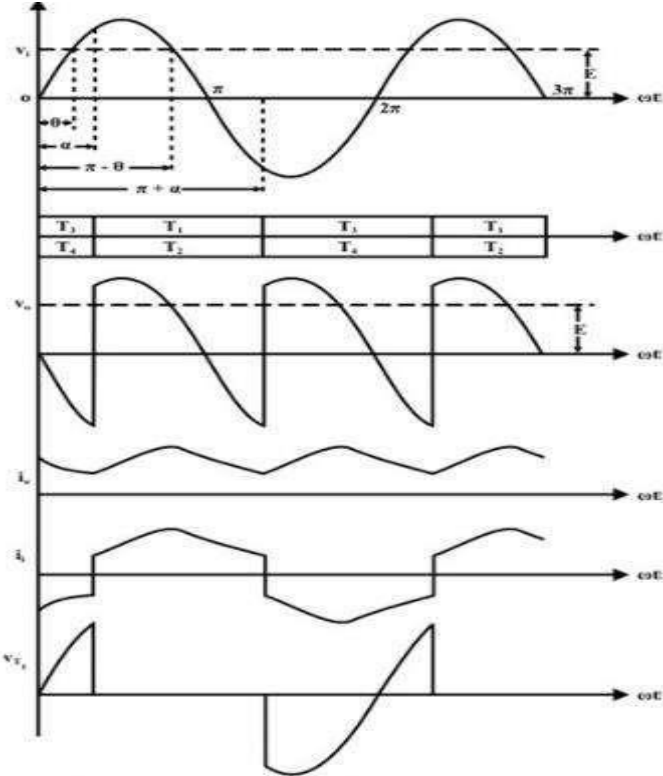


Figure: 2.10 single phase full converter circuit with RL load input and output waveforms

Operation of this mode can be divided between four modes

Mode 1 (α to π)

- In positive half cycle of applied ac signal, SCR's T1 & T2 are forward bias & can be turned on at an angle α .
- Load voltage is equal to positive instantaneous ac supply voltage. The load current is positive, ripple free, constant and equal to I_o .
- Due to positive polarity of load voltage & load current, load inductance will store energy.

Mode 2 (π to $\pi+\alpha$)

- At $\omega t = \pi$, input supply is equal to zero & after π it becomes negative. But inductance opposes any change through it.
- In order to maintain a constant load current & also in same direction. A self induced emf appears across 'L' as shown.
- Due to this induced voltage, SCR's T1 & T2 are forward bias in spite the negative supply voltage.
- The load voltage is negative & equal to instantaneous ac supply voltage whereas load current is positive.
- Thus, load acts as source & stored energy in inductance is returned back to the ac supply.

Mode 3 ($\pi+\alpha$ to 2π)

- At $\omega t = \pi + \alpha$ SCR's T3 & T4 are turned on & T1, T2 are reversed bias.
- Thus, process of conduction is transferred from T1, T2 to T3, T4.
- Load voltage again becomes positive & energy is stored in inductor
- T3, T4 conduct in negative half cycle from $(\pi + \alpha)$ to 2π
- With positive load voltage & load current energy gets stored

Mode 4 (2π to $2\pi+\alpha$)

- At $\omega t = 2\pi$, input voltage passes through zero.
- Inductive load will try to oppose any change in current if in order to maintain load current constant & in the same direction.
- Induced emf is positive & maintains conducting SCR's T3 & T4 with reverse polarity also.

- Thus VL is negative & equal to instantaneous ac supply voltage. Whereas load current continues to be positive.
- Thus load acts as source & stored energy in inductance is returned back to ac supply
- At $\omega t = \alpha$ or $2\pi + \alpha$, T3 & T4 are commutated and T1, T2 are turned on.

$$V = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t \, (\omega t) = \frac{2V_m}{\pi} \cos \alpha$$

Single phase fully controlled converters with RLE load

The circuit diagram of a full wave bridge rectifier using thyristors is shown in figure below. It consists of four SCRs which are connected between single phase AC supply and a load.

This rectifier produces controllable DC by varying conduction of all SCRs.

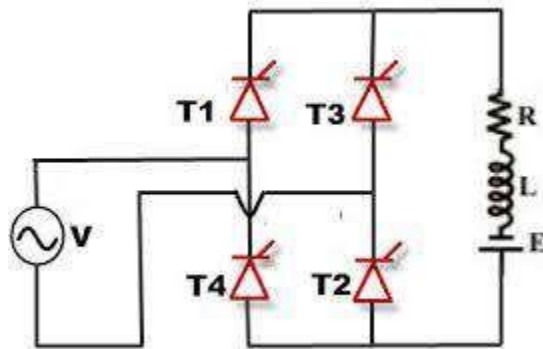


Figure: 2.11 single phase full converter circuit with RLE load

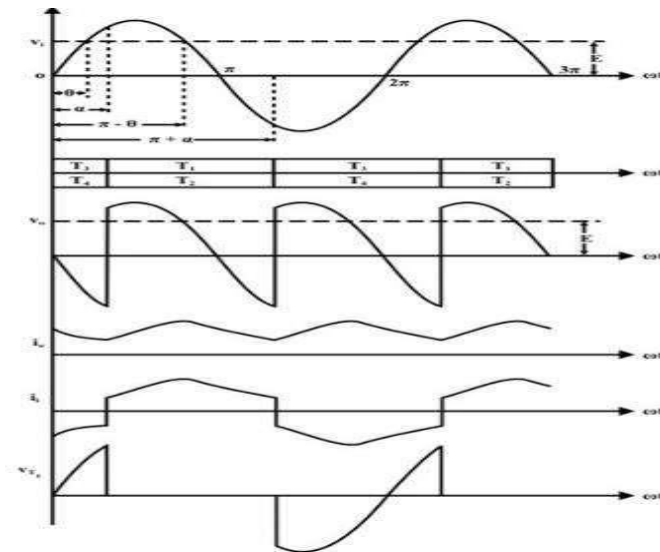


Figure: 2.12 single phase full converter circuit with RLE load input and output waveforms

In positive half-cycle of the input, Thyristors T1 and T2 are forward biased while T3 and T4 are reverse biased. Thyristors T1 and T2 are triggered simultaneously at some firing angle in the positive half cycle, and T3 and T4 are triggered in the negative half cycle.

The load current starts flowing through them when they are in conduction state. The load for this converter can be RL or RLE depending on the application.

By varying the conduction of each thyristor in the bridge, the average output of this converter gets controlled. The average value of the output voltage is twice that of half-wave rectifier.

The average output voltage is

$$V_{oav} = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t \, d(\omega t) = \frac{2V_m}{\pi} \cos \alpha$$

Line commutated converters

single phase half wave converter

1. Average DC load voltage: (V_{oav})

$$V_{oav} = \frac{1}{T} \int_0^T V_m \sin \omega t \, d(\omega t) \quad \text{where T is time period}$$

$$V_{oav} = \frac{1}{2\pi} \left[\int_{\alpha}^{\pi} V_m \sin \omega t \, d(\omega t) + \int_{\pi}^{2\pi+\alpha} 0 \, d(\omega t) \right]$$

$$= \frac{1}{2\pi} \left[\int_{\alpha}^{\pi} V_m \sin \omega t \, d(\omega t) \right]$$

$$= \frac{V_m}{2\pi} [-\cos \omega t]_{\alpha}^{\pi}$$

$$= \frac{V_m}{2\pi} [\cos \pi - \cos \alpha]$$

$$= \frac{V_m}{2\pi} [1 + \cos \alpha]$$

$$I_{oav} = \frac{V_{oav}}{R_m}$$

If $\alpha = 180^\circ$ $V_{oavg} = 0$

2. Average DC load current is given as

$$I_{oavg} = \frac{V_{oavg} R}{R}$$

$$I_{oavg} = \frac{V_m}{2\pi R} [1 + \cos\alpha]$$

3. RMS load voltage

$$V_{rms} = \left\{ \frac{1}{T} \int_0^T V_m^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2}$$

$$V_{rms} = \left\{ \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2}$$

$$V_{rms} = \frac{V_m}{2\sqrt{\pi}} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right)^{1/2}$$

$$I_{rms} = \frac{V_m}{R} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right)^{1/2}$$

If $\alpha = 180^\circ$ $V_{rms} = 0$

The RMS voltage may be varied from 0 to $\frac{V_m}{2}$ by varying α from 180 to 0

4. Power delivered to the resistive load is given

$$P_L = (\text{RMS load voltage})(\text{RMS load current})$$

$$= V_{rms} \times I_{rms}$$

$$= V_{rms}^2 = I_{rms}^2 \times R$$

5. Input volt amperes = (RMS source voltage)(RMS line current)

$$= V_s I_{rms}$$

$$= V_s \frac{\sqrt{2} V_s}{R 2 \sqrt{\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

$$= \frac{V_s^2}{\sqrt{2\pi} X R} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

6. Input power factor: It is defined as the ratio of total mean input power to the total rms input volt amperes

form factor: Form factor is defined as the ratio of RMS voltage to the average DC voltage

$$\text{Factor} = \frac{V_{\text{rms}}}{V_{\text{avg}}}$$

8. Effective value of the AC component of the output voltage

$$V_{\text{ac}} = [V_{\text{rms}}^2 - V_{\text{avg}}^2]^{1/2}$$

9. Ripple factor (R_f)

It is defined as the ratio of AC component to the DC. Where ripple is the amount of AC component present in DC component

$$R_f = \frac{V_{\text{ac}}}{V_{\text{avg}}} = \frac{[V_{\text{rms}}^2 - V_{\text{avg}}^2]^{1/2}}{V_{\text{avg}}} = \left[\left(\frac{V_{\text{rms}}}{V_{\text{avg}}} \right)^2 - 1 \right]^{1/2} = \sqrt{FF^2 - 1}$$

10. Transformer Utilization Factor (TUF):

It is defined as the ratio of output DC power to the volt ampere rating of the transformer

$$\text{TUF} = \frac{P_{\text{dc}}}{\text{VA rating of secondary winding of the transformer}}$$

11. Rectifier efficiency:

It is defined as the ratio of output DC power to the input ac power

$$\eta = \frac{V_{\text{avg}} I_{\text{avg}}}{V_{\text{rms}} I_{\text{rms}}}$$

12. Peak inverse voltage (PIV):

It is defined as the maximum voltage that an SCR can be subjected to in the reverse biased condition

In the case of Half wave rectifier it is V_m

Effect of source inductance in single phase rectifier

Fig. below shows a single phase fully controlled converter with source inductance. For simplicity it has been assumed that the converter operates in the continuous conduction mode. Further, it has been assumed that the load current ripple is negligible and the load can be replaced by a dc current source the magnitude of which equals the average load current. Fig. shows the corresponding waveforms

It is assumed that the Thyristors T3 and T4 were conducting at $t = 0$. T1 and T2 are fired at $\omega t = \alpha$. If

there were no source inductance T3 and T4 would have commutated as soon as T1 and T2 are turned ON.

The input current polarity would have changed instantaneously. However, if a source inductance is present the commutation and change of input current polarity cannot be instantaneous. Therefore, when T1 and T2 are turned ON T3 T4 does not commutate immediately. Instead, for some interval all four

Thyristors continue to conduct as shown in Fig. 2.14. This interval is called “overlap” interval.

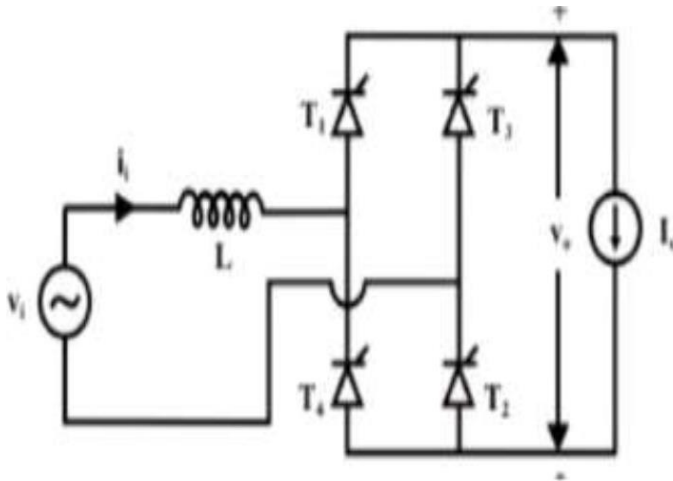


Figure: 2.13 single phase full converter circuit with source inductance

UNIT – II

Single phase and three phase controlled rectifiers

Phase control technique – Single phase Line commutated converters

Unlike diode rectifiers, PCRs or phase controlled rectifiers has an advantage of regulating the output voltage. The diode rectifiers are termed as uncontrolled rectifiers. When these diodes are switched with Thyristors, then it becomes phase control rectifier. The o/p voltage can be regulated by changing the firing angle of the Thyristors. The main application of these rectifiers is involved in speed control of DC motor.


What is a Phase Controlled Rectifier?

The term PCR or Phase controlled rectifier is a one type of rectifier circuit in which the diodes are switched by Thyristors or SCRs (Silicon Controlled Rectifiers). Whereas the diodes offer no control over the o/p voltage, the Thyristors can be used to differ the output voltage by adjusting the firing angle or delay. A phase control Thyristor is activated by applying a short pulse to its gate terminal and it is deactivated due to line commutation or natural. In case of heavy inductive load, it is deactivated by firing another Thyristor of the rectifier during the negative half cycle of i/p voltage.

Types of Phase Controlled Rectifier

The phase controlled rectifier is classified into two types based on the type of i/p power supply. And each kind includes a semi, full and dual converter.

Figure: 2.1. Classification of rectifiers

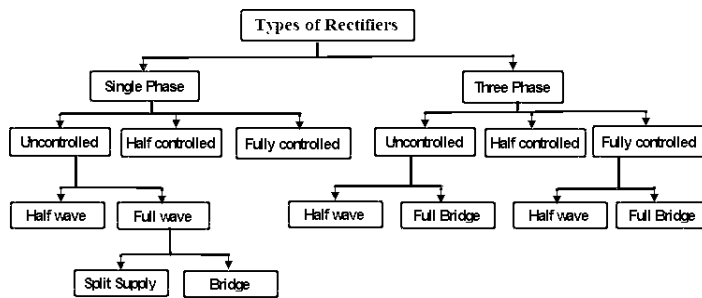

Single-phase Controlled Rectifier

This type of rectifier which works from single phase AC i/p power supply

Controlled Rectifiers are classified into different types

Half wave Controlled Rectifier: This type of rectifier uses a single Thyristor device to provide o/p control only in one half cycle of input AC supply, and it offers low DC output.

Full wave Controlled Rectifier: This type of rectifier provides higher DC output

- Full wave controlled rectifier with a center tapped transformer requires two Thyristors.
- Full wave bridge controlled rectifiers do not need a center tapped transformer

Three-phase Controlled Rectifier

This type of rectifier which works from three phase AC i/p power supply

- A semi converter is a one quadrant converter that has one polarity of o/p voltage and current.
- A full converter is a two quadrants converter that has polarity of o/p voltage can be either +ve or -ve but, the current can have only one polarity that is either +ve or -ve.
- Dual converter works in four quadrants – both o/p voltage and o/p current can have both the polarities.

Operation of Phase Controlled Rectifier

The basic working principle of a PCR circuit is explained using a single phase half wave PCR circuit with a RL load resistive shown in the following circuit.

A single phase half wave Thyristor converter circuit is used to convert AC to DC power

conversion. The i/p AC supply is attained from a transformer to offer the required AC supply voltage to the Thyristor converter based on the o/p DC voltage required. In the above circuit, the primary and secondary AC supply voltages are denoted with V_P and V_S .

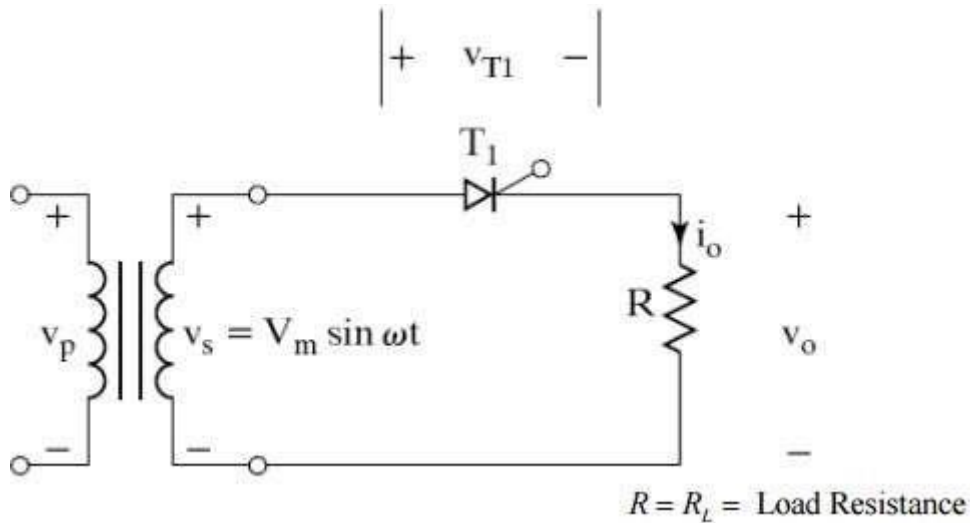


Figure: 2.2. Single phase half wave rectifier circuit

During the +ve half cycle of i/p supply when the upper end of the transformer secondary winding is at a +ve potential with respect to the lower end, the Thyristor is in a forward biased state.

The thyristor is activated at a delay angle of $\omega t = \alpha$, by applying an appropriate gate trigger pulse to the gate terminal of thyristor. When the thyristor is activated at a delay angle of $\omega t = \alpha$, the thyristor behaves and assuming a perfect thyristor. The thyristor acts as a closed switch and the i/p supply voltage acts across the load when it conducts from $\omega t = \alpha$ to π radians. For a purely resistive load, the load current i_o that flows when the thyristor T1 is on, is given by the expression.

$$i_o = v_o / R_L, \text{ for } \alpha \leq \omega t \leq \pi$$

Applications of Phase Controlled Rectifier

Phase controlled rectifier applications include paper mills, textile mills using DC motor drives and DC motor control in steel mills.

- AC fed traction system using a DC traction motor.
- Electro-metallurgical and Electrochemical processes.
- Reactor controls.

- Magnet power supplies.
- Portable hand instrument drives.

- Flexible speed industrial drives.
- Battery charges.
- High voltage DC transmission.
- UPS (Uninterruptible power supply systems).

Operation of half converter with R and RL loads

Single Phase Half Wave Controlled Rectifier with 'R' load:

As shown in figure below primary of transformer is connected to ac mains supply with which SCR becomes forward bias in positive half cycle. T1 is triggered at an angle α , T1 conducts and voltage is applied across R.

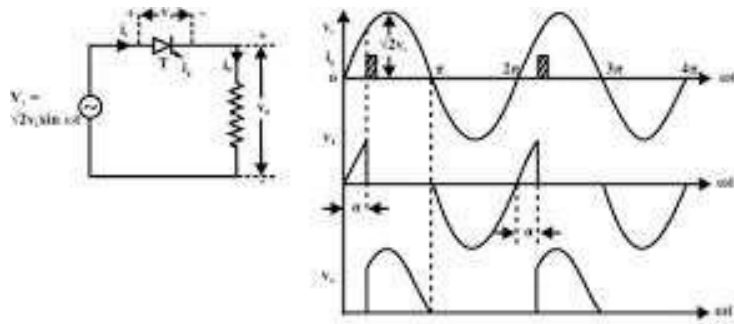


Figure: 2.3 Single phase half wave rectifier with R load with waveforms

The load current i_o flows through 'R' the waveforms for voltage & current are as shown above. As load is resistive, Output current is given as,

$$I_o = \frac{V_o}{R}$$

Hence shape of output current is same as output voltage

As T1 conducts only in positive half cycle as it is reversed bias in negative cycle, the ripple frequency of output voltage is-

fripple= 50 Hz (supply frequency) Average output voltage is given as,

$$V_o(Avg) = \frac{1}{T} \int_0^T V_o(\omega t) d\omega t$$

i.e Area under one cycle.

Therefore $T=2\pi$ & $V_o(\omega t) = V_m \sin \omega t$ from α to π & for rest of the period $V_o(\omega t)=0$

$$\begin{aligned} \therefore V_o(Avg) &= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin(\omega t) d\omega t \\ &= \frac{V_m}{2\pi} [-\cos \omega t]_{\alpha}^{\pi} \\ &= \frac{V_m}{2\pi} (1 + \cos \alpha) \end{aligned}$$

Power transferred to load,

$$P_o(Avg) = \frac{V_o^2(Avg)}{R}$$

Thus, power & voltage can be controlled by firing angle.

Single Phase Half Wave Controlled Rectifier with 'RL' load:

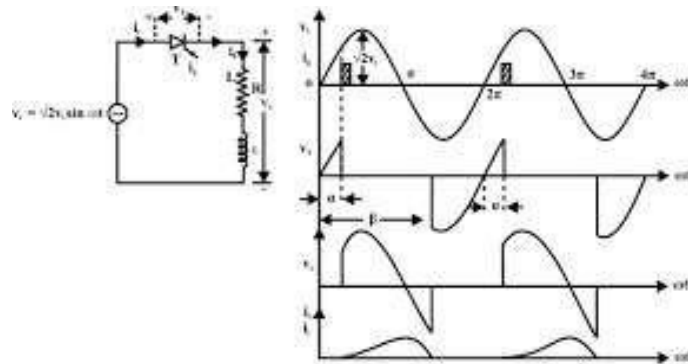


Figure: 2.4 Single phase half wave rectifier with RL load with waveforms

Figure above shows the single phase half wave rectifier with RL Load.

Normally motors are inductive loads $L =$ armature of field coil inductance

$R =$ Resistance of coil.

- In positive half cycle, SCR starts conduction at firing angle " α ".
- Drop across SCR is small & neglected so output voltage is equal to supply voltage.
- Due to ' R_L ' load, current through SCR increases slowly.
- At ' π ', supply voltage is at zero where load current is at its max value.
- In positive half cycle, inductor stores energy & that generates the voltage.
- In negative half cycle, the voltage developed across inductor, forward biases SCR & maintains its conduction.
- Basically with the property of inductance it opposes change in current.
- Output current & supply current flows in same loop, so all the time $i_o = i_s$.
- After π the energy of inductor is given to mains & there is flow of ' i_o '. The energy reduces as if gets consumed by circuit so current also reduces.
- At ' β ' energy stored in inductance is finished, hence ' i_o ' becomes zero & 'T1' turns off.
- ' i_o ' becomes zero from ' β ' to ' $2\pi + \alpha$ ' hence it is discontinuous conduction.

The average output voltage

$$V_{avg} = \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m \sin \omega t \, d(\omega t) = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta)$$

$$I = \frac{V_{avg}}{2\pi R} (\cos \alpha - \cos \beta)$$

$$\text{RMS load voltage } V_{or} = \left\{ \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2}$$

$$= \frac{V_m}{2\sqrt{\pi}} [(\beta - \alpha) - \frac{1}{2} \{ \sin 2\beta - \sin 2\alpha \}]^{1/2}$$

Single phase half controlled converter with RLE load

The diode D2 and D4 conducts for the positive and negative half cycle of the input voltage waveform respectively. On the other hand T1 starts conduction when it is fired in the positive half cycle of the input voltage waveform and continuous conduction till T3 is fired in the negative half cycle. Fig. shows the circuit diagram and the waveforms of a single phase half controlled converter supplying an R – L – E load.

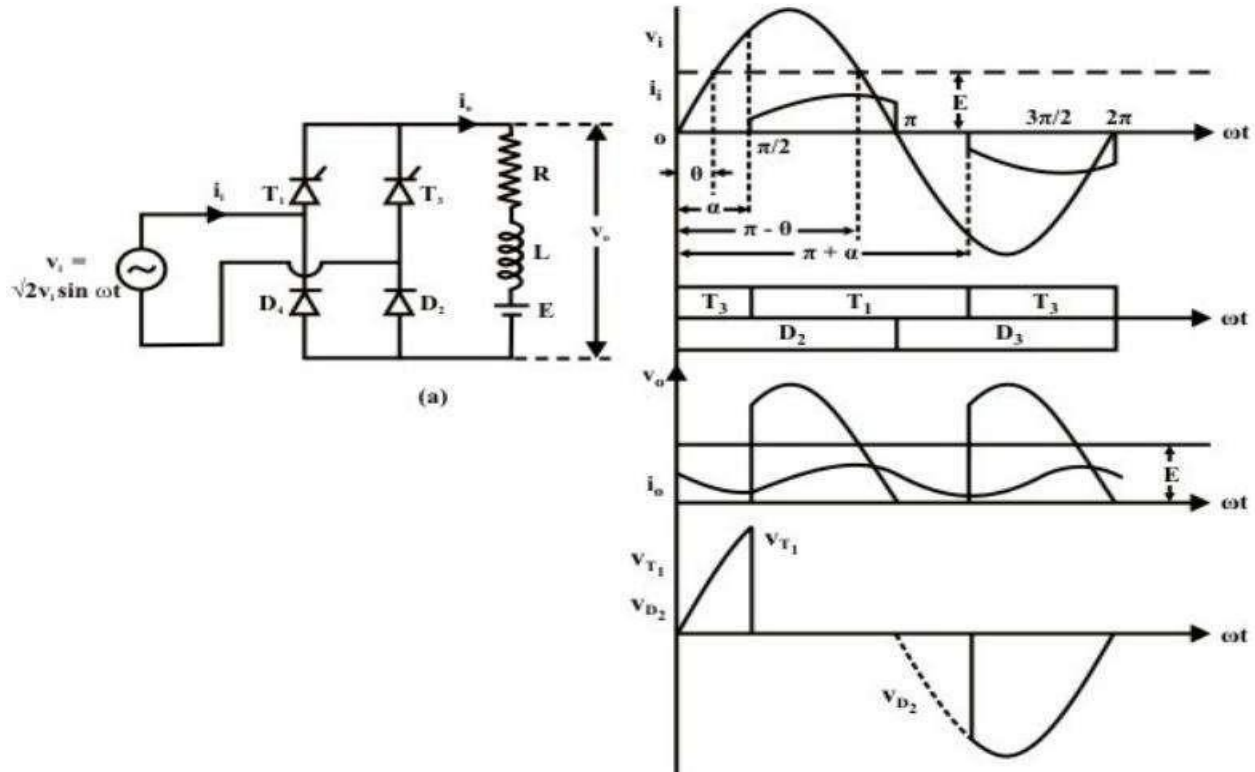


Figure: 2.5 single phase half controlled converter with RLE load

Referring to Fig T1 D2 starts conduction at $\omega t = \alpha$. Output voltage during this period becomes equal to

- i. At $\omega t = \pi$ as v_i tends to go negative D4 is forward biased and the load current commutates from D2 to D4 and freewheels through D4 and T1. The output voltage remains clamped to zero till T3 is fired at $\omega t = \pi + \alpha$. The T3 D4 conduction mode continues upto $\omega t = 2\pi$. Where upon load current again free wheels through T3 and D2 while the load voltage is clamped to zero. From the discussion in the previous paragraph it can be concluded that the output voltage (hence the output current) is periodic over half the input cycle. Hence

$$V_{oav} = \frac{1}{\pi} \int_0^{\pi} v_o d\omega t = \frac{1}{\pi} \int_{\alpha}^{\pi} \sqrt{2}V_i \sin \omega t d\omega t = \frac{\sqrt{2}V_i}{\pi} (1 + \cos\alpha)$$

$$I_{ov} = \frac{V_{oav} - E}{R} = \frac{\sqrt{2}V_i}{\pi R} (1 + \cos\alpha - \pi \sin\theta)$$

Single phase half controlled converter with RLE load and freewheeling diode

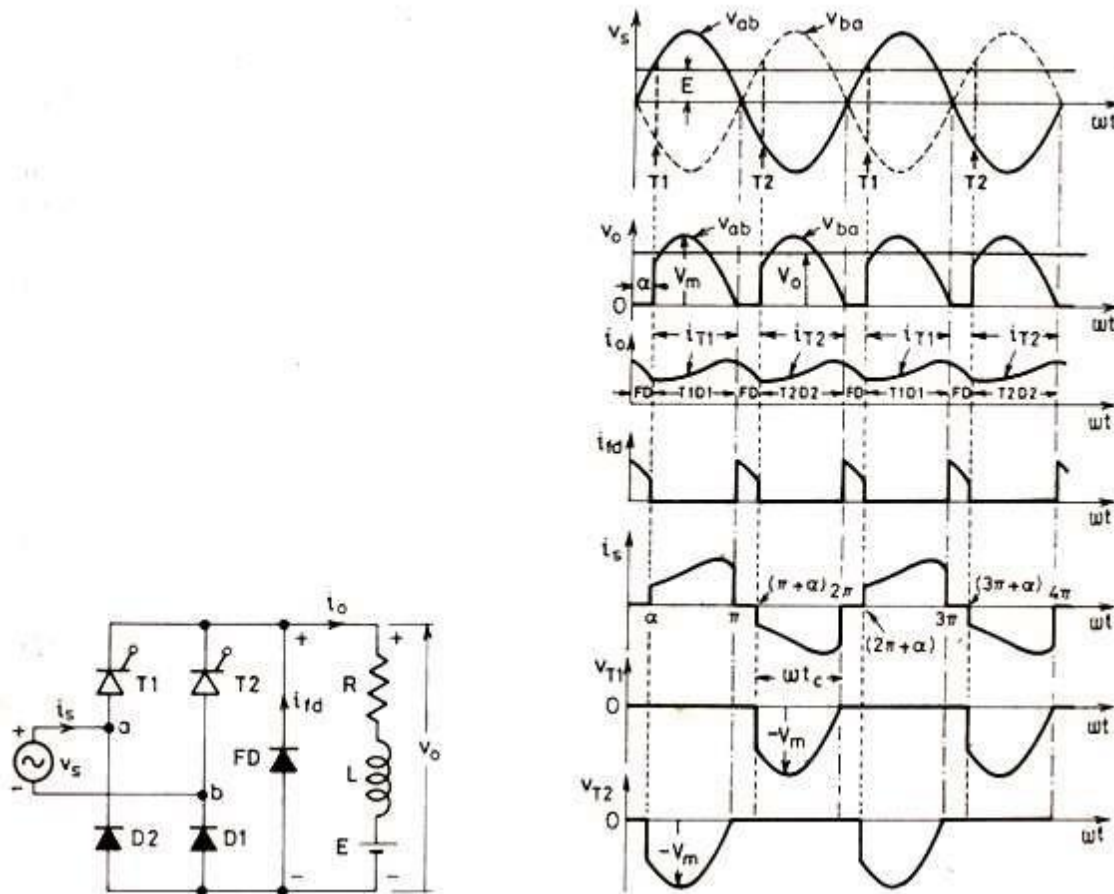


Figure: 2.6 single phase half controlled converter with RLE load and freewheeling diode

Single phase full wave controlled rectifier

Single Phase Full Wave Controlled Rectifier with 'R' load:

Figure below shows the Single phase Full Wave Controlled Rectifiers with R load

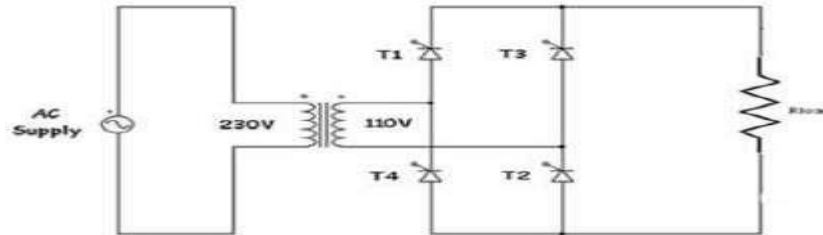


Figure: 2.7 single phase full converter circuit with R load

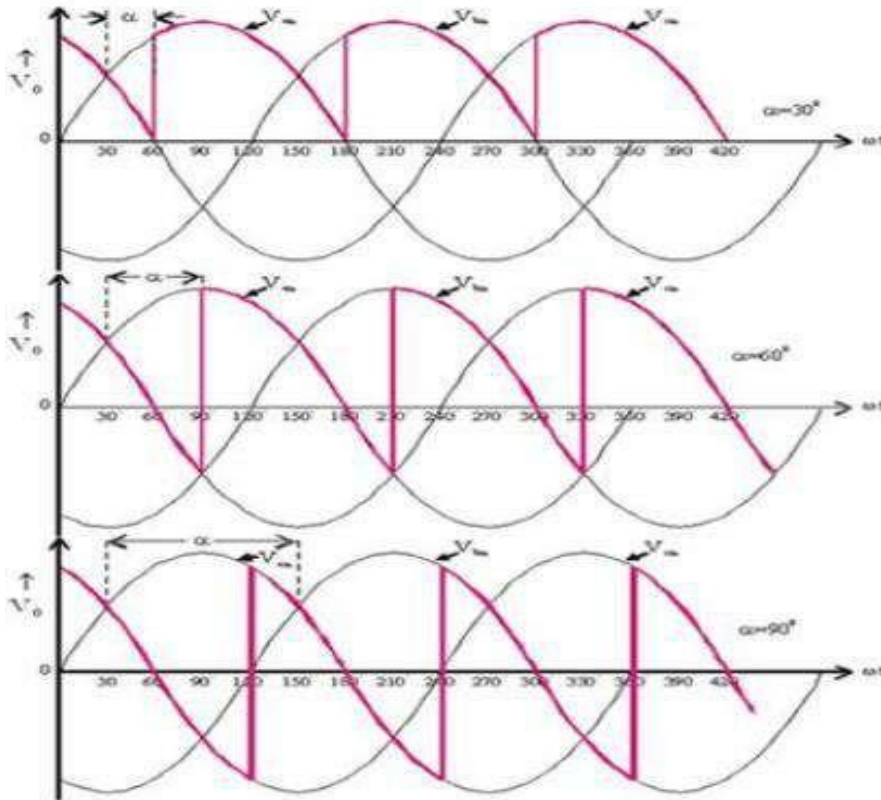


Figure: 2.8 single phase full converter circuit with R load input and output waveforms

•

The single phase fully controlled rectifier allows conversion of single phase AC into DC. Normally this is used in various applications such as battery charging, speed control of DC motors and front end of UPS(Uninterruptible Power Supply) and SMPS (Switched Mode Power Supply).

•

T

A

If four devices used are Thyristors. The turn-on instants of these devices are dependent on the firing signals that are given. Turn-off happens when the current through the device reaches zero and it is reversebiased at least for duration equal to the turn-off time of the device specified in the data sheet.

- In positive half cycle Thyristors T1 & T2 are fired at an angle α .

•

When T1 & T2 conducts $V_o = V_s$ $I_o = i_s = V_o/R = V_s/R$

- In negative half cycle of input voltage, SCR's T3 & T4 are triggered at an angle of $(\pi + \alpha)$
- Here output current & supply current are in opposite direction

$\therefore i_s = -i_o$

T3 & T4 becomes off at 2π .

$$V = \int_0^{\pi + \alpha} V_m \sin \omega t \, (\omega t) = \frac{2V_m}{\pi} \cos \alpha$$

Single Phase Full Wave Controlled Rectifier with 'RL' load:

Figure below shows Single phase Full Wave Controlled Rectifiers with RL load.

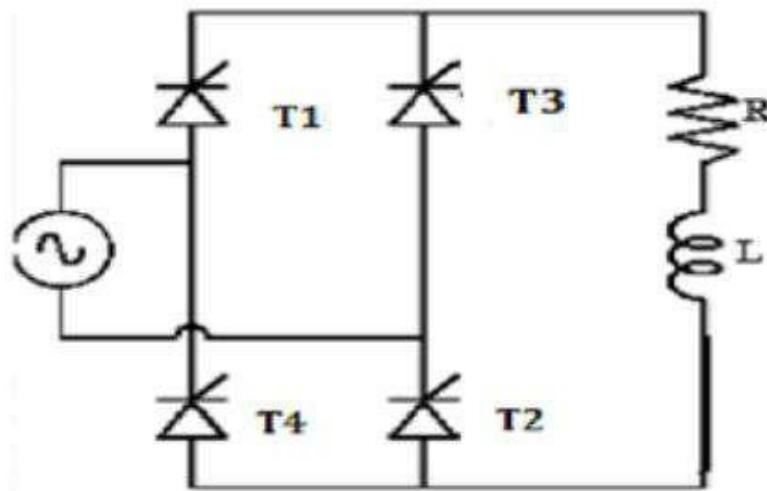


Figure: 2.9 single phase full converter circuit with RL load

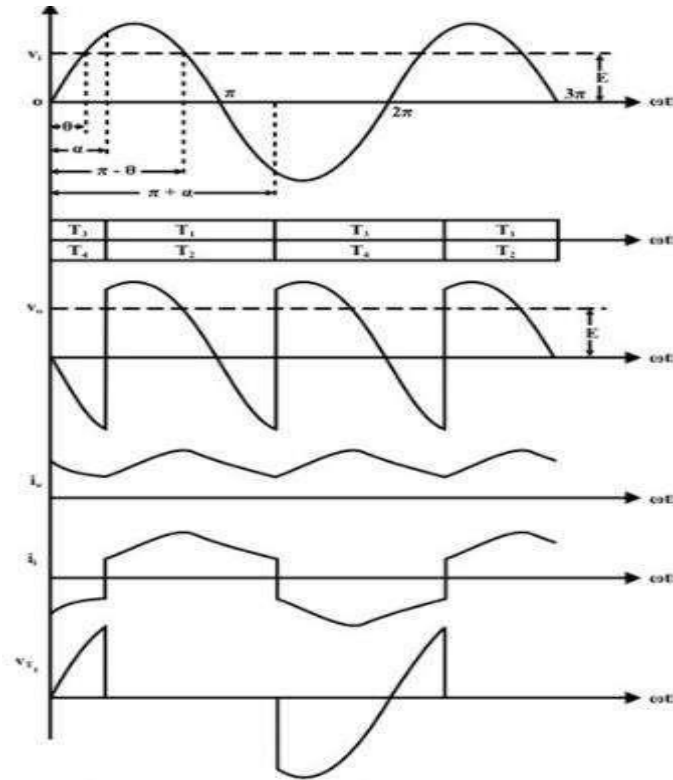


Figure: 2.10 single phase full converter circuit with RL load input and output waveforms

Operation of this mode can be divided between four modes

Mode 1 (α to π)

- In positive half cycle of applied ac signal, SCR's T1 & T2 are forward bias & can be turned on at an angle α .
- Load voltage is equal to positive instantaneous ac supply voltage. The load current is positive, ripple free, constant and equal to I_o .
- Due to positive polarity of load voltage & load current, load inductance will store energy.

Mode 2 (π to $\pi + \alpha$)

- At $\omega t = \pi$, input supply is equal to zero & after π it becomes negative. But inductance opposes any change through it.
- In order to maintain a constant load current & also in same direction. A self induced emf appears

across

'L' as shown.

- Due to this induced voltage, SCR's T1 & T2 are forward bias in spite the negative supply voltage.
- The load voltage is negative & equal to instantaneous ac supply voltage whereas load current is positive.
- Thus, load acts as source & stored energy in inductance is returned back to the ac supply.

Mode 3 ($\pi+\alpha$ to 2π)

- At $\omega t=\pi+\alpha$ SCR's T3 & T4 are turned on & T1, T2 are reversed bias.
- Thus, process of conduction is transferred from T1,T2 to T3,T4.
- Load voltage again becomes positive & energy is stored in inductor
- T3, T4 conduct in negative half cycle from $(\pi+\alpha)$ to 2π
- With positive load voltage & load current energy gets stored

Mode 4 (2π to $2\pi+\alpha$)

- At $\omega t=2\pi$, input voltage passes through zero.
- Inductive load will try to oppose any change in current if in order to maintain load current constant & in the same direction.
- Induced emf is positive & maintains conducting SCR's T3 & T4 with reverse polarity also.

Thus VL is negative & equal to instantaneous ac supply voltage. Whereas load current continues to be positive.

- Thus load acts as source & stored energy in inductance is returned back to ac supply
- At $\omega t=\alpha$ or $2\pi+\alpha$, T3 & T4 are commutated and T1,T2 are turned on.

$$V = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t (wt) = \frac{2V_m}{\pi} \cos \alpha$$

Single phase fully controlled converters with RLE load

The circuit diagram of a full wave bridge rectifier using thyristors is shown in figure below. It consists of four SCRs which are connected between single phase AC supply and a load.

This rectifier produces controllable DC by varying conduction of all SCRs.

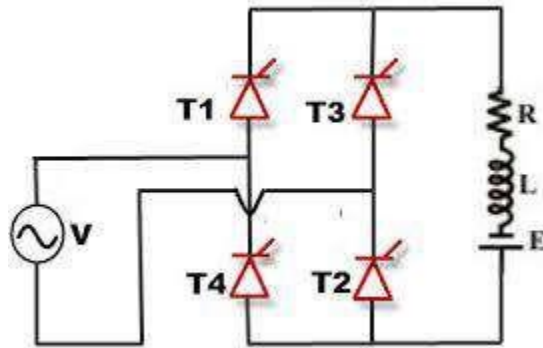


Figure: 2.11 single phase full converter circuit with RLE load

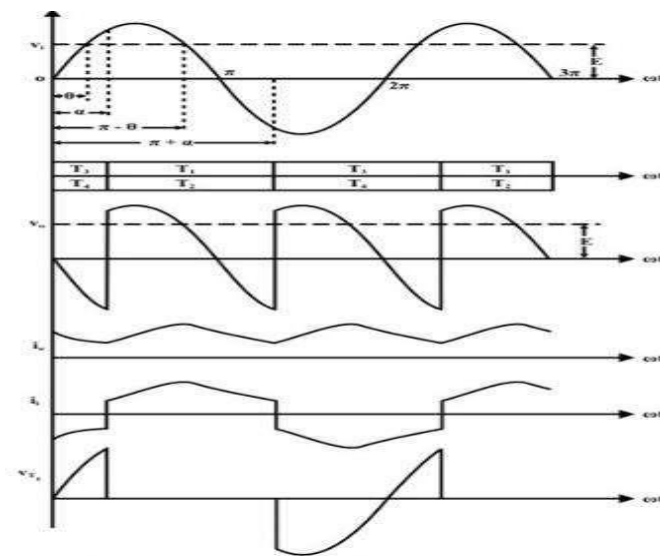


Figure: 2.12 single phase full converter circuit with RLE load input and output waveforms

In positive half-cycle of the input, Thyristors T1 and T2 are forward biased while T3 and T4 are reversebiased. Thyristors T1 and T2 are triggered simultaneously at some firing angle in the positive half cycle, and T3 and T4 are triggered in the negative half cycle.

The load current starts flowing through them when they are in conduction state. The load for this converter can be RL or RLE depending on the application.

By varying the conduction of each thyristor in the bridge, the average output of this converter gets controlled. The average value of the output voltage is twice that of half-wave rectifier.

The average output voltage is

$$V = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t \, (\omega t) = \frac{2V_m}{\pi} \cos \alpha$$

Line commutated converters

For single phase half wave converter

1. Average DC load voltage: (V_{oavg})

$$V_{oavg} = \frac{1}{T} \int_0^T V_m \sin \omega t \, d(\omega t) \quad \text{where } T \text{ is time period}$$

$$V_{oavg} = \frac{1}{2\pi} \left[\int_{\alpha}^{\pi} V_m \sin \omega t \, d(\omega t) + \int_{\pi}^{2\pi+\alpha} 0 \, d(\omega t) \right]$$

$$= \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \, d(\omega t)$$

$$= \frac{V_m}{2\pi} [-\cos \omega t]_{\alpha}^{\pi}$$

$$= \frac{V_m}{2\pi} [\cos \pi - \cos \alpha]$$

$$= \frac{V_m}{2\pi} [1 + \cos \alpha]$$

$$I_{oavg} = \frac{V_{oavg}}{R}$$

If $\alpha = 180^\circ$ $V_{oavg} = 0$

2. Average DC load current is given as

$$I_{oavg} = \frac{V_{oavg}}{R}$$

$$I_{oavg} = \frac{V_m}{2\pi R} [1 + \cos \alpha]$$

3. RMS load voltage

$$V_{\text{rms}} = \left\{ \int_0^T V_m^2 \sin^2 \omega t \, dt \right\}^{1/2}$$

$$V_{\text{rms}} = \left\{ \int_{\frac{\alpha}{\pi}}^{\frac{2\pi}{\pi}} V_m^2 \sin^2 \omega t \, d(\omega t) \right\}^{1/2}$$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{\pi}} \left[\pi - \alpha + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

$$I_{\text{rms}} = \frac{V_m}{R} \left[\pi - \alpha + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

If $\alpha = 180^\circ$ $V_{\text{rms}} = 0$

The RMS voltage may be varied from 0 to $\frac{V_m}{\sqrt{2}}$ by varying α from 180° to 0°

4. Power delivered to the resistive load is given

$$P_L = (\text{RMS load voltage}) (\text{RMS load current})$$

$$= V_{\text{rms}} \times I_{\text{rms}}$$

$$= \frac{V_m^2}{R} \left[\pi - \alpha + \frac{1}{2} \sin 2\alpha \right]$$

5. Input volt amperes = (RMS source voltage) (RMS line current)

$$= V_s I_{\text{rms}}$$

$$= \frac{V_s \sqrt{2} V_m}{R \sqrt{\pi}} \left[\pi - \alpha + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

$$= \frac{V_s^2}{\sqrt{2\pi} R} \left[\pi - \alpha + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

=

6. Input power factor: It is defined as the ratio of total mean input power to the total rms input volt amperes

$$\begin{aligned} \text{Input power factor} &= \frac{\frac{\sqrt{2}V_s}{2\sqrt{\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}}{V_s} \\ &= \frac{1}{\sqrt{2\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2} \end{aligned}$$

Form factor: Form factor is defined as the ratio of RMS voltage to the average DC voltage

$$\text{Form factor} = \frac{V_{\text{rms}}}{V_{\text{avg}}}$$

8. Effective value of the AC component of the output voltage

$$V_{\text{ac}} = [V_{\text{rms}}^2 - V_{\text{avg}}^2]^{1/2}$$

9. Ripple factor (R_f)

It is defined as the ratio of AC component to the DC. Where ripple is the amount of AC

$$R_f = \frac{V_{\text{ac}}}{V_{\text{avg}}} = \frac{[V_{\text{rms}}^2 - V_{\text{avg}}^2]^{1/2}}{V_{\text{avg}}} = \left[\left(\frac{V_{\text{rms}}}{V_{\text{avg}}} \right)^2 - 1 \right]^{1/2} = \sqrt{F^2 - 1}$$

component present in DC component

10. Transformer Utilization Factor (TUF):

It is defined as the ratio of output DC power to the volt ampere rating of the transformer

$$\text{TUF} = \frac{P_{\text{dc}}}{\text{VA rating of secondary winding of the transformer}}$$

11. Rectifier efficiency:

It is defined as the ratio of output DC power to the input ac power

$$\eta = \frac{V_{avg}I_{avg}}{V_{rms}I_{rms}}$$

12. Peak inverse voltage (PIV):

It is defined as the maximum voltage that an SCR can be subjected to in the reverse biased condition

In the case of Half wave rectifier it is V_m


Effect of source inductance in single phase rectifier

Fig. below shows a single phase fully controlled converter with source inductance. For simplicity it has been assumed that the converter operates in the continuous conduction mode. Further, it has been assumed that the load current ripple is negligible and the load can be replaced by a dc current source the magnitude of which equals the average load current. Fig. shows the corresponding waveforms

It is assumed that the Thyristors T3 and T4 were conducting at $t = 0$. T1 and T2 are fired at $\omega t = \alpha$. If

there were no source inductance T3 and T4 would have commutated as soon as T1 and T2 are turned ON.

The input current polarity would have changed instantaneously. However, if a source inductance is present the commutation and change of input current polarity cannot be instantaneous. Therefore, when T1 and T2 are turned ON T3 and T4 does not commutate immediately. Instead, for some interval all four Thyristors continue to conduct as shown in Fig. 2.14. This interval is called “overlap” interval.

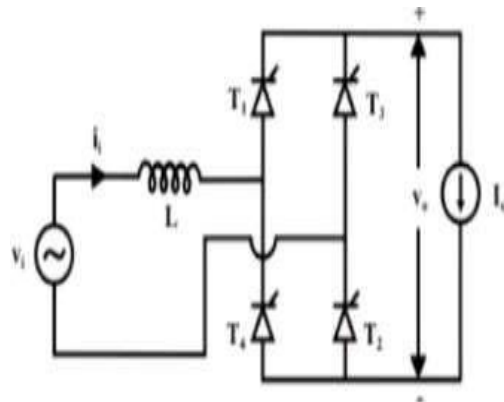

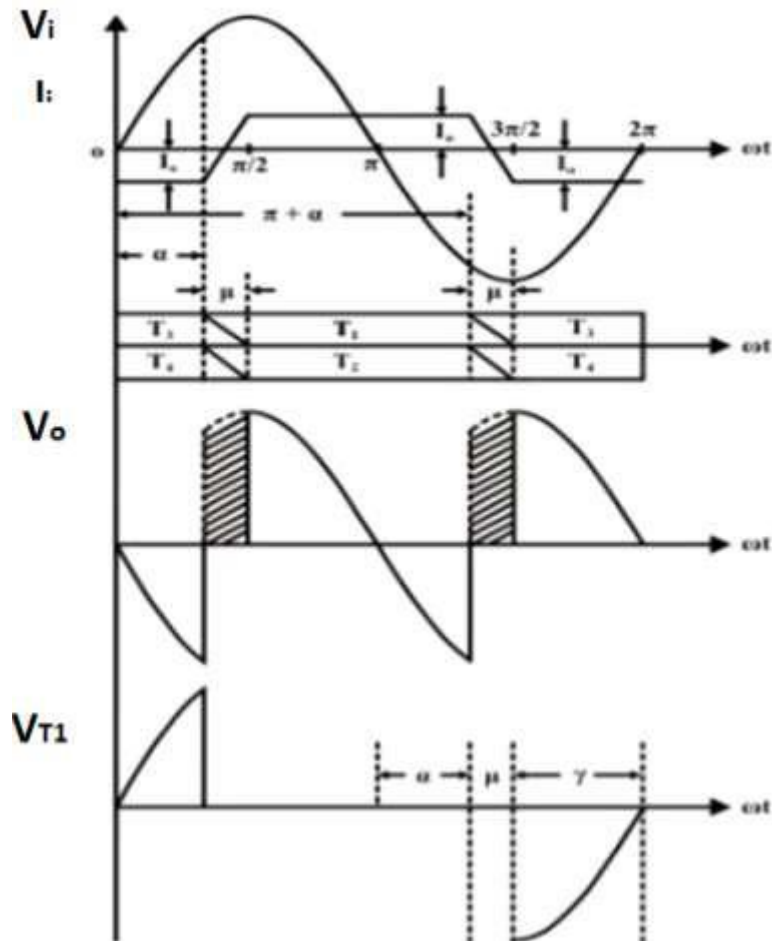


Figure: 2.14 single phase full converter output waveforms with source inductance

1. During overlap interval the load current freewheels through the thyristors and the output voltage is clamped to zero. On the other hand, the input current starts changing polarity as the current through T1 and T2 increases and T3 T4 current decreases. At the end of the overlap interval the current through T3 and T4 becomes zero and they commute, T1 and T2 starts conducting the full load current
2. The same process repeats during commutation from T1 T2 to T3T4 at $\omega t = \pi + \alpha$. From Fig. 2.14 it is clear that, commutation overlap not only reduces average output dc voltage but also reduces the extinction angle γ which may cause commutation failure in the inverting mode of operation if α is very close to 180° .
3. In the following analysis an expression of the overlap angle " μ " will be determined. From the equivalent circuit of the converter during overlap period.

$$L \frac{di_i}{dt} = v_i \text{ for } \alpha \leq \omega t + \mu$$

$$i_i(\omega t = \alpha) = -I_0$$

$$i_i = I - \frac{\sqrt{2}V_i}{\omega L} \cos \omega t$$

$$\therefore i_i|_{\omega t = \alpha} = I - \frac{\sqrt{2}V_i}{\omega L} \cos \alpha = -I_0$$

$$I = \frac{\sqrt{2}V_i}{\omega L} \cos \alpha - I_0$$

$$\therefore i_i = \frac{\sqrt{2}V_i}{\omega L} (\cos \alpha - \cos \omega t) - I_0$$

$$\text{at } \omega t = \alpha + \mu \quad i_i = I_0$$

$$I_0 = \frac{\sqrt{2}V_i}{\omega L} (\cos \alpha - \cos(\alpha + \mu)) - I_0$$

$$\therefore \cos \alpha - \cos(\alpha + \mu) = \frac{\sqrt{2}\omega L}{V_0} I_0$$

$$V_0 = \frac{I}{\pi} \int_{\alpha}^{\alpha+\pi} V_i d\omega t$$

$$\text{or } V_0 = \frac{I}{\pi} \int_{\alpha+\mu}^{\alpha+\pi} \sqrt{2}v_i \sin \omega t d\omega t$$

$$= \frac{\sqrt{2}v_i}{\pi} [\cos(\alpha + \mu) - \cos(\pi + \alpha)]$$

$$= \frac{\sqrt{2}v_i}{\pi} [\cos \alpha + \cos(\alpha + \mu)]$$

$$\therefore V_0 = 2\sqrt{2} \frac{v_i}{\pi} [\cos \alpha - \cos(\alpha + \mu)]$$

$$\therefore V_0 = \frac{2\sqrt{2}}{\pi} v_i \cos \alpha - \frac{2}{\pi} \omega L I_0$$

The Equation can be represented by the following equivalent circuit

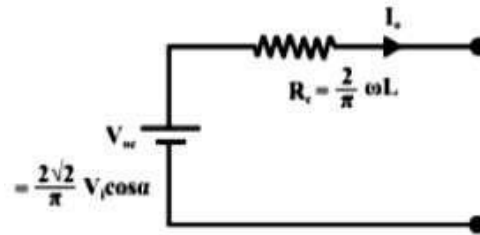


Figure: 2.15 Equivalent circuit of the given equation

Equivalent circuit representation of the single phase fully controlled rectifier with source inductance

The simple equivalent circuit of Fig. 2.15 represents the single phase fully controlled converter with source inductance as a practical dc source as far as its average behavior is concerned. The open circuit voltage of this practical source equals the average dc output voltage of an ideal converter (without source inductance) operating at a firing angle of α . The voltage drop across the internal resistance “RC” represents the voltage lost due to overlap shown in Fig. 2.14 by the hatched portion of the V_o waveform. Therefore, this is called the “Commutation resistance”. Although this resistance accounts for the voltage drop correctly there is no power loss associated with this resistance since the physical process of overlap does not involve any power loss. Therefore this resistance should be used carefully where power calculation is involved.

Operation of three phase half wave rectifier with R and RL loads

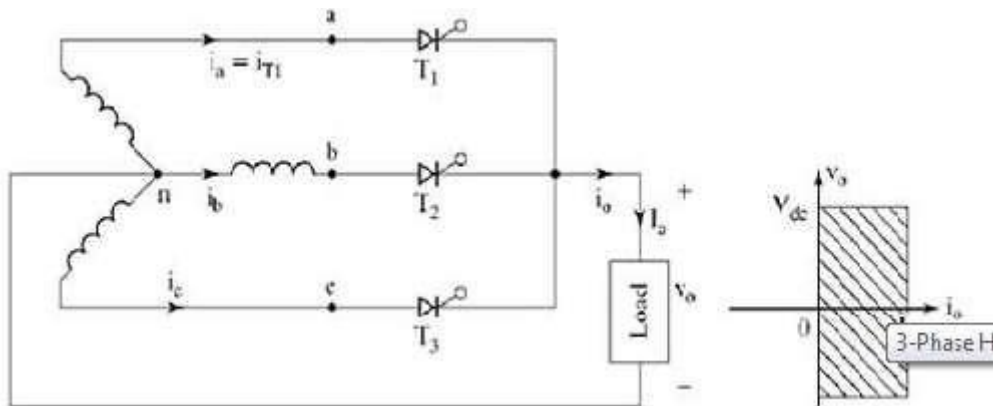


Figure: 2.16 circuit diagram three phase half wave rectifier

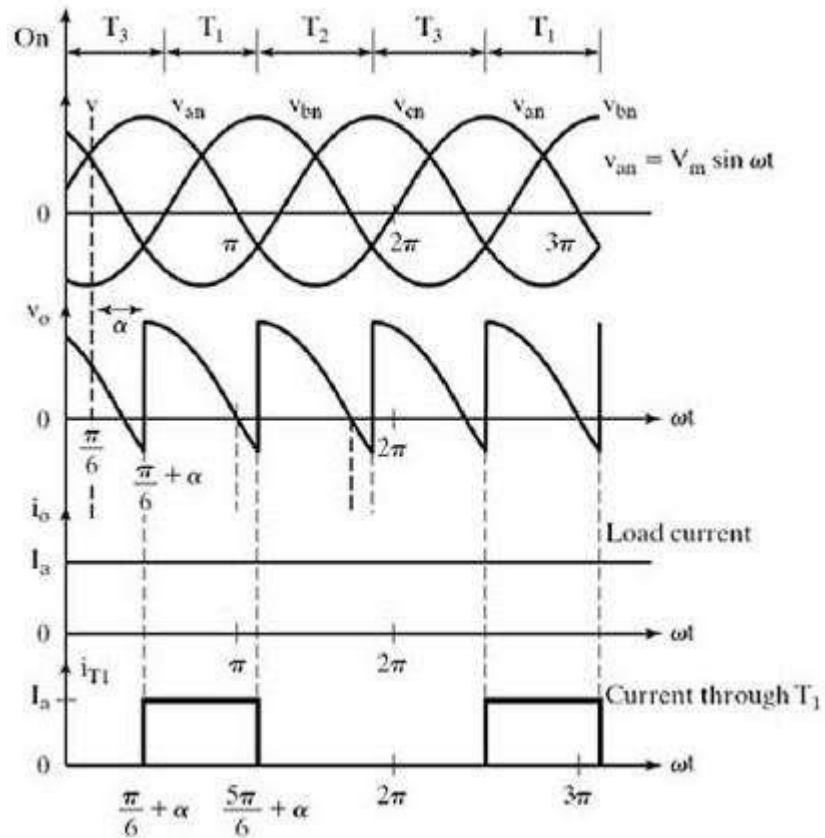


Figure: 2.17 input and output waveforms of three phase half wave rectifier

Three phase supply voltage equations

We define three line neutral voltages (3 phase voltages) as follows $V_{RN} = V_{an} = V_m \sin \omega t$

$\sin \omega t$ where V_m is the maximum voltage

$V_{RN} = V_{an} = V_m \sin \omega t$ where V_m is the maximum voltage

$$V_{YN} = V_{bn} = V_m \sin \left(\omega t - \frac{2\pi}{3} \right)$$

$$V_{BN} = V_{cn} = V_m \sin \left(\omega t - \frac{4\pi}{3} \right)$$

The **3-phase half wave converter** combines three **single phase half wave controlled rectifiers in one** single circuit feeding a common load. The thyristor T_1 in series with one of the supply phase windings ' $a-n$ ' acts as one half wave controlled rectifier. The second thyristor T_2 in series with the supply phase winding ' $b-n$ ' acts as the second half wave controlled rectifier. The third thyristor T_3 in series with the supply phase winding acts as the third half wave controlled rectifier.

The 3-phase input supply is applied through the star connected supply transformer as shown in the figure. The common neutral point of the supply is connected to one end of the load while the other end of the load connected to the common cathode point.

When the thyristor T_1 is triggered at $\omega t = (\pi/6 + \alpha) = (30^\circ + \alpha)$, the phase voltage V_{an} appears across the load when T_1 conducts. The load current flows through the supply phase winding ' $a-n$ ' and through thyristor T_1 as long as T_1 conducts.

When thyristor T_2 is triggered at $\omega t = (5\pi/6 + \alpha)$, T_1 becomes reverse biased and turns-off. The load current flows through the thyristor and through the supply phase winding ' $b-n$ '. When T_2 conducts the phase voltage v_{bn} appears across the load until the thyristor T_3 is triggered.

When the thyristor T_3 is triggered at $\omega t = (3\pi/2 + \alpha) = (270^\circ + \alpha)$, T_2 is reversed biased and hence T_2 turns-off. The phase voltage V_{an} appears across the load when T_3 conducts.

When T_1 is triggered again at the beginning of the next input cycle the thyristor T_3 turns off as it is reverse biased naturally as soon as T_1 is triggered. The figure shows the 3-phase input supply voltages, the output voltage which appears across the load, and the load current assuming a constant and ripple free load current for a highly inductive load and the current through the thyristor T_1 .

For a purely resistive load where the load inductance ' $L = 0$ ' and the trigger angle $\alpha > (\pi/6)$, the load current appears as discontinuous load current and each thyristor is naturally commutated when the polarity of the corresponding phase supply voltage reverses.

The frequency of output

ripple frequency for a **3-phase half wave converter** is f_s , where f_s is the input supply frequency.³

The **3-phase half wave converter** is not normally used in practical converter systems because of the disadvantage that the supply current waveforms contain dc components

(i.e., the supply current waveforms have an average or dc value).

The reference phase voltage is $v_{RN}=v_{an}=V_m\sin\omega t$. The trigger angle is measured from the cross over points of the 3-phase supply voltage waveforms. When the phase supply voltage V_{an} begins its positive half cycle at $\omega t=0$, the first cross over point appears at $\omega t=(\pi/6)$ radians 30° .

The trigger angle α for the thyristor T_1 is measured from the cross over point at . The thyristor T_1 is forward biased during the period $\omega t=30^\circ$ to 150° , when the phase supply voltage v_{an} has higher amplitude than the other phase supply voltages. Hence T_1 can be triggered between 30° to 150° . When the thyristor T_1 is triggered at a trigger angle α , the average or dc output voltage for continuous load current is calculated using the equation

$$\begin{aligned} V_{avg} &= \frac{3}{2\pi} \int_{\frac{\pi}{6}+\alpha}^{\frac{5\pi}{6}+\alpha} V_m \sin \omega t \, d(\omega t) \\ &= \frac{3V_m}{2\pi} \left[-\cos \alpha \right]_{\frac{\pi}{6}+\alpha}^{\frac{5\pi}{6}+\alpha} \\ &= \frac{3\sqrt{3}V_m}{2\pi} \cos \alpha \\ &= \frac{3V_{ml}}{2\pi} \cos \alpha \end{aligned}$$

Operation of three phase half controlled rectifier with R and RL loads


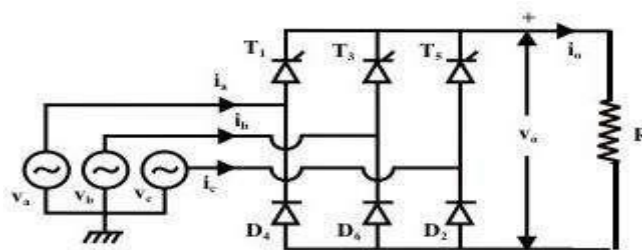


Figure: 2.18 circuit diagram three phase half controlled rectifier

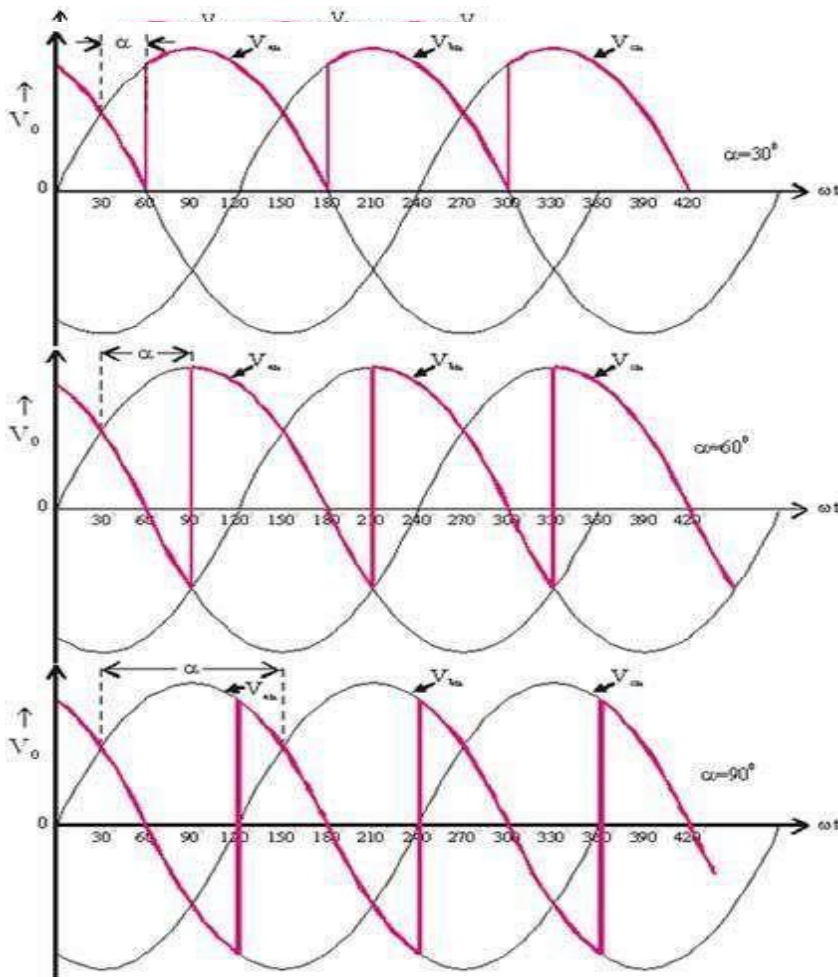Three phase half wave controlled rectifier output voltage waveforms



Three single phase half wave converters can be connected to form a three phase half wave converter. Similarly three phase semi converter uses 3 SCRs T_1, T_3 & T_5 and 3 diodes D_2, D_4 & D_6 . In the circuit shown above when any device conducts, line voltage is applied across load. so line voltage are necessary to draw Phase shift between two line voltages is 60 degree & between two phase voltages it is 120 degree Each phase & line voltage is sine wave with the frequency of 50 Hz. R,Y,B are phase voltages with respect to 'N'.

In the case of a **three-phase half wave controlled** rectifier with resistive load, the thyristor T_1 is triggered at $\omega t = (30^\circ + \alpha)$ and T_1 conducts up to $\omega t = 180^\circ = \pi$ radians. When the phase supply voltage decreases to zero at $\omega t = 180^\circ$, the load current falls to zero and the thyristor T_1 turns off. Thus T_1 conducts from $\omega t = (30^\circ + \alpha)$ to (180°) .

Operation of three phase fully controlled rectifier with R and RL loads

Three phase full converter is a fully controlled bridge controlled rectifier using six thyristors connected in the form of a full wave bridge configuration. All the six thyristors are controlled switches which are turned on at a appropriate times by applying suitable gate trigger signals.

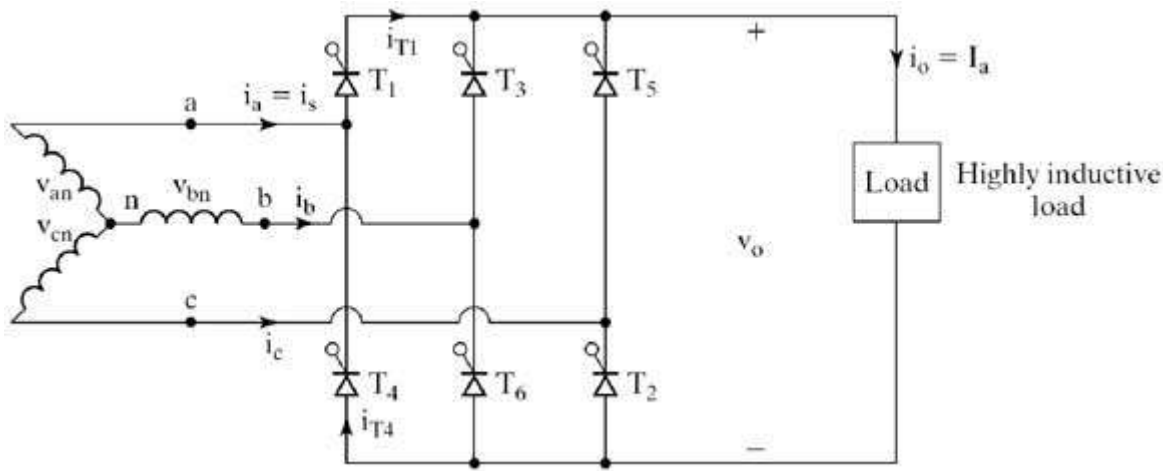


Figure: 2.20 circuit diagram three phase fully controlled rectifier with R and RL load

At $\omega t = (\pi/6 + \alpha)$, thyristor is already conducting when the thyristor is turned on by applying the gating signal to the gate of . During the time period $\omega t = (\pi/6 + \alpha)$ to $(\pi/2 + \alpha)$, thyristors and conduct together and the line to line supply voltage appears across the load.

At $\omega t = (\pi/2 + \alpha)$, the thyristor T_2 is triggered and T_6 is reverse biased immediately and T_6 turns off due to natural commutation. During the time period $\omega t = (\pi/2 + \alpha)$ to $(5\pi/6 + \alpha)$, thyristor T_1 and T_2 conduct together and the line to line supply voltage appears across the load.

The thyristors are numbered in the circuit diagram corresponding to the order in which they are triggered. The trigger sequence (firing sequence) of the thyristors is 12, 23, 34, 45, 56, 61, 12, 23, and so on. The figure shows the waveforms of three phase input supply voltages, output voltage, the thyristor current through T_1 and T_4 , the supply current through the line 'a'.

We define three line neutral voltages (3 phase voltages) as follows

$$V_{RN} = V_{an} = V_m \sin \omega t \text{ where } V_m \text{ is the maximum voltage}$$

$$V_{YN} = V_{bn} = V_m \sin \left(\omega t - \frac{2\pi}{3} \right)$$

$$V_{BN} = V_{cn} = V_m \sin \left(\omega t - \frac{4\pi}{3} \right)$$

The corresponding line to line voltages are

$$V_{RY} = V_{ab} = V_{an} - V_{bn} = \sqrt{3} V_m \sin \left(\omega t + \frac{\pi}{6} \right)$$

$$V_{YB} = V_{bc} = V_{bn} - V_{cn} = \sqrt{3} V_m \sin \left(\omega t - \frac{\pi}{2} \right)$$

$$V_{BR} = V_{ca} = V_{cn} - V_{an} = \sqrt{3} V_m \sin \left(\omega t + \frac{\pi}{2} \right)$$

To derive an expression for the average output voltage of **three phase full converter** with highly inductive load assuming continuous and constant load current

The output load voltage consists of 6 voltage pulses over a period of 2π radians, hence the average output voltage is calculated as


$$V_{avg} = \frac{6}{2\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \alpha} V_{od}(\omega t)$$

$$V_o = V_{ab} = \sqrt{3} V_m \sin \left(\omega t + \frac{\pi}{6} \right)$$

$$V_{avg} = \frac{3}{\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{\pi}{2} + \alpha} \sqrt{3} V_m \sin \left(\omega t + \frac{\pi}{6} \right) d(\omega t)$$


$$= \frac{3\sqrt{3}V_m}{\pi} \cos \alpha$$

$$= \frac{3V_{ml}}{\pi} \cos \alpha$$

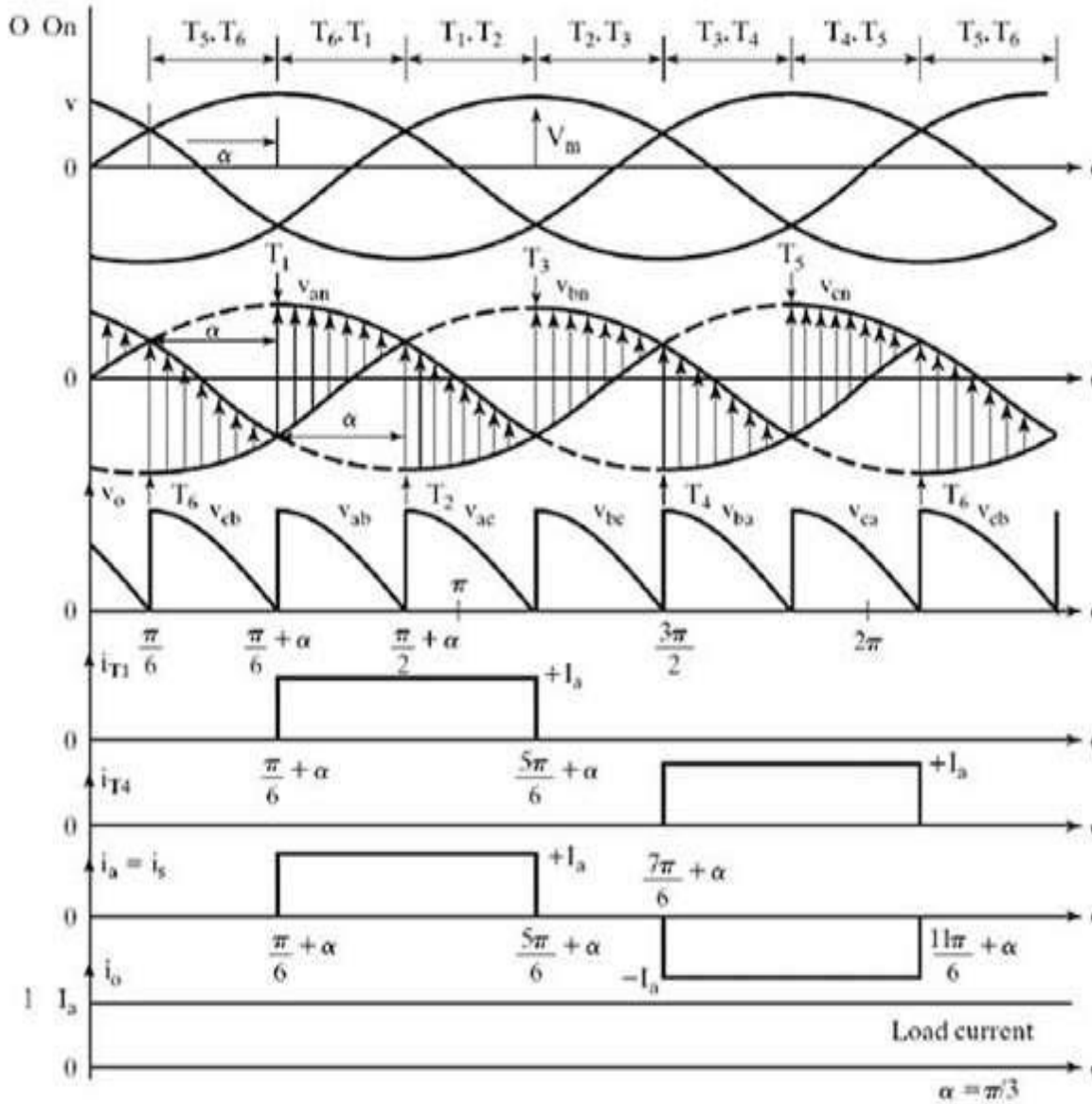

Operation of three phase half wave rectifier with RLE loads

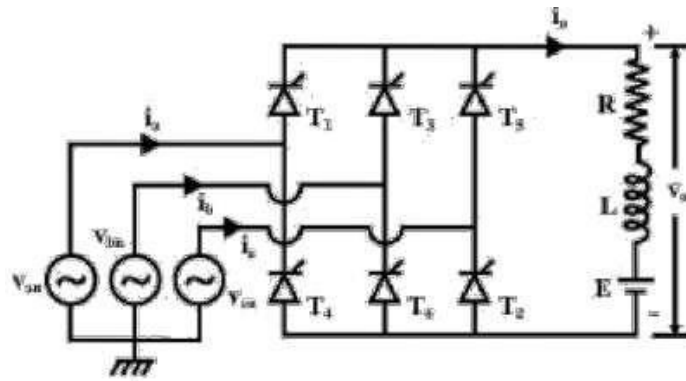A three phase fully controlled converter is obtained by replacing all the six diodes of an uncontrolled converter by six thyristors as shown in Figure



For any current to flow in the load at least one device from the top group (T1, T3, T5) and one from the bottom group (T2, T4, T6) must conduct. It can be argued as in the case of an uncontrolled converter only one device from these two groups will conduct.

Then from symmetry consideration it can be argued that each thyristor conducts for 120° of the input cycle. Now the thyristors are fired in the sequence $T1 \rightarrow T2 \rightarrow T3 \rightarrow T4 \rightarrow T5 \rightarrow T6 \rightarrow T1$ with 60° interval between each firing. Therefore thyristors on the same phase leg are fired at an interval of 180° and hence can not conduct simultaneously. This leaves only six possible conduction mode for the converter in the continuous conduction mode of operation. These are T1T2, T2T3, T3T4, T4T5, T5T6, T6T1. Each conduction mode is of 60° duration and appears in the sequence mentioned. Each of these line voltages can be associated with the firing of a thyristor with the help of the conduction table-1. For example the thyristor T1 is fired at the end

of T5 T6 conduction interval. During this period the voltage across T1 was v_{ac} . Therefore T1 is fired α

angle after the positive going zero crossing of v_{ac} . similar observation can be made about other thyristors.

Fig. 2.23 shows the waveforms of different variables. To arrive at the waveforms it is necessary to draw the conduction diagram which shows the interval of conduction for each thyristor and can be drawn with the help of the phasor diagram of fig. 2.22. If the converter firing angle is α each thyristor is fired " α "

angle after the positive going zero crossing of the line voltage with which it's firing is

associated. Once the conduction diagram is drawn all other voltage waveforms can be drawn from the line voltage waveforms and from the conduction table of fig. 2.22. Similarly line currents can be drawn from the output current and the conduction diagram. It is clear from the waveforms that output voltage and current waveforms are periodic over one sixth of the input cycle. Therefore this converter is also called

the “six pulse” converter. The input current on the other hand contains only odds harmonics of the input frequency other than the triplex (3rd, 9th etc.) harmonics. The next section will analyze the operation of this converter in more details.



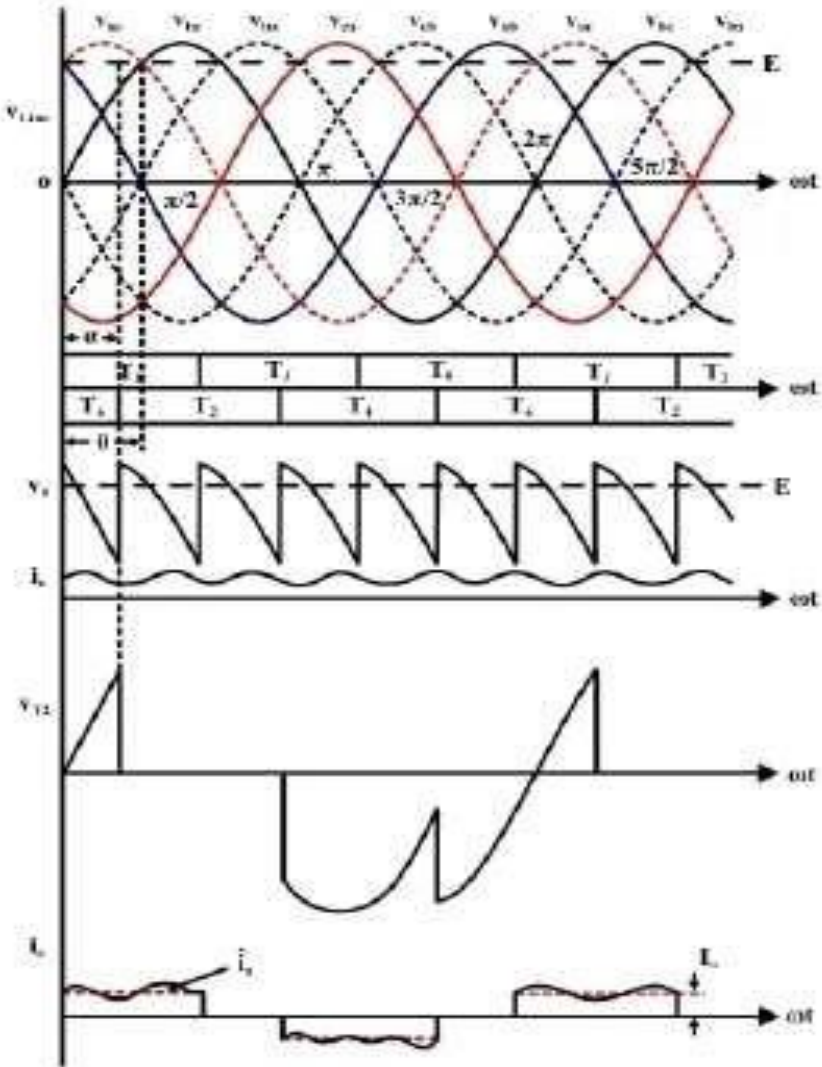
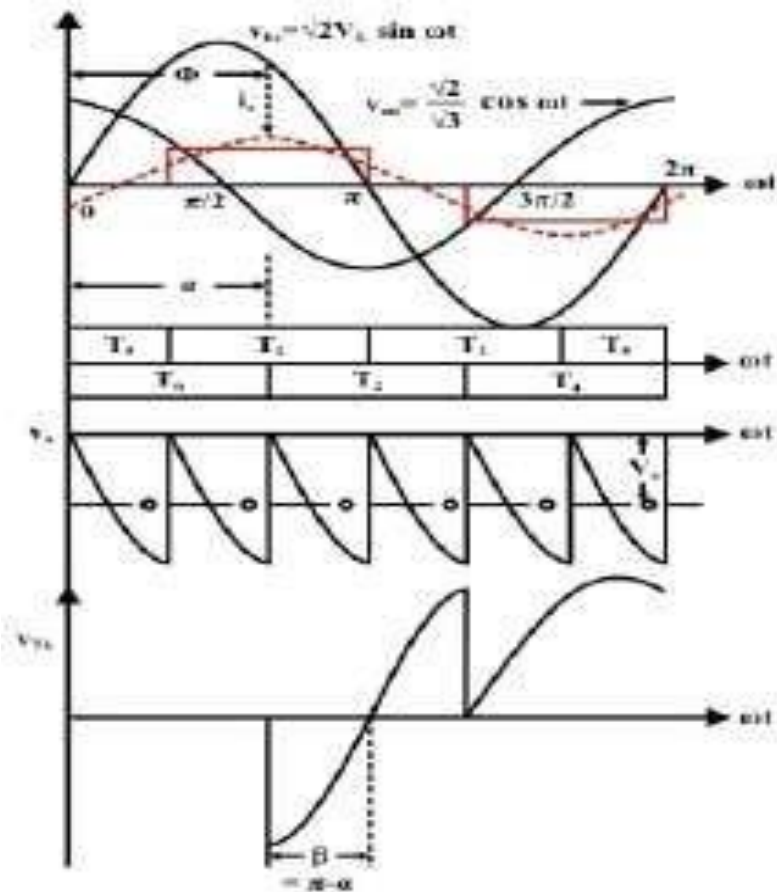


Figure: 2.23 Input and output waveforms of three phase fully controlled rectifier in rectifier mode

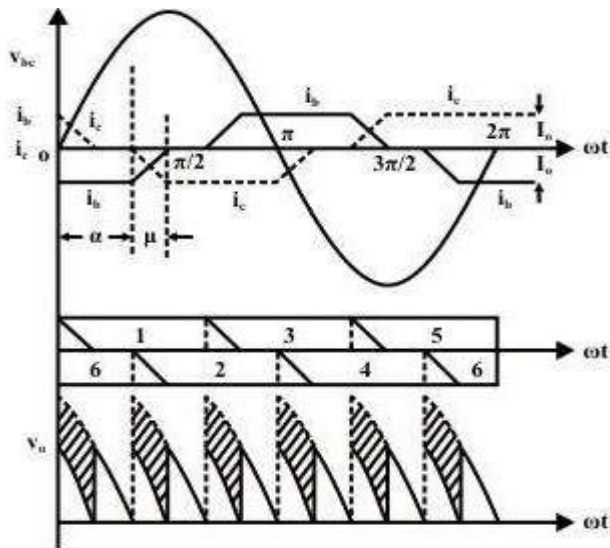

Effect of source inductance in three phase rectifiers

The three phase fully controlled converter was analyzed with ideal source with no internal impedance. When the source inductance is taken into account, the qualitative effects on the performance of the converter is similar to that in the case of a single phase converter. Fig. 2.25 shows such a converter. As in the case of a single phase converter the load is assumed to be highly inductive such that the load can be replaced by a current source.

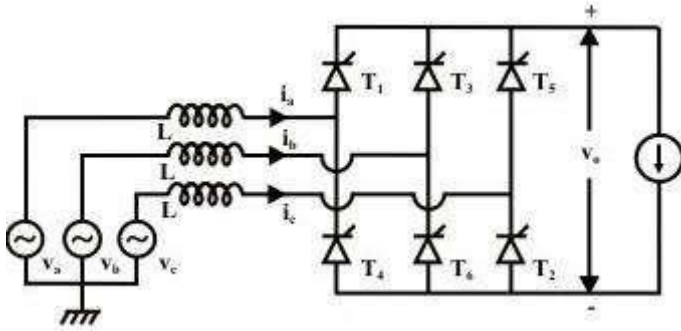

As in the case of a single phase converter, commutations are not instantaneous due to the presence of source inductances. It takes place over an overlap period of " μ_1 " instead. During the overlap period three thyristors instead of two conducts. Current in the outgoing thyristor gradually decreases to zero while the incoming thyristor current increases and equals the total load current at the end of the overlap period. If the duration of the overlap period is greater than 60° four thyristors may also conduct clamping the output voltage to zero for some time. However, this situation is not very common and will not be discussed any further in this lesson. Due to the conduction of two devices during commutation either from the top group or the bottom group the instantaneous output voltage during the overlap period drops (shown by the hatched portion of Fig. 2.26 resulting in reduced average voltage. The exact amount of this reduction can be calculated as follows.

for $\mu \leq 60^\circ$. It can be shown that for this condition to be satisfied

$$I_0 \leq \frac{V_L}{\sqrt{2}\omega L} \cos\left(\alpha - \frac{\pi}{3}\right)$$

To calculate the dc voltage

For $\alpha \leq \omega t \leq \alpha + \mu$

$$v_0 = v_a - v_b + L \frac{di_b}{dt} = \frac{3}{2} v_a$$

for $\alpha + \mu \leq \omega t \leq \alpha + \frac{\pi}{3}$ $v_0 = V_{ac}$

$$\therefore V_0 = \frac{3}{\pi} \left[\int_{\alpha}^{\alpha+\mu} \frac{3}{2} v_a d\omega t + \int_{\alpha+\mu}^{\alpha+\frac{\pi}{3}} v_{ac} d\omega t \right]$$

$$= \frac{3}{\pi} \left[\int_{\alpha}^{\alpha+\mu} \left(v_{ac} + \frac{3}{2} v_a - v_{ac} \right) + \int_{\alpha+\mu}^{\alpha+\frac{\pi}{3}} v_{ac} d\omega t \right]$$

$$= \frac{3}{\pi} \left[\int_{\alpha}^{\alpha+\frac{\pi}{3}} v_{ac} d\omega t + \int_{\alpha}^{\alpha+\mu} \left(\frac{v_a}{2} + v_0 \right) d\omega t \right]$$

$$= \frac{3\sqrt{2}}{\pi} V_L \cos\alpha - \frac{3}{2\pi} \int_{\alpha}^{\alpha+\mu} v_{bc} d\omega t$$

or
$$V_0 = \frac{3\sqrt{2}}{\pi} V_L \cos\alpha - \frac{3\sqrt{2}V_L}{2\pi} \int_{\alpha}^{\alpha+\mu} \sin\omega t d\omega t$$

$$= \frac{3\sqrt{2}}{\pi} V_L \cos\alpha - \frac{3\sqrt{2}V_L}{2\pi} [\cos\alpha - \cos(\alpha + \mu)]$$

$$V_0 = \frac{3\sqrt{2}}{\pi} V_L \cos\alpha - \frac{3}{\pi} \omega L I_0$$

Introduction to dual converters

Dual converter, the name itself says two converters. It is really an electronic converter or circuit which comprises of two converters. One will perform as rectifier and the other will perform as inverter. Therefore, we can say that double processes will occur at a moment. Here, two full converters are arranged in anti-parallel pattern and linked to the same dc load. These converters can provide four quadrant operations. The basic block diagram is shown below

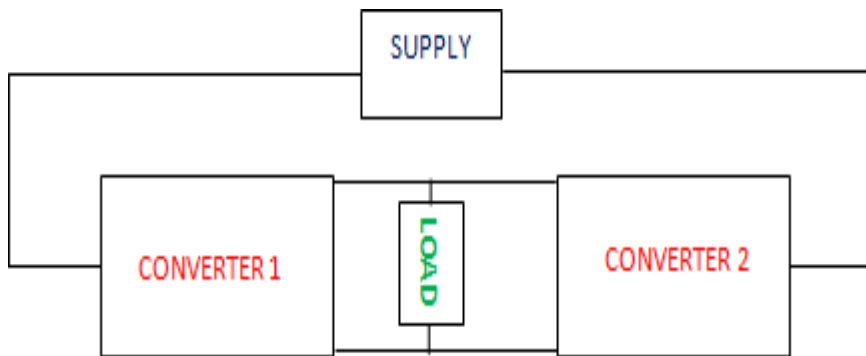


Figure: 2.28 Block diagram of dual converter

Modes of Operation of Dual Converter


There are two functional modes: Non-circulating current mode and circulating mode.

Non Circulating Current Mode

- One converter will perform at a time. So there is no circulating current between the converters.
- During the converter 1 operation, firing angle (α_1) will be $0 < \alpha_1 < 90^\circ$; V_{dc} and I_{dc} are positive.
- During the converter 2 operation, firing angle (α_2) will be $0 < \alpha_2 < 90^\circ$; V_{dc} and I_{dc} are negative.

Circulating Current Mode

- Two converters will be in the ON condition at the same time. So circulating current is present.
- The firing angles are adjusted such that firing angle of converter 1 (α_1) + firing angle of converter 2 (α_2) = 180° .
- Converter 1 performs as a controlled rectifier when firing angle be $0 < \alpha_1 < 90^\circ$ and Converter 2 performs as an inverter when the firing angle be $90^\circ < \alpha_2 < 180^\circ$. In this condition, V_{dc} and I_{dc} are positive.
- Converter 1 performs as an inverter when firing angle be $90^\circ < \alpha_1 < 180^\circ$ and Converter 2 performs as a controlled rectifier when the firing angle be $0 < \alpha_2 < 90^\circ$. In this condition, V_{dc} and I_{dc} are negative.
- The four quadrant operation is shown below

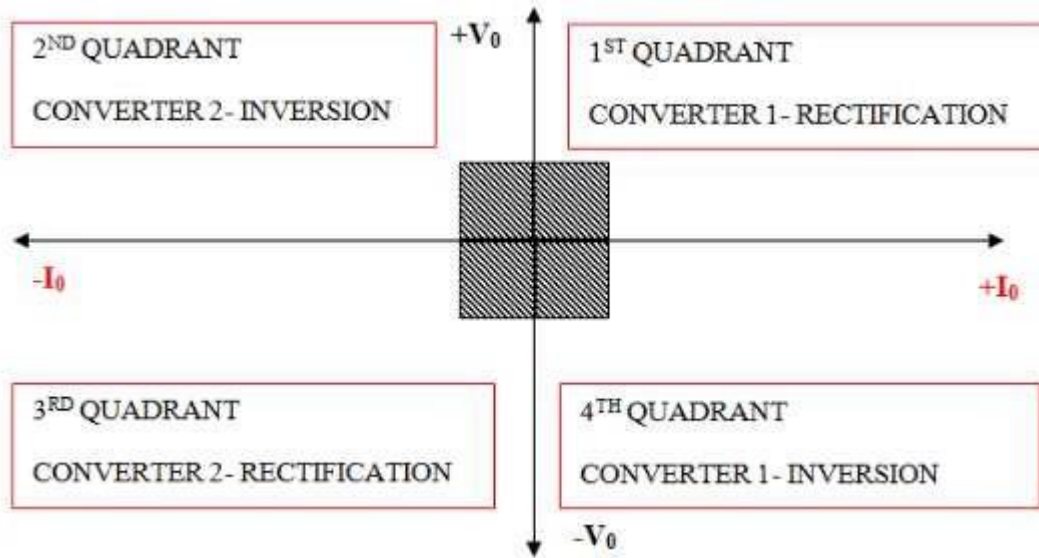

Ideal Dual Converter

The term ‘ideal’ refers to the ripple free output voltage. For the purpose of unidirectional flow of DC current, two diodes (D_1 and D_2) are incorporated between the converters. However, the direction of current can be in any way. The average output voltage of the converter 1 is V_{o1} and converter 2 is V_{o2} . To make the output voltage of the two converters in same polarity and magnitude, the firing angles of the Thyristors have to be controlled.

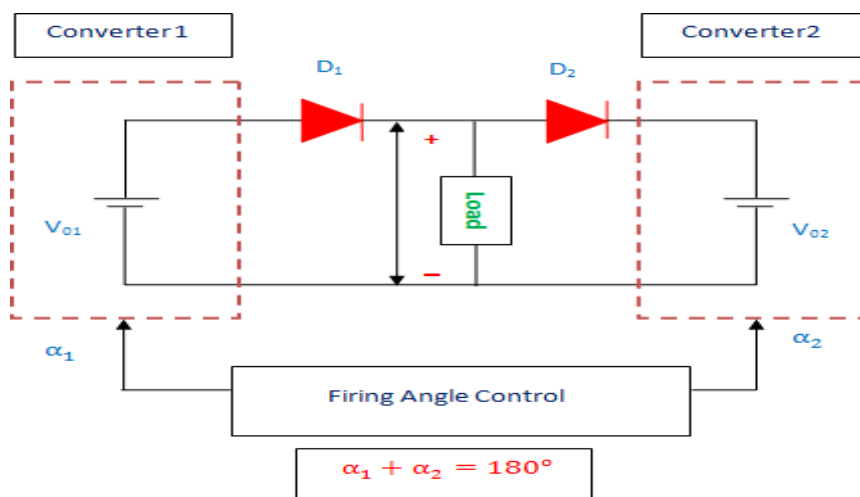


Figure: 2.30 Ideal dual converter

Single Phase Dual Converter

The source of this type of converter will be single-phase supply. Consider, the converter is in non-circulating mode of operation. The input is given to the converter 1 which converts the AC to DC by the method of rectification. It is then given to the load after filtering. Then, this DC is provided to the converter 2 as input. This converter performs as inverter and converts this DC to AC. Thus, we get AC as output. The circuit diagram is shown below.

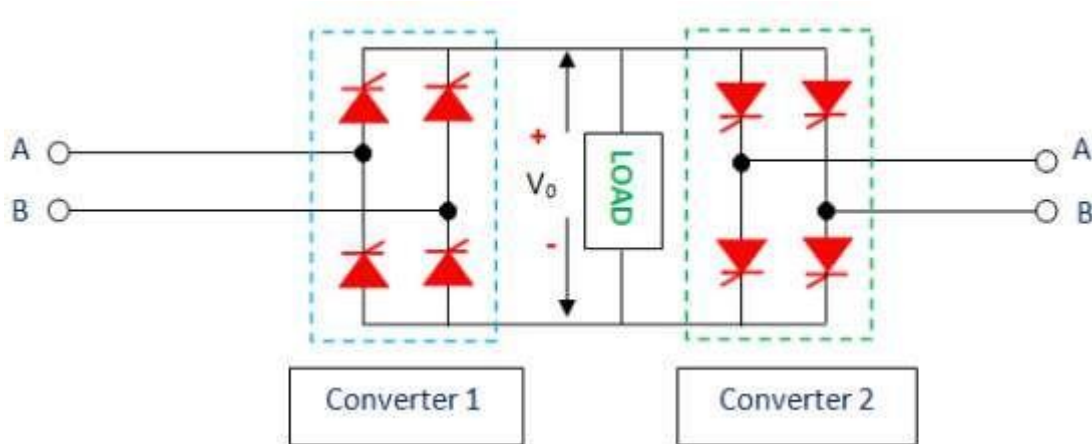


Figure: 2.31 Single phase Dual converter


Average output voltage of Single-phase converter = $\frac{2V_m \cos \alpha}{\pi}$ Average output voltage of Three-phase converter = $\frac{3V_m \cos \alpha}{\pi}$

For converter 1, the average output voltage, $V_{01} = V_{max} \cos \alpha_1$ For converter 2, the average output voltage, $V_{02} = V_{max} \cos \alpha_2$

$$\begin{aligned} V_0 &= V_{01} = -V_{02} \\ V_{max} \cos \alpha_1 &= -V_{max} \cos \alpha_2 \\ \cos \alpha_1 &= \cos(180^\circ - \alpha_2) \text{ or } \cos \alpha_2 = \cos(180^\circ + \alpha_2) \end{aligned}$$

Output voltage, $\alpha_1 + \alpha_2 = 180^\circ$ And $\alpha_1 - \alpha_2 = 180^\circ$

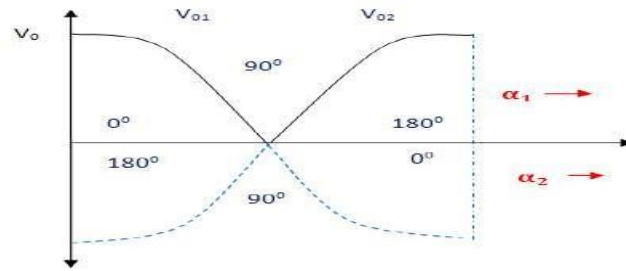The firing angle can never be greater than 180° . So, $\alpha_1 + \alpha_2 = 180^\circ$



Three Phase Dual Converter

Here, three-phase rectifier and three-phase inverter are used. The processes are similar to single-phase dual converter. The three-phase rectifier will do the conversion of the three-phase AC supply to the DC. This DC is filtered and given to the input of the second converter. It will do the DC to AC conversion and the output that we get is the three-phase AC. Applications where the output is up to 2 megawatts. The circuit is shown below.

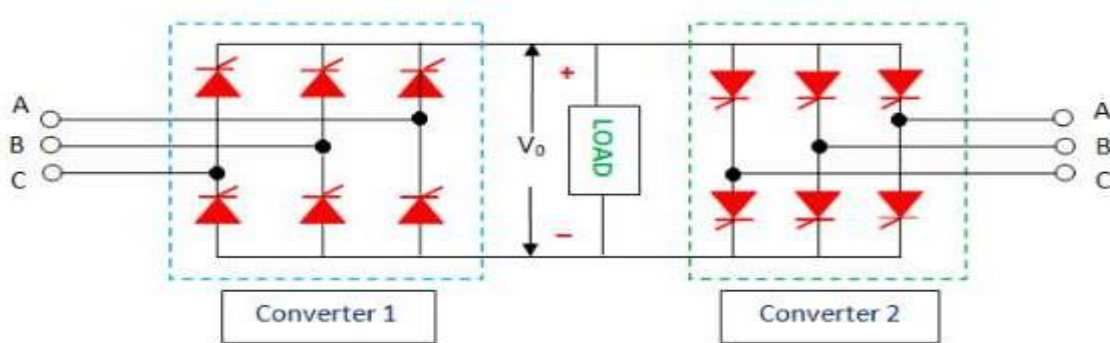


Figure: 2.33 Three phase dual converter

Application of Dual Converter

- Direction and Speed control of DC motors.
- Applicable wherever the reversible DC is required.
- Industrial variable speed DC drives

UNIT-III

DC-DC CONVERTERS (CHOPPER/SMPS)

INTRODUCTION:

A chopper is a device that converts fixed DC input to a variable DC output voltage directly. Essentially, a chopper is an electronic [switch](#) that is used to interrupt one signal under the control of another .


Chopper is fed through a constant DC voltage source and its output is variable DC voltage. The average value of output DC voltage may be less than or higher than the input DC voltage source. A simple diagram defining the chopper is shown below.



A chopper is a DC equivalent to an AC transformer having continuously variable turn ratio. Like a transformer, a it can be used to [step-up](#) or [step-down](#) the fixed DC input voltage. On this basis, there are two types of chopper: Step-up and Step-down Chopper. A chopper whose average value of DC output voltage is more than the fixed DC input voltage is called Step-up Chopper. While, a chopper whose average value of DC output voltage is less than the DC input voltage is called Step-down chopper.

Working Principle of Chopper:

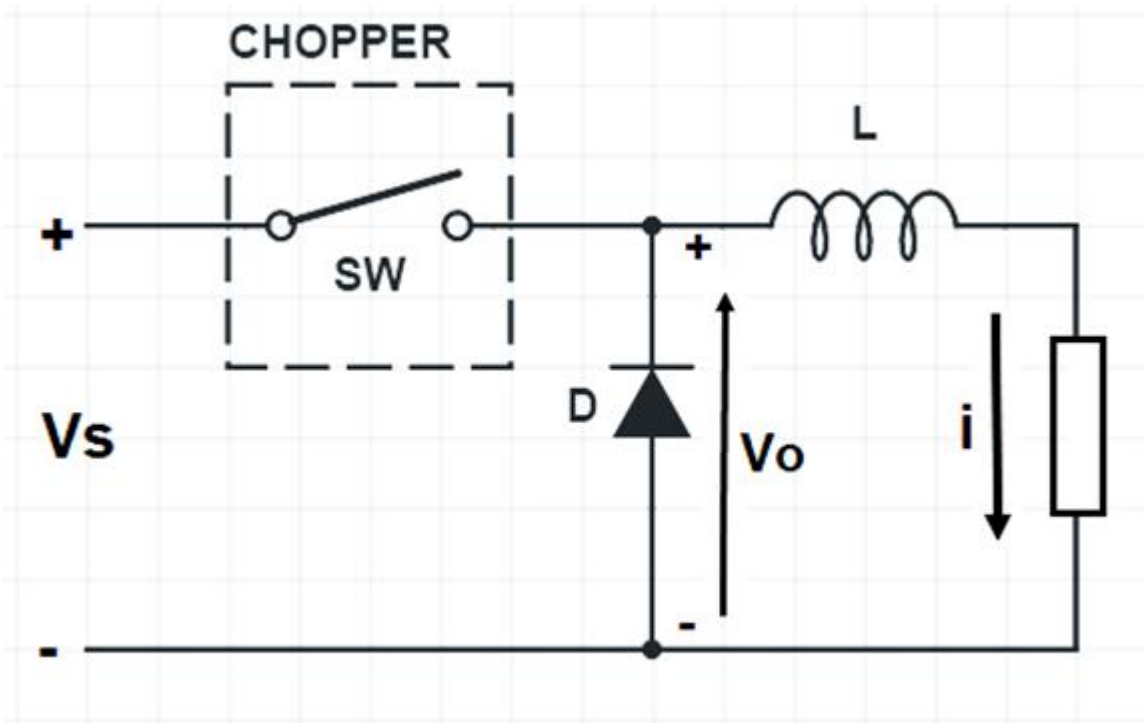A chopper is a high speed ON/OFF switch. It connected source to load and disconnects the load from the source at a fast speed. Figure below represents the simple circuit to show its working principle.



In this circuit, the switch SW is chopper. This switch can be made ON

ELEMENTARY CHOPPER WITH AN ACTIVE SWITCH AND DIODE:

Elementary chopper with an active switch and diode. A chopper is a DC equivalent to an AC transformer having continuously variable turn ratio. Like a transformer, it can be used to step up or step down the fixed DC input voltage. On this basis, there are two types of chopper: Step-up and Step-down Chopper.

CONCEPT OF DUTY RATIO:-

The duty cycle is between 0 and 1. It can be 0 if the chopper switch is never on and it can be 1 when the chopper switch is always on. $f = 1/T = \alpha/T_{on}$.

AVERAGE INDUCTOR VOLTAGE:

The average voltage output (V_o) in a step up chopper is **greater than the voltage input** (V_s). The figure below shows a configuration of a step up chopper.


Classification of Choppers

Depending on the voltage output, choppers are classified as –

- Step Up chopper boost converter
- Step Down Chopper Buck converter Step Up/Down Chopper Buck–boost converter


Step Up Chopper :

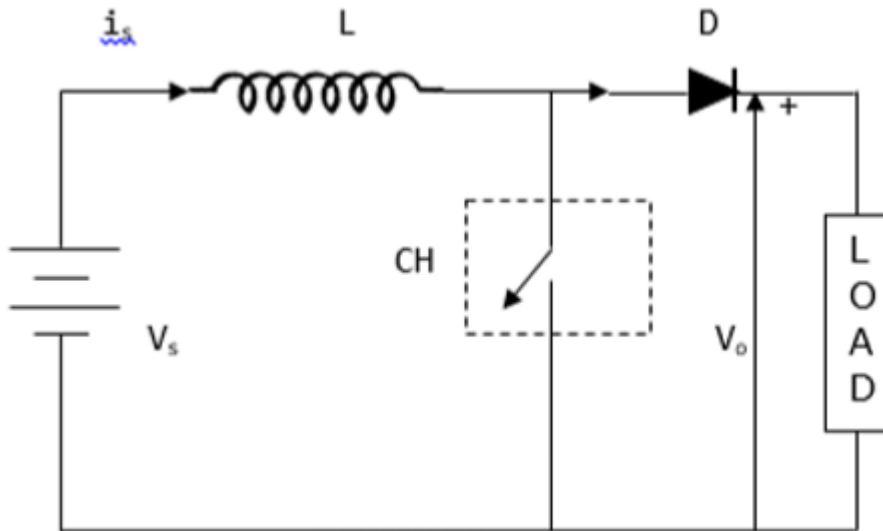The average voltage output (V_o) in a step up chopper is greater than the voltage input (V_s). The figure below shows a configuration of a step up chopper.



Current and Voltage Waveforms

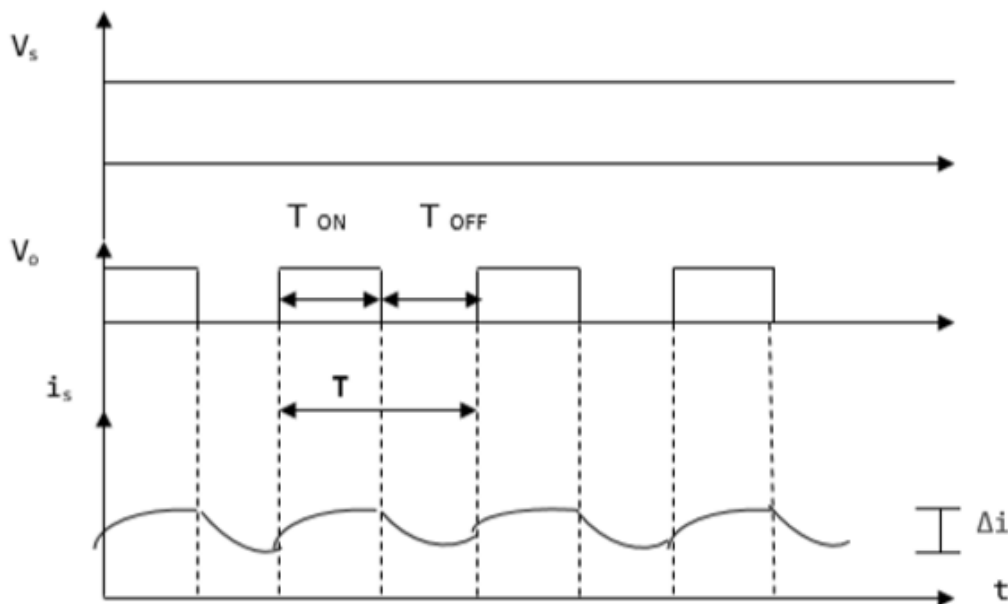V_o average voltage output is positive when chopper is switched ON and negative when the chopper is OFF as shown in the waveform below.



Where

T_{ON} – time interval when chopper is ON

T_{OFF} – time interval when chopper is OFF

V_L – Load voltage

V_s – Source voltage

T – Chopping time period = $T_{ON} + T_{OFF}$

V_o is given by –

$$V_o = \frac{1}{T} \int_{T_{ON}} V_s dt$$

$$L \frac{di}{dt} = V_s, \quad \frac{\Delta i}{T_{ON}} = \frac{V_s}{L}$$

$$\Delta i = \frac{V_s}{L} T_{ON}$$

Δi is the inductor peak to peak current. When the chopper CH is OFF, discharge occurs through the inductor L. Therefore, the summation of the V_s and V_L is given as follows –

$$V_0 = V_s + V_L, \quad V_L = V_0 - V_s$$

$$L \frac{di}{dt} = V_0 - V_s$$

$$L \frac{\Delta i}{T_{OFF}} = V_0 - V_s$$

$$s, \quad \Delta i = \frac{V_0 - V_s}{L} T_{OFF}$$

$$V_o = \frac{1}{T} \int_{T_{ON}} V_s dt$$

Equating Δi from ON state to Δi from OFF state gives –

$$\frac{V_s}{L} T_{ON} = \frac{V_0 - V_s}{L} T_{OFF}, \quad V_s (T_{ON} + T_{OFF}) = V_0 T_{OFF}$$

$$V_0 = \frac{T V_s}{T_{OFF}} = \frac{V_s}{\frac{(T_{ON} + T_{OFF})}{T}}$$

This gives the average voltage output as,

$$V_0 = \frac{V_s}{1 - D}$$

When the chopper CH is switched ON, the load is short circuited and, therefore, the voltage output for the period T_{ON} is zero. In addition, the inductor is charged during this time. This gives $V_s = V_L$

This give the average voltage output as,

$$V_0 = V_S(1-D)$$

The above equation shows that V_0 can be varied from V_S to infinity. It proves that the output voltage will always be more than the voltage input and hence, it boosts up or increases the voltage level.

Step Down Chopper

This is also known as a buck converter. In this chopper, the average voltage output V_0 is less than the input voltage V_S . When the chopper is ON, $V_0 = V_S$ and when the chopper is off, $V_0 = 0$

When the chopper is ON –


$$V_S = (V_L + V_0), \quad V_L = V_S - V_0, \quad L \frac{di}{dt} = V_S - V_0,$$

$$L \frac{\Delta i}{T_{ON}} = V_S - V_0$$

Thus, peak-to-peak current load is given by,

$$\Delta i = \frac{V_S - V_0}{L} T_{ON}$$

Circuit Diagram

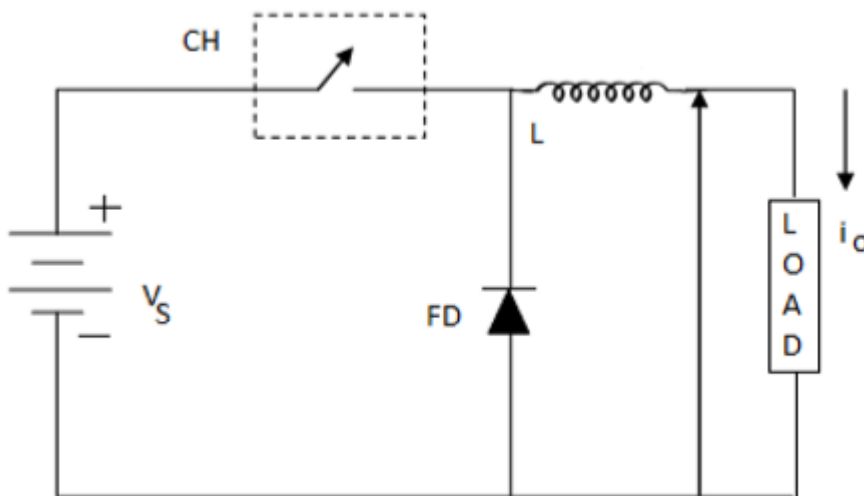

Where **FD** is free-wheel diode.

When the chopper is OFF, polarity reversal and discharging occurs at the inductor. The current passes through the free-wheel diode and the inductor to the load. This gives

Rewritten as –

$$L \frac{di}{dt} = V_0 \dots \dots \dots (i)$$

Rewritten as – $L \frac{\Delta i}{T_{OFF}} = V_0$

$$\Delta i = V_0 \frac{T_{OFF}}{L} \dots \dots \dots (ii)$$

Equating equations *i* and *ii* gives;

$$\frac{V_S - V_0}{L} T_{ON} = \frac{V_0}{L} T_{OFF}$$

$$\frac{V_S - V_0}{V_0} = \frac{T_{OFF}}{T_{ON}}$$

$$\frac{V_S}{V_0} = \frac{T_{ON} - T_{OFF}}{T_{ON}}$$

The above equation gives;

$$V_0 = \frac{T_{ON}}{T} V_S = D V_S$$

Equation *i* gives –

$$\Delta i = \frac{V_S - D V_S}{L} D T, \text{ from } D = \frac{T_{ON}}{T}$$


$$= \frac{V_S - (1-D) D}{L f}$$

$$f = \frac{1}{T} = \text{chopping frequency}$$

\ Current and Voltage Waveforms


The current and voltage waveforms are given below –

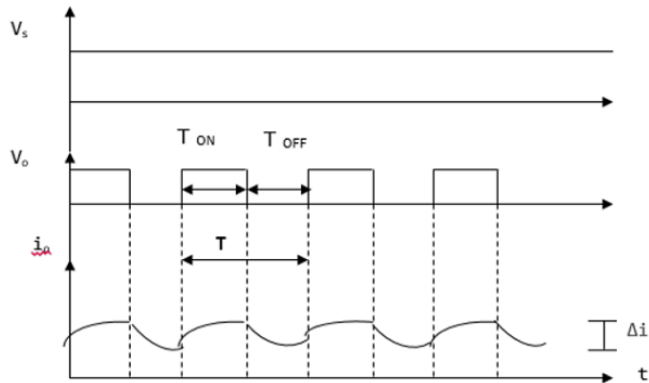For a step down chopper the voltage output is always less than the voltage input. This is shown by the waveform below.



Step Up/ Step Down Chopper

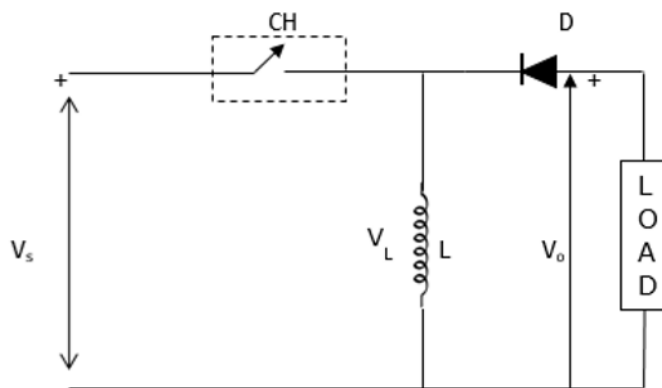This is also known as a buck-boost converter. It makes it possible to increase or reduce the voltage input level. The diagram below shows a buck-boost chopper.



When the chopper is switched ON, the inductor L becomes charged by the source voltage V_s .

$$L \frac{di}{dt} = V_s$$

$$\Delta i = \frac{V_s}{L} T_{ON} = \frac{V_s}{L} T \frac{T_{ON}}{T} = \frac{DV_s}{Lf}$$

Because -

$$D = \frac{T_{ON}}{T} \quad \text{and}$$

Therefore, $V_s = \frac{f}{1} \dots \dots \dots (iii)$

When the chopper is switched OFF, the inductor's polarity reverses and this causes it to discharge through the diode and the load.

Hence,

$$V_0 = -V_L$$

$$L \frac{di}{dt} = -V_0$$

$$L \frac{\Delta i}{T_{OFF}} = -V_0 \quad , \quad \text{thus}$$

$$\Delta i = -\frac{V_0}{L} T_{OFF} \dots \dots \dots (iv)$$

Evaluating equation *iii* and *iv* gives -

$$\frac{DV_s}{Lf} = -\frac{V_0}{L} T_{OFF} \quad ,$$

$$DV_S = -DV_S = -V_0 T_{OFF} f$$

$$DV_S = -V_0 \frac{T - T_{ON}}{T} = -V_0 \left(1 - \frac{T_{ON}}{T}\right),$$

$$V_0 = -\frac{DV_S}{1-D}$$

Because $D = \frac{T_{ON}}{T} = \frac{T - T_{OFF}}{1-D}$

This gives,

$$V_0 = \frac{DV_S}{1-D}$$

D can be varied from 0 to 1. When, $D = 0$; $V_O = 0$

When $D = 0.5$, $V_O = V_S$

When, $D = 1$, $V_O = \infty$.

Hence, in the interval $0 \leq D \leq 0.5$, output voltage varies in the range $0 \leq V_o < V_s$ and we get step down or Buck operation. Whereas, in the interval $0.5 \leq D \leq 1$, output voltage varies in the range $V_s \leq V_o \leq \infty$ and we get step up or Boost operation.


BUCK CONVERTER:-

Buck Converter is a type of **chopper circuit** that is designed to perform step-down conversion of the applied dc input signal. In the case of buck converters, the fixed dc input signal is changed into another dc signal at the output which is of lower value. This means it is designed to produce a dc signal as its output that possesses a lower magnitude than the applied input.

It is sometimes called **Step-down DC to DC Converter** or **Step-down Chopper** or **Buck Regulator**.

Operating Principle of Buck Converter

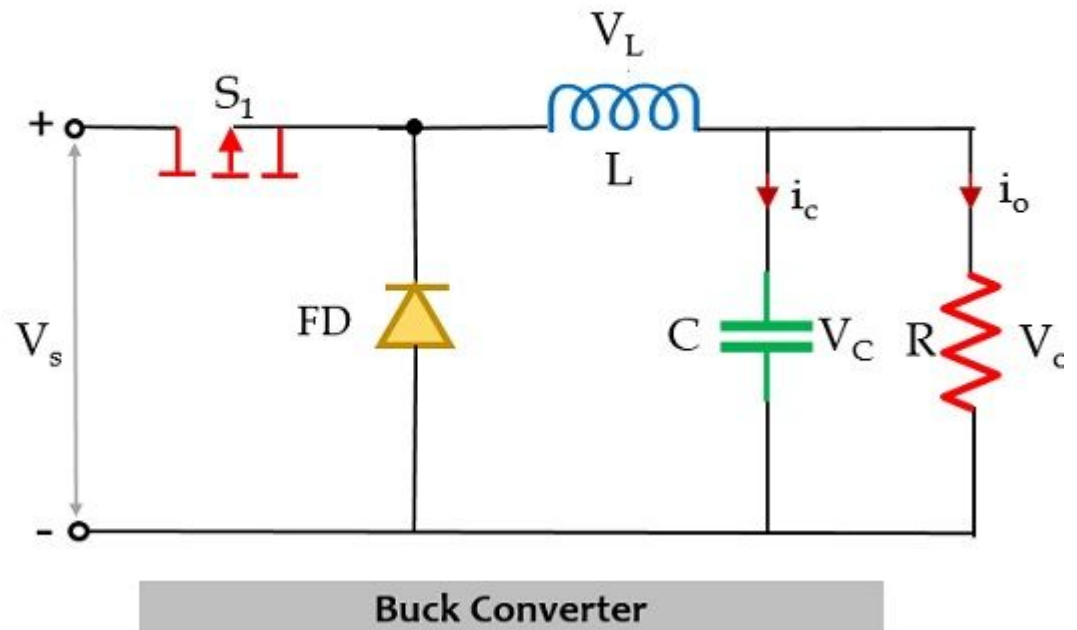
The figure given below shows the circuit representation of Buck Converter:



In the above figure, it is clearly shown that along with the power electronics solid-state device which acts as a switch for the circuit, there is another switch in the circuit which is a freewheeling diode. The combination of these two switches forms a connection with a low-pass LC filter in order to reduce current or voltage ripples. This helps in generating regulated dc output. A pure resistor is connected across this whole arrangement that acts as a load of the circuit.

The whole operation of the circuit takes place in two modes. The first mode is the one when the power MOSFET i.e., switch S_1 is closed.

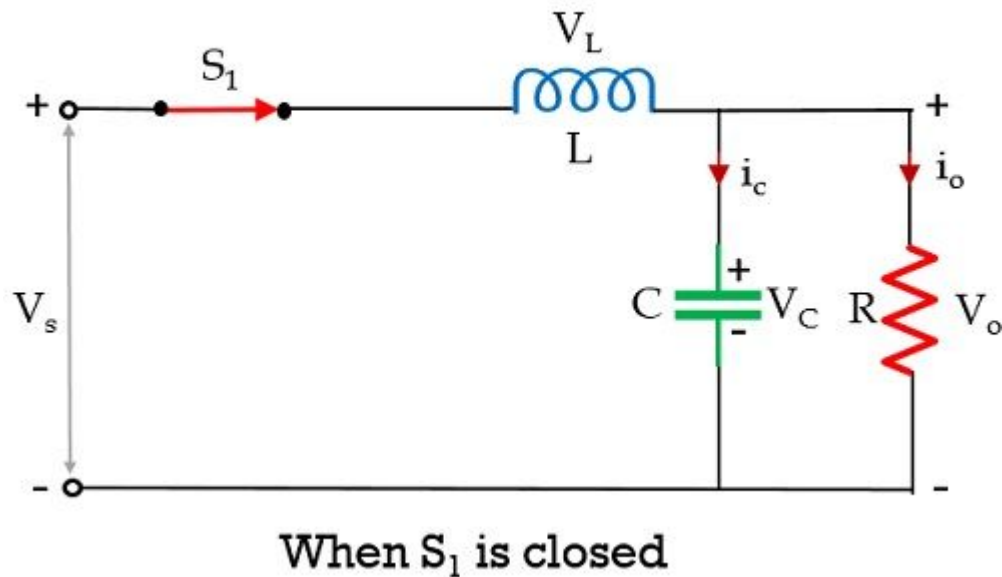In this mode of operation, switch S_1 is in closed condition thus allows the flow of current to take place through it.



Initially when a fixed dc voltage is applied across the input terminal of the circuit then in the closed condition of switch S_1 current flows in the circuit in the manner shown above. Due to this flowing current, the inductor in the path stores energy in the form of a magnetic field. Also, there is a capacitor in the circuit and current flows through it also, therefore, it will store the charge and the voltage across it will appear across the load.

However, due to Lenz's law, the energy stored within the inductor will oppose the cause which has produced it and so an induced current will get generated and the polarity across the inductor will get reversed.

Here the total time period is a combination of T_{on} and T_{off} time.

When S1 is in closed condition then $T_{on} = DT$ thus $\Delta t = DT$. Therefore, we can write,

$$\frac{\Delta i_L}{\Delta t} = \frac{V_s - V_{out}}{L}$$
$$\frac{\Delta i_L}{DT} = \frac{V_s - V_{out}}{L}$$

Hence,

$$\Delta i_t = \left(\frac{V_s - V_{out}}{L}\right)DT$$

$$T = T_{on} + T_{off}$$

The duty cycle is written as:

$$D = \frac{T_{on}}{T}$$

On applying KVL, in the above-given circuit,

$$V_s = V_L + V_{out}$$

$$V_L = V_s - V_{out}$$

Also,

$$V_L = L \frac{di_L}{dt} = V_s - V_{out}$$
$$\frac{di_L}{dt} = \frac{V_s - V_{out}}{L}$$


The above equation represents the change in current through the circuit when switch S1 is closed.

Now, the second mode of operation takes place when switch S₂ is closed and S₁ gets open. However, you must be thinking about how automatically, the switch S₂ will be closed. So, as we have discussed that the inductor in the circuit will store the energy so, once S₁ will get open the inductor in the circuit will start acting as the source.

In this mode, the inductor releases the energy which is stored in the previous mode of

operation. As we have discussed that the polarity of the inductor will get reversed therefore this causes the freewheeling diode to come in a forward-biased state which was earlier present in a reverse-biased state due to the applied dc input.

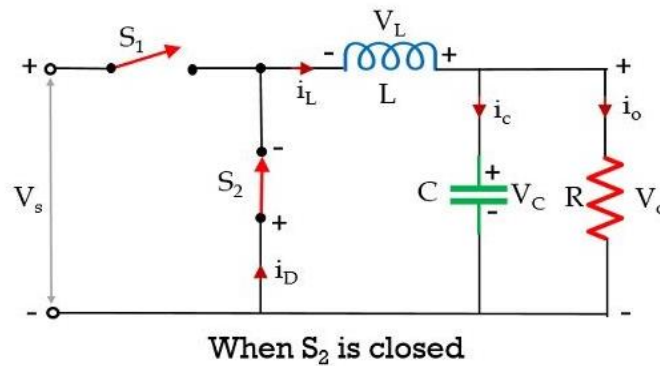Due to this, the flow of current takes place in a way as shown below:



This flow of current will take place till the time the stored energy within the inductor gets completely collapsed. As once the inductor gets completely discharged, the diode comes in reverse biased condition leading to cause opening of switch S_2 , and instantly switch S_1 will get closed and the cycle continues.

Now, let us apply KVL, in the above circuit,

$$0 = V_L + V_{out}$$

$$V_L = L \frac{di_L}{dt} = -V_{out}$$

$$T = T_{on} + T_{off}$$

$$T = DT + T_{off}$$

$$T_{off} = T - DT$$

$$T_{off} = (1 - D)T$$

$$V_L = L \frac{\Delta i_L}{\Delta t} = -V_{out}$$

$$T_{off} = \Delta t = (1 - D)T$$

$$L \frac{\Delta i_L}{(1 - D)T} = -V_{out}$$

This equation represents the rate of change in current through the inductor when the switch S1 is open.

As we know that the net change of current through the inductor in one complete cycle is zero. Thus,

$$\Delta i_L = - \frac{V_{out}}{L} (1 - D)T$$

$$\Delta i_{L(S1-closed)} + \Delta i_{L(S1-open)} = 0$$


$$\frac{V_s - V_{out}}{L} DT + \left\{ - \frac{V_{out}}{L} (1 - D)T \right\} = 0$$

$$\frac{V_s DT}{L} - \frac{V_{out} DT}{L} - \frac{V_{out} T}{L} + \frac{V_{out} DT}{L} = 0$$

$$\left(\frac{V_s DT}{L} \right) = \frac{V_{out} T}{L}$$

$$V_{out} = DV_s$$

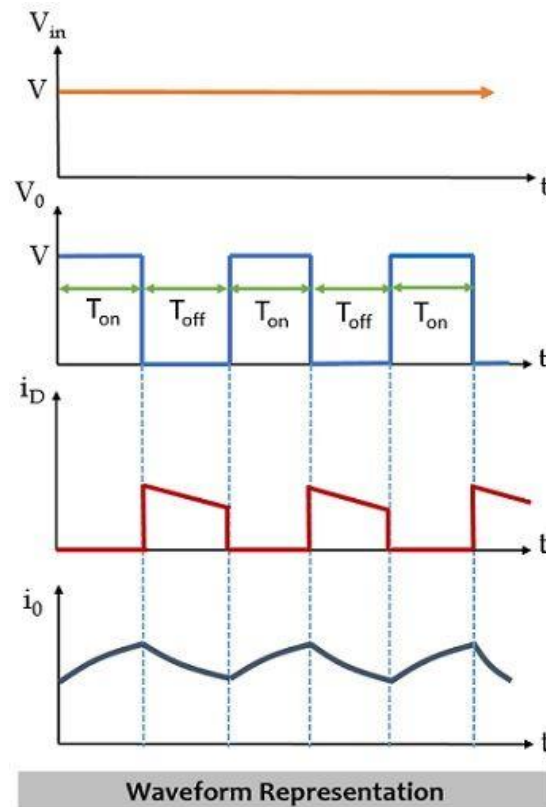The figure given below represents the waveform representation of Buck Converter:



Hence, we can say, buck converters are used to provide a lower value of dc signal from a fixed dc input.


Buck-Boost Converter:

The buck–boost converter is a type of DC-to-DC converter (also known as **chopper**) that has an output **voltage** magnitude that is either greater than or less than the input voltage magnitude. It is used to “step up” the **DC voltage**, similar to a **transformer** for AC circuits.

It is equivalent to a fly back converter using a single inductor instead of a transformer. Two different topologies are called buck–boost converter.

DC-DC converters are also known as **choppers**. Here we will have a look at **Buck Boost converter** which can operate as a DC-DC Step-Down converter or a DC-DC Step-Up converter depending upon the duty cycle, D.

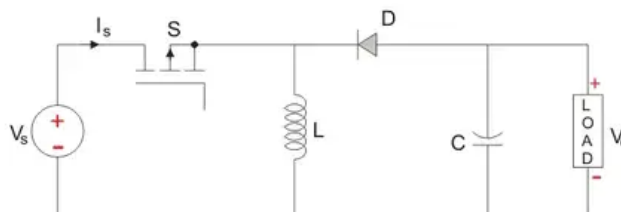A typical Buck-Boost converter is shown below.




The input **voltage source** is connected to a solid state device. The second switch used is a **diode**. The diode is connected, in reverse to the direction of power flow from source, to a **capacitor** and the load and the two are connected in parallel as shown in the figure above.

The controlled switch is turned on and off by using Pulse Width Modulation (PWM). PWM can be time based or frequency based.

Time based Modulation is mostly used for DC-DC converters. It is simple to construct and use.

The frequency remains constant in this type of PWM modulation. The **Buck Boost converter** has two modes of operation. The first mode is when the switch is on and conducting.

Mode I : Switch is ON, Diode is OFF:-

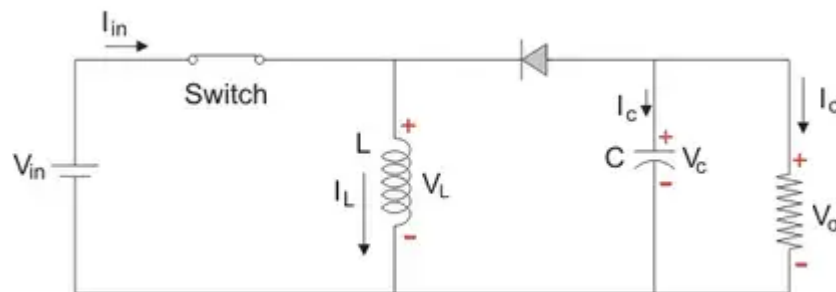

The Switch is ON and therefore represents a short circuit ideally offering zero resistance to the flow of current so when the switch is ON all the current will flow through the switch and the inductor and back to the DC input source.

The inductor stores charge during the time the switch is ON and when the solid state switch is OFF the polarity of the Inductor reverses so that current flows through the load and through the diode and back to the inductor. So the direction of current through the inductor remains the same.

Let us say the switch is on for a time T_{ON} and is off for a time T_{OFF} . We define the time period, T , as

and the switching frequency,

$$T = T_{ON} + T_{OFF}$$

and the switching frequency,

$$f_{switching} = \frac{1}{T}$$

Let us now define another term, the duty cycle,

$$D = \frac{T_{ON}}{T}$$

Let us analyse the **Buck Boost converter** in steady state operation for this mode using KVL.

$$\therefore V_{in} = V_L$$

$$\therefore V_L = L \frac{di_L}{dt} = V_{in}$$

$$\frac{di_L}{dt} = \frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{DT} = \frac{V_{in}}{L}$$


Since the switch is closed for a time $T_{ON} = DT$ we can say that $\Delta t = DT$.

$$(\Delta i_L)_{closed} = \left(\frac{V_{in}}{L} \right) DT$$

While performing the analysis of the Buck-Boost converter we have to keep in mind that

1. The inductor current is continuous and this is made possible by selecting an appropriate value of L.
2. The inductor current in steady state rises from a value with a positive slope to a maximum value during the ON state and then drops back down to the initial value with a negative slope. Therefore the net change of the inductor current over any one complete cycle is zero.

Mode II : Switch is OFF, Diode is ON:-

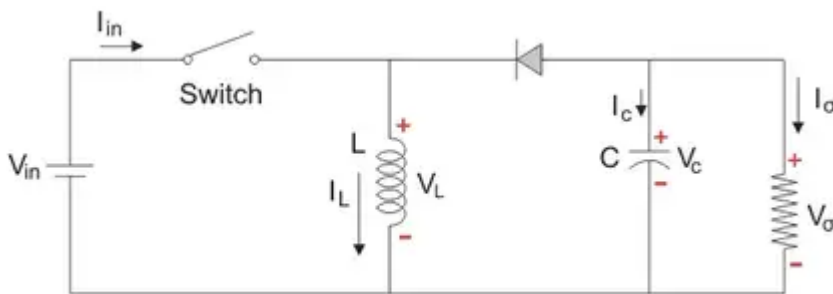

In this mode the polarity of the inductor is reversed and the energy stored in the inductor is released and is ultimately dissipated in the load resistance and this helps to maintain the flow of current in the same direction through the load and also step-up the output voltage as the inductor is now also acting as a source in conjunction with the input source. But for analysis we keep the original conventions to analyse the circuit using KVL.

Let us now analyse the **Buck Boost converter** in steady state operation for Mode II using KVL.

$$\begin{aligned} \therefore V_L &= V_o \\ \therefore V_L &= L \frac{di_L}{dt} = V_o \\ \frac{di_L}{dt} &= \frac{\Delta i_L}{\Delta t} = \frac{\Delta i_L}{(1-D)T} = \frac{V_o}{L} \end{aligned}$$

Since the switch is open for a time
 $T_{OFF} = T - T_{ON} = T - DT = (1 - D)T$

we can say that

$$\Delta t = (1 - D)T$$


$$(\Delta i_L)_{open} = \left(\frac{V_o}{L} \right) (1 - D)T$$

It is already established that the net change of the inductor current over any one complete cycle is zero.


$$\begin{aligned} \therefore (\Delta i_L)_{closed} + (\Delta i_L)_{open} &= 0 \\ \left(\frac{V_o}{L} \right) (1 - D)T + \left(\frac{V_{in}}{L} \right) DT &= 0 \\ \frac{V_o}{V_{in}} &= \frac{-D}{1 - D} \end{aligned}$$

We know that D varies between 0 and 1. If $D > 0.5$, the output voltage is larger than the input; and if $D < 0.5$, the output is smaller than the input. But if $D = 0.5$ the output voltage is equal to the input voltage.

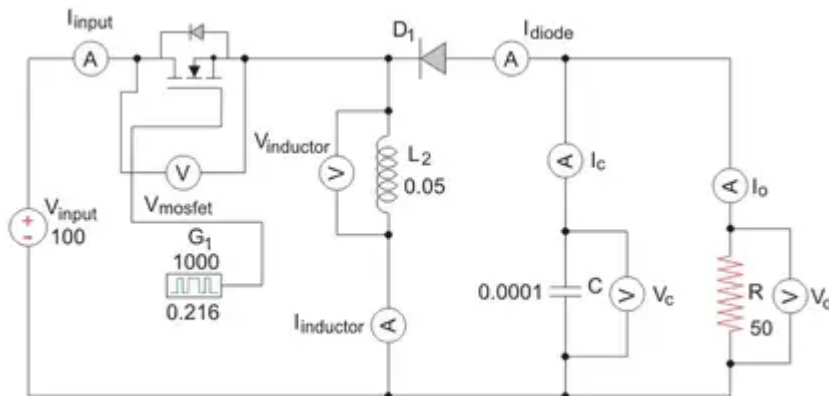
A circuit of a Buck-Boost converter and its waveforms is shown below.



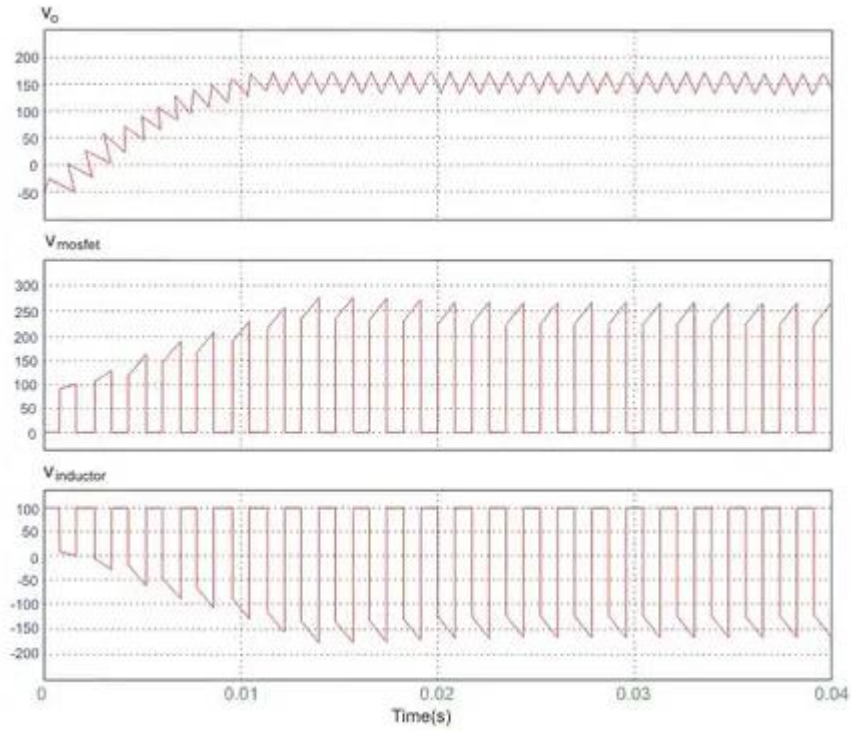The inductance, L, is 50mH and the C is 100μF and the resistive load is 50Ω. The switching frequency is 1 kHz. The input voltage is 100 V DC and the duty cycle is 0.5.



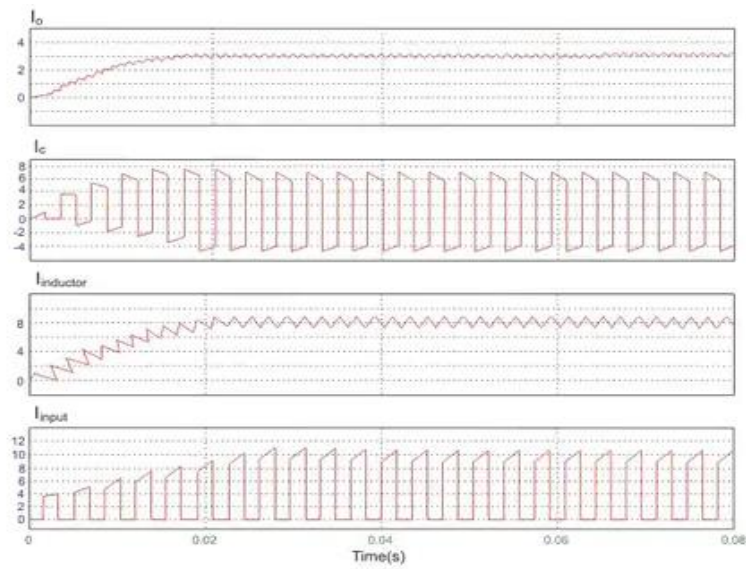The voltage waveforms are as shown above and the current waveforms are as shown in the figure below.



AC-DC CONVERTERS(INVERTERS)

Introduction to Inverters

The word 'inverter' in the context of power-electronics denotes a class of power conversion (or power conditioning) circuits that operates from a dc voltage source or a dc current source and converts it into ac voltage or current. The inverter does reverse of what ac-to-dc converter does (refer to ac to dc converters). Even though input to an inverter circuit is a dc source, it is not uncommon to have this dc derived from an ac source such as utility ac supply. Thus, for example, the primary source of input power may be utility ac voltage supply that is converted to dc by an ac to dc converter and then 'inverted' back to ac using an inverter. Here, the final ac output may be of a different frequency and magnitude than the input ac of the utility supply

A single phase Half Bridge DC-AC inverter is shown in Figure below

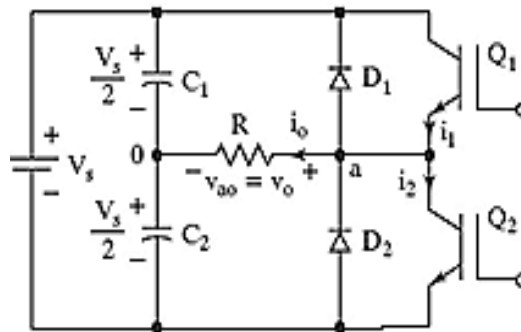


Figure: 5.1 Single phase Half Bridge DC-AC inverter with R load

The analysis of the DC-AC inverters is done taking into accounts the following assumptions and conventions.

- 1) The current entering node a is considered to be positive.
- 2) The switches S1 and S2 are unidirectional, i.e. they conduct current in one direction.
- 3) The current through S1 is denoted as i_1 and the current through S2 is i_2 .

The switching sequence is so design is shown in Figure below. Here, switch S1 is on for the time duration $0 \leq t \leq T_1$ and the switch S2 is on for the time duration $T_1 \leq t \leq T_2$. When switch S1 is turned on, the instantaneous voltage across the load is $v_o = V_{in}/2$

When the switch S2 is only turned on, the voltage across the load is $v_o = -V_{in}/2$.

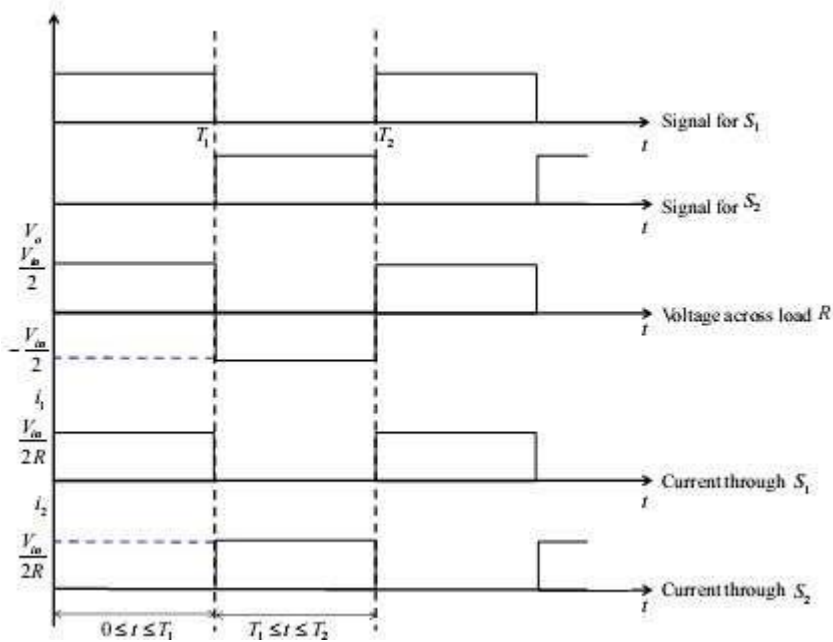


Figure: 5.2 Single phase Half Bridge DC-AC inverter output waveforms

The r.m.s value of output voltage v_o is given by,

$$V_{o,rms} = \left(\frac{1}{T_1} \int_0^{T_1} \frac{V_{in}^2}{4} dt \right) = \frac{V_{in}}{2}$$

The instantaneous output voltage v_o is rectangular in shape. The instantaneous value of v_o can be

expressed in Fourier series as,

$$v_o = \frac{a_0}{2} + \sum_{n=1}^{\infty} a_n \cos(n\omega t) + b_n \sin(n\omega t)$$

Due to the quarter wave symmetry along the time axis, the values of a_0 and a_n are zero. The value of b_n is given by,

$$b_n = \frac{1}{\pi} \left[\int_{-\pi/2}^0 \frac{-V_{in}}{2} d(\omega t) + \int_0^{\pi/2} \frac{V_{in}}{2} d(\omega t) \right] = \frac{2V_{in}}{n\pi}$$

Substituting the value of b_n from above equation, we get


$$v_o = \sum_{n=1,3,5,\dots}^{\infty} \frac{2V_{in}}{n\pi} \sin(n\omega t)$$

The current through the resistor (i_L) is given by,


$$i_L = \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{R} \frac{2V_{in}}{n\pi} \sin(n\omega t)$$

Half Bridge DC-AC Inverter with L Load and R-L Load

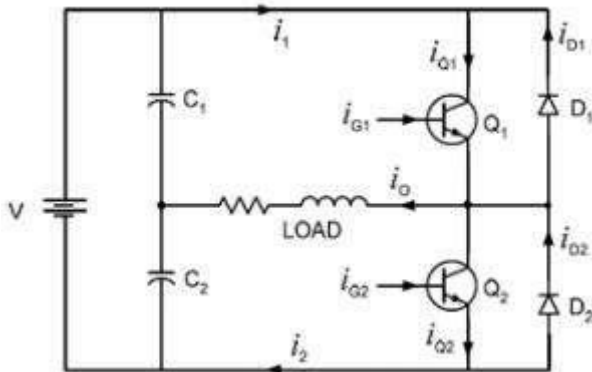The DC-AC converter with inductive load is shown in Figure below. For an inductive load, the load current cannot change immediately with the output voltage.



The working of the DC-AC inverter with inductive load is as follows:
 Case 1: In the time interval $0 \leq t \leq T_1$ the switch S1 is on and the current flows through the inductor from points a to b. When the switch S1 is turned off (case 1) at $t = T_1$, the load current would continue to flow through the capacitor C2 and diode D2 until the current falls to zero, as shown in Figure below.

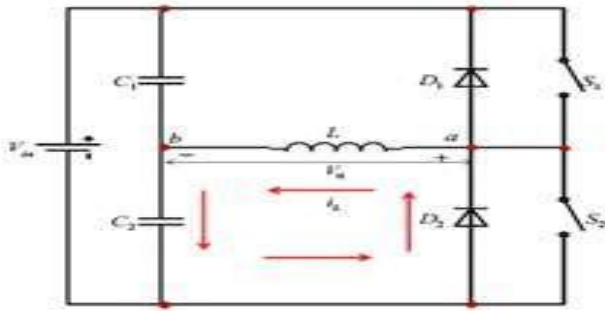

Case 2: Similarly, when \$S_2\$ is turned off at \$t = T_1\$, the load current flows through the diode \$D_1\$ and capacitor \$C_1\$ until the current falls to zero, as shown in Figure below.

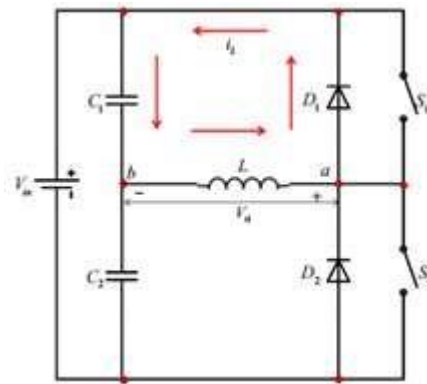


Figure: 5.5 Single phase Half Bridge DC-AC inverter with L load

When the diodes \$D_1\$ and \$D_2\$ conduct, energy is feedback to the dc source and these diodes are known as feedback diodes. These diodes are also known as freewheeling diodes. The current for purely inductive load is given by,

$$i_L = \sum_{n=1,3,5,\dots}^{\infty} \frac{1}{\omega n L} \frac{2V_{in}}{n\pi} \sin\left(n\omega t - \frac{\pi}{2}\right)$$

Similarly, for the R – L load. The instantaneous load current is obtained as,

$$i_L = \sum_{n=1,3,5,\dots}^{\infty} \frac{2V_{in}}{n\pi \sqrt{R^2 + (n\omega L)^2}} \sin(n\omega t - \theta_n)$$

Where,

$$\theta_n = \tan^{-1}\left(\frac{n\omega L}{R}\right)$$

Operation of single phase full bridge inverter

A single phase bridge DC-AC inverter is shown in Figure below. The analysis of the single phase DC-AC inverters is done taking into account following assumptions and conventions.

- 1) The current entering node a in Figure 8 is considered to be positive.
- 2) The switches S1, S2, S3 and S4 are unidirectional, i.e. they conduct current in one direction.

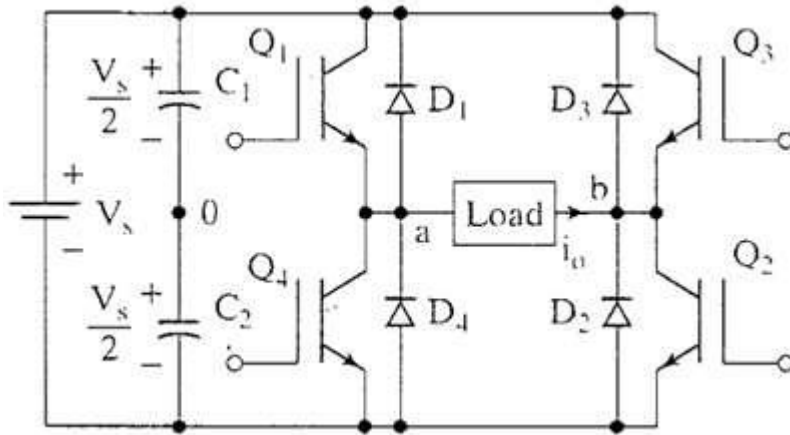


Figure: 5.6 Single phase Full Bridge DC-AC inverter with R load

When the switches S1 and S2 are turned on simultaneously for a duration $0 \leq t \leq T1$,
the the input

voltage V_{in} appears across the load and the current flows from point a to b.

$Q1 - Q2$ ON, $Q3 - Q4$ OFF $\implies v_o = V_s$

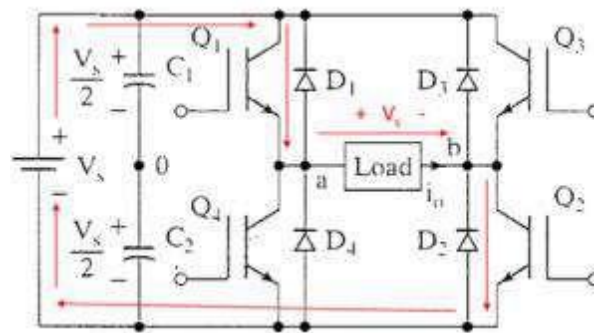


Figure: 5.7 Single phase Full Bridge DC-AC inverter with R load

If the switches S3 and S4 turned on duration $T1 \leq t \leq T2$, the voltage across the load the load
is reversed

and the current through the load flows from point b to a. $Q1 - Q2$ OFF, $Q3 - Q4$ ON $\implies v_o$
 $= -V_s$

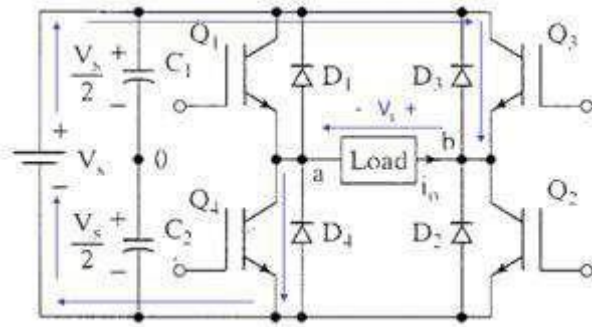


Figure: 5.8 Single phase Full Bridge DC-AC inverter with R load current directions

The voltage and current waveforms across the resistive load are shown in Figure below


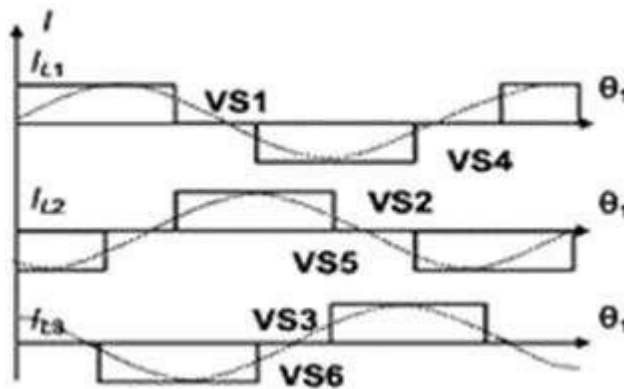


Figure: 5.9 Single phase Full Bridge DC-AC inverter waveforms

Single Phase Full Bridge Inverter for R-L load:

A single-phase square wave type voltage source inverter produces square shaped output voltage for a single-phase load. Such inverters have very simple control logic and the power switches need to operate at much lower frequencies compared to switches in some other types of inverters. The first generation inverters, using thyristor switches, were almost invariably square wave inverters because thyristor switches could be switched on and off only a few hundred times in a second. In contrast, the present day switches like IGBTs are much faster and used at switching frequencies of several kilohertz. Single-phase inverters mostly use half bridge or full bridge topologies. Power circuits of these topologies are shown in Figure below.

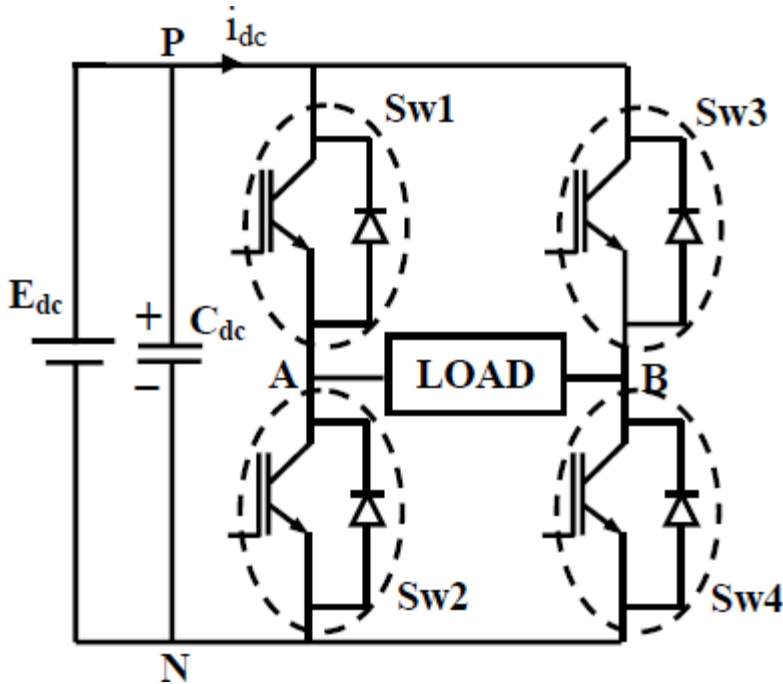

The above topology is analyzed under the assumption of ideal circuit conditions. Accordingly, it is assumed that the input dc voltage (E_{dc}) is constant and the switches are lossless. In full bridge topology has two such legs. Each leg of the inverter consists of two series connected electronic switches shown within dotted lines in the figures. Each of these switches consists of an IGBT type controlled switch across which an uncontrolled diode is put in anti-parallel manner. These switches are capable of conducting bi-directional current but they need to block only one polarity of voltage. The junction point of the switches in each leg of the inverter serves as one output point for the load.



Three phase inverters are normally used for high power applications. The advantages of a three phase inverter are:

- The frequency of the output voltage waveform depends on the switching rate of the switches and hence can be varied over a wide range.


•

he direction of rotation of the motor can be reversed by changing the output phase sequence of

•• A current leaving a node point a , b or c and entering the neutral point n is assumed to be positive.

• All the three resistances are equal, $R_a = R_b = R_c = R$.

In this mode of operation each switch conducts for 180° . Hence, at any instant of time **three switches** remain **on**. When S_1 is **on**, the terminal a gets connected to the positive terminal of input DC source. Similarly, when S_4 is **on**, terminal a gets connected to the negative terminal of input DC source. There are six possible modes of operation in a cycle and each mode is of 60° duration and the explanation of each mode is as follows:

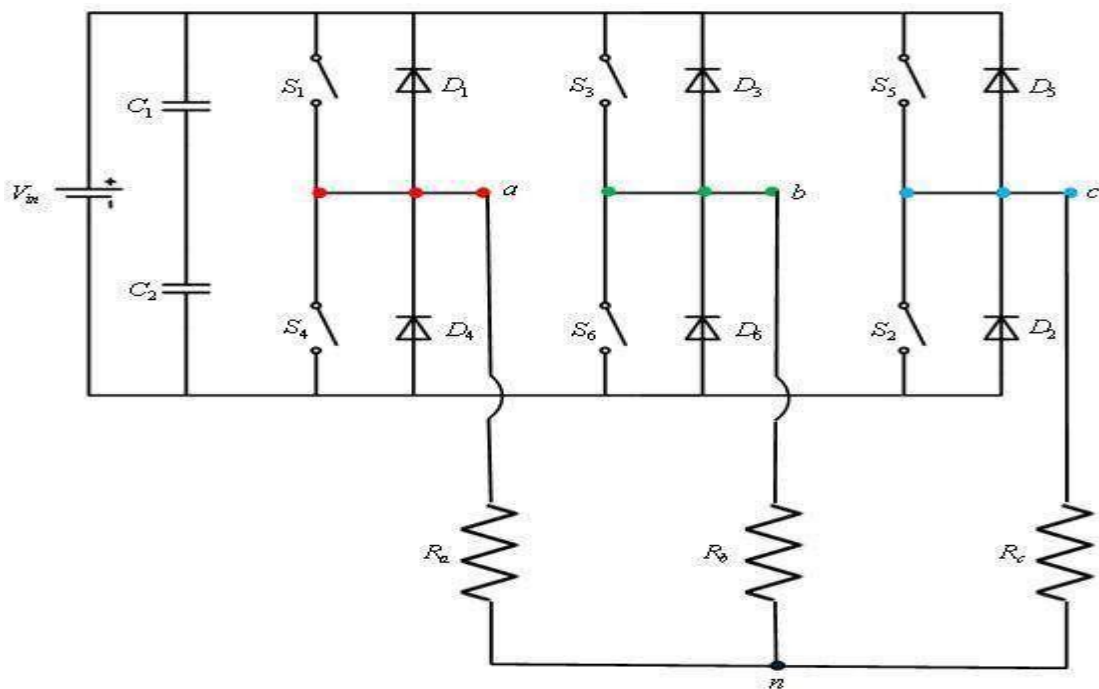

Mode 1 : In this mode the switches S_5 , S_6 and S_1 are turned **on** for time interval $0 \leq \omega t \leq \frac{\pi}{3}$.

As a result of this the terminals a and c are connected to the positive terminal of the input DC source and the terminal b is connected to the negative terminal of the DC source. The current flow through R_a , R_b and R_c is shown in Figure and the equivalent circuit is shown in Figure. The equivalent resistance of the circuit shown in **Figure** is

$$R_{eq} = R + \frac{R}{2} = \frac{3R}{2} \quad (1)$$

The current i delivered by the DC input source is

$$i = \frac{V_{in}}{R_{eq}} = \frac{2 V_{in}}{3 R} \quad (2)$$

The currents i_a and i_b are

$$i_a = i_c = \frac{1 V_{in}}{3 R} \quad (3)$$

Keeping the current convention in mind, the current i_b is

$$i_b = -i = -\frac{2 V_{in}}{3 R} \quad (4)$$

Having determined the currents through each branch, the voltage across each branch is

$$v_{an} = v_{cn} = i_a R = \frac{V_m}{3}; \quad v_{bn} = i_b R = -\frac{2V_m}{3} \quad (5)$$


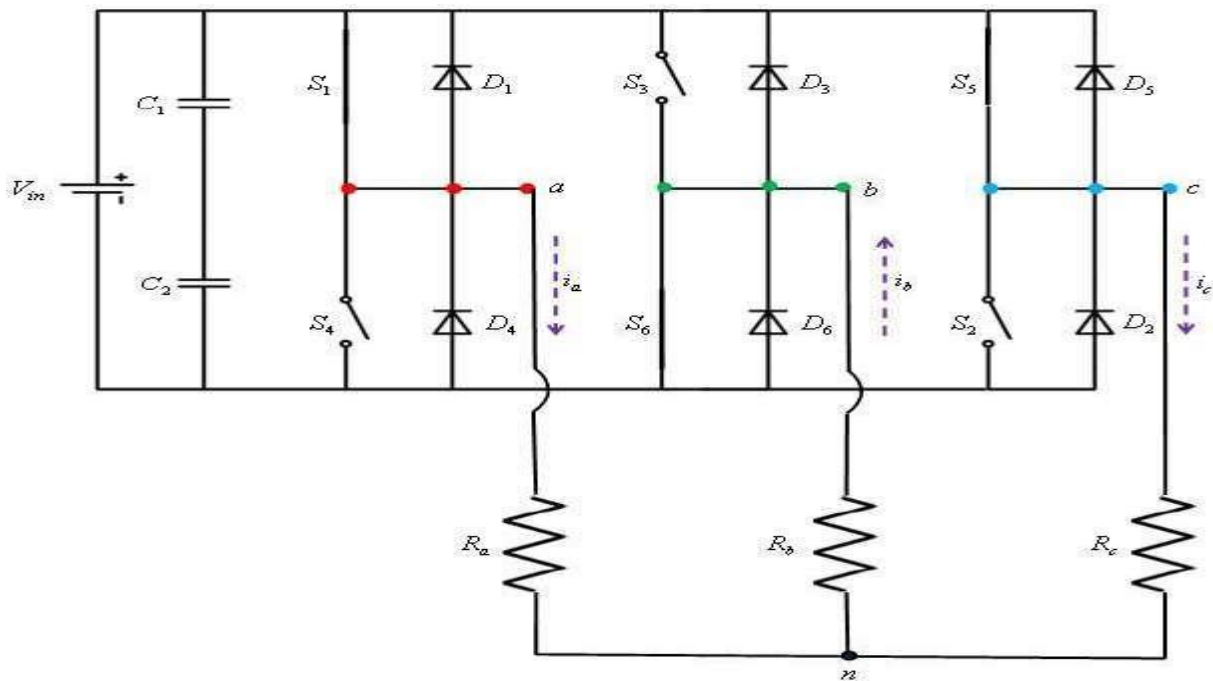


Figure: 5.17 Mode 1 operation of three phase bridge inverter with star connected load

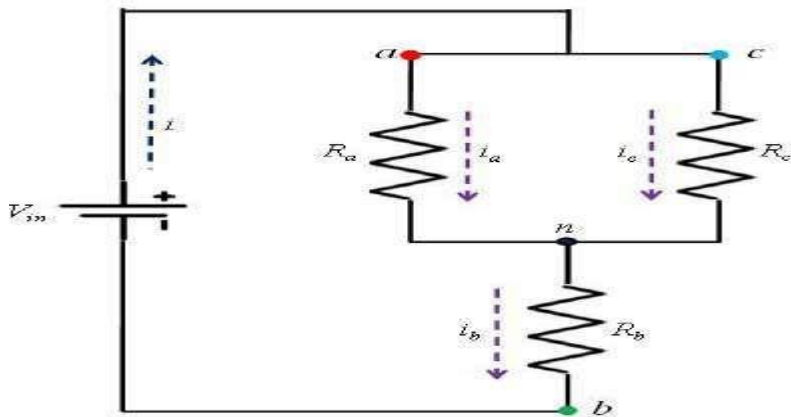

Mode 2 : In this mode the switches S_6 , S_1 and S_2 are turned *on* for time interval $\frac{\pi}{3} \leq \omega t \leq \frac{2\pi}{3}$. The current flow and the equivalent circuits are shown in **Figure** and **Figure** respectively. Following the reasoning given for *mode 1*, the currents through each branch and the voltage drops are given by

$$i_b = i_c = \frac{1}{3} \frac{V_{in}}{R}; \quad i_a = -\frac{2}{3} \frac{V_{in}}{R} \quad (6)$$

$$v_{bn} = v_{cn} = \frac{V_{in}}{3}; \quad v_{an} = -\frac{2V_{in}}{3} \quad (7)$$

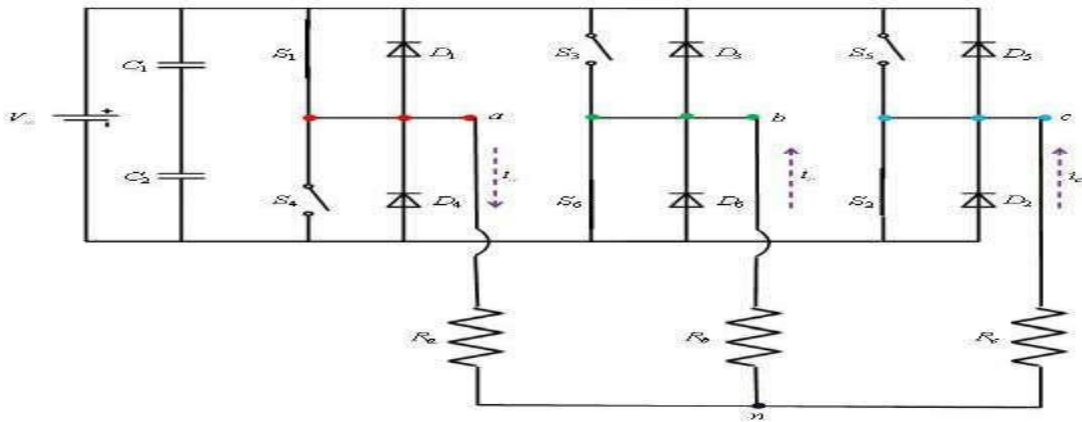


Figure: 5.19 Mode 2 operation of three phase bridge inverter with star connected load

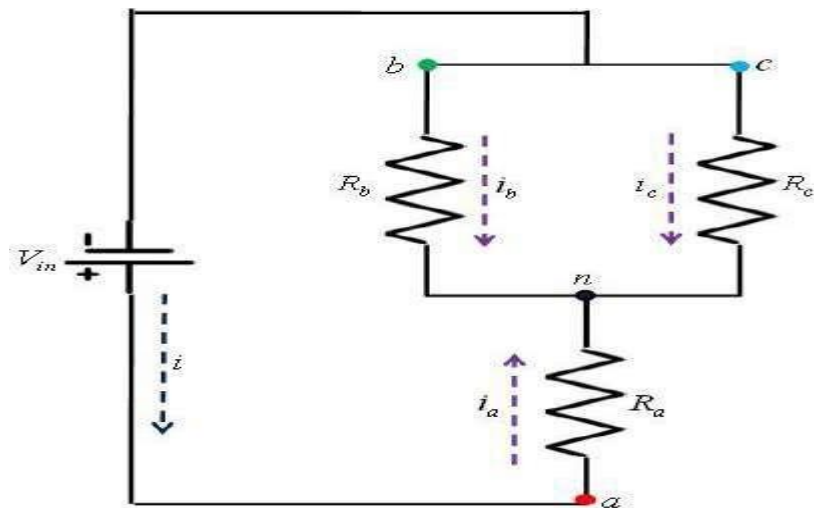


Figure: 5.20 Current flow in Mode 2 operation

Mode 3 : In this mode the switches S_1 , S_2 and S_3 are **on** for $\frac{2\pi}{3} \leq \omega t \leq \pi$. The current flow and the equivalent circuits are shown in **Figure** and **figure** respectively. The magnitudes of currents and voltages are:

$$i_a = i_b = \frac{1}{3} \frac{V_{in}}{R}; i_c = -\frac{2}{3} \frac{V_{in}}{R} \quad (8)$$

$$v_{an} = v_{bn} = \frac{V_{in}}{3}; v_{cn} = -\frac{2V_{in}}{3} \quad (9)$$

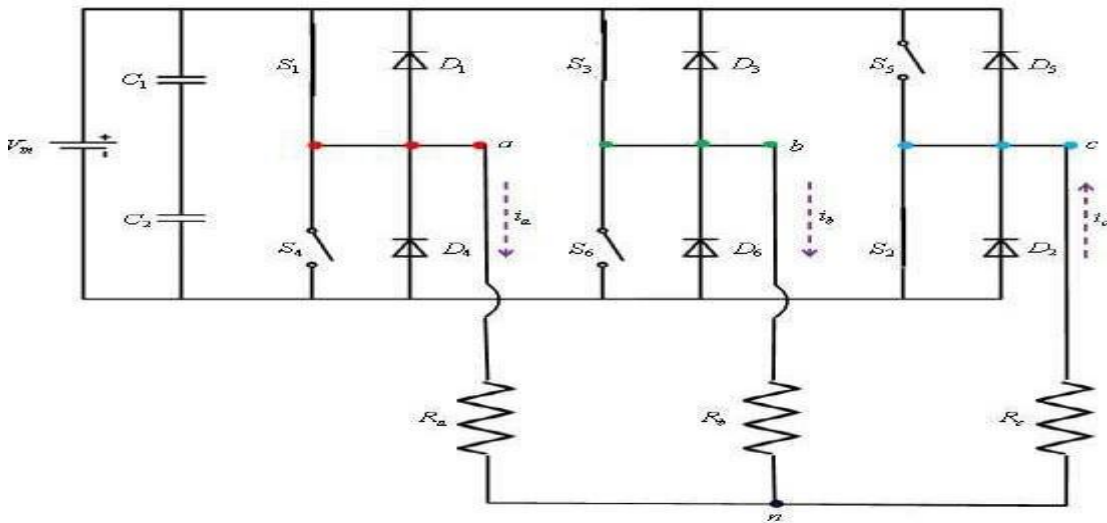


Figure: 5.21 Mode 3 operation of three phase bridge inverter with star connected load

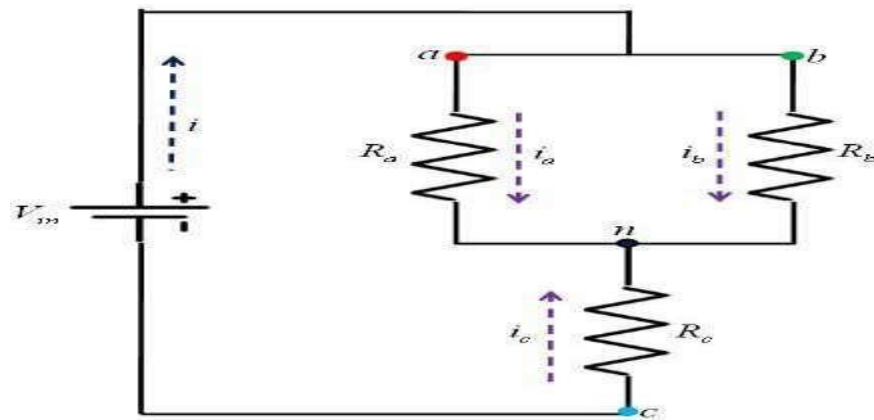


Figure: 5.23 Current flow in Mode 3 operation

For *modes 4, 5* and *6* the equivalent circuits will be same as *modes 1, 2* and *3* respectively.

The voltages and currents for each mode are:

$$\left. \begin{aligned} i_a = i_c = -\frac{1}{3} \frac{V_{in}}{R}, i_b = \frac{2}{3} \frac{V_{in}}{R} \\ v_{an} = v_{cn} = -\frac{V_{in}}{3}, V_{bn} = \frac{2V_{in}}{3} \end{aligned} \right\} \text{for mode 4} \quad (10)$$

$$\left. \begin{aligned} i_b = i_c = -\frac{1}{3} \frac{V_{in}}{R}, i_a = \frac{2}{3} \frac{V_{in}}{R} \\ v_{bn} = v_{cn} = -\frac{V_{in}}{3}, V_{an} = \frac{2V_{in}}{3} \end{aligned} \right\} \text{for mode 5} \quad (11)$$

$$\left. \begin{aligned} i_a = i_b = -\frac{1}{3} \frac{V_{in}}{R}, i_c = \frac{2}{3} \frac{V_{in}}{R} \\ v_{an} = v_{bn} = -\frac{V_{in}}{3}, V_{cn} = \frac{2V_{in}}{3} \end{aligned} \right\} \text{for mode 6} \quad (12)$$

The plots of the phase voltages (v_{an} , v_{bn} and v_{cn}) and the currents (i_a , i_b and i_c) are shown in **Figure**

Having known the phase voltages, the line voltages can also be determined as:

$$\begin{aligned} v_{ab} &= v_{an} - v_{bn} \\ v_{bc} &= v_{bn} - v_{cn} \\ v_{ca} &= v_{cn} - v_{an} \end{aligned} \quad (13)$$

The plots of line voltages are also shown in **Figure** and the phase and line voltages can be expressed in terms of Fourier series as:

Mode 2 : In this mode the switches S_6 , S_1 and S_2 are turned **on** for time interval $\frac{\pi}{3} \leq \omega t \leq \frac{2\pi}{3}$.

The current flow and the equivalent circuits are shown in **Figure** and **Figure** respectively.

Following the reasoning given for *mode 1*, the currents through each branch and the voltage drops are given by

$$i_b = i_c = \frac{1}{3} \frac{V_{in}}{R}; i_a = -\frac{2}{3} \frac{V_{in}}{R} \quad (6)$$

$$v_{bn} = v_{cn} = \frac{V_{in}}{3}; v_{an} = -\frac{2V_{in}}{3} \quad (7)$$

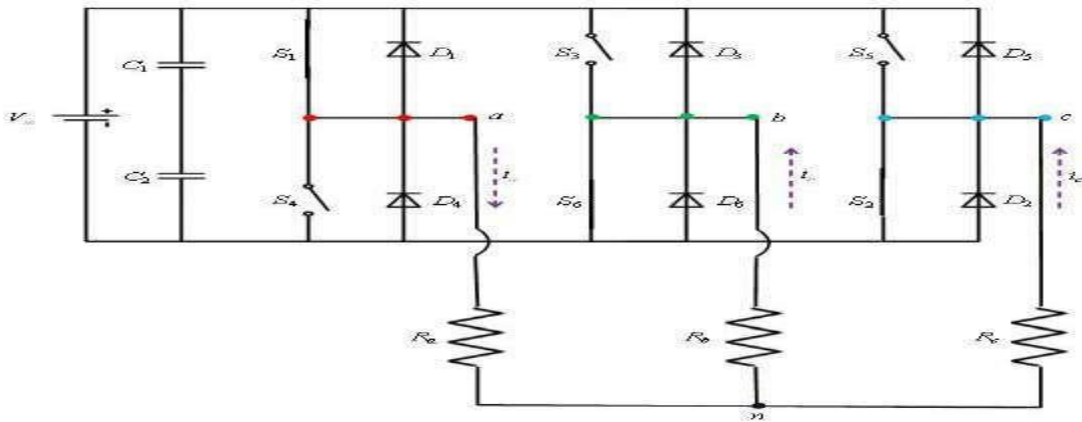


Figure: 5.19 Mode 2 operation of three phase bridge inverter with star connected load

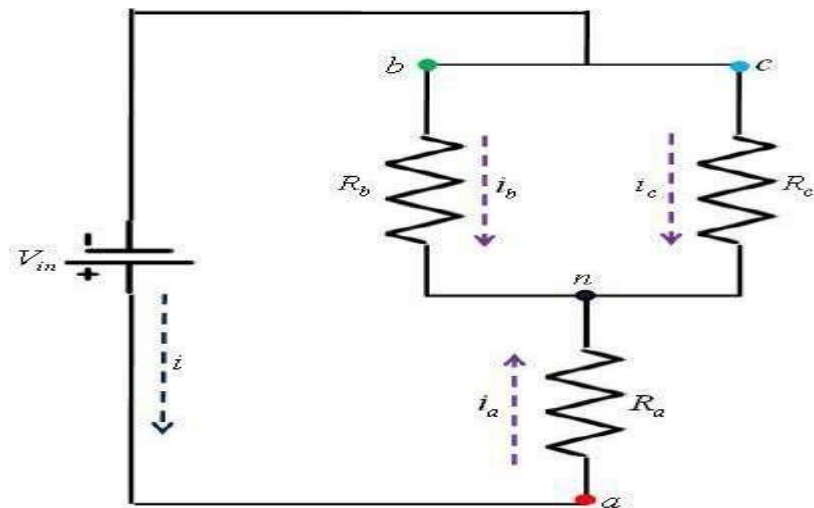


Figure: 5.20 Current flow in Mode 2 operation

Mode 3 : In this mode the switches S_1 , S_2 and S_3 are **on** for $\frac{2\pi}{3} \leq \omega t \leq \pi$. The current flow and the equivalent circuits are shown in **Figure** and **figure** respectively. The magnitudes of currents and voltages are:

$$i_a = i_b = \frac{1}{3} \frac{V_{in}}{R}; \quad i_c = -\frac{2}{3} \frac{V_{in}}{R} \quad (8)$$

$$v_{an} = v_{bn} = \frac{V_{in}}{3}; \quad v_{cn} = -\frac{2V_{in}}{3} \quad (9)$$

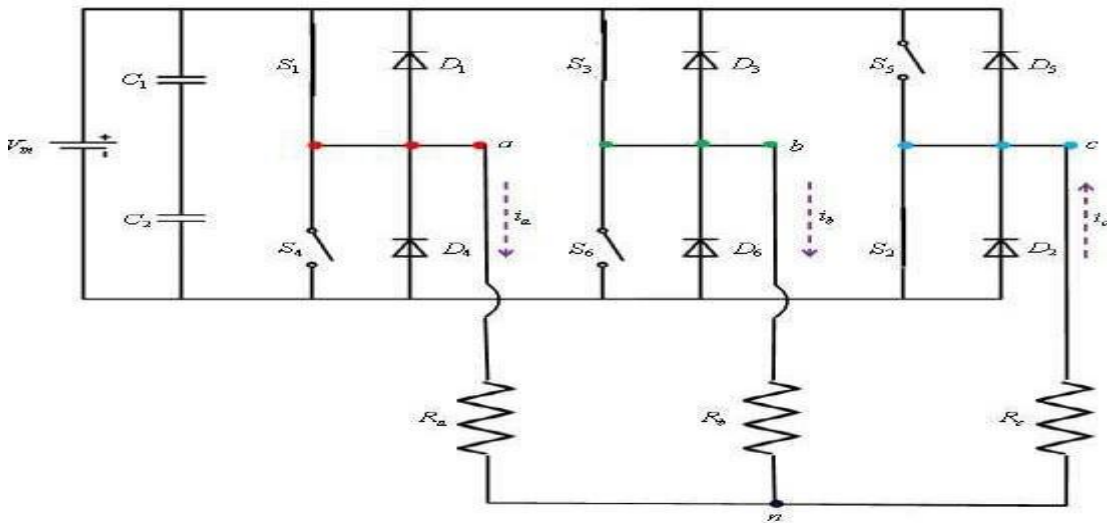


Figure: 5.21 Mode 3 operation of three phase bridge inverter with star connected load

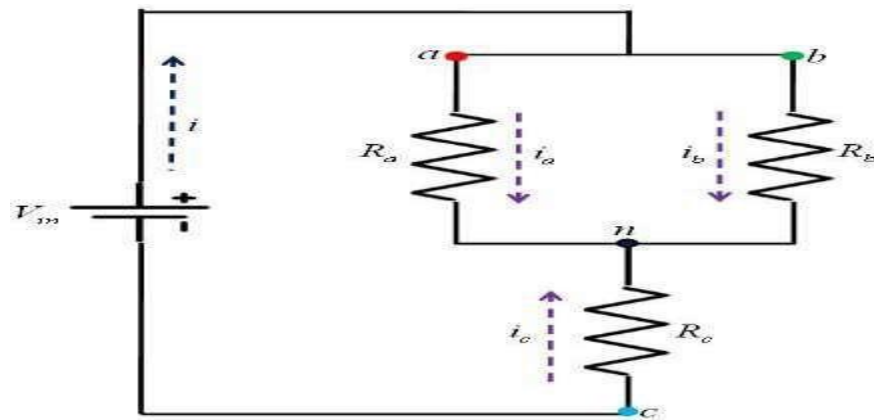


Figure: 5.23 Current flow in Mode 3 operation

For **modes 4, 5** and **6** the equivalent circuits will be same as **modes 1, 2** and **3** respectively.

The voltages and currents for each mode are:

$$\left. \begin{aligned} i_a = i_c = -\frac{1}{3} \frac{V_{in}}{R}; i_b = \frac{2}{3} \frac{V_{in}}{R} \\ v_{an} = v_{cn} = -\frac{V_{in}}{3}; v_{bn} = \frac{2V_{in}}{3} \end{aligned} \right\} \text{for mode 4} \quad (10)$$

$$\left. \begin{aligned} i_b = i_c = -\frac{1}{3} \frac{V_{in}}{R}; i_a = \frac{2}{3} \frac{V_{in}}{R} \\ v_{bn} = v_{cn} = -\frac{V_{in}}{3}; v_{an} = \frac{2V_{in}}{3} \end{aligned} \right\} \text{for mode 5} \quad (11)$$

$$\left. \begin{aligned} i_a = i_b = -\frac{1}{3} \frac{V_{in}}{R}; i_c = \frac{2}{3} \frac{V_{in}}{R} \\ v_{an} = v_{bn} = -\frac{V_{in}}{3}; v_{cn} = \frac{2V_{in}}{3} \end{aligned} \right\} \text{for mode 6} \quad (12)$$

The plots of the phase voltages (v_{an} , v_{bn} and v_{cn}) and the currents (i_a , i_b and i_c) are shown in **Figure**

Having known the phase voltages, the line voltages can also be determined as:

$$\begin{aligned} v_{ab} &= v_{an} - v_{bn} \\ v_{bc} &= v_{bn} - v_{cn} \\ v_{ca} &= v_{cn} - v_{an} \end{aligned} \quad (13)$$


The plots of line voltages are also shown in **Figure** and the phase and line voltages can be expressed in terms of Fourier series as:

$$\begin{aligned} v_{an} &= \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_{in}}{3n\pi} \left[1 + \sin \frac{n\pi}{2} \sin \frac{n\pi}{6} \right] \sin(n\omega t) \\ v_{bn} &= \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_{in}}{3n\pi} \left[1 + \sin \frac{n\pi}{2} \sin \frac{n\pi}{6} \right] \sin\left(n\omega t - \frac{2n\pi}{3}\right) \\ v_{cn} &= \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_{in}}{3n\pi} \left[1 + \sin \frac{n\pi}{2} \sin \frac{n\pi}{6} \right] \sin\left(n\omega t - \frac{4n\pi}{3}\right) \end{aligned}$$

$$v_{ab} = v_{an} - v_{bn} = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_{in}}{n\pi} \sin \frac{n\pi}{2} \sin \frac{n\pi}{3} \sin \left(n\alpha t + \frac{n\pi}{6} \right)$$

$$v_{bc} = v_{bn} - v_{cn} = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_{in}}{n\pi} \sin \frac{n\pi}{2} \sin \frac{n\pi}{3} \sin \left(n\alpha t - \frac{n\pi}{2} \right)$$
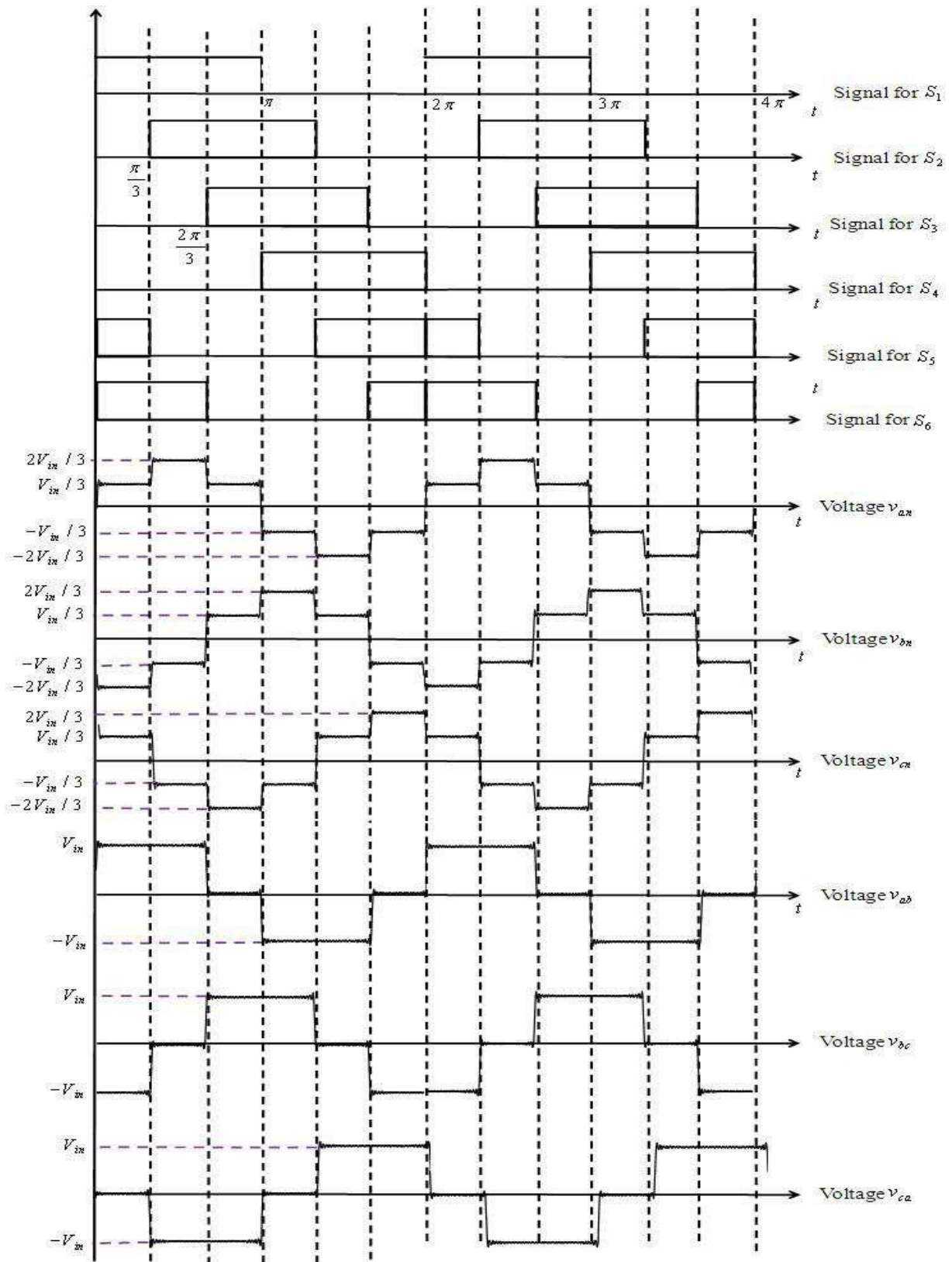
$$v_{ca} = v_{cn} - v_{an} = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_{in}}{n\pi} \sin \frac{n\pi}{2} \sin \frac{n\pi}{3} \sin \left(n\alpha t - \frac{7n\pi}{6} \right)$$



Three Phase DC-AC Converters with 120 degree conduction mode

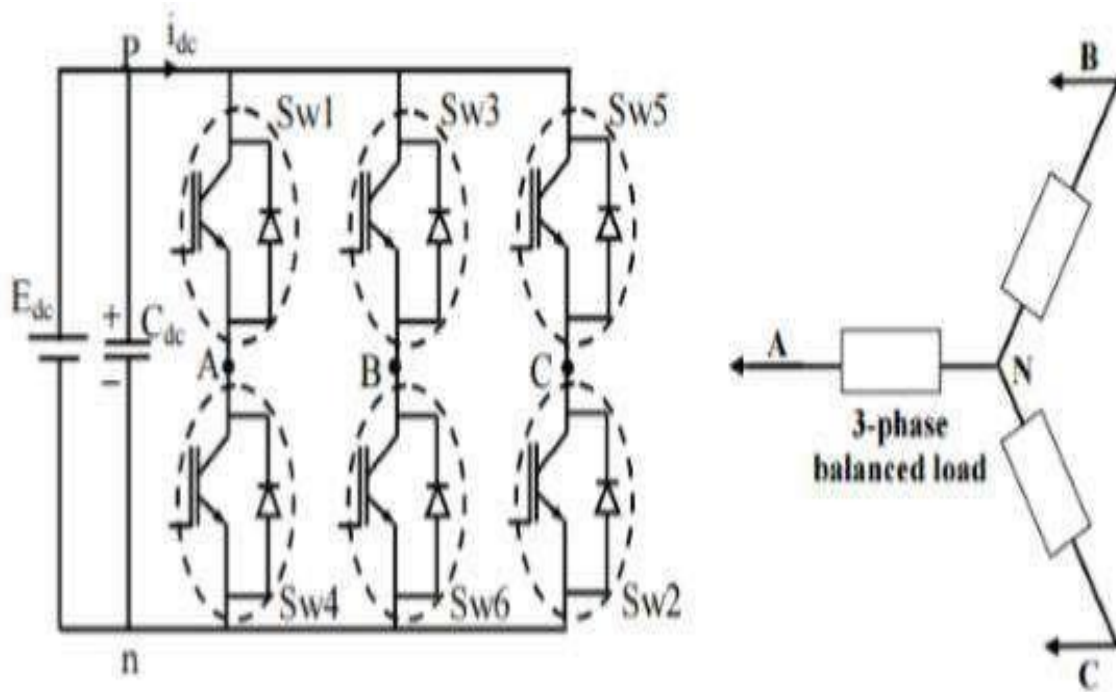


Figure: 5.25 Circuit diagram of three phase bridge inverter

120° mode of conduction


In this mode of conduction, each electronic device is in a conduction state for 120°. It is most suitable for a delta connection in a load because it results in a six-step type of waveform across any of its phases. Therefore, at any instant only two devices are conducting because each device conducts at only 120°.

The terminal A on the load is connected to the positive end while the terminal B is connected to the negative end of the source. The terminal C on the load is in a condition called floating state. Furthermore, the phase voltages are equal to the load voltages as shown below.

Phase voltages = Line voltages $V_{AB} = V$

$$V_{BC} = -V/2$$

$$V_{CA} = -V/2$$

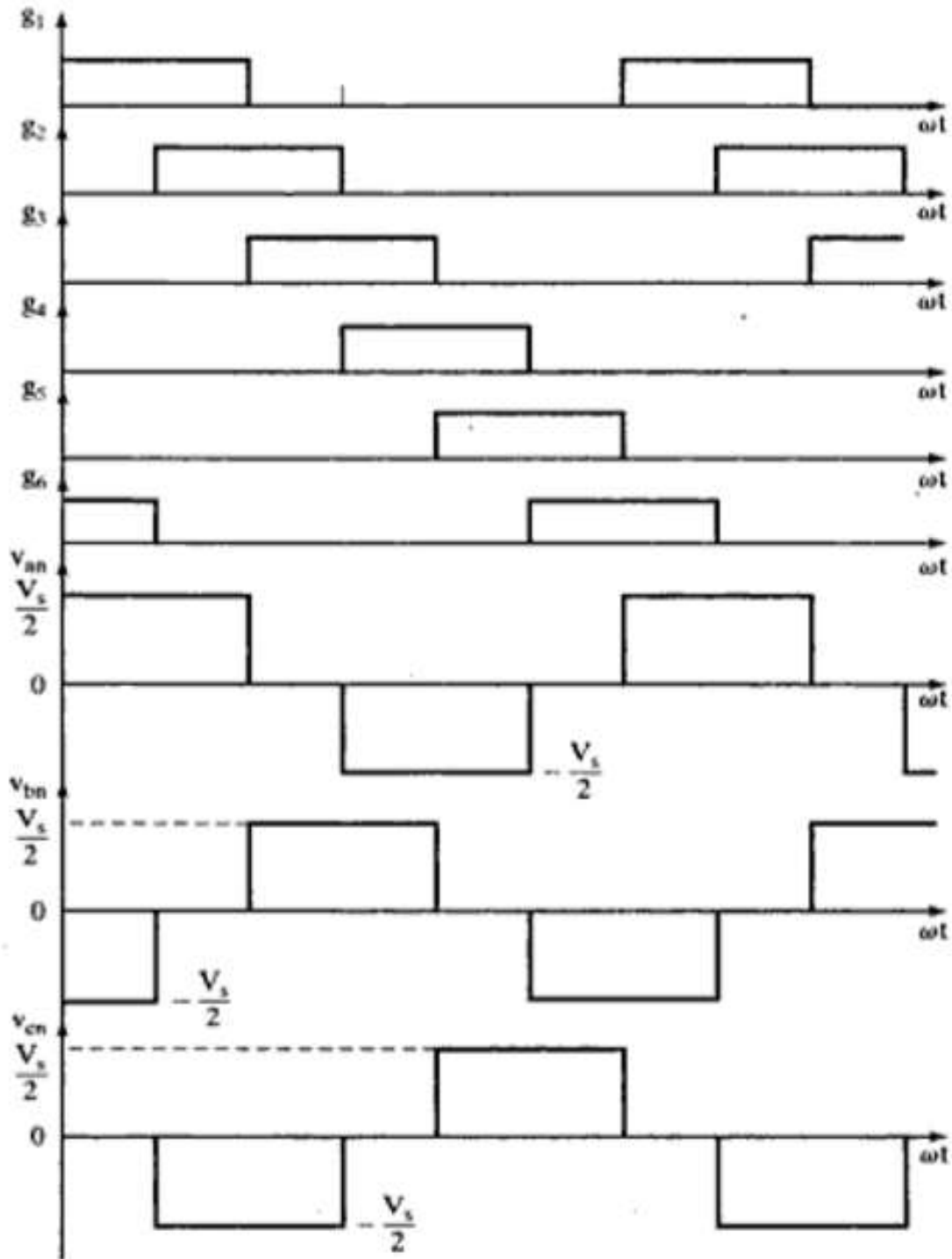

Voltage control techniques for inverters

Pulse width modulation techniques

PWM is a technique that is used to reduce the overall harmonic distortion (THD) in a load current. It uses a pulse wave in rectangular/square form that results in a variable average waveform value $f(t)$, after its pulse width has been modulated. The time period for modulation

is given by T. Therefore, waveform average value is given by

$$y = \frac{1}{T} \int_0^T f(t) dt$$

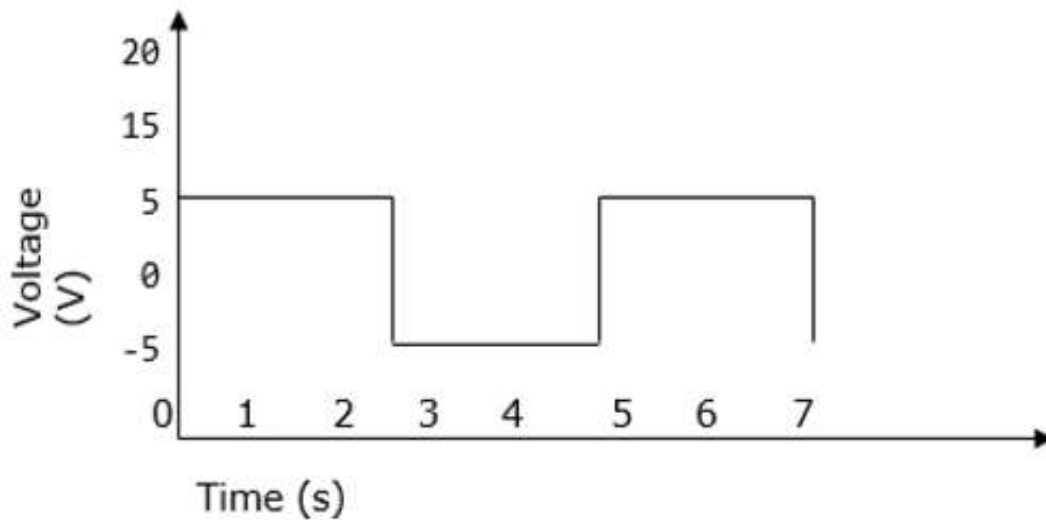


Figure: 5.27 Square waveform used for PWM technique

Sinusoidal Pulse Width Modulation

In a simple source voltage inverter, the switches can be turned ON and OFF as needed. During each cycle, the switch is turned on or off once. This results in a square waveform. However, if the switch is turned on for a number of times, a harmonic profile that is improved waveform is obtained.

The sinusoidal PWM waveform is obtained by comparing the desired modulated waveform with a triangular waveform of high frequency. Regardless of whether the voltage of the signal is smaller or larger than that of the carrier waveform, the resulting output voltage of the DC bus is either negative or positive.

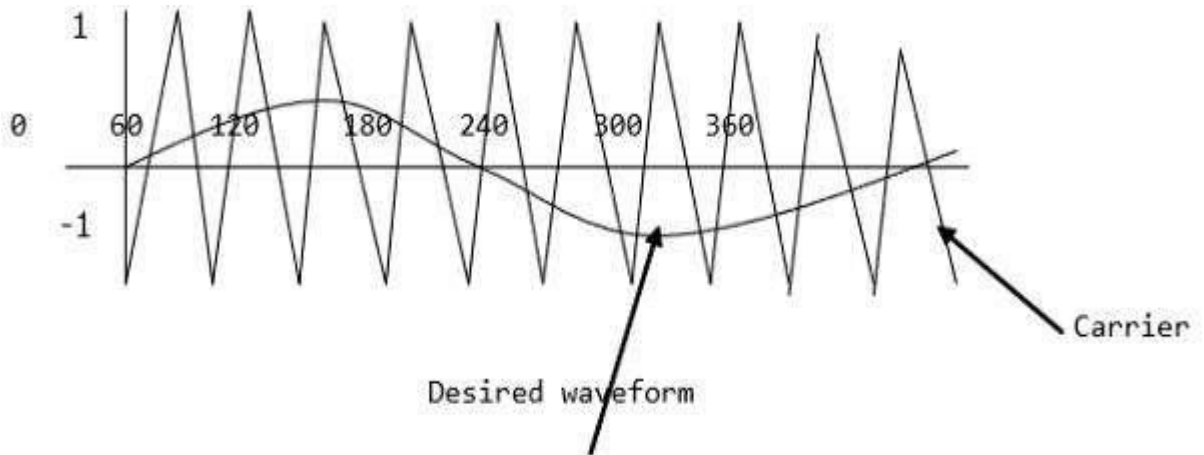


Figure: 5.28 Sinusoidal PWM waveform

The sinusoidal amplitude is given as A_m and that of the carrier triangle is given as A_c . For sinusoidal PWM, the modulating index m is given by A_m/A_c .

Modified Sinusoidal Waveform PWM

A modified sinusoidal PWM waveform is used for power control and optimization of the power factor. The main concept is to shift current delayed on the grid to the voltage grid by modifying the PWM converter. Consequently, there is an improvement in the efficiency of power as well as optimization in power factor.

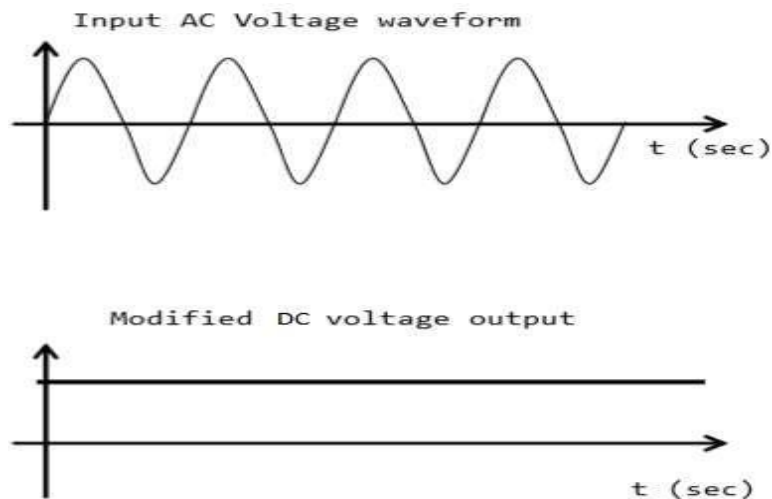


Figure: 5.29 Modified sinusoidal PWM waveform

Multiple PWM

The multiple PWM has numerous outputs that are not the same in value but the time period over which they are produced is constant for all outputs. Inverters with PWM are able to operate at high voltage output.

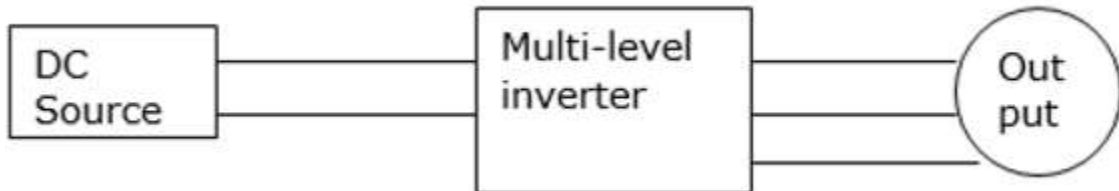


Figure: 5.30 Block diagram of multiple PWM technique

The waveform below is a sinusoidal wave produced by a multiple PWM

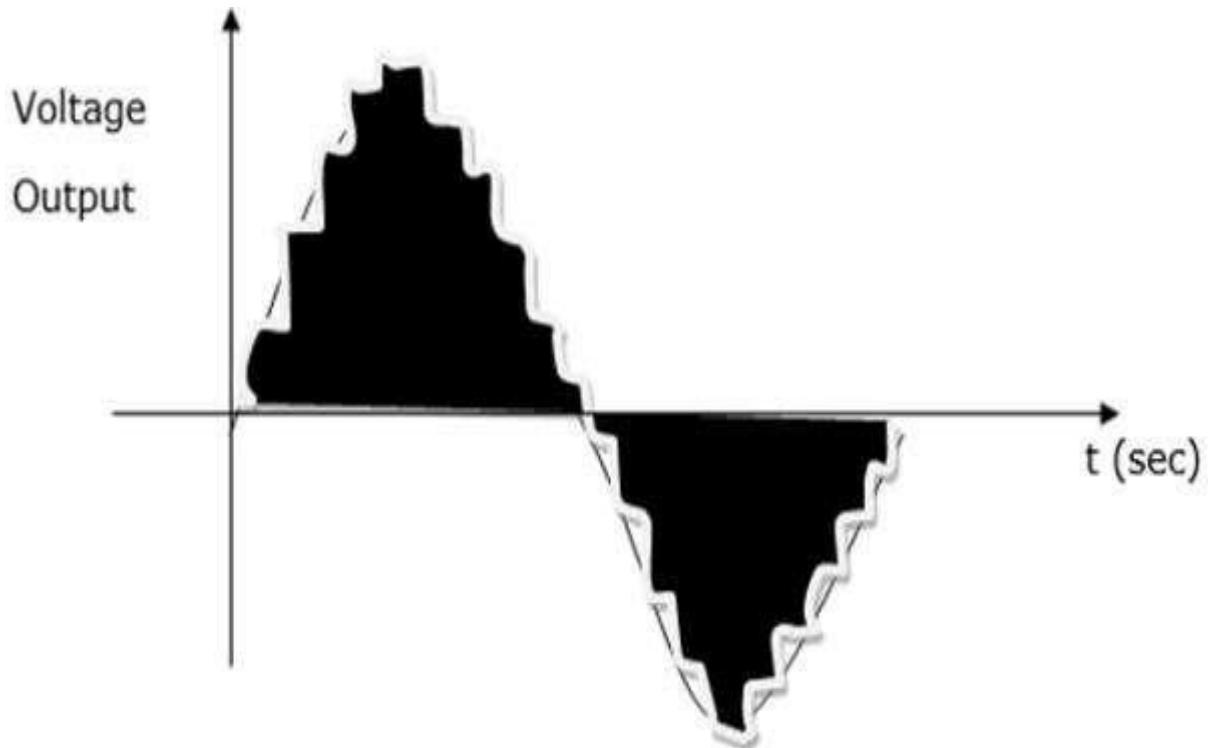


Figure: 5.31 Waveform of multiple PWM technique

Operation of sinusoidal pulse width modulation

The sinusoidal PWM (SPWM) method also known as the triangulation, sub harmonic, or sub oscillation

method, is very popular in industrial applications. The SPWM is explained with reference to Figure, which is the half-bridge circuit topology for a single-phase inverter.

For realizing SPWM, a high-frequency triangular carrier wave is compared with a sinusoidal reference of the desired frequency. The intersection of the two waves determines the switching instants and commutation of the modulated pulse. The PWM scheme is illustrated in Figure, in which v_c is the peak value of the triangular carrier wave and v_r is that of the reference, or modulating signal. The figure shows the triangle and modulation signal with some arbitrary frequency and magnitude. In the inverter of Figure the switches are controlled based on the comparison of the control signal and the triangular wave which are mixed in a comparator. When the sinusoidal wave has a magnitude higher than the triangular wave, the comparator output is high, otherwise it is low.

$$v_r > v_c \quad S_{11} \text{ is on, } V_{out} = \frac{V_d}{2}$$

and

$$v_r < v_c \quad S_{12} \text{ is on, } V_{out} = -\frac{V_d}{2}$$


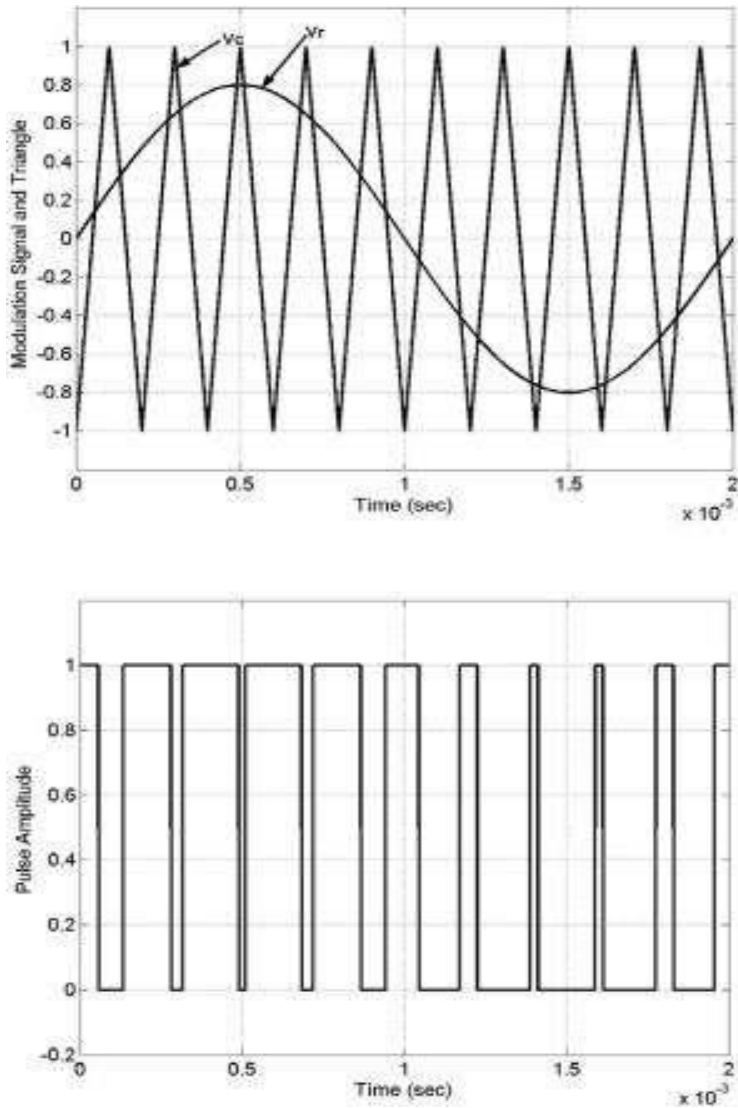


Figure: 5.33 Sine-Triangle Comparison and switching pulses of half bridge PWM inverter

The comparator output is processed in a trigger pulse generator in such a manner that the output voltage wave of the inverter has a pulse width in agreement with the comparator output pulse width. The magnitude ratio of V_r/V_c is called the modulation index (MI) and it controls the harmonic content of the output voltage waveform. The magnitude of the fundamental component of output voltage is proportional to MI. The amplitude of the triangular wave is generally kept constant. The frequency modulation ratio is defined as


$$M_F = \frac{f_r}{f_m}$$

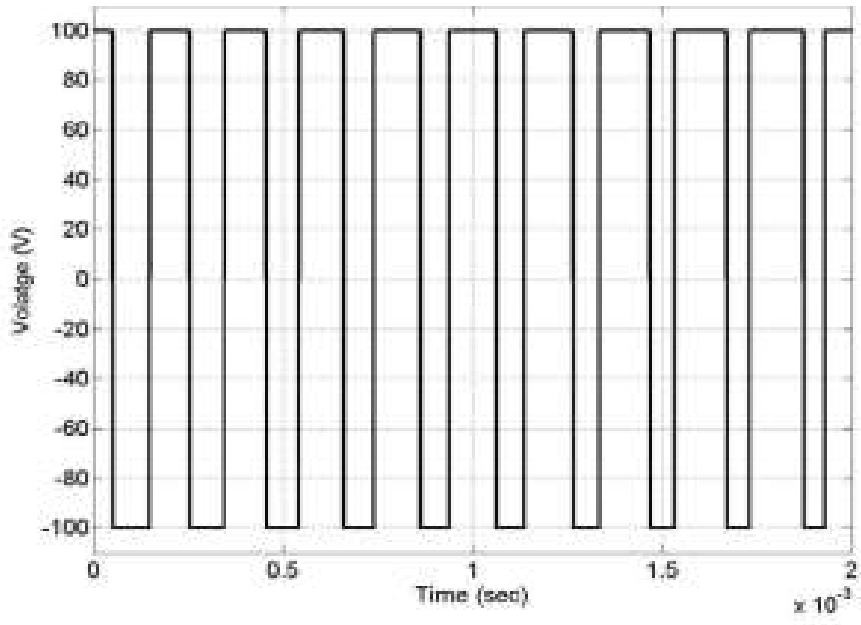

UNIT-V

AC-AC CONVERTERS:

AC voltage controllers (ac line voltage controllers) are employed to vary the RMS value of the alternating voltage applied to a load circuit by introducing Thyristors between the load and a constant voltage ac source. The RMS value of alternating voltage applied to a load circuit is controlled by controlling the triggering angle of the Thyristors in the ac voltage controller circuits. In brief, an ac voltage controller is a type of thyristor power converter which is used to convert a fixed voltage, fixed frequency ac input supply to obtain a variable voltage ac output. The RMS value of the ac output voltage and the ac power flow to the load is controlled by varying (adjusting) the trigger angle ' α '

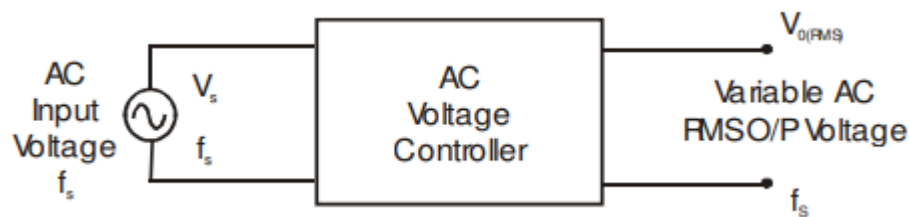

• Type of Ac Voltage Controllers

The ac voltage controllers are classified into two types based on the type of input ac supply applied to the circuit. www.getmyuni.com Page 217

- Single Phase AC Controllers.
- Three Phase AC Controllers. Single phase ac controllers operate with single phase ac supply voltage of 230V RMS at 50Hz in our country. Three phase ac controllers operate with 3 phase ac supply of 400V RMS at 50Hz supply frequency. Each type of controller may be sub divided into
 - Uni-directional or half wave ac controller.
 - Bi-directional or full wave ac controller. In brief different types of ac voltage controllers are •
- Single phase half wave ac voltage controller (uni-directional controller)
- Single phase full wave ac voltage controller (bi-directional controller)
- Three phase half wave ac voltage controller (uni-directional controller).
- Three phase full wave ac voltage controller (bi-directional controller).

Applications of Ac Voltage Controllers

- Lighting / Illumination control in ac power circuits.
- Induction heating.
- Industrial heating & Domestic heating.
- Transformer tap changing (on load transformer tap changing).
- Speed control of induction motors (single phase and poly phase ac induction motor)

Principle of AC Phase Control :

The basic principle of ac phase control technique is explained with reference to a single phase half wave ac voltage controller (unidirectional controller) circuit shown in the below figure. The half wave ac controller uses one thyristor and one diode connected in parallel across each other in opposite direction that is anode of thyristor T1 is connected to the cathode of diode D1 and the cathode of T1 is connected to the anode of D1 . The output voltage across the load resistor 'R' and

hence the ac power flow to the load is controlled by varying the trigger angle ' α '. The trigger angle or the delay angle ' α ' refers to the value of ωt or the instant at which the thyristor T1 is triggered to turn it ON, by applying a suitable gate trigger pulse between the gate and cathode lead. The thyristor T1 is forward biased during the positive half cycle of input ac supply. It can be triggered and made to conduct by applying a suitable gate trigger pulse only during the positive half cycle of input supply. When T1 is triggered it conducts and the load current flows through the thyristor T1, the load and through the transformer secondary winding.

By assuming T1 as an ideal thyristor switch it can be considered as a closed switch when it is ON during the period $\omega t = \alpha$ to π radians. The output voltage across the load follows the input supply voltage when the thyristor T1 is turned-on and when it conducts from $\omega t = \alpha$ to π radians. When the input supply voltage decreases to zero at $\omega t = \pi$, for a resistive load the load current also falls to zero at $\omega t = \pi$ and hence the thyristor T1 turns off at $\omega t = \pi$. Between the time period $\omega t = \pi$ to 2π , when the supply voltage reverses and becomes negative the diode D1 becomes forward biased and hence turns ON and conducts. The load current flows in the opposite direction during $\omega t = \pi$ to 2π radians when D1 is ON and the output voltage follows the negative half cycle of input supply.


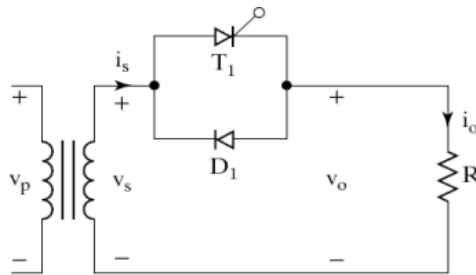


Fig 6.4: Halfwave AC phase controller (Unidirectional Controller)

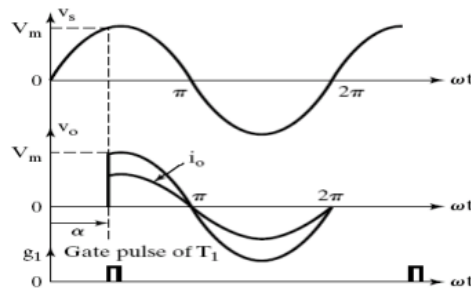

Output Load Voltage

$$v_o = v_L = 0; \text{ for } \omega t = 0 \text{ to } \alpha$$

$$v_o = v_L = V_m \sin \omega t; \text{ for } \omega t = \alpha \text{ to } 2\pi.$$

Output Load Current

$$i_o = i_L = \frac{v_o}{R_L} = \frac{V_m \sin \omega t}{R_L}; \text{ for } \omega t = \alpha \text{ to } 2\pi.$$

$$i_o = i_L = 0; \text{ for } \omega t = 0 \text{ to } \alpha.$$

(i) To Derive an Expression for rms Output Voltage $V_{O(RMS)}$.

$$V_{O(RMS)} = \sqrt{\frac{1}{2\pi} \left[\int_{\alpha}^{2\pi} V_m^2 \sin^2 \omega t . d(\omega t) \right]}$$

$$V_{O(RMS)} = \sqrt{\frac{V_m^2}{2\pi} \left[\int_{\alpha}^{2\pi} \left(\frac{1 - \cos 2\omega t}{2} \right) . d(\omega t) \right]}$$

$$V_{O(RMS)} = \sqrt{\frac{V_m^2}{4\pi} \left[\int_{\alpha}^{2\pi} (1 - \cos 2\omega t) . d(\omega t) \right]}$$

$$V_{O(RMS)} = \frac{V_m}{2\sqrt{\pi}} \sqrt{\left[\int_{\alpha}^{2\pi} d(\omega t) - \int_{\alpha}^{2\pi} \cos 2\omega t . d\omega t \right]}$$

$$V_{O(RMS)} = \frac{V_m}{2\sqrt{\pi}} \sqrt{\left[\frac{(\omega t)}{\alpha} \Big|_{\alpha}^{2\pi} - \left(\frac{\sin 2\omega t}{2} \right) \Big|_{\alpha}^{2\pi} \right]}$$

$$V_{O(RMS)} = \frac{V_m}{2\sqrt{\pi}} \sqrt{\left(2\pi - \alpha \right) - \left(\frac{\sin 2\omega t}{2} \right) \Big|_{\alpha}^{2\pi}}$$

$$V_{O(RMS)} = \frac{V_m}{2\sqrt{\pi}} \sqrt{\left(2\pi - \alpha \right) - \left\{ \frac{\sin 4\pi}{2} - \frac{\sin 2\alpha}{2} \right\}} \quad ; \sin 4\pi = 0$$

$$V_{O(RMS)} = \frac{V_m}{2\sqrt{\pi}} \sqrt{\left(2\pi - \alpha \right) + \frac{\sin 2\alpha}{2}}$$

$$V_{O(RMS)} = \frac{V_m}{\sqrt{2}\sqrt{2\pi}} \sqrt{\left(2\pi - \alpha \right) + \frac{\sin 2\alpha}{2}}$$

$$V_{O(RMS)} = \frac{V_m}{\sqrt{2}} \sqrt{\frac{1}{2\pi} \left[\left(2\pi - \alpha \right) + \frac{\sin 2\alpha}{2} \right]}$$

$$V_{O(RMS)} = V_{i(RMS)} \sqrt{\frac{1}{2\pi} \left[\left(2\pi - \alpha \right) + \frac{\sin 2\alpha}{2} \right]}$$

$$V_{O(RMS)} = V_s \sqrt{\frac{1}{2\pi} \left[\left(2\pi - \alpha \right) + \frac{\sin 2\alpha}{2} \right]}$$


Where, $V_{i(RMS)} = V_s = \frac{V_m}{\sqrt{2}}$ = RMS value of input supply voltage (across the

transformer secondary winding).

Single Phase Full Wave Ac Voltage Controller (Ac Regulator) or Rms Voltage Controller with Resistive Load :

Single phase full wave ac voltage controller circuit using two SCRs or a single triac is generally used in most of the ac control applications. The ac power flow to the load can be controlled in both the half cycles by varying the trigger angle ' α ' .

The RMS value of load voltage can be varied by varying the trigger angle ' α ' . The input supply current is alternating in the case of a full wave ac voltage controller and due to the symmetrical nature of the input supply current waveform there is no dc component of input supply current i.e., the average value of the input supply current is zero. A single phase full wave ac voltage controller with a resistive load is shown in the figure below. It is possible to control the ac power flow to the load in both the half cycles by adjusting the trigger angle ' α ' . Hence the full wave ac voltage controller is also referred to as to as to a bi directional controller.

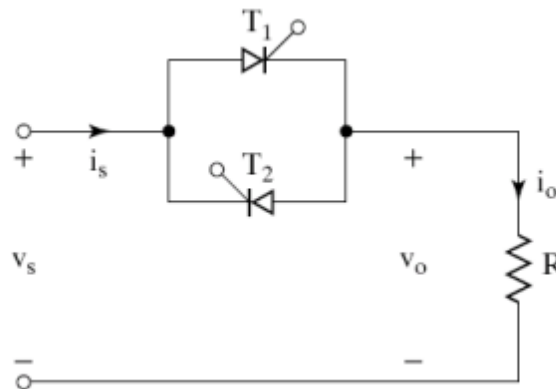

The thyristor T1 is forward biased during the positive half cycle of the input supply voltage. The thyristor T1 is triggered at a delay angle of ' α ' ($0 \leq \alpha \leq \pi$) . Considering the ON thyristor T1 as an ideal closed switch the input supply voltage appears across the load resistor RL and the output voltage $v_o = v_s$ during $\omega t = \alpha$ to π radians. The load current flows through the ON thyristor T1 and through the load resistor RL in the downward direction during the conduction time of T1 from $\omega t = \alpha$ to π radians.

At $\omega t = \pi$, when the input voltage falls to zero the thyristor current (which is flowing through the load resistor RL) falls to zero and hence T1 naturally turns off . No current flows in the circuit during $\omega t = \pi$ to $(\pi + \alpha)$.

The thyristor T2 is forward biased during the negative cycle of input supply and when thyristor T2 is triggered at a delay angle $(\pi + \alpha)$, the output voltage follows the negative half cycle of input from $\omega t = (\pi + \alpha)$ to 2π . When T2 is ON, the load current flows in the reverse direction (upward direction) through T2 during $\omega t = (\pi + \alpha)$ to 2π radians. The time interval (spacing) between the gate trigger pulses of T1 and T2 is kept at π radians or 180° . At $\omega t = 2\pi$ the input supply voltage falls to zero and hence the load current also falls to zero and thyristor T2 turn off naturally.

- (i) To Derive an Expression for the Rms Value of Output (Load) Voltage The RMS value of output voltage (load voltage) can be found using the expression

$$V_{O(RMS)}^2 = V_{L(RMS)}^2 = \frac{1}{2\pi} \int_0^{2\pi} v_L^2 d(\omega t);$$

For a full wave ac voltage controller, we can see that the two half cycles of output voltage waveforms are symmetrical and the output pulse time period (or output pulse repetition time) is π radians. Hence we can also calculate the RMS output voltage by using the expression given below.


$$V_{L(RMS)}^2 = \frac{1}{\pi} \int_0^{\pi} V_m^2 \sin^2 \omega t .d \omega t$$

$$V_{L(RMS)}^2 = \frac{1}{2\pi} \int_0^{2\pi} v_L^2 .d(\omega t) ;$$

$$v_L = v_o = V_m \sin \omega t ; \text{ For } \omega t = \alpha \text{ to } \pi \text{ and } \omega t = (\pi + \alpha) \text{ to } 2\pi$$

Hence,

$$\begin{aligned} V_{L(RMS)}^2 &= \frac{1}{2\pi} \left[\int_{\alpha}^{\pi} (V_m \sin \omega t)^2 d(\omega t) + \int_{\pi+\alpha}^{2\pi} (V_m \sin \omega t)^2 d(\omega t) \right] \\ &= \frac{1}{2\pi} \left[V_m^2 \int_{\alpha}^{\pi} \sin^2 \omega t .d(\omega t) + V_m^2 \int_{\pi+\alpha}^{2\pi} \sin^2 \omega t .d(\omega t) \right] \\ &= \frac{V_m^2}{2\pi} \left[\int_{\alpha}^{\pi} \frac{1 - \cos 2\omega t}{2} d(\omega t) + \int_{\pi+\alpha}^{2\pi} \frac{1 - \cos 2\omega t}{2} d(\omega t) \right] \end{aligned}$$

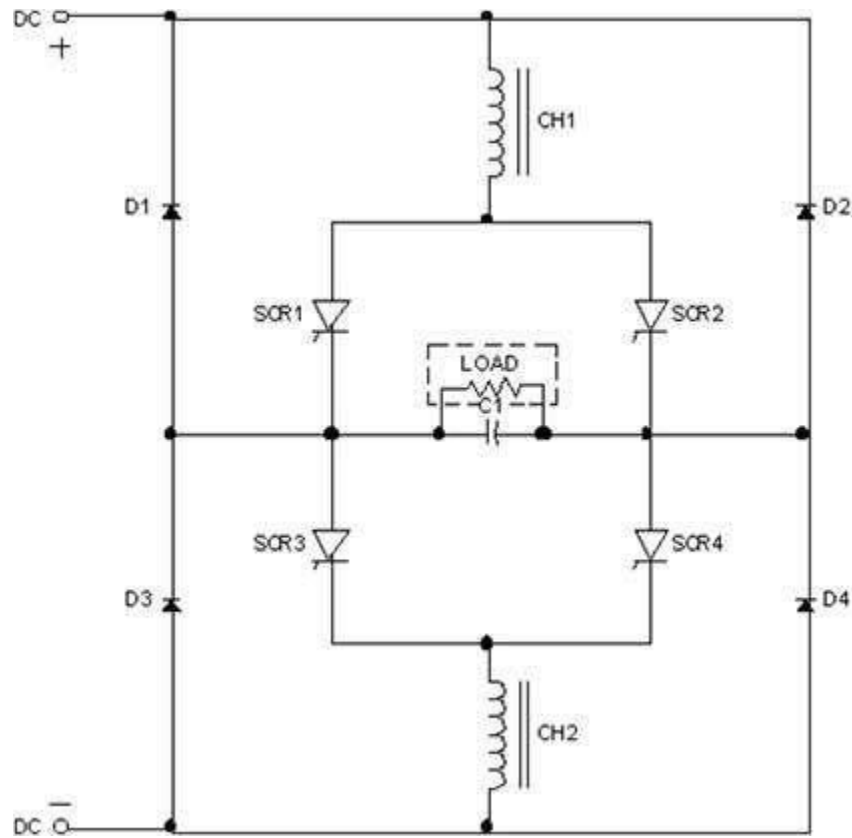

$$\begin{aligned}
 &= \frac{V_m^2}{2\pi \times 2} \left[\int_{\alpha}^{\pi} d(\omega t) - \int_{\alpha}^{\pi} \cos 2\omega t \cdot d(\omega t) + \int_{\pi+\alpha}^{2\pi} d(\omega t) - \int_{\pi+\alpha}^{2\pi} \cos 2\omega t \cdot d(\omega t) \right] \\
 &= \frac{V_m^2}{4\pi} \left[(\omega t) \Big|_{\alpha}^{\pi} + (\omega t) \Big|_{\pi+\alpha}^{2\pi} - \left[\frac{\sin 2\omega t}{2} \right]_{\alpha}^{\pi} - \left[\frac{\sin 2\omega t}{2} \right]_{\pi+\alpha}^{2\pi} \right] \\
 &= \frac{V_m^2}{4\pi} \left[(\pi - \alpha) + (\pi - \alpha) - \frac{1}{2}(\sin 2\pi - \sin 2\alpha) - \frac{1}{2}(\sin 4\pi - \sin 2(\pi + \alpha)) \right] \\
 &= \frac{V_m^2}{4\pi} \left[2(\pi - \alpha) - \frac{1}{2}(0 - \sin 2\alpha) - \frac{1}{2}(0 - \sin 2(\pi + \alpha)) \right] \\
 &= \frac{V_m^2}{4\pi} \left[2(\pi - \alpha) + \frac{\sin 2\alpha}{2} + \frac{\sin 2(\pi + \alpha)}{2} \right] \\
 &= \frac{V_m^2}{4\pi} \left[2(\pi - \alpha) + \frac{\sin 2\alpha}{2} + \frac{\sin(2\pi + 2\alpha)}{2} \right]
 \end{aligned}$$

Therefore,


$$V_{L(RMS)}^2 = \frac{V_m^2}{4\pi} [(2\pi - 2\alpha) + \sin 2\alpha]$$

$$V_{L(RMS)} = V_s \sqrt{\frac{1}{\pi} \left[(\pi - \alpha) + \frac{\sin 2\alpha}{2} \right]}$$

Single Phase Full Wave Ac Voltage Controller (Bidirectional Controller) With RL Load:

In this section we will discuss the operation and performance of a single phase full wave ac voltage controller with RL load. In practice most of the loads are of RL type. For example if we consider a single phase full wave ac voltage controller controlling the speed of a single phase ac induction motor, the load which is the induction motor winding is an RL type of load, where R represents the motor winding resistance and L represents the motor winding inductance.


A single phase full wave ac voltage controller circuit (bidirectional controller) with an RL load using two thyristors T1 and T2 (T1 and T2 are two SCRs) connected in parallel is shown in the figure below. In place of two thyristors a single Triac can be used to implement a full wave ac controller, if a suitable Triac is available for the desired RMS load current and the RMS output voltage ratings.

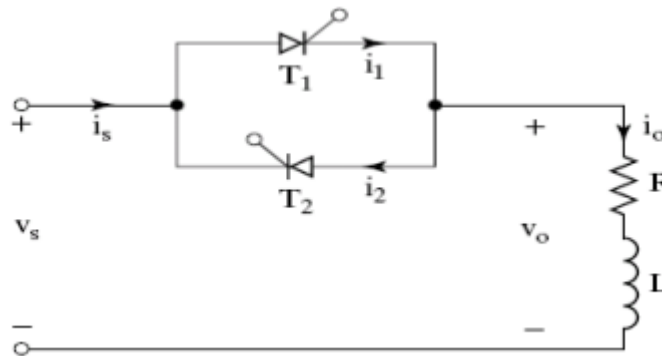


The thyristor T1 is forward biased during the positive half cycle of input supply. Let us assume that T1 is triggered at $\omega t = \alpha$, by applying a suitable gate trigger pulse to T1 during the positive half cycle of input supply. The output voltage across the load follows the input supply voltage when T1 is ON. The load current i_o flows through the thyristor T1 and through the load in the downward direction. This load current pulse flowing through T1 can be considered as the positive current pulse. Due to the inductance in the load, the load current i_o flowing through T1 would not fall to zero at $\omega t = \pi$, when the input supply voltage starts to become negative.

The thyristor T1 will continue to conduct the load current until all the inductive energy stored in the load inductor L is completely utilized and the load current through T1 falls to zero at $\omega t = \beta$, where β is referred to as the Extinction angle, (the value of ωt) at which the load current falls to zero. The extinction angle β is measured from the point of the beginning of the positive half cycle of input supply to the point where the load current falls to zero. The thyristor T1 conducts from $\omega t = \alpha$ to β . The conduction angle of T1 is $(\beta - \alpha)$, which depends on the delay angle α and the load impedance

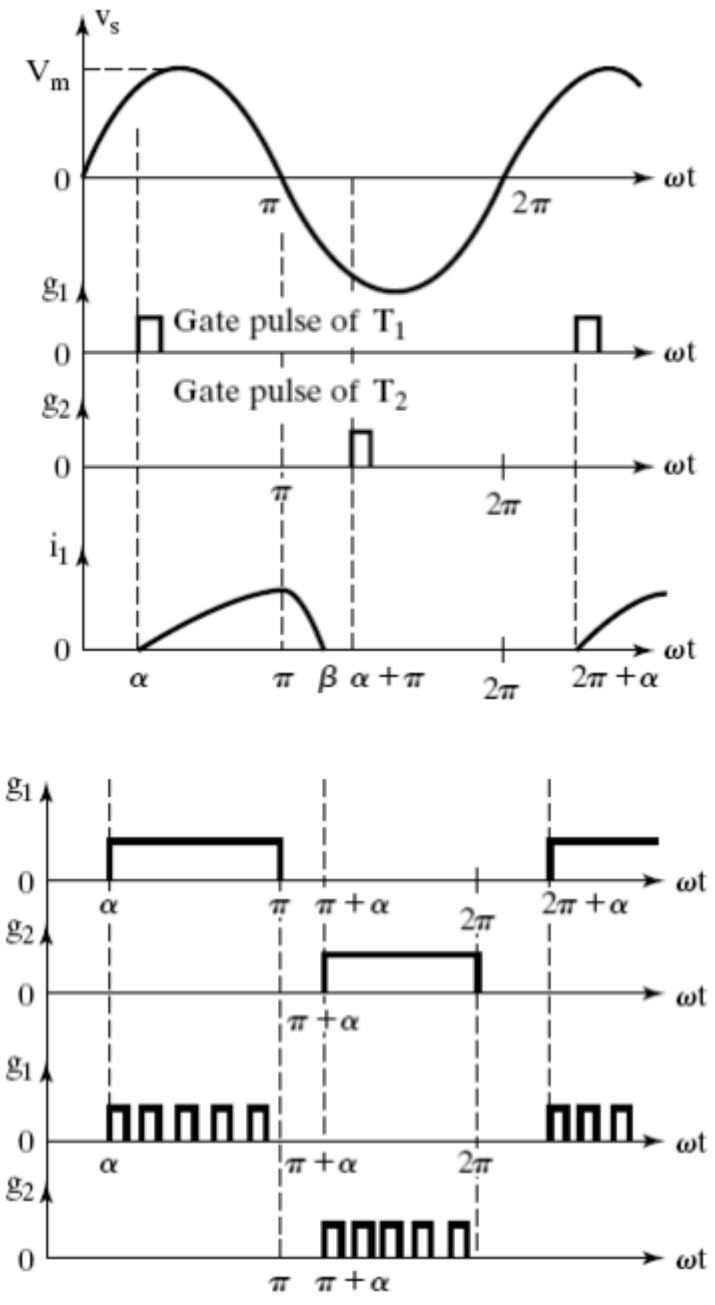angle ϕ . The waveforms of the input supply voltage, the gate trigger pulses of T1 and T2, the thyristor current, the load current and the load voltage waveforms appear as shown in the figure below



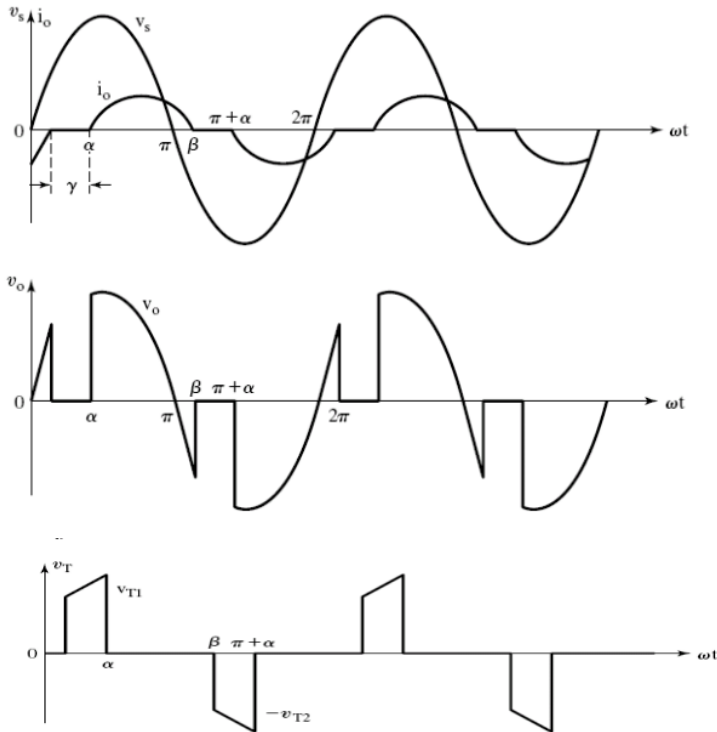Waveforms of single phase full wave ac voltage controller with RL load for $\alpha > \phi$. Discontinuous load current operation occurs for $\alpha > \phi$ and $\beta < \pi + \alpha$; i.e., $\beta < \pi + \alpha$, conduction angle



(i) To Derive an Expression for the Output (Inductive Load) Current, During t to = When Thyristor T1 Conducts

Considering sinusoidal input supply voltage we can write the expression for the supply voltage as $V_s = V_m \sin \omega t$ = instantaneous value of the input supply voltage.

Let us assume that the thyristor T1 is triggered by applying the gating signal to T1 at $\omega t = \alpha$. The load current which flows through the thyristor T1 during $\omega t = \alpha$ to β can be found from the equation

$$L \left(\frac{di_o}{dt} \right) + Ri_o = V_m \sin \omega t \ ;$$

The solution of the above differential equation gives the general expression for the output load current which is of the form

Where $V_m = \sqrt{2}V_s$ = maximum or peak value of input supply voltage.

$$\omega \quad Z = \sqrt{R^2 + (\omega L)^2} = \text{Load impedance.}$$

$$\omega \quad \phi = \tan^{-1} \left(\frac{\omega L}{R} \right) = \text{Load impedance angle (power factor angle of load).}$$

$$\tau = \frac{L}{R} = \text{Load circuit time constant.}$$


Therefore the general expression for the output load current is given by the equation

$$i_o = \frac{V_m}{Z} \sin(\omega t - \phi) + A_1 e^{-\frac{R}{L}t};$$

therefore we obtain the final expression for the inductive load current of a single phase full wave ac voltage controller with RL load as

$$i_o = \frac{V_m}{Z} \left[\sin(\omega t - \phi) - \sin(\alpha - \phi) e^{-\frac{R}{\omega L}(\omega t - \alpha)} \right]; \quad \text{Where } \alpha \leq t \leq \pi.$$

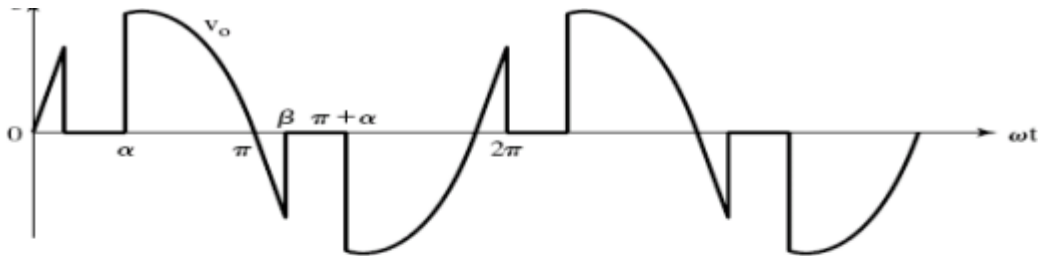(ii) To Derive an Expression For rms Output Voltage V_o (RMS) V of a Single Phase Full-Wave Ac Voltage Controller with RL Load.



When $\alpha > \phi$, the load current and load voltage waveforms become discontinuous as shown in the figure above.

$$V_{O(RMS)} = \left[\frac{1}{\pi} \int_{\alpha}^{\beta} V_m^2 \sin^2 \omega t \, d(\omega t) \right]^{1/2}$$

Output $v_o = V_m \sin \omega t$, for $t = \alpha$ to π , when T_1 is ON.

$$V_{O(RMS)} = \left[\frac{V_m^2}{\pi} \int_{\alpha}^{\beta} \frac{(1 - \cos 2\omega t)}{2} \, d(\omega t) \right]^{1/2}$$

$$V_{O(RMS)} = \left[\frac{V_m^2}{2\pi} \left\{ (\omega t) \Big|_{\alpha}^{\beta} - \left(\frac{\sin 2\omega t}{2} \right) \Big|_{\alpha}^{\beta} \right\} \right]^{1/2}$$

$$V_{O(RMS)} = \left[\frac{V_m^2}{2\pi} \left\{ (\beta - \alpha) - \frac{\sin 2\beta}{2} + \frac{\sin 2\alpha}{2} \right\} \right]^{1/2}$$

$$V_{O(RMS)} = V_m \left[\frac{1}{2\pi} \left\{ (\beta - \alpha) + \frac{\sin 2\alpha}{2} - \frac{\sin 2\beta}{2} \right\} \right]^{1/2}$$


$$V_{O(RMS)} = \frac{V_m}{\sqrt{2}} \left[\frac{1}{\pi} \left\{ (\beta - \alpha) + \frac{\sin 2\alpha}{2} - \frac{\sin 2\beta}{2} \right\} \right]^{1/2}$$

$$\phi = \tan^{-1} \left(\frac{\omega L}{R} \right) = 0 ;$$

$$\beta = \pi \text{ radians} = 180^\circ$$

Introduction to Cyclo converters

The **Cycloconverter** has been traditionally used only in very high power drives, usually above one megawatt, where no other type of drive can be used. Examples are cement tube mill drives above 5 MW, the 13 MW German-Dutch wind tunnel fan drive, reversible rolling mill drives and ship propulsion drives. The reasons for this are that the traditional **Cycloconverter** requires a large number of thyristors, at least 36 and usually more for good motor performance, together with a very complex control circuit, and it has some performance limitations, the worst of which is an output frequency limited to about one third the input frequency .

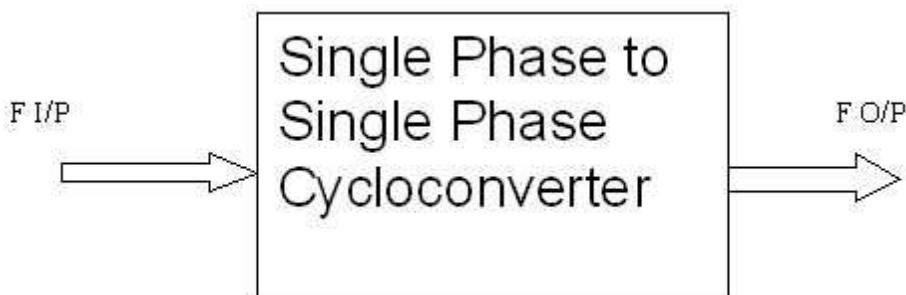

The **Cycloconverter** has four thyristors divided into a positive and negative bank of two

thyristors each. When positive current flows in the load, the output voltage is controlled by phase control of the two positive bank thyristors whilst the negative bank thyristors are kept off and vice versa when negative current flows in the load. An idealized output waveform for a sinusoidal load current and a 45 degrees load phase angle is shown in Figure 3.11. It is important to keep the non conducting thyristor bank off at all times, otherwise the mains could be shorted via the two thyristor banks, resulting in waveform distortion and possible device failure from the shorting current. A major control problem of the **Cycloconverter** is how to swap between banks in the shortest possible time to avoid distortion whilst ensuring the two banks do not conduct at the same time. A common addition to the power circuit that removes the requirement to keep one bank off is to place a centre tapped inductor called a circulating current inductor between the outputs of the two banks. Both banks can now conduct together without shorting the mains. Also, the circulating current in the inductor keeps both banks operating all the time, resulting in improved output waveforms. This technique is not often used, though, because the circulating current inductor tends to be expensive and bulky and the circulating current reduces the power factor on the input

In a **1- ϕ Cycloconverter**, the output frequency is less than the supply frequency. These converters require natural commutation which is provided by AC supply. During positive half cycle of supply, Thyristors P1 and N2 are forward biased. First triggering pulse is applied to P1 and hence it starts conducting.

As the supply goes negative, P1 gets off and in negative half cycle of supply, P2 and N1 are forward biased. P2 is triggered and hence it conducts. In the next cycle of supply, N2 in positive half cycle and N1 in negative half cycle are triggered. Thus, we can observe that here the output frequency is 1/2 times the supply frequency.

Operation Principles

The following sections will describe the operation principles of the **Cycloconverter** starting from the simplest one, **single-phase to single-phase (1 ϕ -1 ϕ) Cycloconverter**.

Single-phase to Single-phase (1 Φ -1 Φ) Cycloconverter


To understand the operation principles of **Cycloconverters**, the single-phase to single-


phase **Cycloconverter** (Fig. 3.12) should be studied first. This converter consists of back-to-back connection of two full-wave rectifier circuits. Fig 3.13 shows the operating waveforms for this converter with a resistive load.

Zero Firing angle, i.e. thyristors act like diodes. Note that the firing angles are named as α_P for the positive converter and α_N for the negative converter. The input voltage, v_s is an ac voltage at a frequency, f_i as shown in Fig. 3.13. For easy understanding assume that all the thyristors are fired at $\alpha=0^\circ$

Consider the operation of the **Cycloconverter** to get one-fourth of the input frequency at the output. For the first two cycles of v_s , the positive converter operates supplying current to the load. It rectifies the input voltage; therefore, the load sees 4 positive half cycles as seen in Fig.

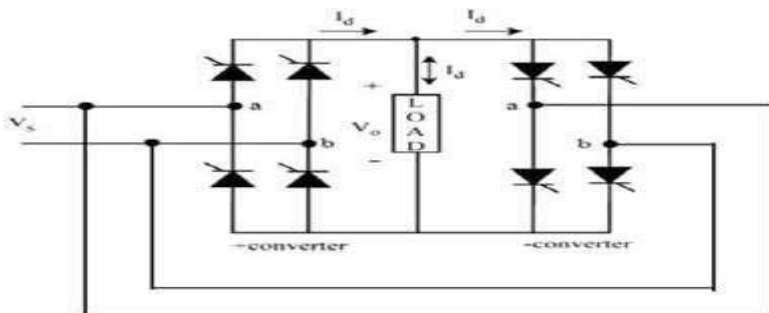3.13. In the next two cycles, the negative converter operates supplying current to the load in the reverse direction. The current waveforms are not shown in the figures because the resistive load current will have the same waveform as the voltage but only scaled by the resistance. Note that when one of the converters operates the other one is disabled, so that there is no current circulating between the two rectifiers.



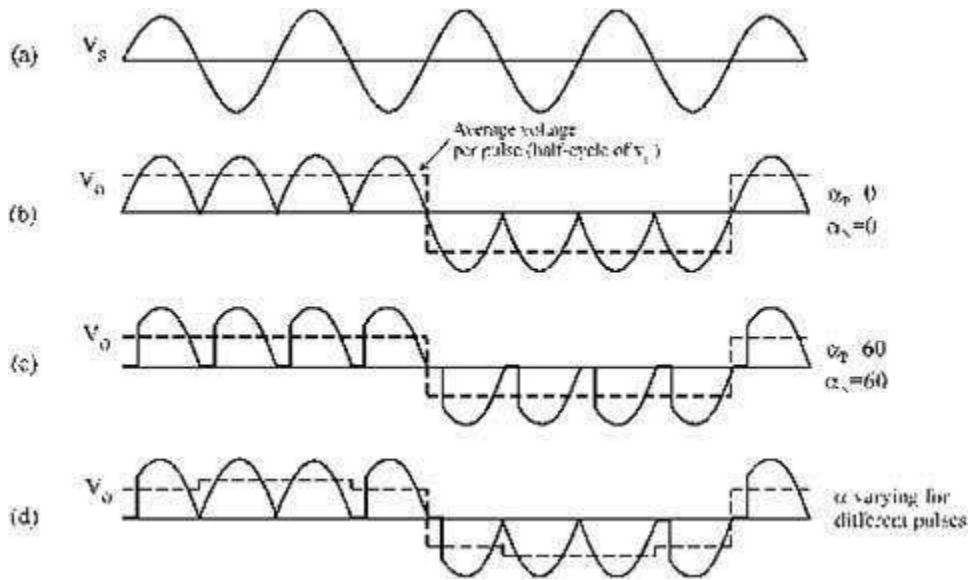

Single phase midpoint Cyclo converters

Basically, these are divided into two main types, and are given below

Step-down cyclo-converter

It acts like a step-down transformer that provides the output frequency less than that of input, $f_o < f_i$.

Step-up cyclo-converter

It provides the output frequency more than that of input, $f_o > f_i$.

In case of step-down cyclo-converter, the output frequency is limited to a fraction of input frequency, typically it is below 20Hz in case 50Hz supply frequency. In this case, no separate commutation circuits are needed as SCRs are line commutated devices.

But in case of step-up cyclo-converter, forced commutation circuits are needed to turn OFF SCRs at desired frequency. Such circuits are relatively very complex. Therefore, majority of cyclo-converters are of step-down type that lowers the frequency than input frequency.

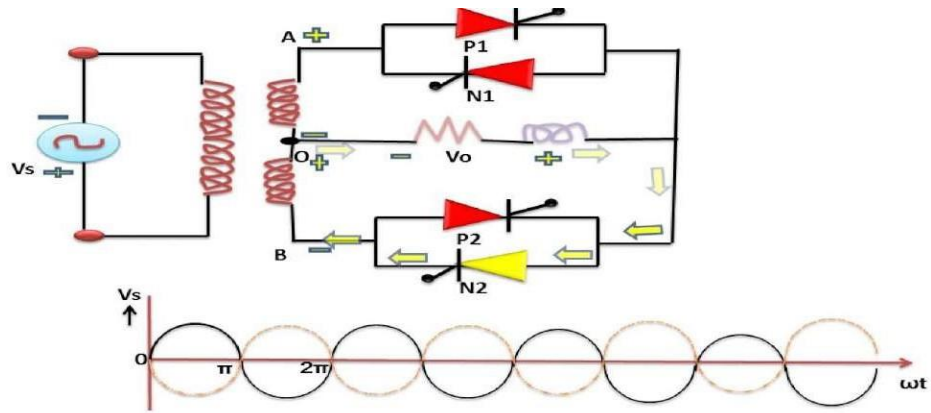


Figure 3.14 circuit diagram of midpoint cycloconverter

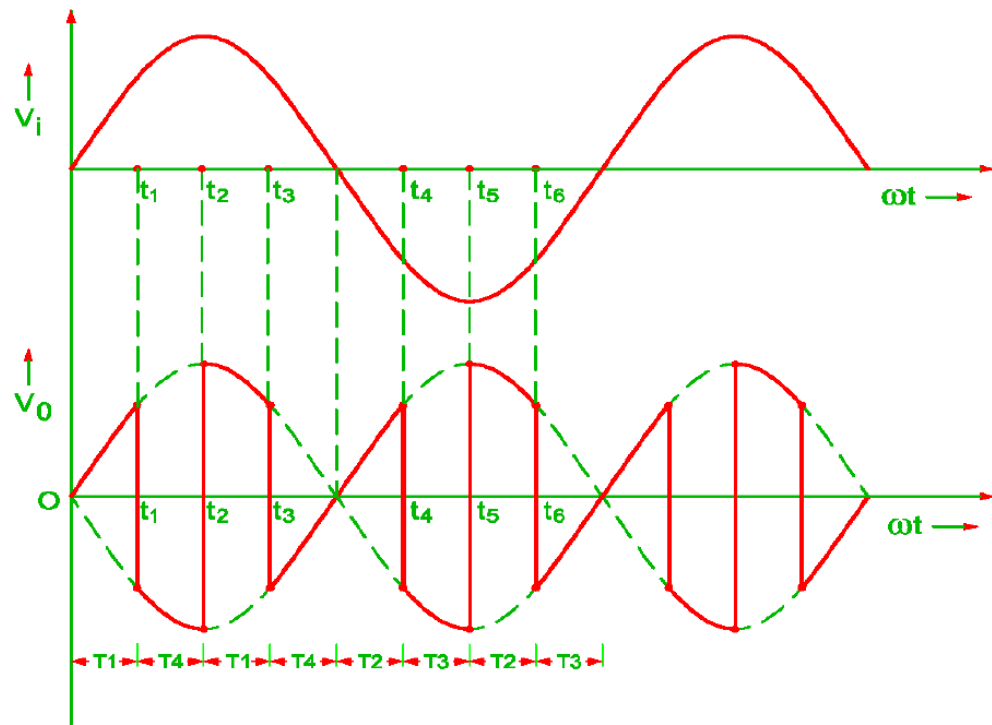


Figure 3.15 Input and output waveforms of midpoint cycloconverter

It consists of single phase transformer with mid tap on the secondary winding and four thyristors. Two of these thyristors P1, P2 are for positive group and the other two N1, N2 are for the negative group. Load is connected between secondary winding midpoint 0 and the load terminal. Positive directions for output voltage and output current are marked in figure 3.14

In figure 3.14 during the positive half cycle of supply voltage terminal a is positive with respect to terminal b. therefore in this positive half cycle, both p1 and N2 are forward biased from $\omega t = 0$ to π . As such SCR P1 is turned on at $\omega t = 0$ so that load voltage is positive with terminal A and 0 negative. Now the load voltage is positive. At instant t_1 P1 is force commutated and forward biased thyristor N2 is turned on so that load voltage is negative with terminal 0 and A negative. Now the load voltage is negative. Now N2 is force commutated and P1 is turned on the load voltage is positive this is a continuous process and will get step up cyclo converter output

Bridge configuration of single phase Cyclo converter

The equivalent circuit of a cyclo-converter is shown in figure below. Here each two quadrant phase controlled converter is represented by a voltage source of desired frequency and consider that the output power is generated by the alternating current and voltage at desired frequency.

The diodes connected in series with each voltage source represent the unidirectional conduction of each two quadrant converter. If the output voltage ripples of each converter are neglected, then it becomes ideal and represents the desired output voltage.

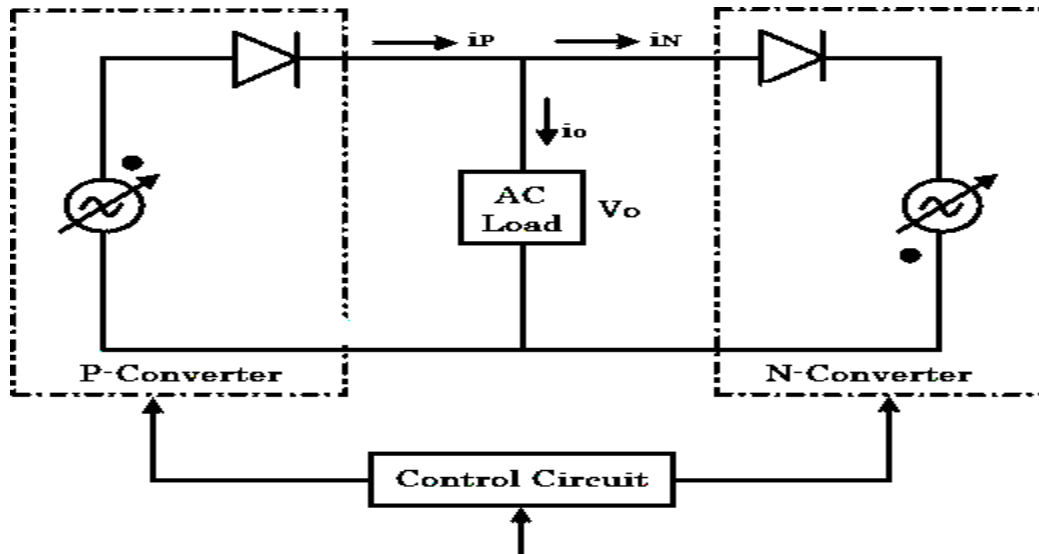


Figure 3.16 Block diagram of bridge type cycloconverter

If the firing angles of individual converters are modulated continuously, each converter produces same sinusoidal voltages at its output terminals.

So the voltages produced by these two converters have same phase, voltage and frequency. The average power produced by the cyclo-converter can flow either to or from the output terminals as the load current can flow freely to and from the load through the positive and negative converters.

Therefore, it is possible to operate the loads of any phase angle (or power factor), inductive or capacitive through the cyclo-converter circuit.

Due to the unidirectional property of load current for each converter, it is obvious that positive converter carries positive half-cycle of load current with negative converter remaining in idle during this period.

Similarly, negative converter carries negative half cycle of the load current with positive converter remaining in idle during this period, regardless of the phase of current with respect to voltage.

This means that each converter operates both in rectifying and inverting regions during the period of its associated half cycles

Single-phase to single-phase cyclo-converters

These are rarely used in practice; however, these are required to understand fundamental principle of cyclo-converters.

It consists of two full-wave, fully controlled bridge thyristors, where each bridge has 4 thyristors, and each bridge is connected in opposite direction (back to back) such that both positive and negative voltages can be obtained as shown in figure below. Both these bridges are excited by single phase, 50 Hz AC supply.


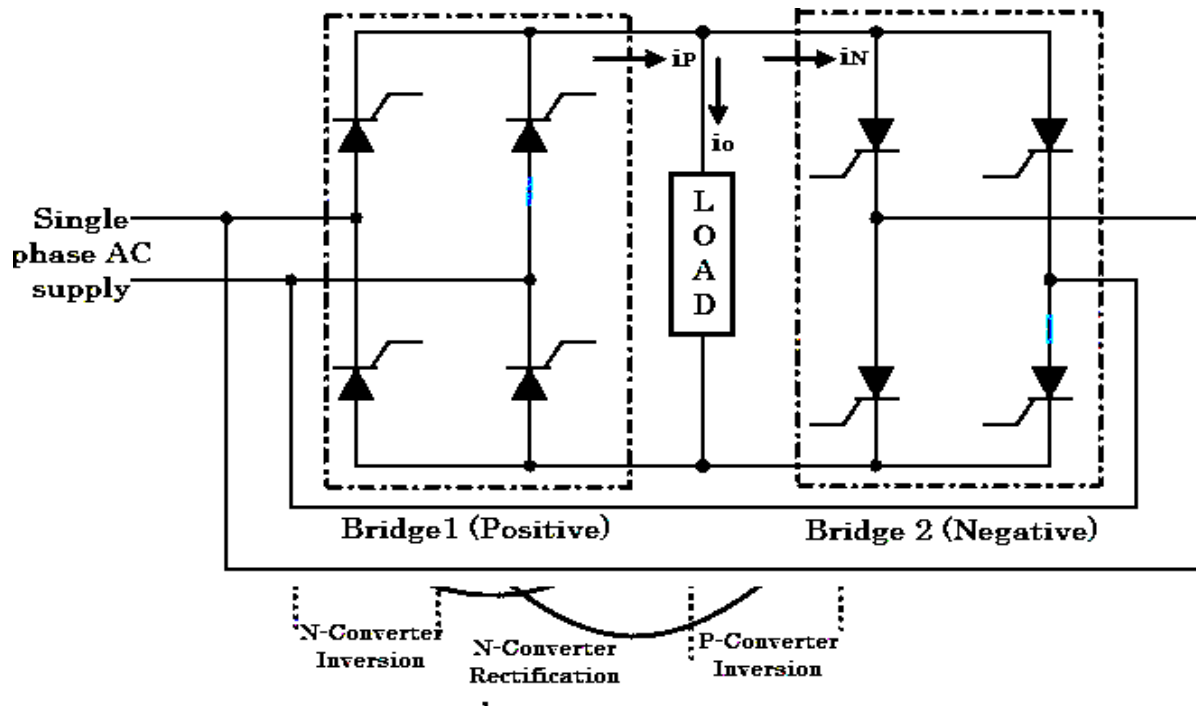


Figure 3.18 Circuit diagram of bridge type cycloconverter

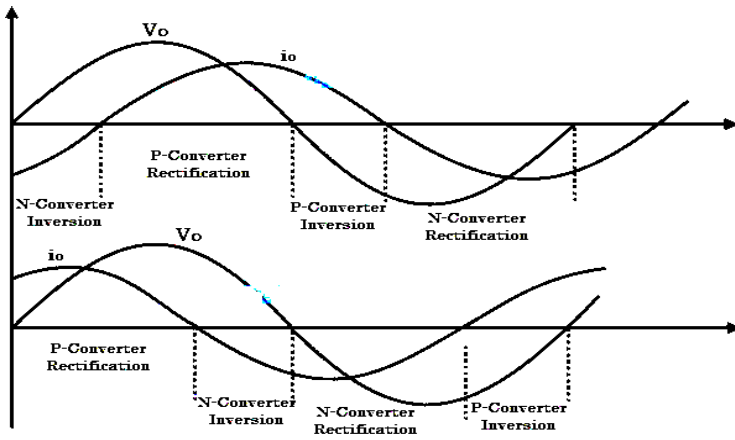During positive half cycle of the input voltage, positive converter (bridge-1) is turned ON and it supplies the load current. During negative half cycle of the input, negative bridge is turned ON and it supplies load current. Both converters should not conduct together that cause short circuit at the input.



To avoid this, triggering to thyristors of bridge-2 is inhibited during positive half cycle of load current, while triggering is applied to the thyristors of bridge-1 at their gates. During negative half cycle of load.

By controlling the switching period of thyristors, time periods of both positive and negative half cycles are changed and hence the frequency. This frequency of fundamental output voltage can be easily reduced in steps, i.e., 1/2, 1/3, 1/4 and so on.

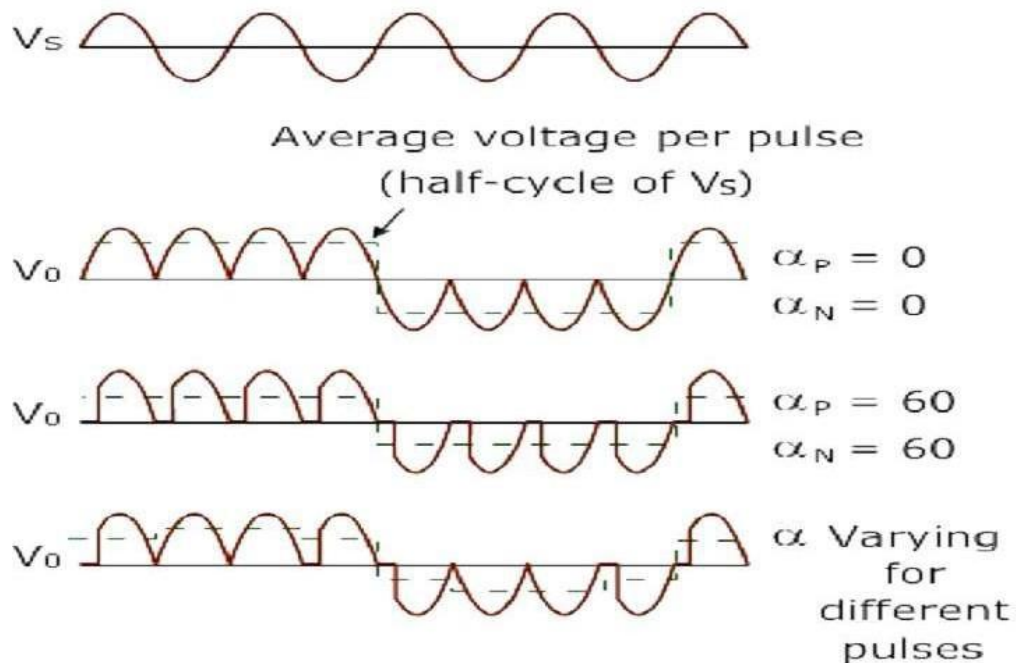


Figure 3.19 Input and output waveforms of bridge type cycloconverter

The above figure shows output waveforms of a cyclo-converter that produces one-fourth of the input frequency. Here, for the first two cycles, the positive converter operates and supplies current to the load.

It rectifies the input voltage and produce unidirectional output voltage as we can observe four positive half cycles in the figure. And during next two cycles, the negative converter operates and supplies loadcurrent.

Here current waveforms are not shown because it is a resistive load in where current (with lessmagnitude) exactly follows the voltage.

Here one converter is disabled if another one operates, so there is no circulating current between two converters. Since the discontinuous mode of control scheme is complicated, most cyclo-converters are operated on circulating current mode where continuous current is allowed to flow between the converters with a reactor.

This circulating current type cyclo-converter can be operated on with both purely resistive (R) and inductive (R-L) loads.

Circulating Current mode of operations:

In this case, both of the converters operate at all times producing the same fundamental output voltage. The firing angles of the converters satisfy the firing angle condition, thus when one converter is in rectification mode the other one is in inversion mode and vice versa. If both of the converters are producing pure sine waves, then there would not be any circulating current because the instantaneous potential difference between the outputs of the converters would be zero. In reality, an IGR is connected between the outputs of two phase controlled converters (in either rectification or inversion mode). This is the difference of the instantaneous output voltages produced by the two converters. Note that it is zero when both of the converters produce the same instantaneous voltage. The center tap voltage of IGR is the voltage applied to the load and it is the mean of the voltages applied to the ends of IGR, thus the load voltage ripple is reduced.

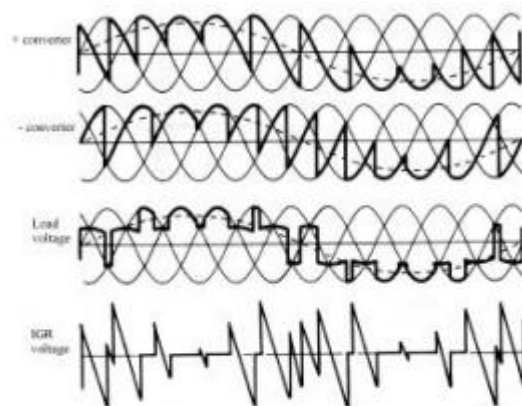


Fig. 11 Circulating mode operation waveforms
a) + converter output voltage
b) - converter output voltage
c) load voltage
d) IGR voltage

The circulating current cycloconverter applies a smoother load voltage with less harmonics compared to the blocking mode case. Moreover, the control is simple because there is no current reversal problem. However, the bulky IGR is a big disadvantage for this converter. In addition to this, the number of devices conducting at any time is twice that of the blocking mode converter.

Due to these disadvantages, this cycloconverter is not attractive. The blocked mode cycloconverter and the circulating current cycloconverter can be combined to give a hybrid system, which has the advantages of both. The resulting cycloconverter looks like a circulating mode cycloconverter circuit, but depending on the polarity of the output current only one converter is enabled and the other one is disabled as with the blocking mode cycloconverters. When the load current decreases below a threshold, both of the converters are enabled. Thus, the current has a smooth reversal. When the current increases above a threshold in the other direction, the outgoing converter is disabled. This hybrid cycloconverter operates in the blocking mode most of the time so a smaller IGR can be used. The efficiency is slightly higher than that of the circulating current cycloconverter but much less than the blocking mode cycloconverter. Moreover, the distortion caused by the blocking mode operation disappears due to the circulating current operation around zero current. Moreover, the control of the converter is still less complex than that of the blocking mode cycloconverter.

Advantages :-

- It is an ac to ac converter therefore no "dc link" is required to be used as in case of the inverters.
- The power flow is bidirectional, from source to load or load to source.

Disadvantages of Cycloconverter :

- It is possible to change the output frequency only in steps. ...
- Output voltage waveform distortion may creep in at low operating frequencies.
- Control Circuit is very complex and difficult to design.
- Input power factor is poor at large values of (α).

Therefore we
obtain the
final
expression
for the
inductive
load current
of a single
phase full
wave ac
voltage
controller
with RL load
as

A chopper uses high speed to connect and disconnect from a source load. A fixed DC voltage is applied intermittently to the source load by continuously triggering the power switch ON/OFF. The period of time for which the power switch stays ON or OFF is referred to as the chopper's ON and OFF state times, respectively.

Choppers are mostly applied in electric cars, conversion of wind and solar energy, and DC motor regulators.

Figure: 2.28 Block diagram of dual converter



There are two functional modes: Non-circulating current mode and circulating mode.

Non Circulating Current Mode

- One converter will perform at a time. So there is no circulating current between the converters.
- During the converter 1 operation, firing angle (α_1) will be $0 < \alpha_1 < 90^\circ$; V_{dc} and I_{dc} are positive.
- During the converter 2 operation, firing angle (α_2) will be $0 < \alpha_2 < 90^\circ$; V_{dc} and I_{dc} are negative.

Circulating Current Mode

- Two converters will be in the ON condition at the same time. So circulating current is present.
- The firing angles are adjusted such that firing angle of converter 1 (α_1) + firing angle of converter 2 (α_2) = 180° .
- Converter 1 performs as a controlled rectifier when firing angle be $0 < \alpha_1 < 90^\circ$ and Converter 2 performs as an inverter when the firing angle be $90^\circ < \alpha_2 < 180^\circ$. In this condition, V_{dc} and I_{dc} are positive.
- Converter 1 performs as an inverter when firing angle be $90^\circ < \alpha_1 < 180^\circ$ and Converter 2 performs as a controlled rectifier when the firing angle be $0 < \alpha_2 < 90^\circ$ In this condition, V_{dc} and I_{dc} are negative.
- The four quadrant operation is shown below

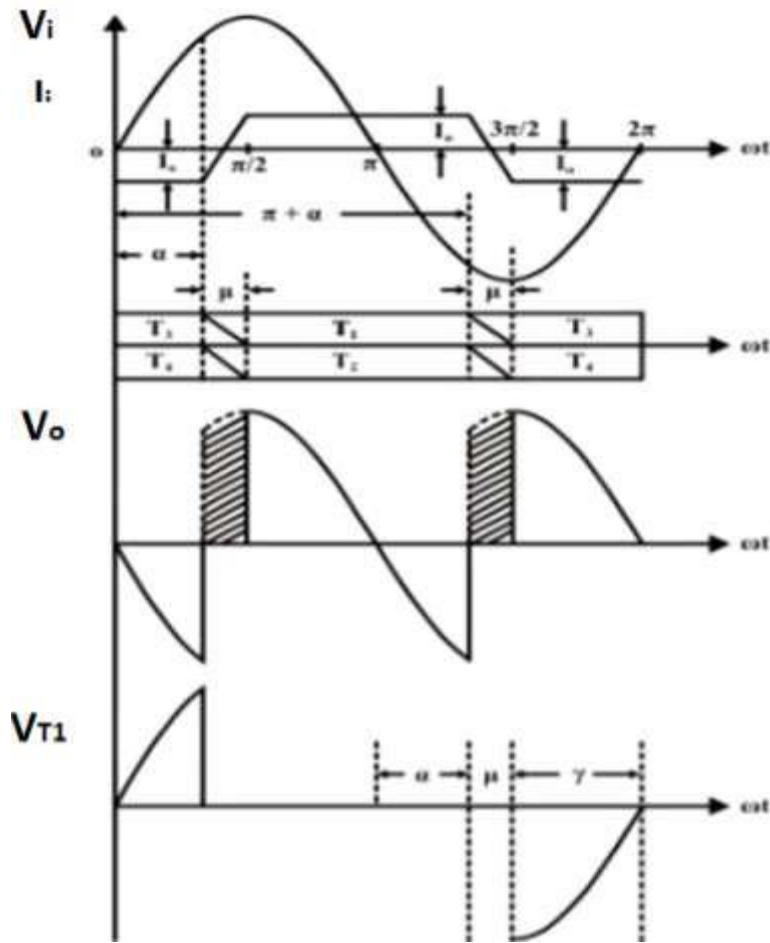


Figure: 2.14 single phase full converter output waveforms with source inductance

4. During overlap interval the load current freewheels through the thyristors and the output voltage is clamped to zero. On the other hand, the input current starts changing polarity as the current through T1 and T2 increases and T3 T4 current decreases. At the end of the overlap interval the current through T3 and T4 becomes zero and they commute, T1 and T2 starts conducting the full load current
5. The same process repeats during commutation from T1 T2 to T3T4 at $\omega t = \pi + \alpha$. From Fig. 2.14 it is clear that, commutation overlap not only reduces average output dc voltage but also reduces the extinction angle γ which may cause commutation failure in the inverting mode of operation if α is very close to 180° .
6. In the following analysis an expression of the overlap angle " μ " will be determined. From the equivalent circuit of the converter during overlap period.

$$L \frac{di_i}{dt} = v_i \text{ for } \alpha \leq \omega t + \mu$$

$$i_i(\omega t = \alpha) = -I_0$$

$$i_i = I - \frac{\sqrt{2}V_i}{\omega L} \cos \omega t$$

$$\therefore i_i|_{\omega t = \alpha} = I - \frac{\sqrt{2}V_i}{\omega L} \cos \alpha = -I_0$$

$$I = \frac{\sqrt{2}V_i}{\omega L} \cos \alpha - I_0$$

$$\therefore i_i = \frac{\sqrt{2}V_i}{\omega L} (\cos \alpha - \cos \omega t) - I_0$$

$$\text{at } \omega t = \alpha + \mu \quad i_i = I_0$$

$$I_0 = \frac{\sqrt{2}V_i}{\omega L} (\cos \alpha - \cos(\alpha + \mu)) - I_0$$

$$\therefore \cos \alpha - \cos(\alpha + \mu) = \frac{\sqrt{2}\omega L}{V_0} I_0$$

$$V_0 = \frac{I}{\pi} \int_{\alpha}^{\alpha+\pi} V_i d\omega t$$

$$\text{or } V_0 = \frac{I}{\pi} \int_{\alpha+\mu}^{\alpha+\pi} \sqrt{2}v_i \sin \omega t d\omega t$$

$$= \frac{\sqrt{2}v_i}{\pi} [\cos(\alpha + \mu) - \cos(\pi + \alpha)]$$

$$= \frac{\sqrt{2}v_i}{\pi} [\cos \alpha + \cos(\alpha + \mu)]$$

$$\therefore V_0 = 2\sqrt{2} \frac{v_i}{\pi} [\cos \alpha - \cos(\alpha + \mu)]$$

$$\therefore V_0 = \frac{2\sqrt{2}}{\pi} v_i \cos \alpha - \frac{2}{\pi} \omega L I_0$$

The Equation can be represented by the following equivalent circuit


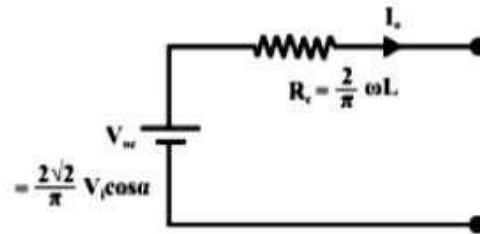


Figure: 2.15 Equivalent circuit of the given equation

Equivalent circuit representation of the single phase fully controlled rectifier with source inductance

The simple equivalent circuit of Fig. 2.15 represents the single phase fully controlled converter with source inductance as a practical dc source as far as its average behavior is concerned. The open circuit voltage of this practical source equals the average dc output voltage of an ideal converter (without source inductance) operating at a firing angle of α . The voltage drop across the internal resistance “RC” represents the voltage lost due to overlap shown in Fig. 2.14 by the hatched portion of the V_o waveform. Therefore, this is called the “Commutation resistance”. Although this resistance accounts for the voltage drop correctly there is no power loss associated with this resistance since the physical process of overlap does not involve any power loss. Therefore this resistance should be used carefully where power calculation is involved.

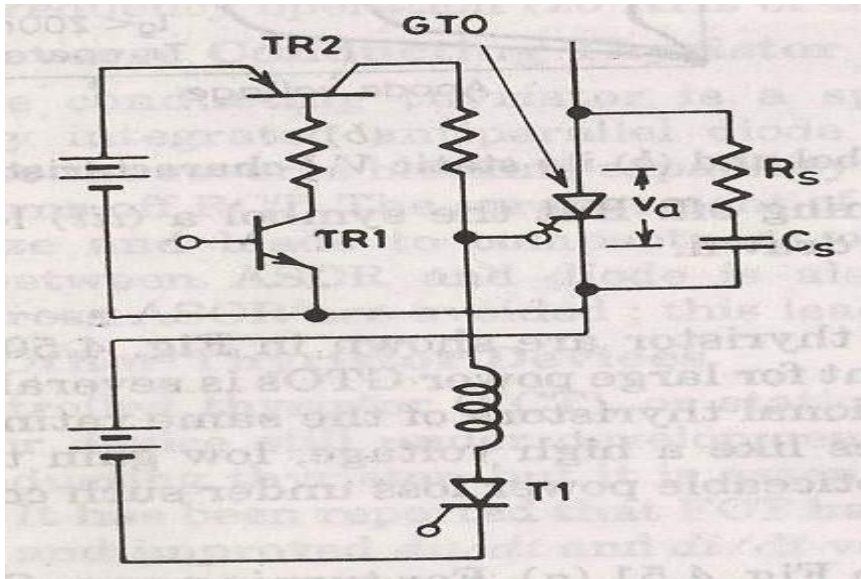

1. F
or turning ON a GTO first TR1 is turned on.
2. T
his in turn switches on TR2 so that a positive gate current pulse is applied to turn on the GTO.
3. T
thyristor T_1 is used to apply a high peak negative gate current pulse.

Gate turn-on characteristics

1. T
The gate turn on characteristics is similar to a thyristor. Total turn on time consists of delay time, rise time, spread time.
2. T
The turn on time can be reduced by increasing its forward gate current.


GATE TURN OFF

Turn off time is different for SCR. Turn off characteristics is divided into 3 pd

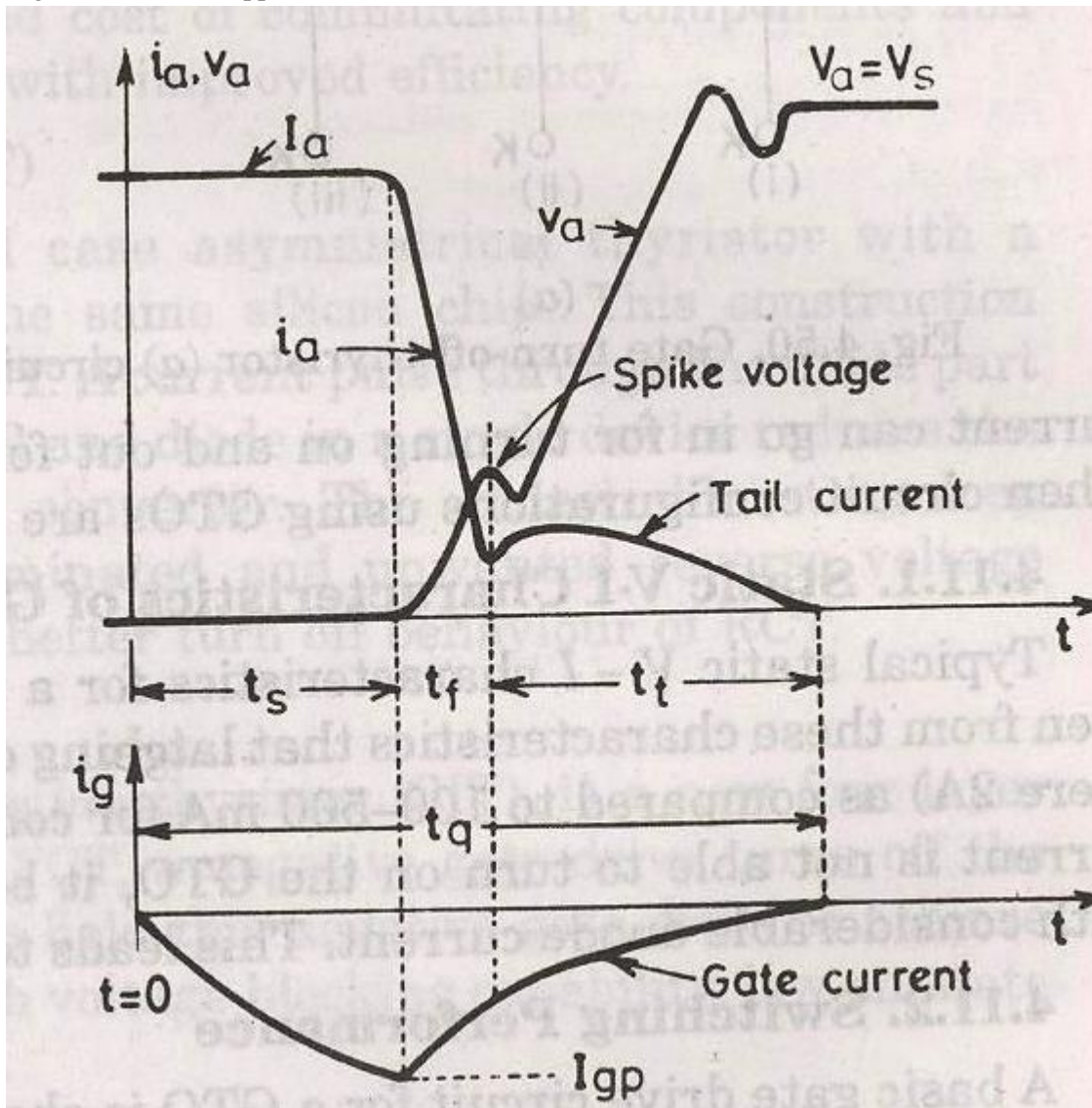1. Storage time
2. Fall time
3. Tail time

$$T_q = t_s + t_f + t_t$$

At normal operating condition gto carries a steady state current. The turn off process starts as soon as negative current is applied after $t=0$.



STORAGE TIME

During the storage pd the anode voltage and current remains constant. The gate current rises depending upon the gate circuit impedance and gate applied voltage. The beginning of pd is as soon as negative gate current is applied. The end of storage pd is marked by fall in anode current and rise in voltage, what we have to do is remove the excess carriers. The excess carriers are removed by negative carriers.


FALL TIME

After t_s , anode current begins to fall rapidly and anode voltage starts rising. After falling to a certain value, then anode current changes its rate to fall. This time is called fall time.

SPIKE IN VOLTAGE

During the time of storage and fall time there is a change in voltage due to abrupt current change. TAIL TIME

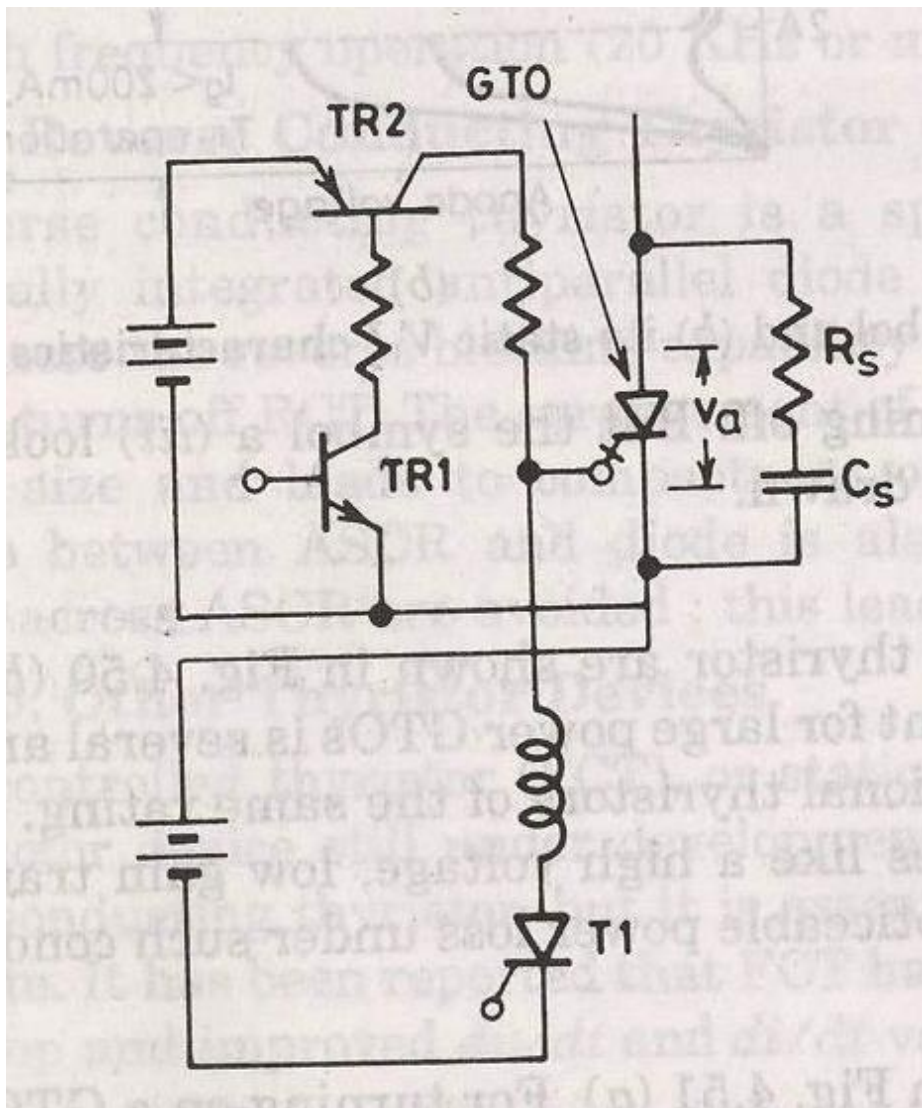During this time, the anode current and voltage continues towards the turn off values. The transient overshoot is due to the snubber parameter and voltage stabilizes to steady state value.




THE TRIAC

As SCR is a unidirectional device, the conduction is from anode to cathode and not from cathode to anode. It conducts in both direction. It is a bidirectional SCR with three terminal.

TRIAC=TRIODE+AC

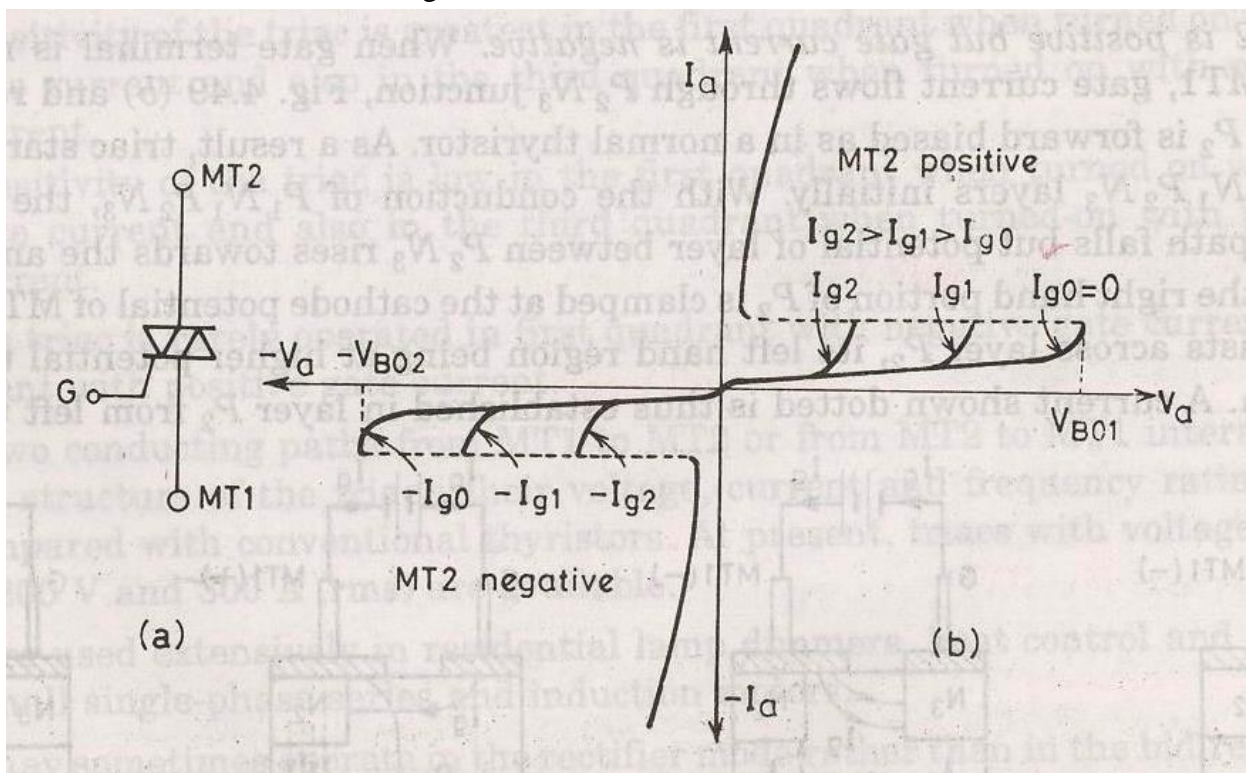Here it is considered to be two SCRS connected in anti parallel. As it conducts in both direction so it is named as MT1, MT2 and gate G.



SALIENT FEATURES

1. Bi directional triode thyristor 2. TRIAC means triode that works on ac 3. It conduct in both direction

4. It is a controlled device


It

5. It
s operation is similar to two devices connected in anti parallel with common gateconnection.

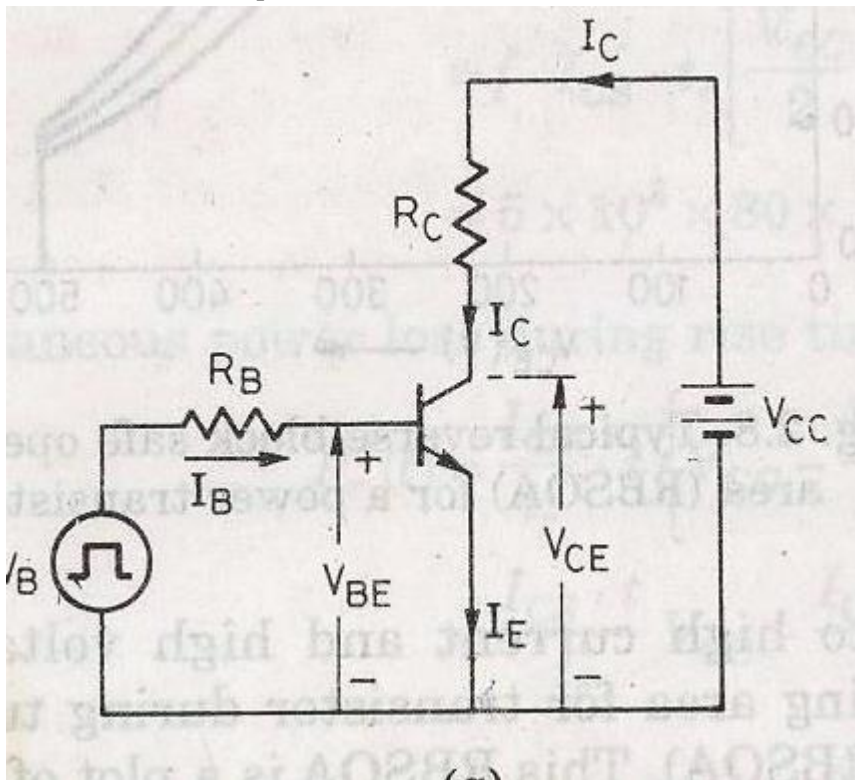6. It
has 3 terminals MT1,MT2 and gate GIts use is control of power in ac.


POWER BJT

Power BJT means a large voltage blocking in the OFF state and high current carrying capability in the ON state. In most power application, base is the input terminal. Emitter is the common terminal. Collector is the output terminal.



SIGNAL LEVEL OF BJT

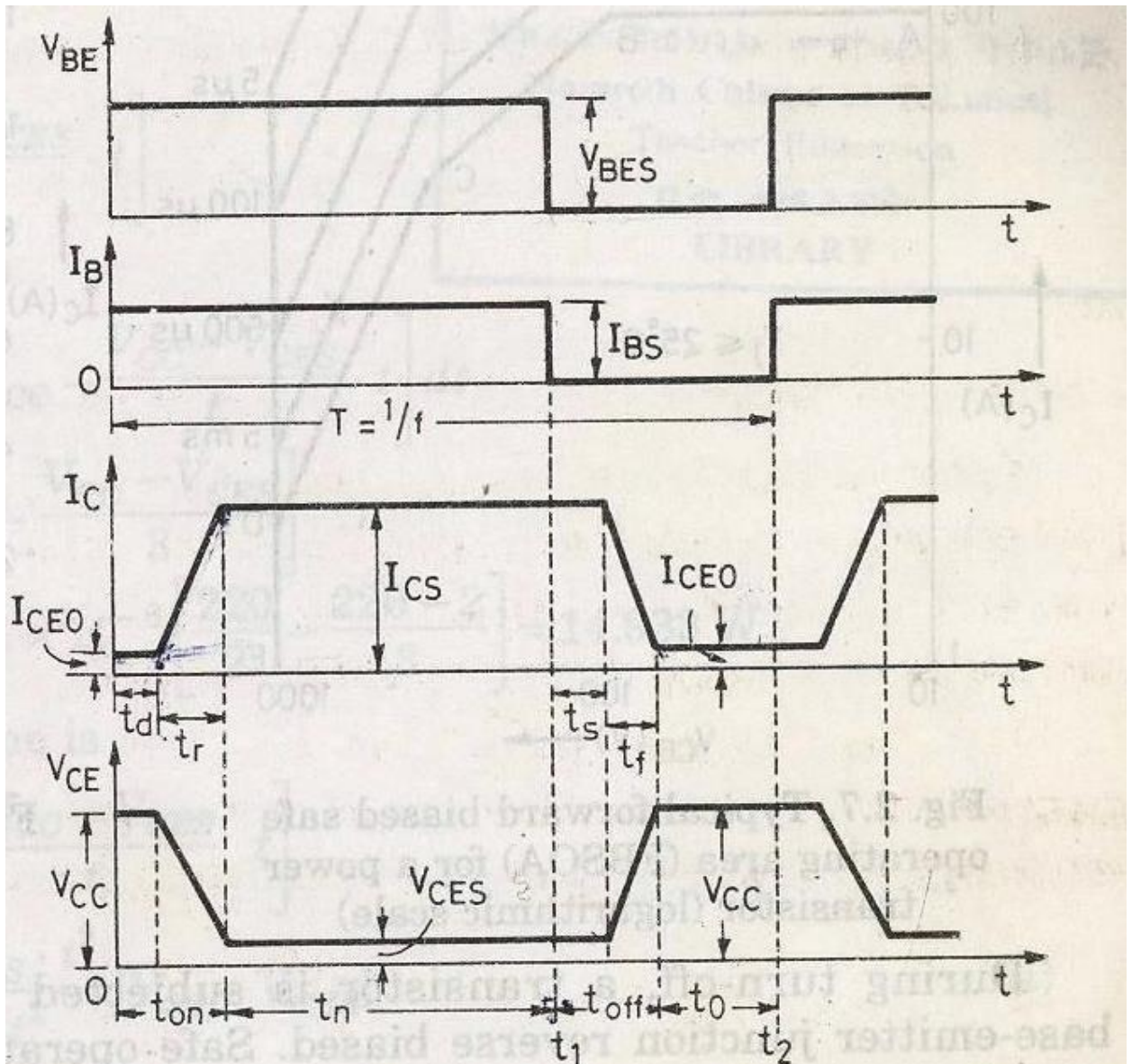$n+$ doped emitter layer ,doping of base is more than collector.Depletion layer exists more towards the collector than emitter



POWER BJT CONSTRUCTION

The maximum collector-emitter voltage that can be sustained across the junction, when it is carrying substantial collector current.

V_{ce0} = maximum collector and emitter voltage that can be sustained by the device. V_{cbo} = collector base breakdown voltage with emitter open

PRIMARY BREAKDOWN

It is due to conventional avalanche breakdown of the C-B junction and its associated large flow of current. The thickness of the depletion region determines the breakdown voltage of the transistor. The base thickness is made as small as possible, in order to have good amplification capability. If the thickness is too small, the breakdown voltage is compromised. So a compromise has to be made between the two.

THE DOPING LEVELS-

1. The doping of the emitter layer is quite large. 2. The base doping is moderate.

3. n- region is lightly doped.

4. n+ region doping level is similar to emitter. 1. THICKNESS OF DRIFT REGION-

It determines the breakdown length of the transistor. 2. THE BASE THICKNESS –

Small base thickness- good amplification capability

Too small base thickness- the breakdown voltage of the transistor has to be compromised.

For a relatively thick base, the current gain will be relatively small. So it is increased the gain. Monolithic designs for darlington connected BJT pair have been developed.

SECONDARY BREAKDOWN

Secondary breakdown is due to large power dissipation at localized site within the semiconductor.

PHYSICS OF BJT OPERATION-

The transistor is assumed to operate in active region. There is no doped collector drift region. It has importance only in switching operation, in active region of operation.

B-E

junction is forward biased and C-B junction is reverse biased. Electrons are injected into base from the emitter. Holes are injected from base into the emitter.

QUASI SATURATION-

Initially we assume that, the transistor is in active region. Base current is allowed to increase then let's see what happens. First collector rises in response to base current. So there is an increase in voltage drop across the collector load. So C-E voltage drops.

Because of increase in collector current, there is an increase in voltage in drift region. This eventually reduces the reverse bias across the C-B junction. So n-p junction gets smaller, at some point the junction becomes forward biased. So now injection of holes from base into collector drift region occurs. Charge neutrality requires the electron to be injected in the drift region of the holes. From where these electrons came. Since a large number of electrons is supplied to the C-B junction via injection from emitter and subsequent diffusion across the base. As excess carrier build up in the drift region begins to occur quasi saturation region is entered. As the injected carriers increase in the drift region is

gradually shorted out and the voltage across the drift region drops. In quasi saturation the drift region is not completely shorted out by high level injection. Hard saturation obtained when excess carrier density reaches the n^+ side.

During quasi saturation, the rate of the collector fall. Hard saturation occurs when excess carriers have completely swept across the drift region .

THYRISTOR PROTECTION

OVER VOLTAGE PROTECTION

Over voltage occurring during the switching operation causes the failure of SCR.

INTERNAL OVERVOLTAGE

It is due to the operating condition of SCR.

During the commutation of SCR, when the anode current decays to zero anode current reverses due to stored charges. First the reverse current rises to peak value, then reverse current reduces abruptly with large di/dt . During series inductance of SCR large transient large voltage i.e $L di/dt$ is generated.

EXTERNAL OVER VOLTAGE


This is due to external supply and load condition. This is because of

1. The interruption of current flow in an inductive circuit.
2. Lightning strokes on the lines feeding the thyristor systems.

Suppose a SCR converter is fed from a transformer, voltage transient occur when transformer primary will energise or de-energised.

This overvoltages cause random turn ON of a SCR. The effect of overvoltage is minimized using

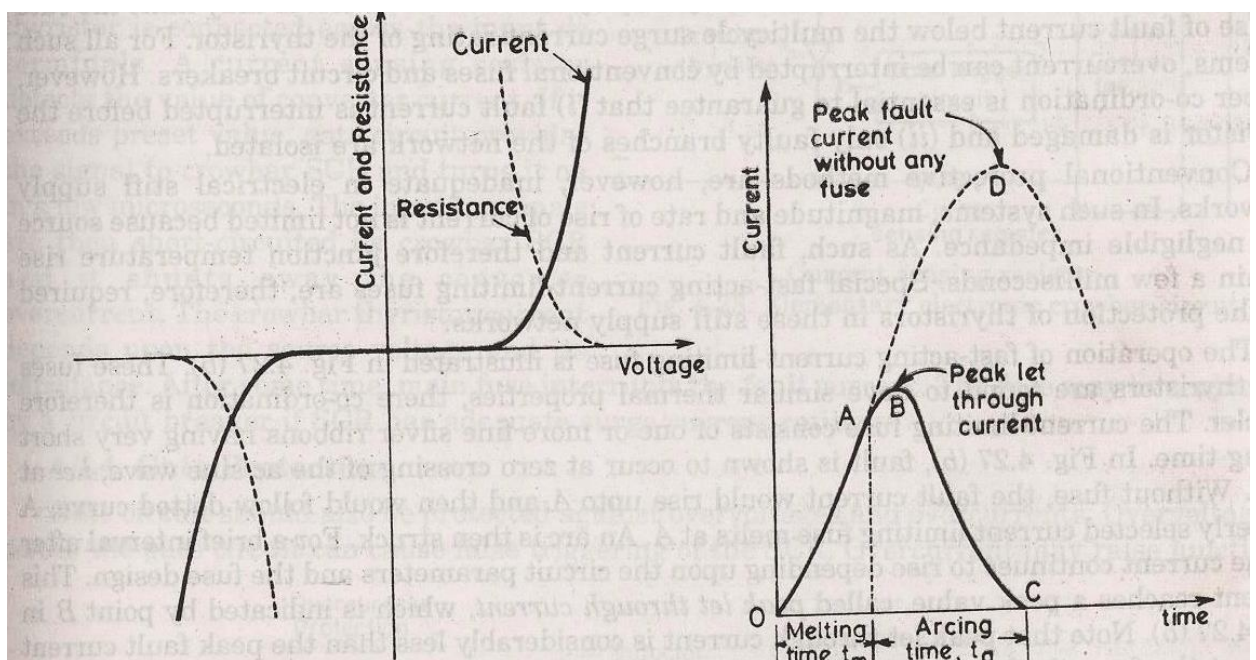1. RC circuits
2. Non linear resistor called voltage clamping device.



Voltage clamping device is a non linear resistor. It is connected between cathode and anode of SCR. The resistance of voltage clamping device decreases with increasing voltages. During normal working condition Voltage clamping (V.C) device has high resistance, drawing only leakage current. When voltage surge appears voltage clamping device offers a low resistance and it create a virtual short circuit across the SCR. Hence voltage across SCR is clamped to a safe value.

When surge condition over voltage clamping device returns to high resistance state.
e.g. of voltage clamping device 1.Selenium thyrector diodes 2.Metal Oxide varistors
3.Avalanche diode supressors

OVER CURRENT PROTECTION

Long duration operation of SCR, during over current causes the junction temp. of SCR to rise above the rated value, causing permanent damage to device.

SCR is protected from overcurrent by using

1.Circuit breakers
2.Fast acting fuses

Proper co-ordination is essential because

1..fault current has to be interrupted before SCR gets damaged.2.only faulty branches of the network has to be replaced.

In stiff supply network, source has negligible impedance. So in such system the magnitude and rate of rise of current is not limited. Fault current hence junction temp rises in a few milliseconds.

POINTS TO BE NOTED-


1. Proper coordination between fast acting fuse and thyristor is essential.
2. The fuse is always rated to carry marginal overload current over definite period.
3. The peak let through current through SCR must be less than sub cycle rating of the SCR.
4. The voltage across the fuse during arcing time is called arcing or recovery voltage and is equal to sum of the source voltage and emf induced in the circuit inductance during arcing time.
5. On abrupt interruption of fuse current, induce emf would be high, which results in high arcing voltage.

Circuit Breaker (C.B)

C.B. has long tripping time. So it is used for protecting the device against continuous overload current or against the surge current for long duration. In order that fuse protects the thyristor reliably the I^2t rating of fuse current must be less than that of SCR.

ELECTRONIC CROWBAR PROTECTION

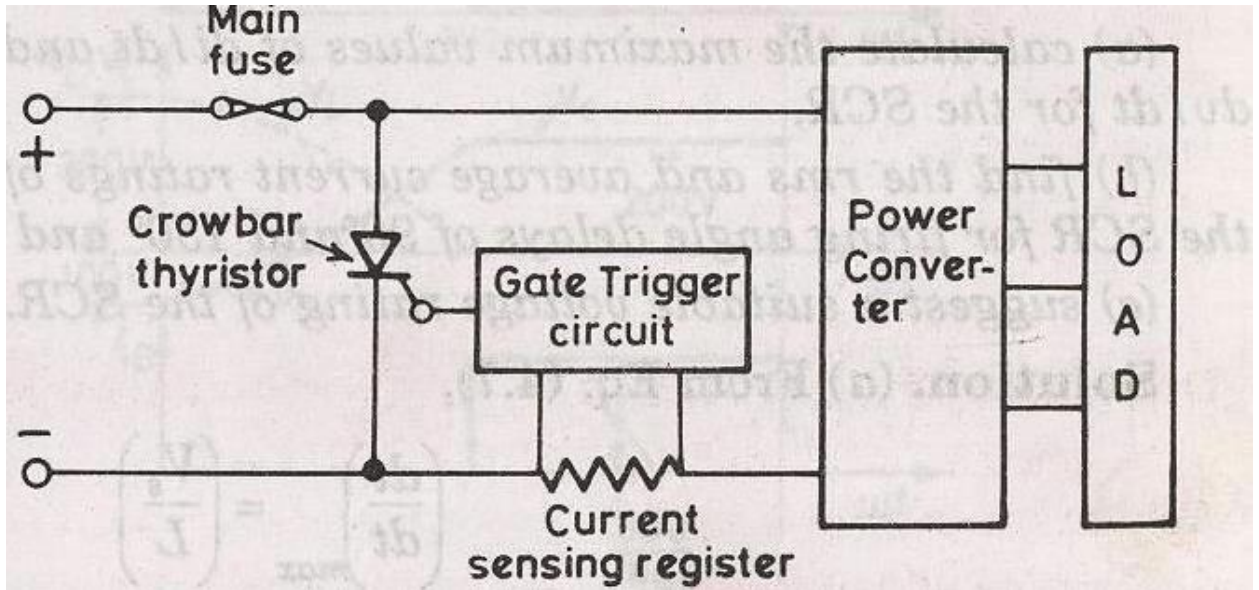For overcurrent protection of power converter using SCR, electronic crowbar are used. It provides rapid isolation of power converter before any damage occurs.




HEAT PROTECTION-

To protect the SCR

1. From the local spots
2. Temp rise

SCRs are mounted over heat sinks.

GATE

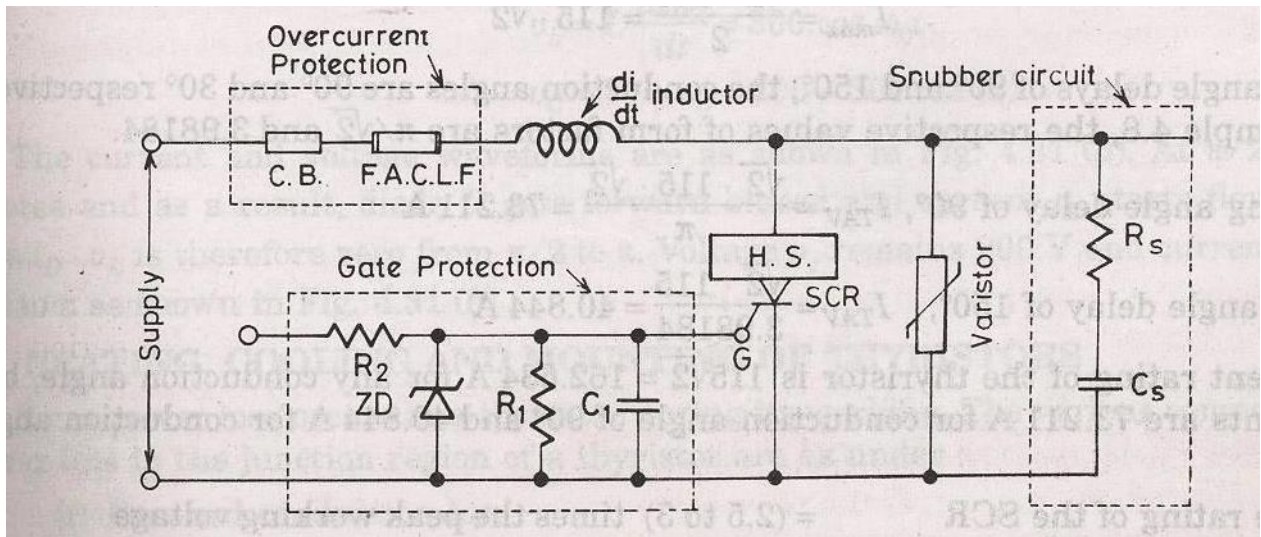

PROTECTION-

Gate circuit should also be protected from


1. Overvoltages
2. Overcurrents

Overvoltage across the gate circuit causes the false triggering of SCR

Overcurrent raise the junction temperature. Overvoltage protection is by zener diode across the gate circuit.


INSULATED GATE BIPOLAR TRANSISTOR(IGBT)-BASIC CONSTRUCTION-

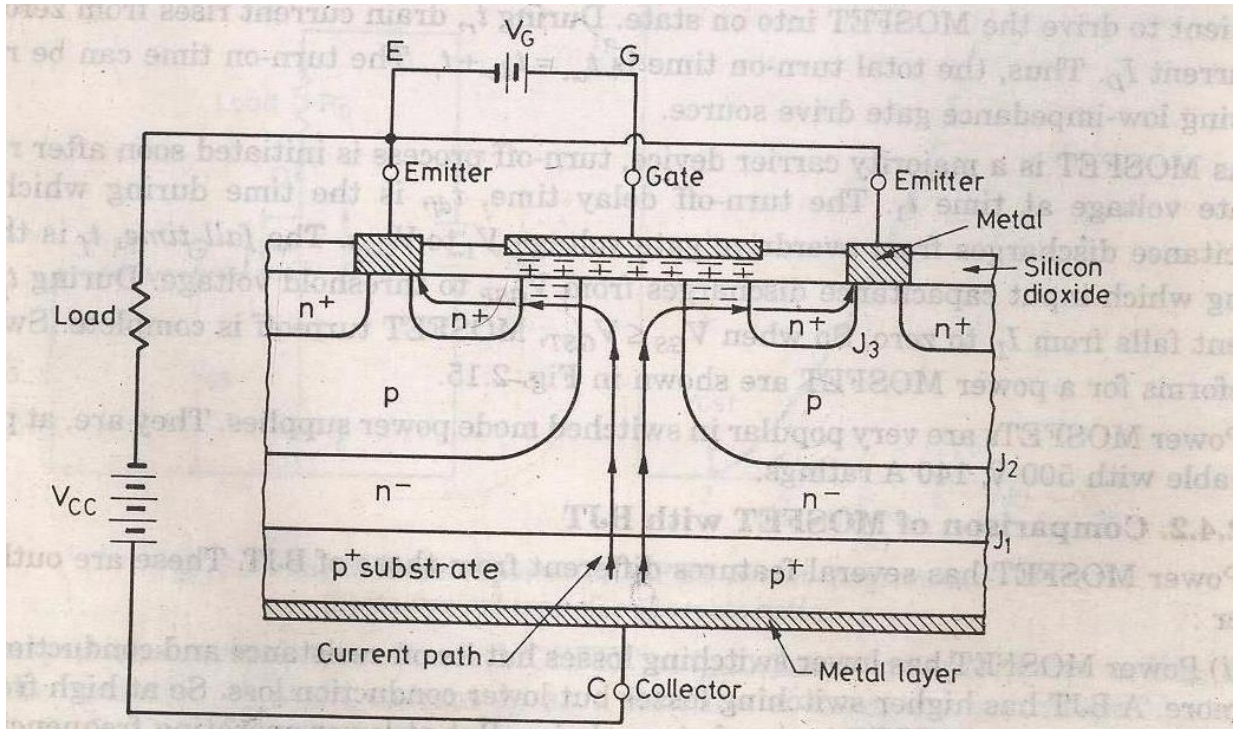The n+ layer substrate at the drain in the power MOSFET is substituted by p+ layer substrate and called as collector. When gate to emitter voltage is positive, n- channel is formed in the p-region. This n- channel short circuit the n- and n+ layer and an electron movement in n channel cause hole injection from p+ substrate layer to n- layer.




POWER MOSFET

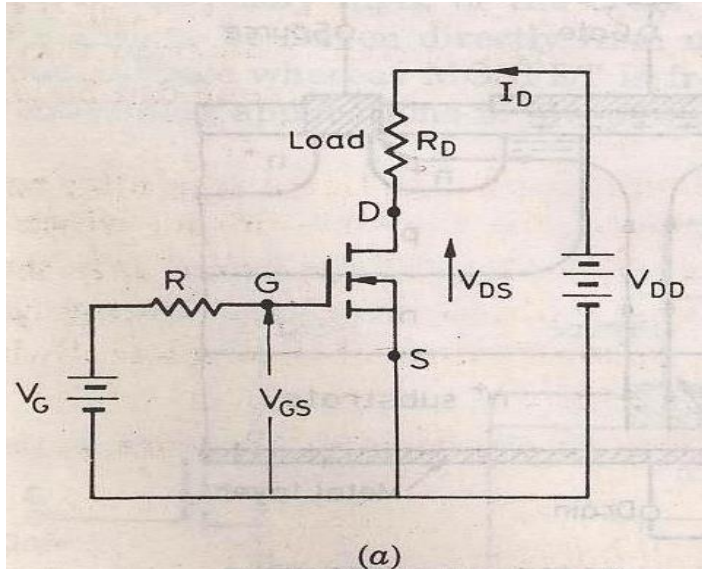A power MOSFET has three terminal device. Arrow indicates the direction of current flow. MOSFET is a voltage controlled device. The operation of MOSFET depends on flow of majority carriers only.



(Circuit diagram)

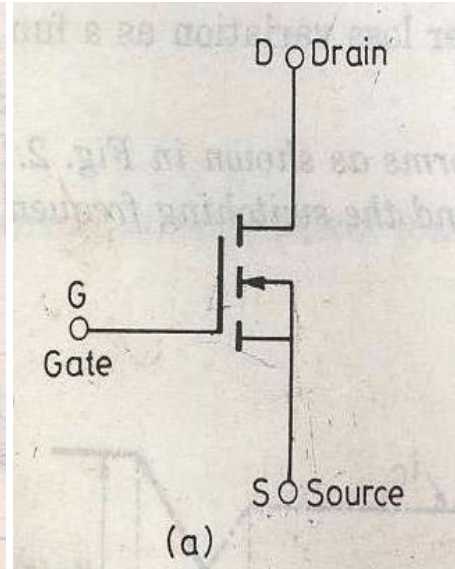

(circuit symbol)

Switching Characteristics:-

The switching characteristic is influenced by

1. Internal capacitance of the device. I

2. I

Internal impedance of the gate drive circuit. Total **turn on time** is divided into

1. T

Turn on delay time 2. Rise time

Turn on time is affected by impedance of gate drive source. During turn on delay time gate to source voltage attains its threshold value V_{GST} .

After t_{dn} and during rise time gate to source voltage rise to V_{Gsp} , a voltage which is insufficient to drive the MOSFET to ON state.

The turn off process is initiated by removing the gate to source voltage. Turn off time is composed of turn off delay time to fall time.

Turn off delay time

To turn off the MOSFET the input capacitance has to be discharged . During t_{df} the input capacitance discharge from V_1 to V_{GSP} . During , fall time ,the input capacitance discharges from V_{GSP} to V_{GST} . During t_f drain current falls from I_D to zero.

So when $V_{Gs} \leq$, MOFSET turn off is complete.

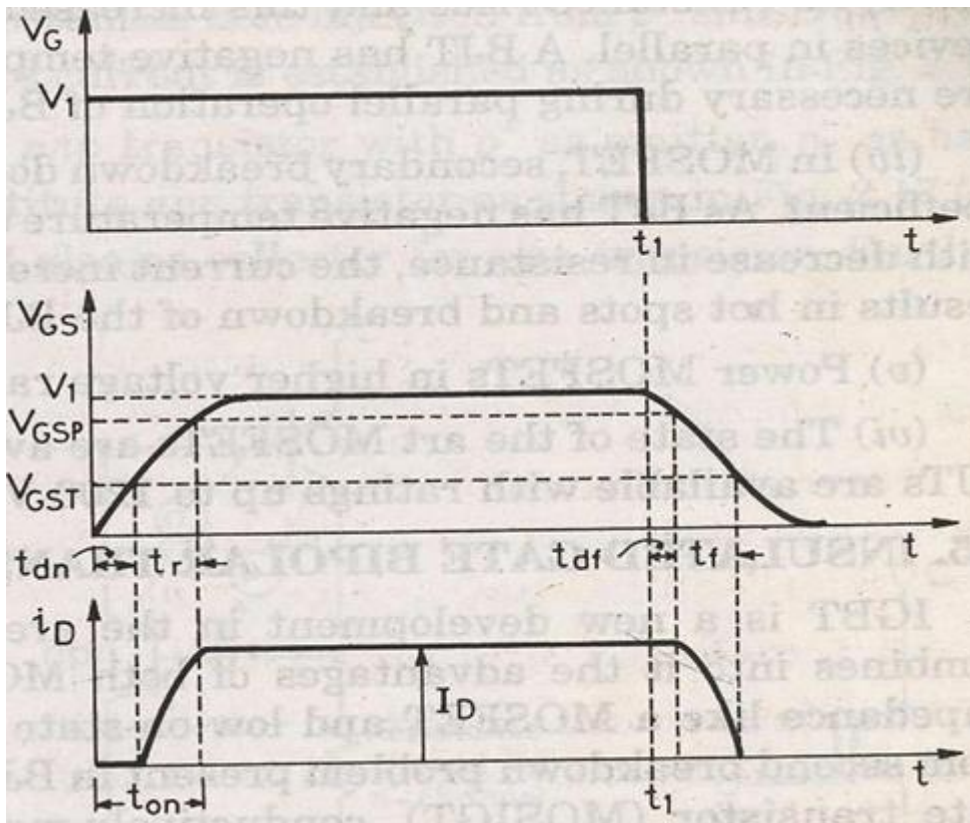


Fig. Switching waveform of power MOSFET

Insulated Gate Bipolar Transistor (IGBT)

IGBT has high input impedance like MOFFSET and low on state power lose as in BJT.

IGBT Characteristics

Here the controlling parameter is gate emitter voltage As IGBT is a voltage controlled device.

When V_{GE} is less than V_{GET} that is gate emitter threshold voltage IGBT is in off state.

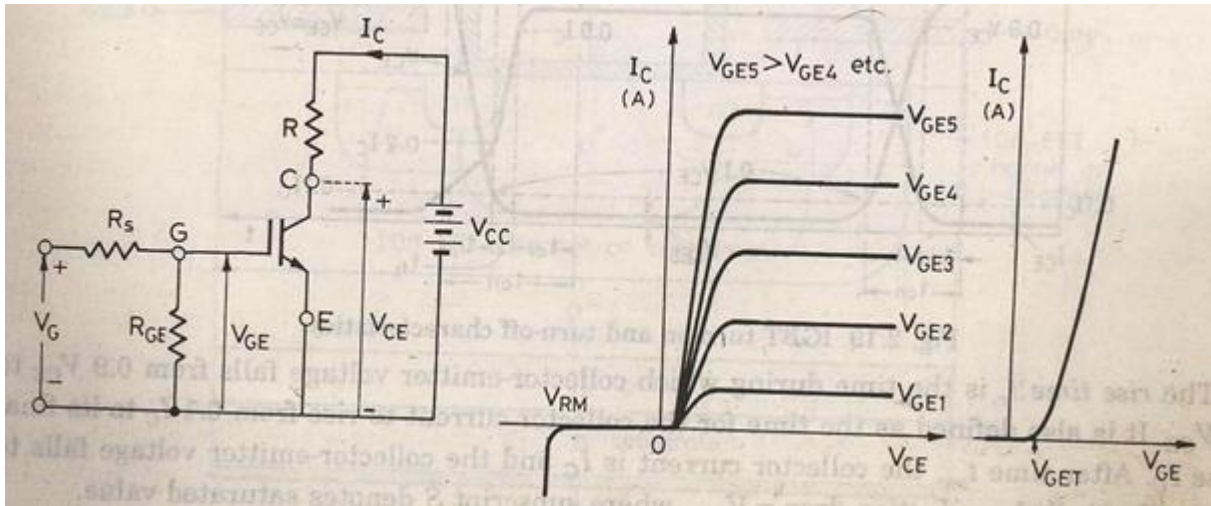


Fig. a

Fig. b.


Fig. c

Fig. a (Circuit diagram for obtaining V-I characteristics)

Fig. b (Static V-I characteristics)

Fig. c (Transfer characteristic)

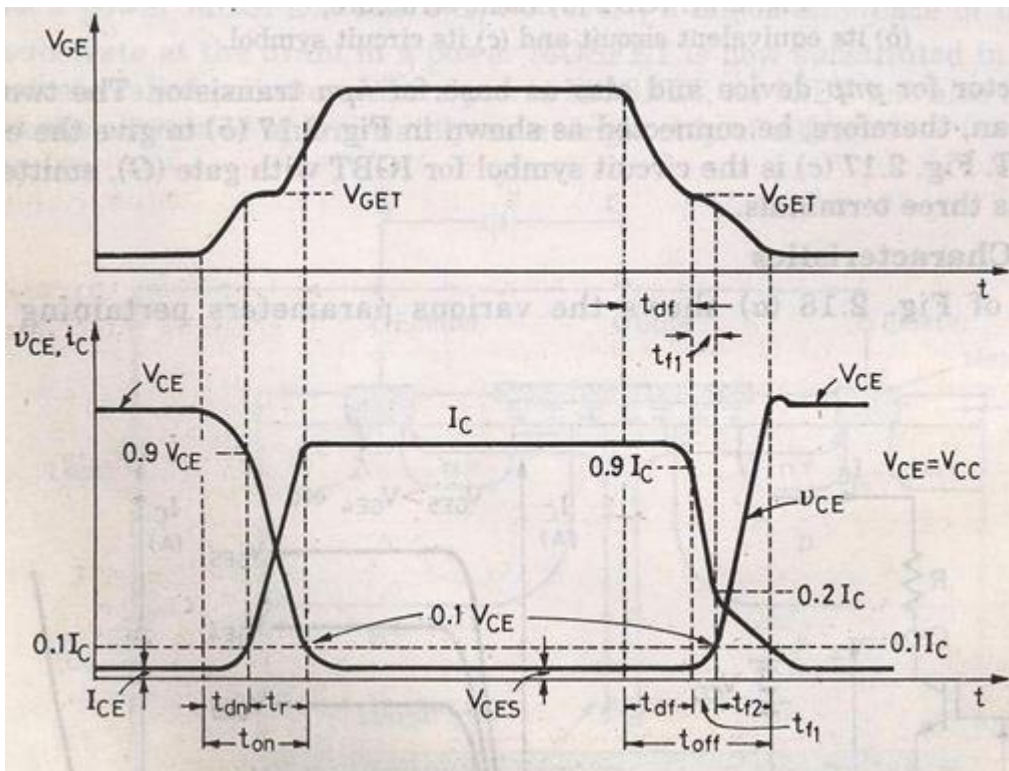Switching characteristics: Figure below shows the turn ON and turn OFF characteristics of IGBT



Turn on time

Time between the instants forward blocking state to forward on -state .

Turn on time = Delay time + Rise time

Delay time = Time for collector emitter voltage fall from V_{CE} to $0.9V_{CE}$

V_{CE} =Initial collector emitter voltage

t_{dn} =collector current to rise from initial leakage current to $0.1I_c$
 I_c = Final value of collector current

Rise time

Collector emitter voltage to fall from $0.9V_{CE}$ to $0.1V_{CE}$.

0.1 I
c to I_c

After t_{on} the device is on state the device carries a steady current of I_c and the collector emitter voltage falls to a small value called conduction drop V_{CES} .

Turn off time

- 1) Delay time t_{df}
- 2) Initial fall time t_{f1}
- 3) Final fall time t_{f2}

$$t_{off} = t_{df} + t_{f1} + t_{f2}$$

t_{df} = Time during which the gate emitter voltage falls to the threshold value V_{GET} .

Collector current falls from I_c to $0.9I_c$ at the end of the t_{df} collector emitter voltage begins to rise.

Turn off time = Collector current falls from 90% to 20% of its initial value I_c OR The time during which collector emitter voltage rise from V_{CE} to $0.1V_{CE}$.

t_{f2} = collector current falls from 20% to 10% of I_c .

During this collector emitter voltage rise $0.1V_{CE}$ to final value of V_{CE} . Series and parallel operation of SCR

SCR are connected in series for h.v demand and in parallel for fulfilling high current demand. String efficiency can be defined as measure of the degree of utilization on SCRs in a string.


String efficiency < 1. Derating factor (DRF)

1 – string efficiency.

If DRF more then

no. of SCRs will more, so string is more reliable.

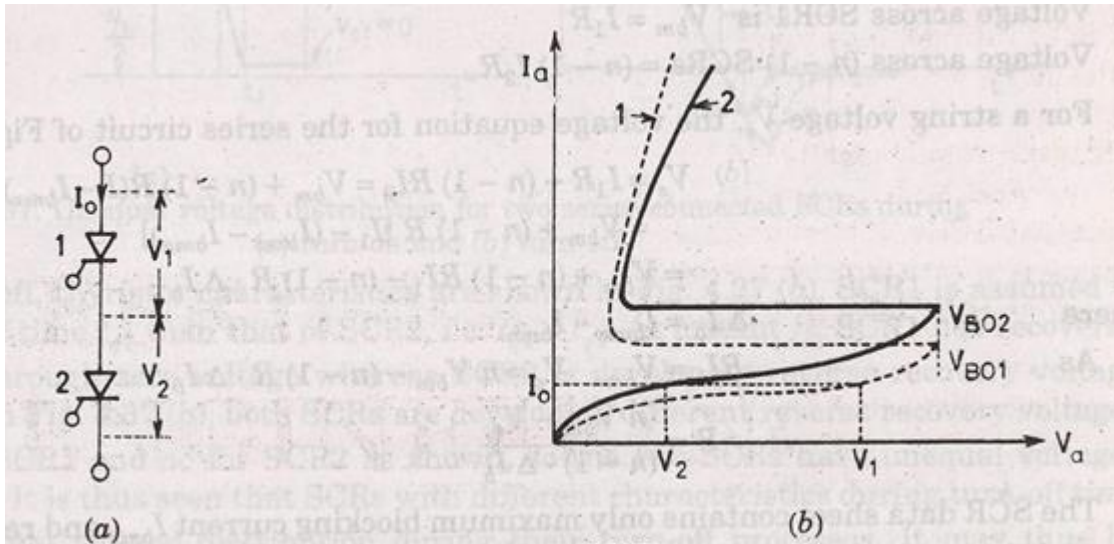Let the rated blocking voltage of the string of a series connected SCR is $2V_1$ as shown in the figure below, But in the string two SCRs are supplied a maximum voltage of V_1+V_2 .



$$\eta = \frac{V_1 + V_2}{2V_1}$$

Significance of string efficiency.

Two SCRs are have same forward blocking voltage ,When system voltage is more then the voltage rating of a single SCR. SCRs are connected in series in a string.

There is a inherent variation in characteristics. So voltage shared by each SCR may not be equal. Suppose, SCR1 leakage resistance > SCR2 leakage resistance. For same leakage current I_0 in the series connected SCRs. For same leakage current SCR1 supports a voltage V_1 , SCR2 supports a voltage V_2 .


So string η for two SCRs = $\frac{V_1+V_2}{2V_1} = 1(1 \pm \frac{V_2}{V_1}) < 1$.

So, $V_1 > V_2$.

The above operation is when SCRs are not turned ON. But in steady state of operation , A uniform voltage distribution in the state can be achieved by connect a suitable resistance across each SCRs , so that parallel combination have same resistance.

But this is a cumbersome work. During steady state operation we connect same value of shunt resistance across each SCRs. This shunt resistance is called *state equalizing circuit*.

Suppose,

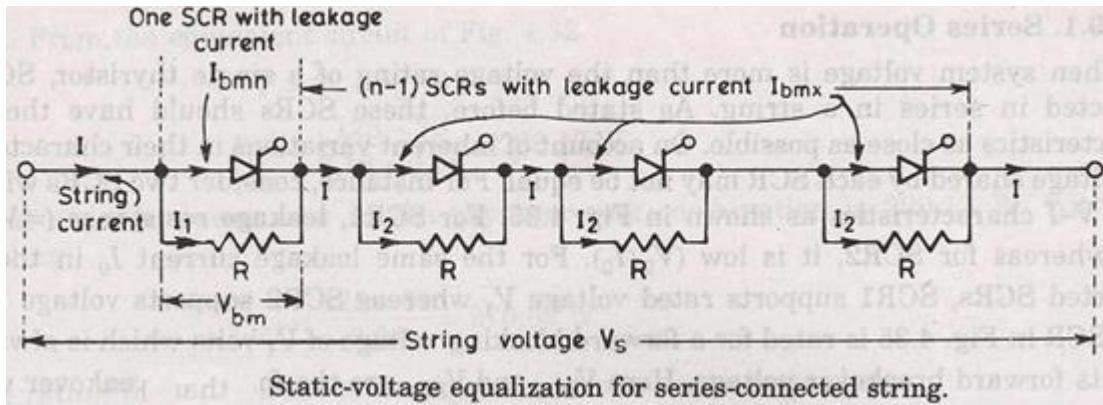

Let SCR1 has lower leakage current , It will block a voltage comparatively larger than other SCRs.

Voltage across SCR1 is $V_{bm} = I_1 R$.

Voltage across (n-1)SCR is $(n-1) I_2 R$, so the voltage equation for the series circuit is $V_s = I_1 R + (n-1) I_2 R = V_{bm} + (n-1) R (I - I_{bmx})$

As $I_1 = I - I_{bmn}$

$I_2 = I - I_{bmx}$

So, $V_s = V_{bm} + (n-1) R [I_1 - (I_{bmx} - I_{bmn})]$ If $\Delta I_b = I_{bmx} - I_{bmn}$

Then $V_s = V_{bm} + (n-1) R (I_1 - \Delta I_b)$ $V_s = V_{bm} + (n-1) R I_1 - (n-1) R \Delta I_b$ $R I_1 = V_{bm}$

So, $V_s = V_{bm} + (n-1) V_{bm} - (n-1) R \Delta I_b$

$= n V_{bm} - (n-1) R \Delta I_b$

$\Rightarrow R = \frac{n V_{bm} - V_s}{(n-1) \Delta I_b}$

SCR data sheet usually contain only maximum blocking current , I_{bmx}


so we assume $I_{bmn} = 0$

So $\Delta I_b = I_{bmx}$

So the value of R calculated is low than actually required.

SCRs having unequal dynamic characteristics:

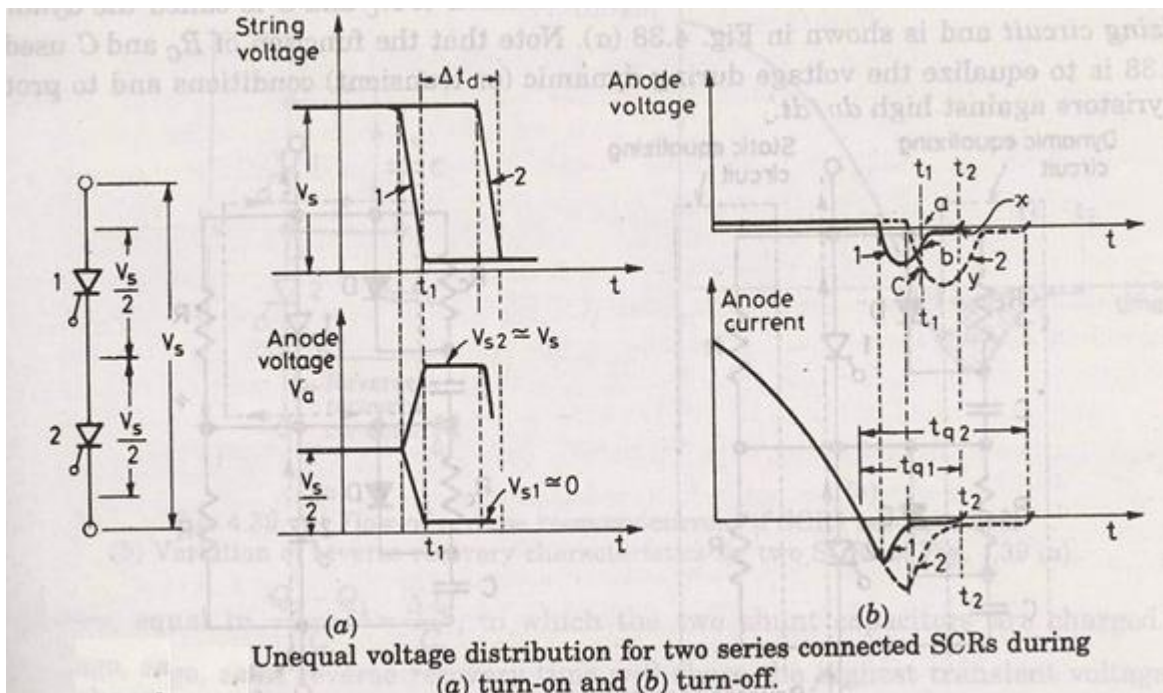It may occur that SCRS may have unequal dynamic characteristics so the voltage distribution across the SCR may be unequal during the transient condition.



SCR 1 and SCR 2 have different dynamic characteristics. Turn ON time of SCR 2 is more than SCR 1 by time Δ .

As string voltage is V_s so voltage shared by each SCRs be $V_s/2$. Now both are gated at same time so SCR 1 will turn ON at t_1 its voltage fall nearly to zero so the voltage shared by SCR2 will be the string voltage if the break over voltage of SCR 2 is less than V_s then SCR 2 will turn ON .

* In case V_s is less than the breakover voltage, SCR 2 will turn ON at instant 2. SCR 1 assumed to have less turn off t_{q1} time then SCR 2, so $t_{q1} < t_{q2}$. At t_2 SCR 1 has recovered while SCR 2 is developing recovery voltage at t_1 both are developing different reverse recovery voltage. At t_2 SCR 1 has recovered while SCR2 is developing reverse recovery voltage .

Conclusion :


* Series connected SCR develop different voltages during turn ON and turn OFF process. Till now we connect a simple resistor across the diode for static voltage equalizing circuit .


* During turn ON and turn OFF capacitance of reverse biased junction determine the voltage distribution across SCRs in a series connected string . As reverse biased junction have different capacitance called *self capacitance* , the voltage distribution during turn ON and turn Off process would be different.

* Under transient condition equal voltage distribution can be achieved by employing shunt capacitance as this shunt capacitance has the effect of that the resultant of shunt and self capacitance tend to be equal. The capacitor is used to limit the dv/dt across the SCR during forward blocking state. When this SCR turned ON capacitor discharges heavy current through the SCR. The discharge current spike is limited by damping resistor R_c . R_c also damps out high frequency oscillation that may arise due to series combination of C and series inductor. R_c & C are called *dynamic equalizing circuit*

Diode D is used during forward biased condition for more effective charging of the capacitor. During capacitor discharge R_c comes into action for limiting current spike and rate of change of current di/dt .

The R_c & C component also provide path to flow reverse recovery current. When one SCR regain its voltage blocking capability. The flow of reverse recovery current is necessary as it facilitates the turning OFF process of series connected SCR string. So C is necessary for both during turn ON and turn OFF process. But the voltage unbalance during turn OFF time is more predominant than turn ON time. So choice of C is based on reverse recovery characteristic of SCR.

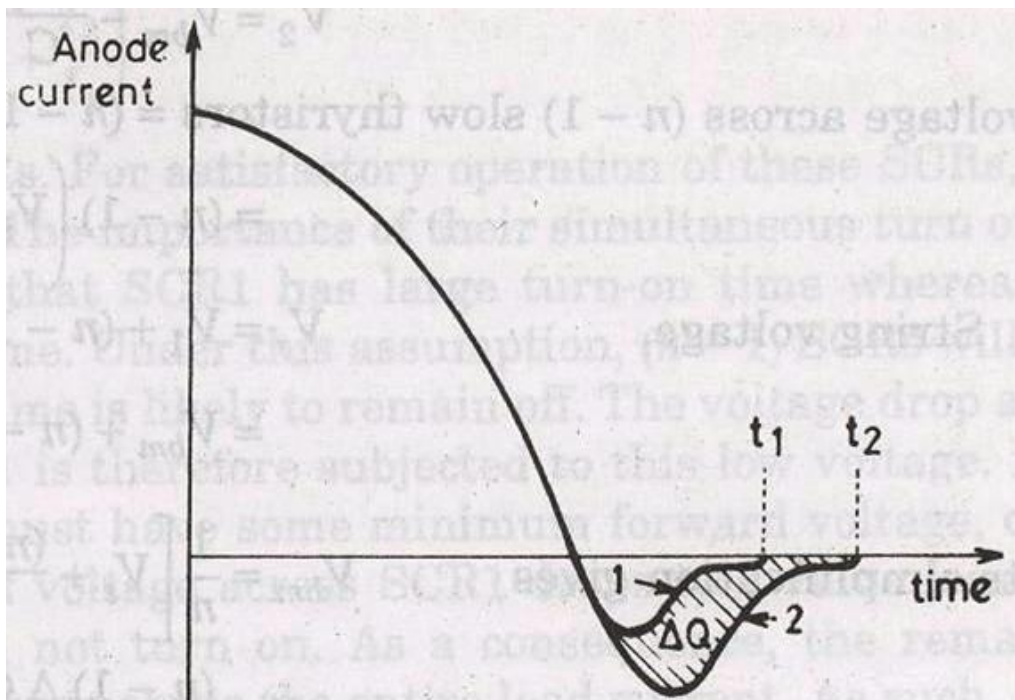

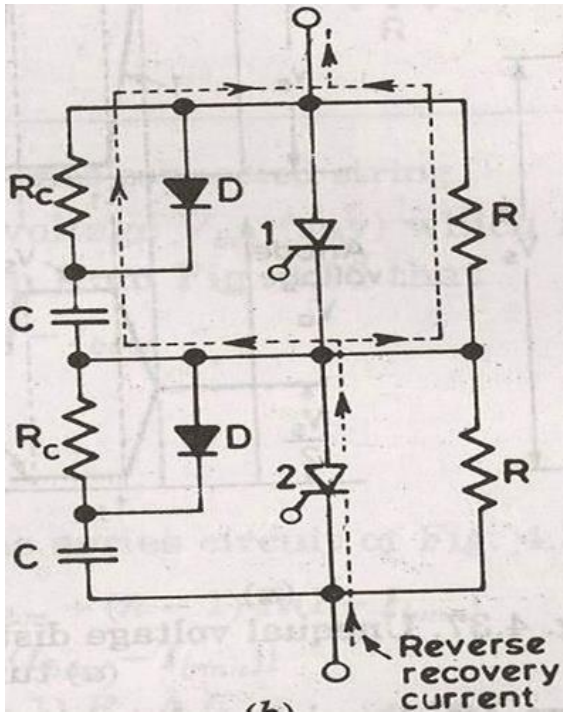

SCR 1 has short recovery time as compared to SCR 2. ΔQ is the difference in reverse recovery charges of two SCR 1 and SCR 2. Now we assume the SCR 1 recovers fast . i.e it goes into blocking state so charge ΔQ can pass through C . The voltage induced by c_1 is $\Delta Q/C$, where is no voltage induced across C_2 .

The difference in voltage to which the two shunt capacitor are charged is $\Delta Q/C$.

Now thyristor with least recovery time will share the highest transient voltage say V_{bm} ,

$$\text{So, } V_{bm} - V_2 = \Delta Q/CS_0,$$

$$V_2 = V_{bm} - \Delta Q/C \quad \text{As}$$

$$V_1 = V_{bm}$$

$$V_S = V_1 + V_2$$

$$= V_{bm} + (V_{bm} - \Delta Q/C)$$

$$V_S = 2V_{bm} - \Delta Q/C$$

$$\Rightarrow \frac{1}{2} (2V_{bm} - \Delta Q/C) = V_{bm}$$

$$\Rightarrow V_2 = V_{bm} - \Delta Q/C$$

$$V_1 = \frac{1}{2} [V_S - \Delta Q/C]$$

Now suppose that there are n series SCRs in a string.

Let us assume that if top SCR has similar to characteristic SCR 1. Then SCR 1 would support a voltage V_{bm}

* If the remaining $(n-1)$ SCR has characteristic that of SCR 2. Then SCR 1 would recover first and support a voltage V_{bm} . The charge $(n-1) \Delta q$ from the remaining $(n-1)$ SCR would pass through C.

$$V_1 = V_{bm}$$

$$V_2 = V_{bm} - \Delta q/C \text{ Voltage across } (n-1) \text{ slow thyristors}$$

$$V = (n-1) (V_{bm} - \Delta q/C) \text{ So,}$$

$$V_S = V_1 + (n-1) V_2$$

$$= V_{bm} + (n-1) (V_{bm} - \Delta q/C)$$


By simplifying we get , $\frac{-}{n}$

$$V_{bm} = \frac{1}{n} [V_S + (n-1) \Delta q/C] \text{ C} = \frac{(n-1) \Delta q}{n V_{bm} - V_S}$$

$$V_2 = (V_S - \Delta q/C) / n .$$

Parallel operation:

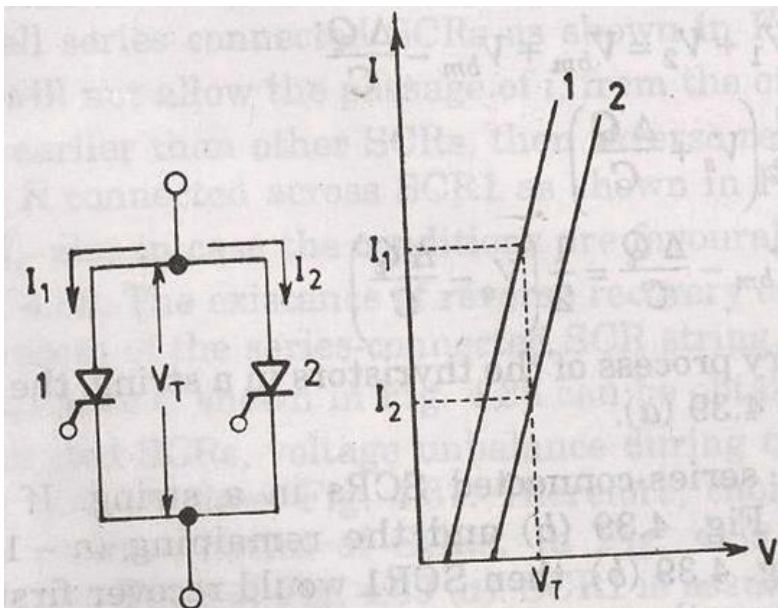When current required by the load is more than the rated current of single thyristor, SCRs are connected in parallel in a string .



For equal sharing of current, SCRs must have same $V - I$ characteristics during forward conduction. V_T across them must be same. For same V_T , SCR 1 share I_1 and SCR 2 share I_2 .

If I_1 is the rated current

$$I_2 < I_1$$

The total current $I_1 + I_2$ and not rated current $2I_1$. Type equation here.

Thus string efficiency,

$$\frac{I_1 + I_2}{2I_1} = \frac{1}{2} (1 + \frac{I_2}{I_1})$$

Middle conductor will have more inductance as compared to other two nearby conductor. As a result less current flow through the middle conductor. Another method is by magnetic coupling.

Thyristor gate characteristics:-

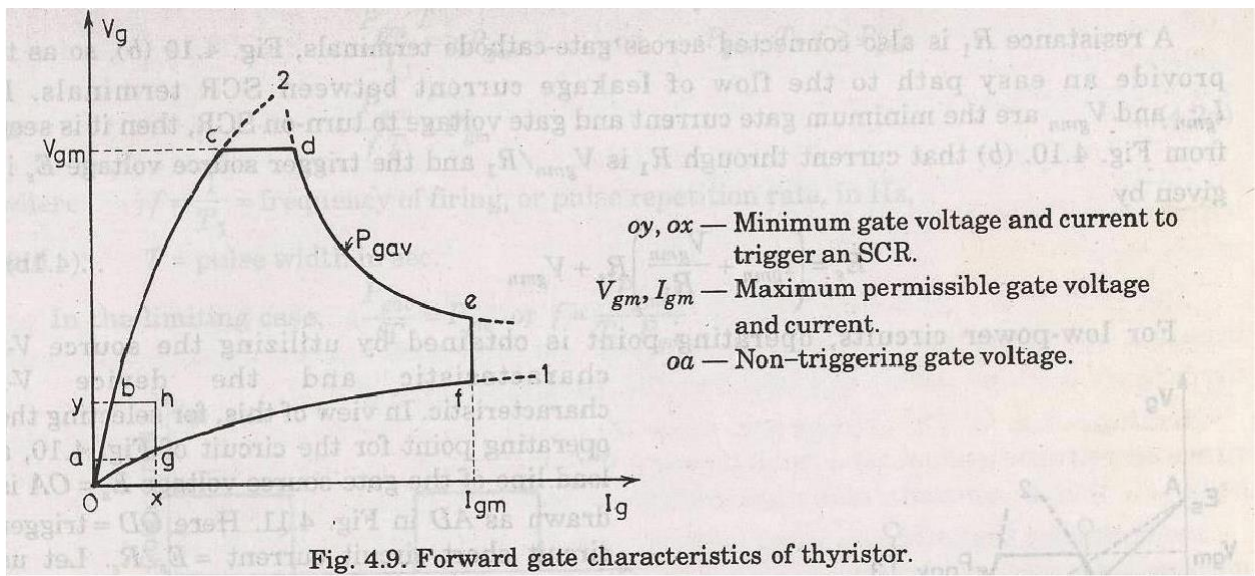


Fig. 4.9. Forward gate characteristics of thyristor.

$V_g = +ve$ gate to cathode voltage.

$I_g = +ve$ gate to cathode current.

As the gate cathode characteristic of a thyristor is a p-n junction, gate characteristic of the device is similar to diode.

Curve 1 the lowest voltage values that must be applied to turn on the SCR.

Curve 2 highest possible voltage values that can be safely applied to get circuit.

V_{gm} = Maximum limit for gate voltage .

I_{gm} = Maximum limit for gate current.


P_{gav} = Rated gate power dissipation for each SCR.

These limits should not be crossed in order to avoid the permanent damage of the device junction J_3 .

OY = Minimum limit of gate voltage to turn ON .OX = minimum limit of gate current to turn ON.

If V_{gm} , I_{gm} , P_{gav} are exceeded the thyristor will damage so the preferred gate drive area of SCR is bcdefghb.

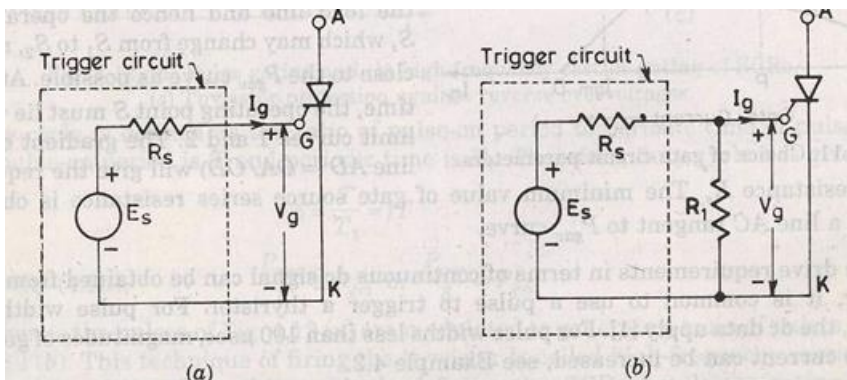oa = The non triggering gate voltage , If firing circuit generates +ve gatesignal prior to the desired instant of triggering the SCR.It should be ensured that this un wanted signal should be less than the non –triggering voltage oa.



$$E_s = V_g + I_g R_s$$

E_s = Gate source voltage

V_g = Gate cathode voltage

I_g = Gate current

R_s = Gate source resistance

R_s = The internal resistance of the trigger source

R_1 is connected across the gate cathode terminal, which provides an easy path to the flow of leakage current between SCR terminal. If I_{gmn} , V_{gmn} are the minimum gate current and gate voltage to turn ON the SCR.

$$E_s = (I_{gmn} + V_{gmn} / R_1) R_s + V_{gmn}$$


MODULE-II

RECTIFIER

Rectifier are used to convert A.C to D.C supply.

Rectifiers can be classified as single phase rectifier and three phase rectifier. Single phase rectifier are classified as 1- Φ half wave and 1- Φ full wave rectifier. Three phase rectifier are classified as 3- Φ half wave rectifier and 3- Φ full wave rectifier. 1- Φ Full wave rectifier are classified as 1- Φ mid point type and 1- Φ bridge type rectifier. 1- Φ bridge type rectifier are classified as 1- Φ half controlled and 1- Φ full controlled rectifier. 3- Φ full wave rectifier are again classified as 3- Φ mid point type and 3- Φ bridge type rectifier. 3- Φ bridge type rectifier are again divided as 3- Φ half controlled rectifier and 3- Φ full controlled rectifier.

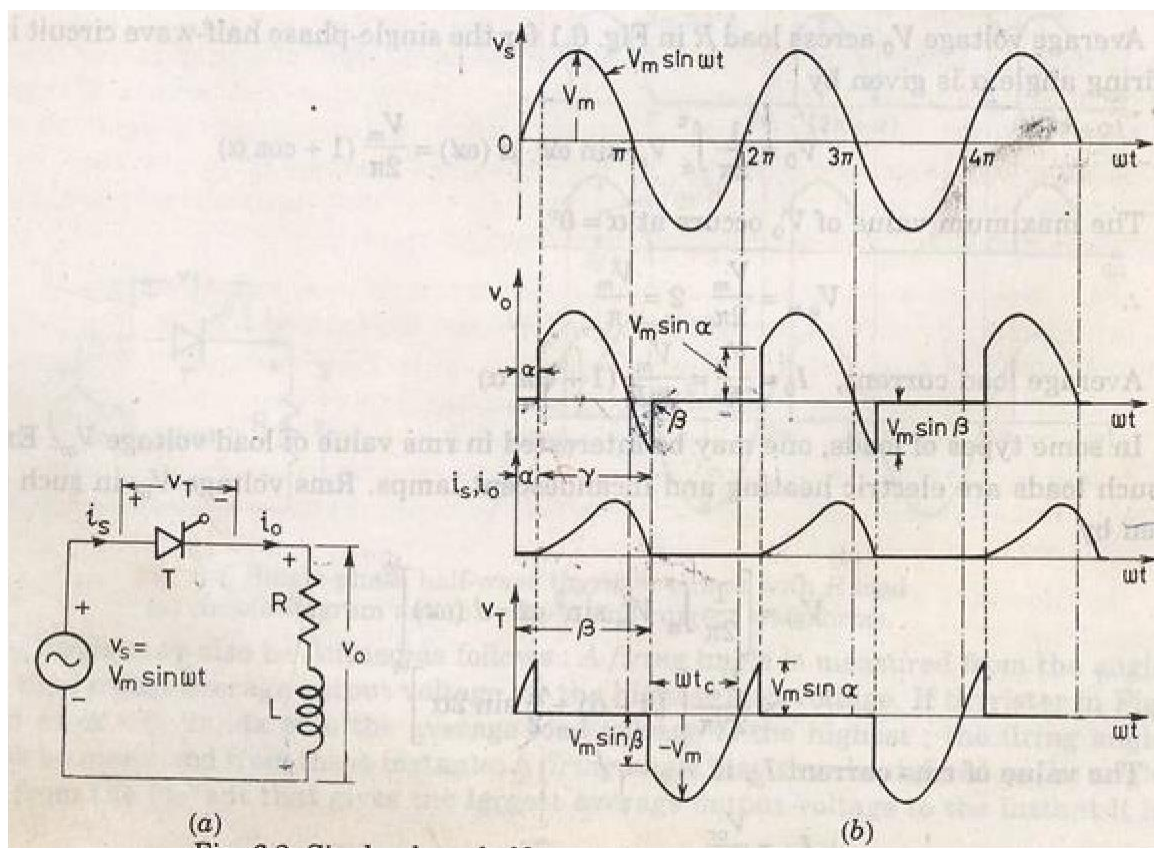Single phase half wave circuit with R-L load



Output current i_o rises gradually. After some time i_o reaches a maximum value and then begins to decrease.

At π , $v_o=0$ but i_o is not zero because of the load inductance L . After π interval SCR is reverse biased but load current is not less than the holding current.

At $\beta > \pi$, i_o reduces to zero and SCR is turned off.

At $2\pi + \beta$ SCR triggers again α is the firing angle.

β is the extinction angle.

ν conduction angle

Analysis for V_T .

At $\omega t = \phi$, $V = V_m \sin \phi$; During ϕ , $V_T = 0$; When $\phi = \pi$, $V_T = V_m \sin \pi$;

$$V_m \sin \omega t = R \frac{di_0}{dt}$$

$$i_s = \frac{V_m}{\sqrt{R^2 + X^2}} \sin(\omega t - \phi)$$

Where,

$$\phi = \tan^{-1} \frac{X}{R}$$

$$X = \omega L$$

Where ϕ is the angle by which I_s lags V_s . The transient component can be obtained as

$$R \frac{di_t}{dt} + i_t = 0$$

$$\text{So } i_t = A e^{-(R/L)t}$$

$$i_0 = i_s + i_t$$

$$\frac{V_m}{Z} \sin(\omega t - \phi) + A e^{-(R/L)t}$$

$$\text{Where } Z = \sqrt{R^2 + X^2}$$

$$\text{At } \alpha = \omega t, i_0 = 0;$$

$$0 = \frac{V_m}{Z} \sin(\alpha - \phi) + A e^{-(R/L)\alpha};$$

$$A = \frac{-V_m}{Z} \sin(\alpha - \phi) e^{(R/L)\alpha}$$

$$i = \frac{V_m}{Z} \sin(\omega t - \phi) - \frac{V_m}{Z} \sin(\alpha - \phi) e^{-R(\omega t - \alpha)/L\omega}$$

Therefore,

$$\omega t = \beta, i_0 = 0;$$

$$\text{So } \sin(\beta - \alpha) = \sin(\alpha - \beta)e^{-(\beta - \alpha)/(\omega L)}$$

β can be obtained from the above equation. The average load voltage can be given by


$$\frac{1}{2\pi} \int_{\alpha}^{\beta} V_m \sin \omega t d(\omega t)$$

$$\frac{V_m}{2\pi} (\cos(\alpha) - \cos(\beta))$$

Average load current

$$I_0 = \frac{V}{R} (\cos \alpha - \cos \beta)$$


Single phase full converter

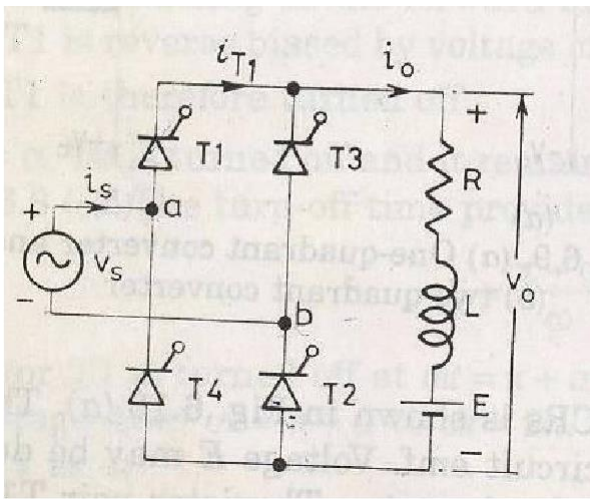


$$\frac{1}{2\pi} \int_{\alpha}^{\beta} V_m \sin(\omega t) d(\omega t)$$

$$\frac{2V_m}{\pi} \cos \alpha$$

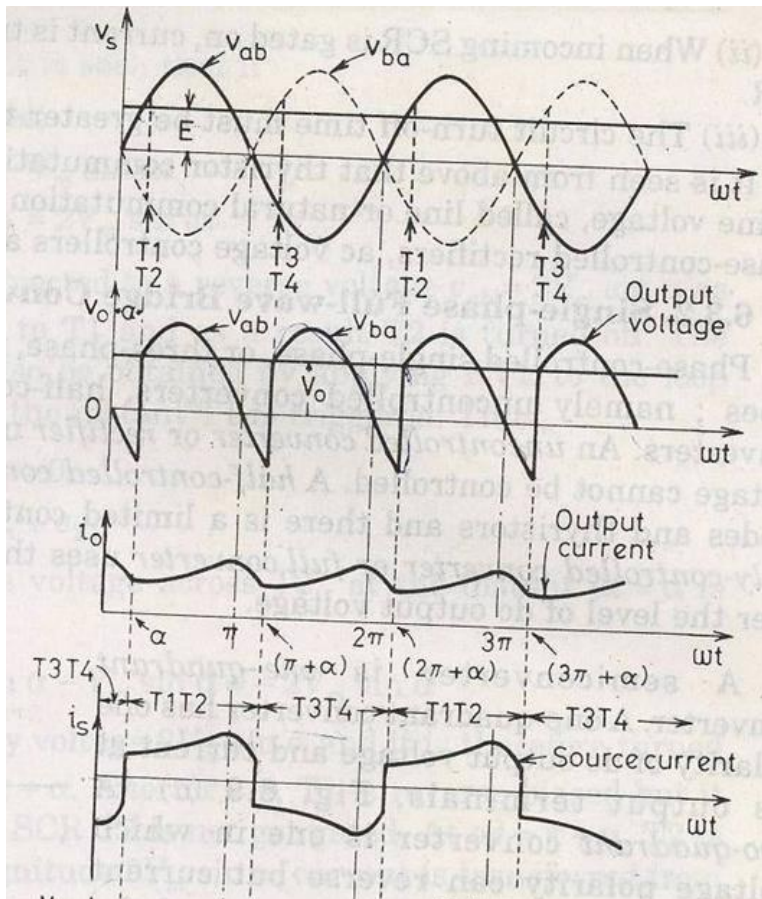T₁, T₂ triggered at α and π radian latter T₃, T₄ are triggered.



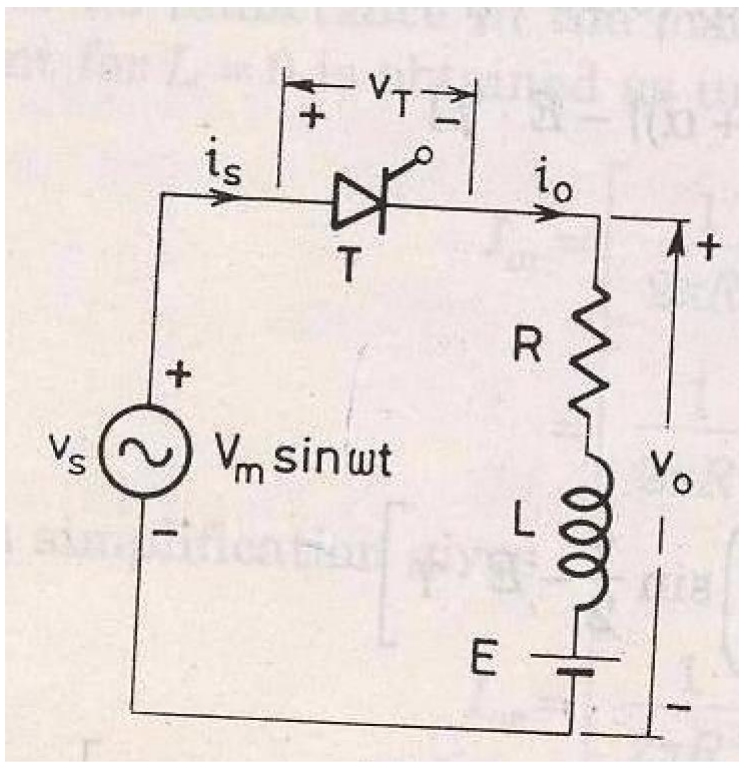Single phase half wave circuit with RLE load



The minimum value of firing angle is

$$V_m \sin(\omega t) - E$$

S

o

$$\frac{V_m \sin \omega t}{V_m} - E$$


□
1

Maximum value of firing angle

$$\frac{\pi}{2} \leq \alpha \leq \frac{3\pi}{2}$$

The voltage differential equation is
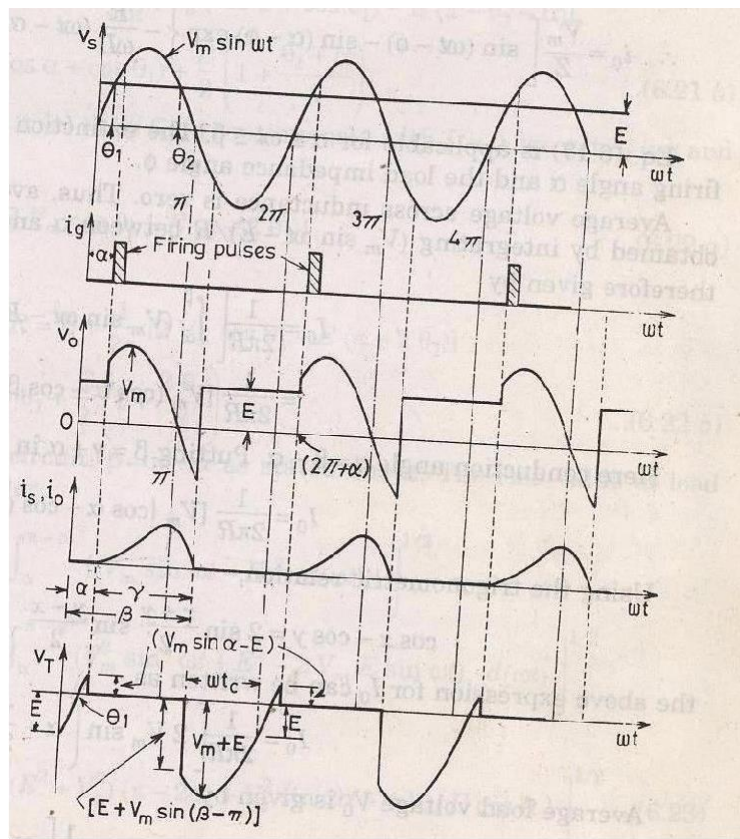
$$V_m \sin(\omega t) - E = R i_0 + L \frac{di_0}{dt}$$



$$i_s = i_{s1} + i_{s2}$$

Due to source volt

$$i_s = \frac{V_m \sin(\omega t)}{Z}$$

Due to DC counter emf

$$i_{s2} = E/R$$

$$i_t = A e^{-(R/L)t}$$

Thus the total current is given by

$$i_{s1} + i_{s2} = i_t$$

$$\frac{V_m}{Z} \sin(\omega t - \phi) = \frac{E}{R} + A e^{-(R/L)t}$$

$$i_s = \frac{V_m}{Z} \sin(\omega t - \phi) - \frac{E}{R} + A e^{-(R/L)t}$$

$$At = t \implies i_0 = 0$$

$$A = \left[\frac{E}{R} - \frac{V_m}{Z} \sin(\phi) \right] e^{R/L}$$

So

$$V_m \left[\frac{R}{Z} \sin(\omega t - \phi) - \frac{R}{Z} \sin(\phi) \right] e^{-R/L} = \left[\frac{R}{Z} \sin(\omega t - \phi) - \frac{R}{Z} \sin(\phi) \right] e^{-R/L}$$

Average voltage across the inductance is zero. Average value of load current is

$$\frac{1}{2\pi} \int_0^{2\pi} \left[\frac{V_m}{Z} \sin(\omega t - \phi) - \frac{E}{R} \right] d(\omega t)$$

$$\left[\frac{V_m}{Z} \cos(\omega t - \phi) - \frac{E}{R} \omega t \right]_0^{2\pi}$$

$$=$$

$$\left[\frac{V_m}{Z} \cos(\omega t - \phi) - \frac{E}{R} \omega t \right]_0^{2\pi}$$

$$= \frac{V_m}{Z} \cos(\phi) - \frac{E}{R}$$

Conduction angle α

$$\alpha = \pi - \phi$$

$$I_0 = \frac{1}{2} \left[\frac{V_m}{Z} \cos(\alpha) - \frac{E}{R} \right]$$

$$\cos A - \cos B = 2 \sin \frac{A+B}{2} \sin \frac{A-B}{2}$$

2

2

S
o

I
o
□

$$\frac{1}{2} \left[\frac{\sin(\frac{\pi}{2} - \nu)}{2} \frac{V}{R} \right]$$

$$E = I_0 R$$

$$E_1 = \frac{V_m}{2} \left[\sin\left(\frac{\omega t}{2}\right) + \sin\left(\frac{3\omega t}{2}\right) + \dots \right]$$

$$E_2 = \frac{V_m}{2} \left[\sin\left(\frac{3\omega t}{2}\right) + \sin\left(\frac{5\omega t}{2}\right) + \dots \right]$$

If load inductance L is zero then

$$\omega L = 0$$

And $\phi = 0$

But $\phi = \frac{V_m}{\omega L} \sin(\omega t)$

So $\phi = \frac{V_m}{\omega L} \sin(\omega t)$

And $\phi = \frac{V_m}{\omega L} \sin(\omega t)$

So average current will be

$$I_0 = \frac{1}{R} \left[\frac{V_m}{2} (\cos\phi_1 - \cos\phi_2) \right]$$

So $V_0 = E + I_0 R$

$$\frac{V_m}{2} (\cos\phi_1 - \cos\phi_2) = \frac{E}{2} (1 - \phi_1^2)$$

For no inductance rms value of load current

$$I_0 = \frac{V_m}{2R} (1 - \phi_1^2)$$

2

$$V_m \sin(\omega t) \cos(\omega t) = \frac{V_m}{2} \sin(2\omega t)$$


Power delivered to load

$$P = I^2 R \quad \text{or} \quad I E$$

Supply power factor

$$P_f = \frac{I^2 R}{I_s I_{or}} \quad \text{or} \quad \frac{0}{I_s I_{or}}$$

Single phase full wave converter:

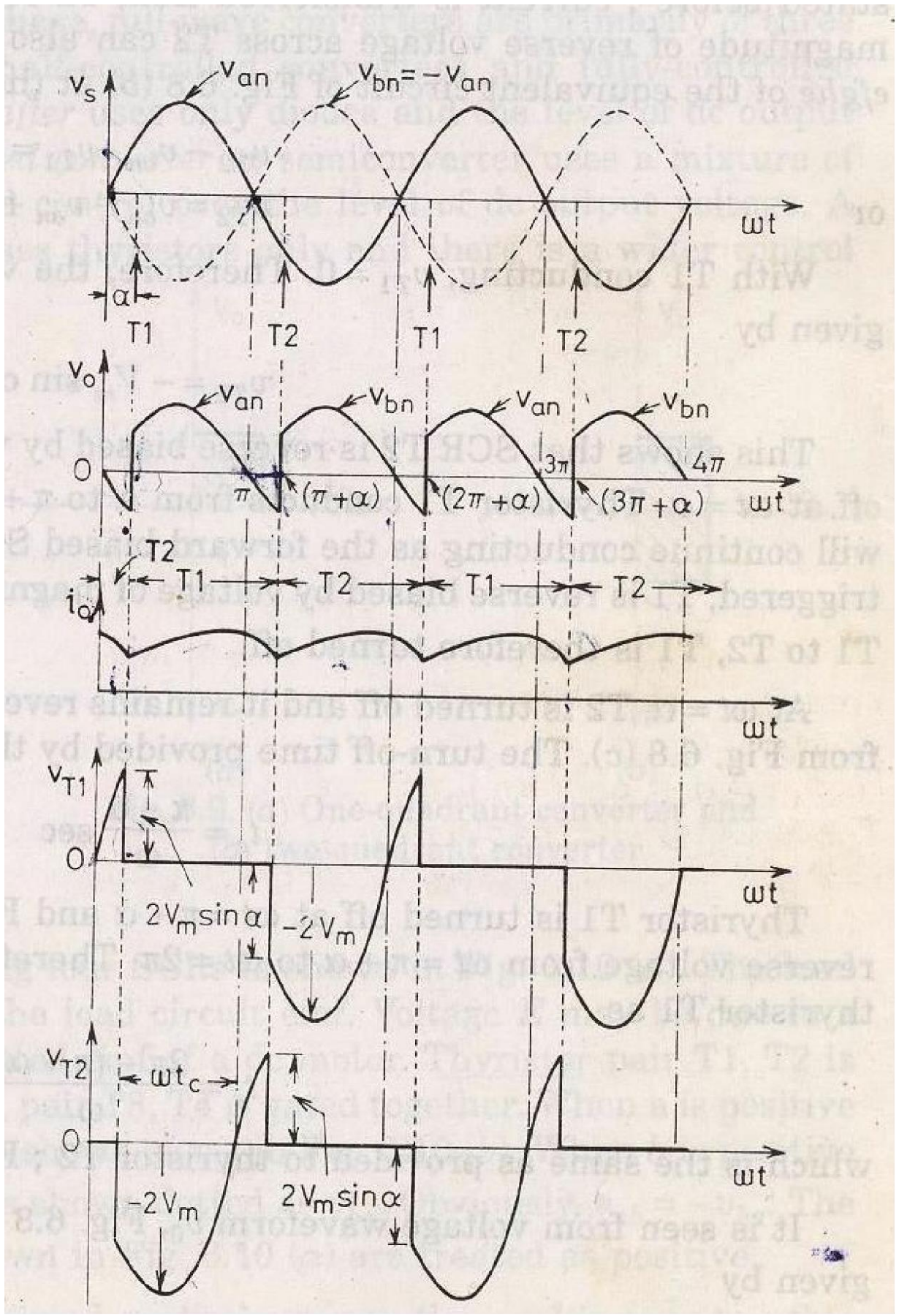


$$V = \int_0^m \sin(\omega t) d(\omega t)$$

$$\frac{V}{0} \dots m$$

$$\frac{2V_m \sin \omega t}{\dots}$$

Single phase semi converter:

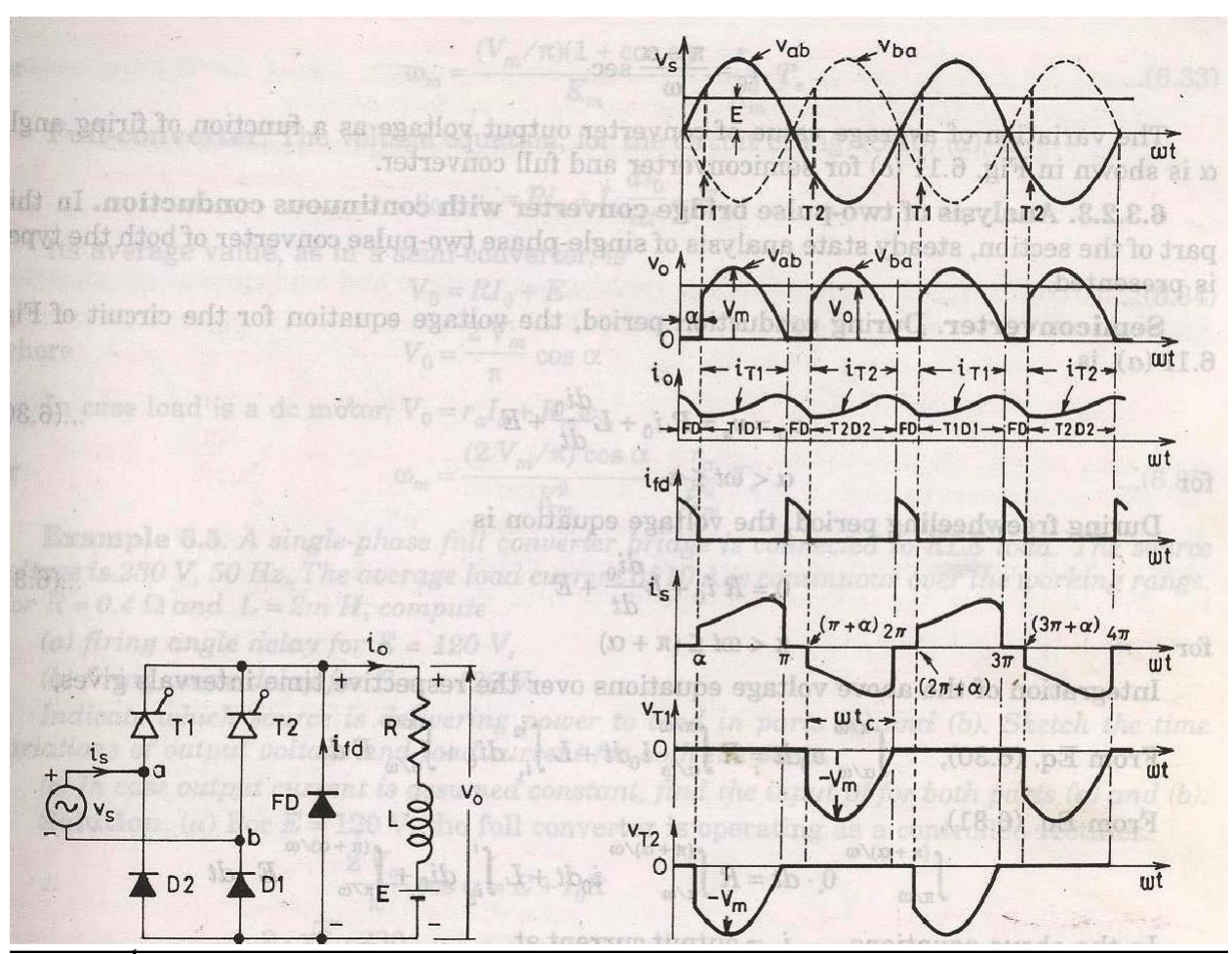

$$V = \int_0^m \sin(\omega t) d(\omega t)$$

$$\frac{V}{0} \dots m$$

$$\frac{V_m \cos \omega t}{\dots}$$

full converter:

steady state analysis

$$\frac{V}{s} = Ri + L \frac{di}{dt} = E$$

$$V_0 = RI_0 = E$$

$$V = \frac{2V_m}{\alpha} \cos \alpha$$

So in case of DC motor load

$$V_0 = r_a I_a = \frac{2V_m}{\alpha} \cos \alpha$$

$$\frac{2V_m}{\alpha} \cos \alpha = r_a I_a$$

$$T = \frac{2}{\pi} I_a$$

$$I_a = \frac{T}{\frac{2}{\pi}}$$

P
u
t

$$P = I_a \frac{T_e}{\frac{2}{\pi}} = \left(\frac{2V_m}{\alpha} \right) \cos \alpha$$

$$I_a = \frac{P}{\frac{2V_m}{\alpha} \cos \alpha} = \frac{r_a T_e}{\alpha^2}$$


So

MODULE - III

CHOPPER

A chopper is a static device that converts fixed DC input voltage to variable output voltage directly. Chopper are mostly used in electric vehicle, mini haulers.

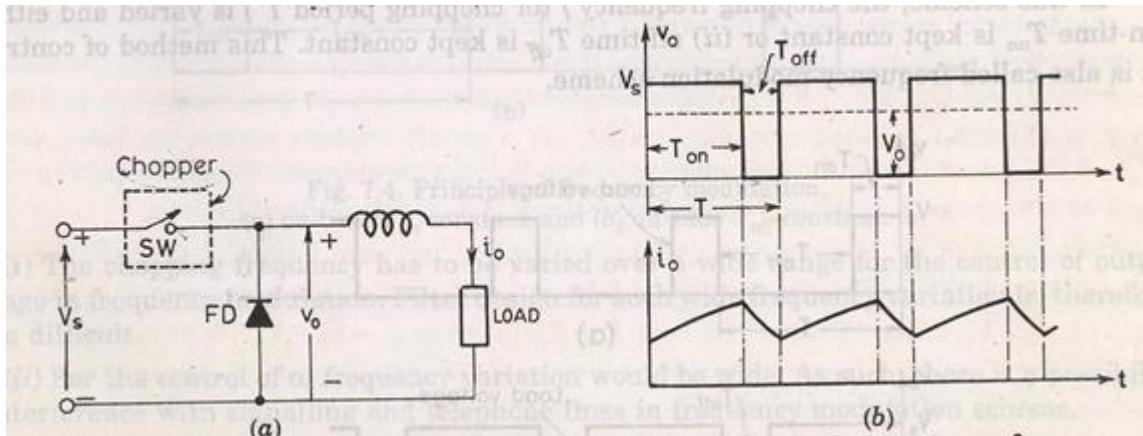Chopper are used for speed control and braking. The systems employing chopper offer smooth control, high efficiency and have fast response.



The average output voltage is

$$V_a = \frac{1}{T} \int_0^{t_1} V_s dt = \frac{t_1}{T} V_s = f t_1 V_s = \alpha V_s$$

The average load current

$$I_a = \frac{V_a}{R} = \frac{\alpha V_s}{R}$$

Where, T=chopping period Duty cycle of chopper =

$$\alpha = \frac{t_1}{T}$$

f=chopping frequency

The rms value of output voltage is

$$V_r = \sqrt{\frac{1}{T} \int_0^{t_1} V_s^2 dt} = \sqrt{\alpha} V_s$$

If we consider the converter to be loss less then the input power is equal to the output power and is given by

$$P_i = \frac{1}{T} \int_0^T V_0 i dt = \frac{1}{T} \int_0^T V^2 R dt$$

$$= \frac{R}{T} \int_0^T V^2 dt$$

The effective input resistance seen by the P source is

$$R_{as} = \frac{V_s}{I_{as}} = \frac{V_s}{\frac{P}{V_s}} = \frac{V_s^2}{P}$$

The duty cycle α can be varied by varying t_1 , T of frequency.

Constant frequency operation:


1) T
 The chopping period T is kept constant and on time is varied. The pulse width modulation, the width of the pulse is varied.

2) V
 Variable frequency operation, the chopping frequency f is varied. Frequency modulation, either on time or off time is kept constant.

This type of control generate harmonics at unpredictable frequency and filter design is often difficult.

TYPES OF CHOPPER:

FIRST QUADRANT OR TYPE A CHOPPER:

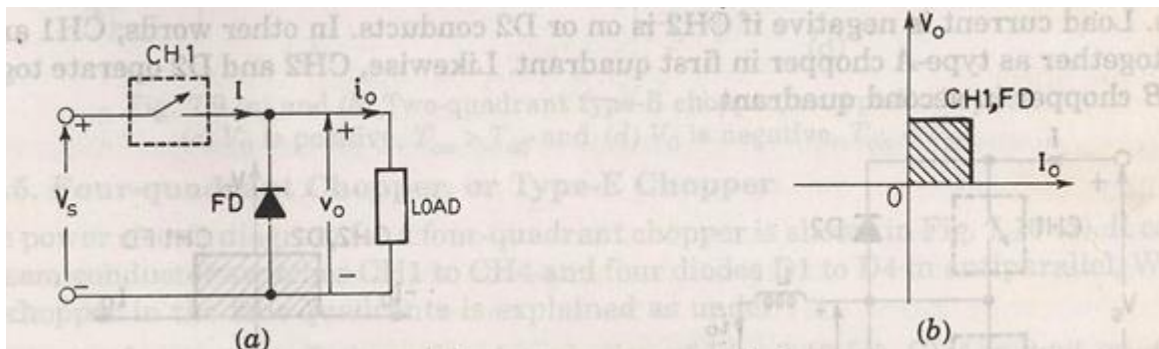


When switch ON

$$V_0 = V_s$$

Current i_o flows in the same direction when switch off. $V_o=0, i_o=0$

So, average value of both the load and the current are positive.

SECOND QUADRANT OR TYPE B CHOPPER:

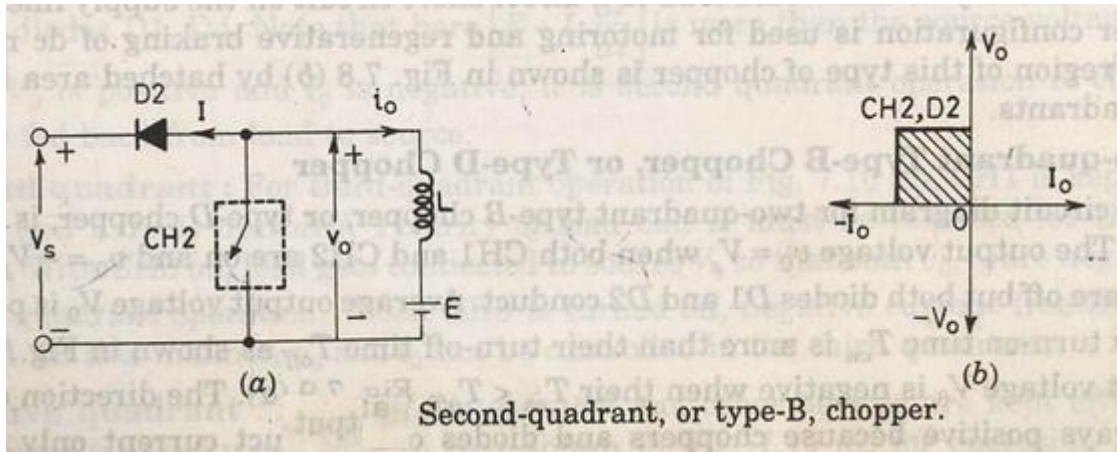

When switch are closed the load voltage E drives current through L and switch. During T_{on}

L
stor
es
ene
rgy
.

$$V_o \text{ exceeds source voltage } V_s.$$

Wh
en
swi
tch
off


$$V_o = E + L \frac{di}{dt}$$

Diode D_2 is forward biased, power is fed back to supply. As V_o is more than source voltage. So such chopper is called step up chopper.

$$V_o = E + L \frac{di}{dt}$$

So current is always negative and V_o is always positive.

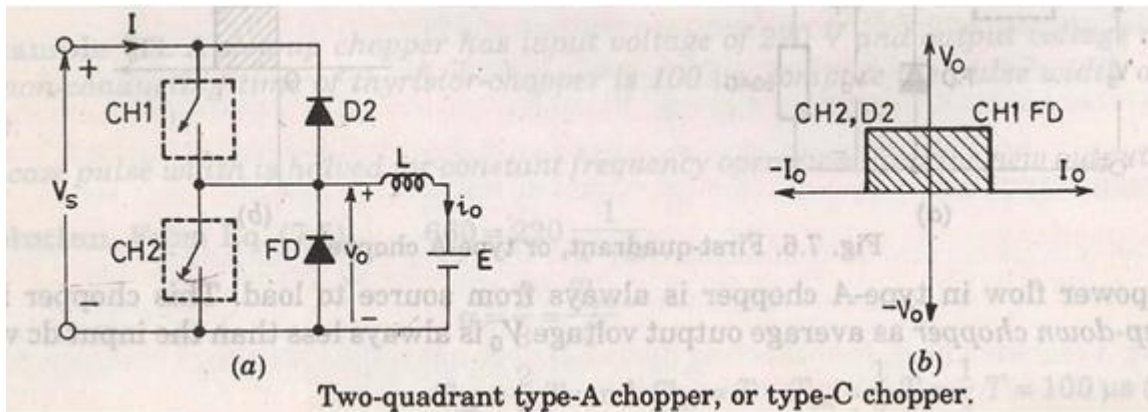TWO QUADRANT TYPE A CHOPPER OR, TYPE C CHOPPER:



Both the switches never switch ON simultaneously as it lead direct short circuit of the supply.


Now when sw2 is closed or FD is on the output voltage V_o is zero. When sw1 is ON or diode D conducts output voltage is V_o is $+V_s$ ' CURRENT ANALYSIS:

When CH1 is ON current flows along i_o . When CH1 is off current continues to flow along i_o as FD is forward biased. So i_o is positive.

Now when CH2 is ON current direction will be opposite to i_o . When sw2 is off D2 turns ON.

Load current is $-i_o$. So average load voltage is always positive. Average load current may be positive or negative.

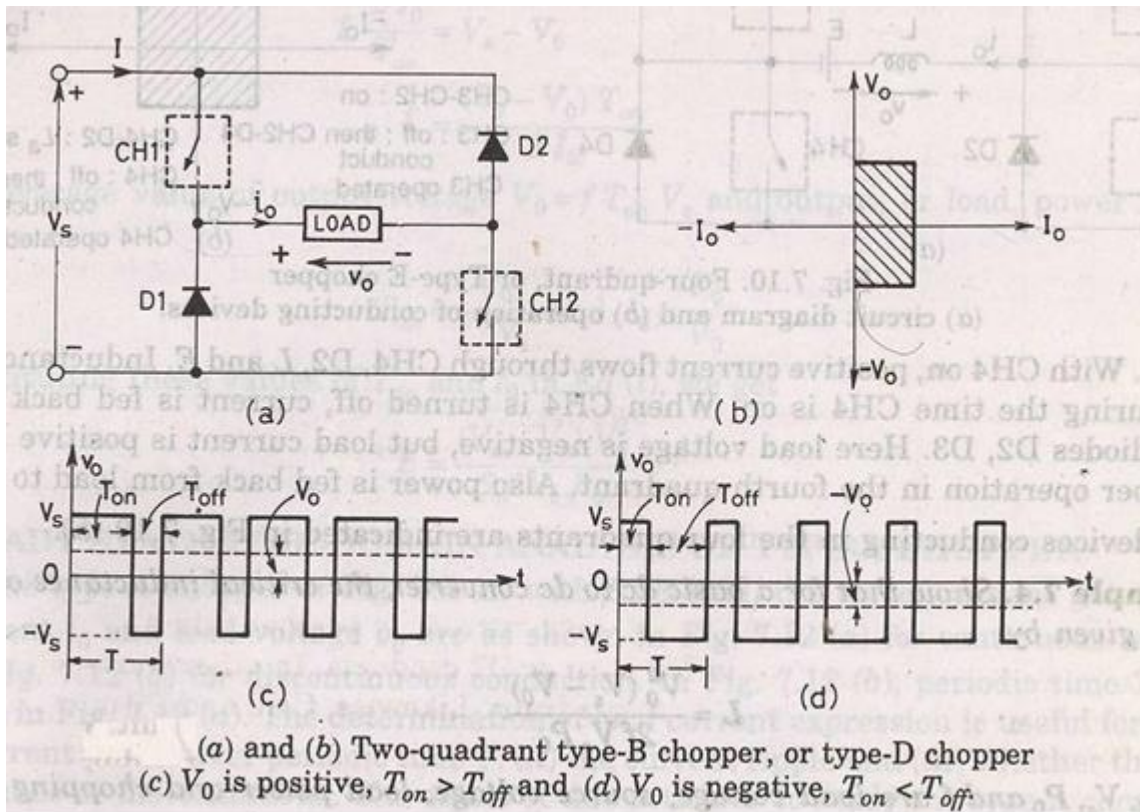TWO QUADRANT TYPE B CHOPPER, OR TYPE D CHOPPER:




When CH1 and CH2 both are on then $V_0 = V_s$.

When CH1 and CH2 are off and D1 and D2 are on $V_0 = -V_s$.

The direction of current is always positive because chopper and diode can only conduct in the direction of arrow shown in fig.

Average voltage is positive when $T_{on} > T_{off}$

FOUR QUADRANT CHOPPER, OR TYPE E CHOPPER

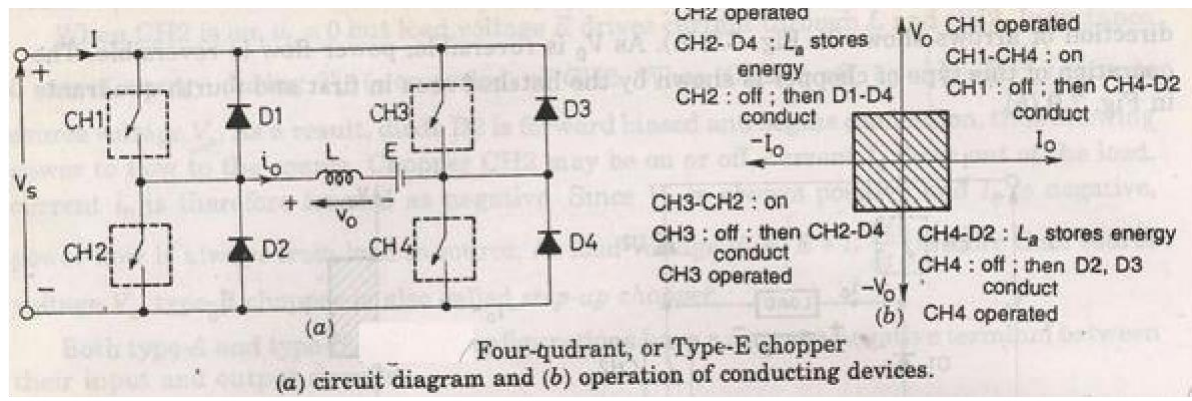

FIRST QUADRANT:

CH4 is kept ON CH3 is off

CH1 is operated $V_o = V_s$

$i_o =$ positive

when CH1 is off positive current free wheels through CH4, D2 so V_o and I_o is in first quadrant.

SECOND QUADRANT:

CH1, CH3, CH4 are off. CH2 is operated.

Reverse current flows and I is negative through L CH2 D4 and E. When CH2 off D1 and D4 is ON and current i_d fed back to source. So

$$E \gg L \frac{di}{dt}$$

dt is more than source voltage V_s .

As i_o is negative and V_o is positive, so second quadrant operation. THIRD QUADRANT:

CH1 OFF, CH2 ON

CH3 operated. So both V_o and i_o is negative.

When CH3 turned off negative current freewheels through CH2 and D4. FOURTH QUADRANT:

CH4 is operated other are off.

Positive current flows through CH4 E L D2.

Inductance L stores energy when current fed to source through D3 and D2. V_0 is negative.

STEADY STATE ANALYSIS OF PRACTICAL BUCK CHOPPER:

The voltage across the inductor L is $e_L = L di/dt$.

$$\frac{V_s - V_a}{L} = \frac{d(i_2 - i_1)}{dt}$$

as

The inductor current falls linearly from I_2 to I_1 in time t_2 as $V_s = 0$.

$$\frac{0 - V_a}{L} = \frac{d(i_1 - i_2)}{dt}$$

If $I_2 - I_1 = \Delta I$ then

$$\frac{V_a}{L} = \frac{\Delta I}{t_2}$$

$$t_2 = \frac{L \Delta I}{V_a}$$

$\Delta I = I_2 - I_1 =$ peak to peak ripple current.

$$\Delta I = \frac{(V_s - V_a)t_1}{L} - \frac{V_a t_2}{L}$$

Now $t_1 = \alpha T$, $t_2 = (1 - \alpha)T$

$$\frac{V_s - V_a}{L} \alpha T = \frac{V_a}{L} (1 - \alpha)T$$

$\alpha < 1$ so it is a step down or buck converter. If the circuit is lossless then $V_s I_s = V_a I_a = \alpha V_s I_a = \alpha I_a$.

Now switching period T can be expressed as

$$T=1/f= t_1+ t_2=\Delta IL/(V_s-V_a) + \Delta IL/(V_a)$$

$$=\Delta ILV_s/V_a(V_s-V_a)$$

So peak to peak ripple current

$$\Delta I = \frac{V_a(V_s - V_a)}{fLV_s}$$

$$\Delta I = \frac{V_a(1 - \frac{V_a}{V_s})}{fL}$$

The peak to peak voltage of the capacitor is

$$V_c = \frac{\Delta I}{8fc}$$

So from above equation

$$V_c = \frac{V_a(V_s - V_a)}{8Lcf^2V_s} \frac{V_s(1 - \frac{V_a}{V_s})}{8Lcf^2}$$

Condition for continuous inductor current and capacitor voltage :

If I_L is the average inductor current

$$\Delta I_L = 2I_L \dots \text{as}$$

$$V_a = V_s$$

$$\frac{V_s(1 - \frac{V_a}{V_s})}{fL}$$

$$\frac{I_2 - I_1}{As} = I_L$$

$$\text{So } I = 2I_L$$

$$\frac{V_s(1 - \frac{V_a}{V_s})}{fL} \dots \text{eq (2)}$$

$$\frac{V_s}{fL} \left(1 - \frac{V_a}{V_s}\right) = \frac{L}{2} \frac{V_a}{R} \dots \text{eq(4)}$$

$$I_a = \frac{V_s}{R}$$

$$I_a = \frac{2V_s}{R}$$

So equation 4 gives

$$L_c = \frac{(1 - \frac{V_a}{V_s})R}{2f}$$

Which is the critical value of inductor

$$L_c = \frac{V_s - V_a}{2f}$$

$$\frac{2V_a - V_s}{8Lf^2} = \frac{V_s - V_a}{2f}$$

$$L_c = \frac{1}{16Lf^2}$$

Peak to peak ripple voltage of capacitor:

$$V_c(t) = V_c(0) + \frac{1}{C} \int_0^t I_a dt$$

$$V_c(t) = V_c(0) + \frac{I_a t}{C}$$

$$V_c(t) = V_c(0) + \frac{I_a t}{C}$$

$$t_1 = \frac{V_a - V_s}{V_{af}}$$

$$t_1 = \frac{V_a - V_s}{V_{af}}$$

$$V_a = 1 - \frac{t_1}{T} V_s$$

$$V_a = 1 - \frac{t_1}{T} V_s$$

$$\frac{1}{t} \int_0^t V_a - V_s V_{af} dt$$

$$\frac{1}{V_c} \int_0^t I_a (V_a - V_s) V_{af} dt$$

$$V_c = \frac{I_a}{fc}$$

Condition for continuous inductor current and capacitor voltage:

If $I_L =$ average inductor current then

$$I_L = \frac{I_a}{2}$$

$$\frac{I_a}{2} = \frac{L}{fL} \frac{2V_s}{(1-D)R}$$

$$V_a = \frac{V_s}{1-D}$$

$$I_a = \frac{2V_s}{(1-D)R}$$

$$\frac{I_a}{2} = \frac{2V_s}{(1-D)R} \frac{L}{fL}$$

$$L_c = \frac{1}{2f} \frac{R}{a}$$

$$V_c = 2V_a$$

$$\frac{I_a}{cf} = \frac{2V_a}{a} = \frac{2I_a R}{a}$$



$$c = \frac{2fR}{a}$$

MODULE – IV

INVERTERS

The device that converts dc power into ac power at desired output voltage and frequency is called an inverter.

Single phase voltage source inverters

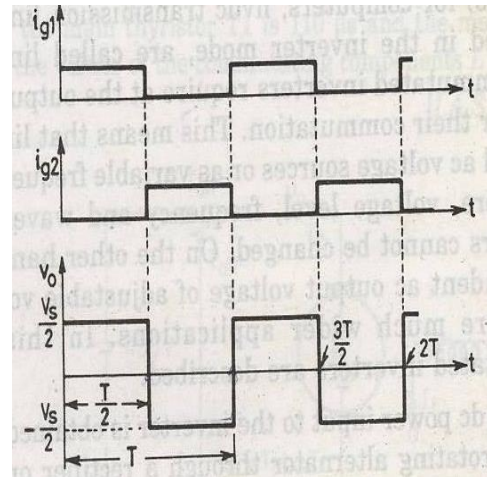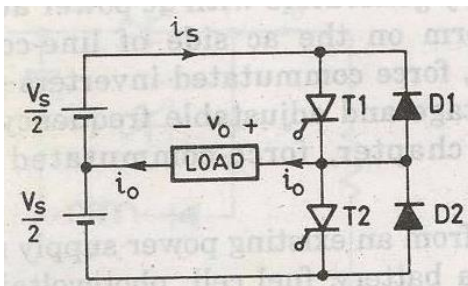

$$\frac{1}{T_0} \int_0^{T_0} v_o dt = \frac{V_s}{2} \int_0^{T/2} dt - \frac{V_s}{2} \int_{T/2}^T dt = 0$$

$$V_{0_{rms}} = \sqrt{\frac{1}{T_0} \int_0^{T_0} v_o^2 dt} = \frac{2V_s}{\sqrt{2\pi}}$$

$$V_{0_{rms}} = \sum_{n=1}^{\infty} \frac{2V_s}{n\pi} \sin(n\omega t)$$

Due to symmetry along x-axis

$$a_0 = 0, a_n = 0$$

$$b_n = \frac{4V_s}{n\pi}$$

The instantaneous output voltage

$$v_o = \sum_{n=1,3,5,\dots}^{\infty} \frac{2V_s}{n\pi} \sin(n\omega t)$$

$$=0, n=2,4,\dots$$

The rms value of the fundamental output voltage

$$V_{0_{rms}} = \frac{2V_s}{\sqrt{2\pi}} = 0.45V_s$$

$$\text{So if } V_0 = \sum_{n=1,3,5,\dots}^{\infty} \frac{2V_s}{n\pi} \sin(n\omega t)$$

$$= \sum_{n=1,3,5,\dots}^{\infty} \frac{2V_s}{n\pi \sqrt{R^2 + (n\omega L)^2}} \sin(n\omega t - \theta_n)$$

$$P_{01} = \frac{2V_s^2}{\sqrt{2\pi} \sqrt{R^2 + (\omega L)^2}} \quad (I)^2 R = \quad [$$

DC Supply Current

Assuming a lossless inverter, the ac power absorbed by the load must be equal to the average power supplied by the dc source.



$$\int_0^T i_s(t) dt = \int_0^T \sqrt{2} V_{01} \sin(\omega t) \sqrt{2} I_0 \sin(\omega t - \theta_1) dt = I_s$$

V_{01} = Fundamental rms output voltage

I_0 = rms load current

θ_1 = the load angle at the fundamental frequency

Single phase full bridge inverter

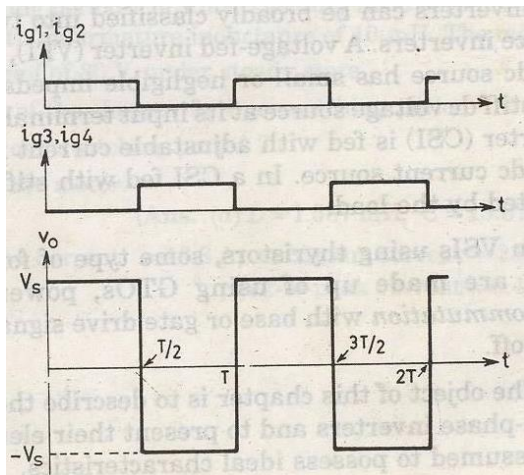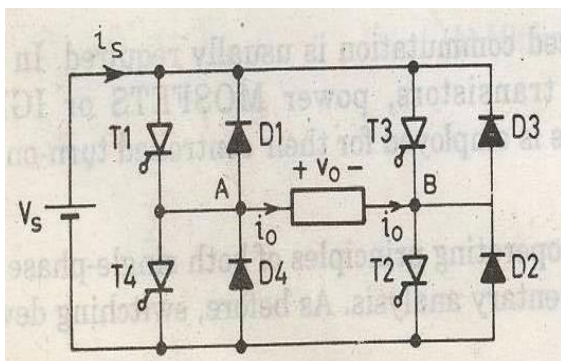

$$\text{For } n=1, V_{01} = \frac{4V_s}{\sqrt{2}\pi} = 0.9V \text{ (The rms of fundamental)}$$

Instantaneous load current i_o for an RL load

$$i_o = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_s}{n\pi \sqrt{R^2 + (n\omega L)^2}} \sin(n\omega t - \theta_n)$$

$$\theta_n = \tan^{-1} \left(\frac{n\omega L}{R} \right)$$


The rms output voltage is

$$V_{01} = \left(\frac{2}{T} \int_0^{T/2} V_s^2 dt \right)^{1/2} = V_s$$

The instantaneous output voltage in a fourier series

$$v_0 = \frac{4V_s}{\pi} \sum_{n=1,3,5,\dots}^{\infty} \sin(n\omega t)$$

Single phase bridge inverter

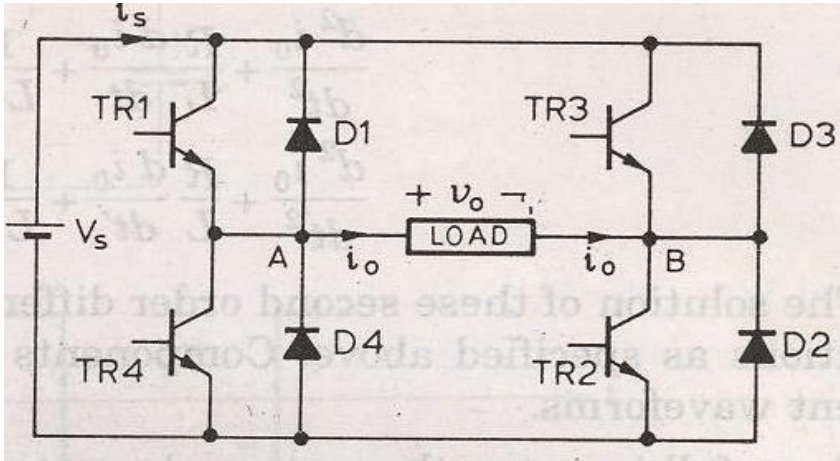


INVERTER

Inverters are of the two types

- 1) VSI
- 2) CSI

Pulse width model

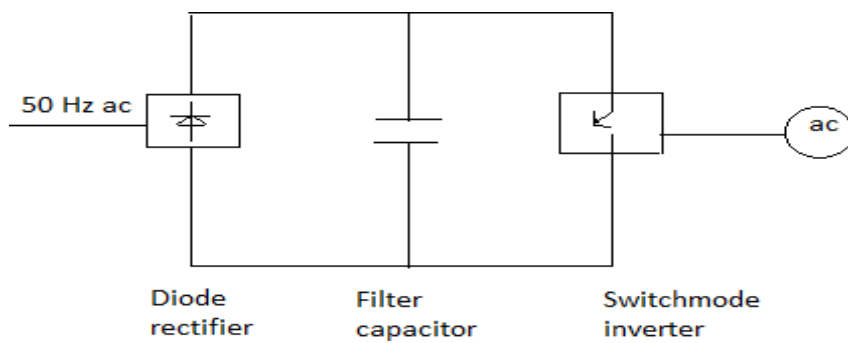

- The VSI can be further divided into general 3 categories:
1. Pulse width modulated inverters
 2. Square wave inverters
 3. Single phase inverter with voltage cancellation



Pulse width modulated inverters


The input dc voltage is of constant magnitude . The diode rectifier is used to rectify the line voltage. The inverter control the magnitude and frequency of the ac output voltage.

This is achieved by PWM technique of inverter switches and this is called PWM inverters.

The sinusoidal PWM technique is one of the PWM technique to shape the output voltage to as close as sinusoidal output.

Basic concepts of switch mode inverter

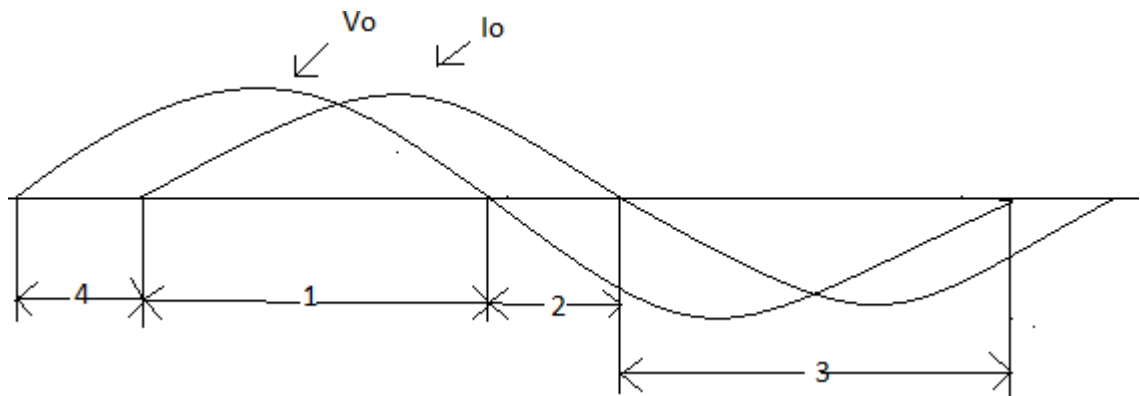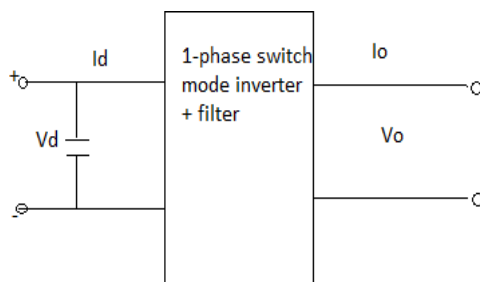

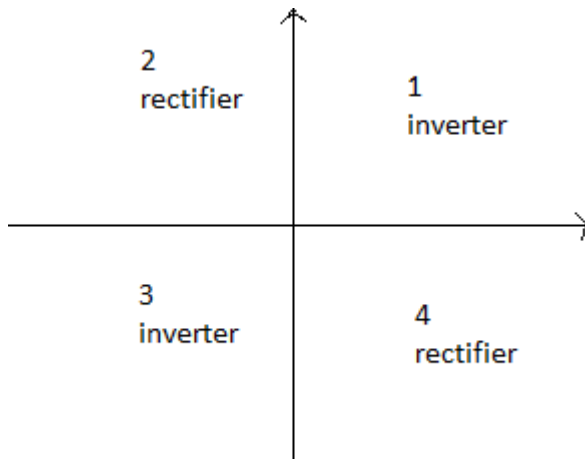

During interval 1 v_0 and i_0 both are positive During interval 3 v_0 and i_0 both are negative

Therefore during 1 and 3 the instantaneous power flow is from dc side to corresponding to inverter mode of operation.

In contrast during interval 2 and 4 v_0 and i_0 are of opposite sign i.e. power flows from ac side to dc side corresponding to rectifier mode of operation.

Pulse width modulated switching scheme

We require the inverter output to be sinusoidal with magnitude and frequency controllable.

In order to produce sinusoidal output voltage at desired frequency a sinusoidal control signal at desired frequency is compared with a triangular waveform as show.

The frequency of the triangular waveform established the inverter switching frequency.

The triangular waveform is called carrier waveform. The triangular waveform establishes switching frequency , which establishes with which the inverter switches are applied.

The control signal has frequency f_s and is used to modulate the switch duty ratio.

f_1 is the desired fundamental frequency of the output voltage.


The amplitude modulation ratio m_a is defined as


$$m_a = \frac{V_{control}}{V_{dc}}$$

$V_{control}$ is the peak amplitude of control signal.

V_{tri} peak amplitude of triangular signal. The frequency modulation ratio m_f

$$m_f = \frac{f_s}{f_1}$$

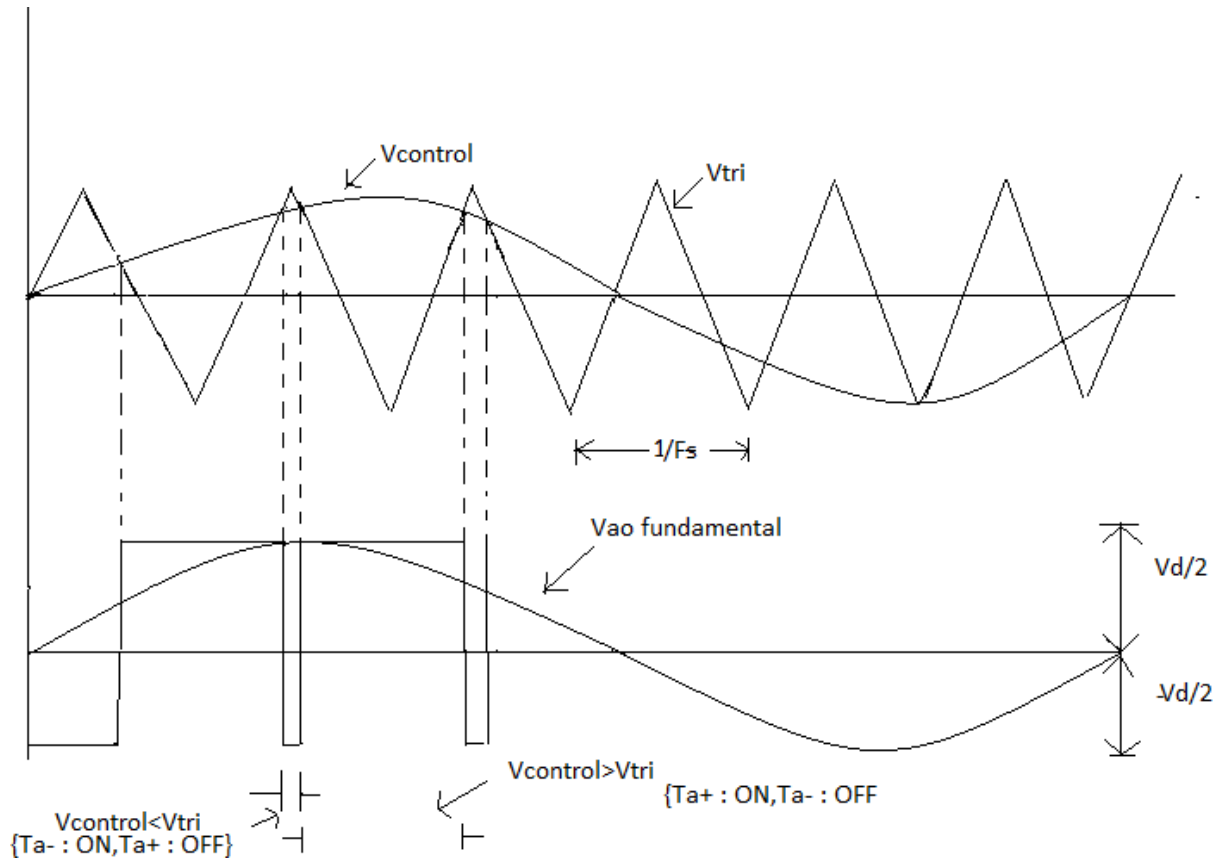

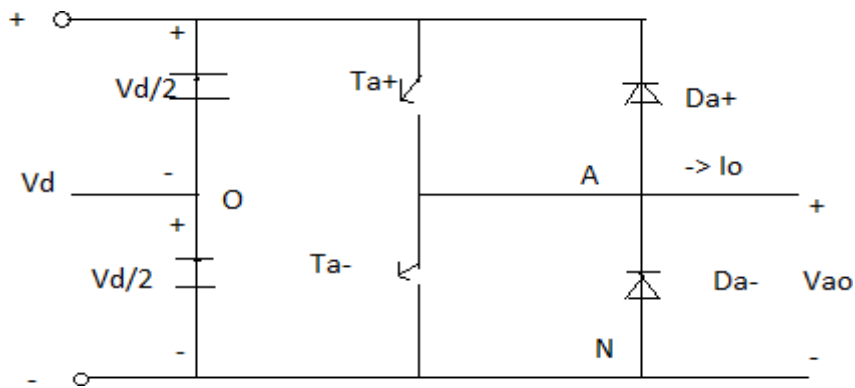

When $V_{control} > V_{tri}$ T^+ is ON $V_{AO} = \frac{1}{2} V_d$

$V_{control} < V_{tri}$ T^- is ON $V_{AO} = -\frac{1}{2} V_d$

So the following inferences can be drawn

The peak amplitude of fundamental frequency is $m_a \times \frac{1}{2} V_d$

$$V_{AO} = m_a \frac{V_d}{2}$$

$$\frac{V_{AO}}{V_{control}} = \frac{m_a}{2} \frac{V_d}{V_{tri}}$$


$$V_{control} \leq \hat{V}_{tri}$$

The foregoing arguments shown why $V_{control}$ is chosen to be sinusoidal to provide sinusoidal output voltage with fewer harmonics

Let the $V_{control}$ vary sinusoidal with frequency f_1 , which is the desired frequency of the inverter output voltage.

$$\text{Let } V_{control} = \hat{V}_{control} \sin \omega_1 t$$

$$\hat{V}_{control} \leq \hat{V}_{tri}$$

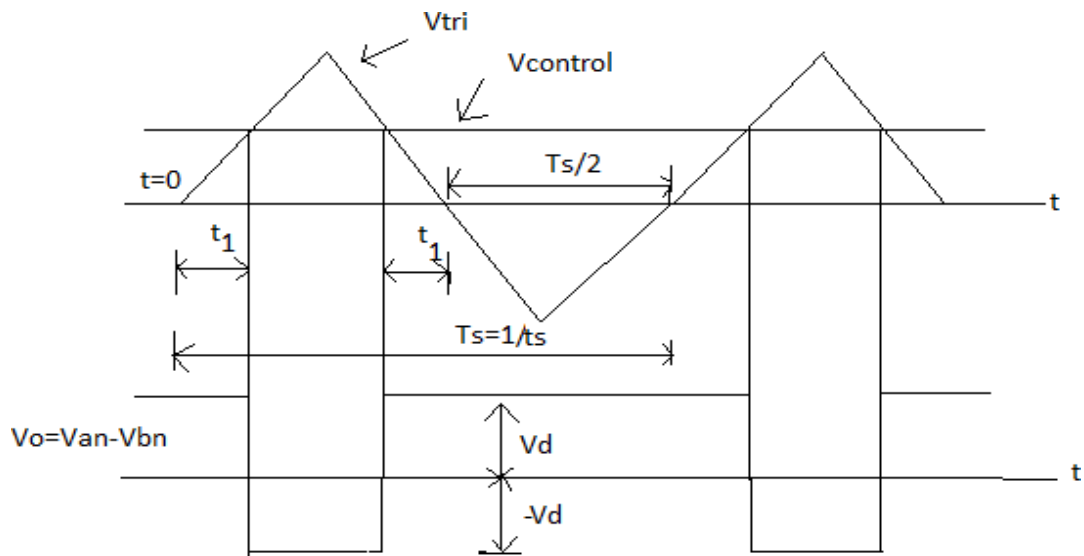

$$\frac{\hat{V}_{tri}}{t} \quad T_{s/4}$$

At $t=t_1$, $v_{tri}=v_{control}$

$$\text{So } \frac{v_{control}}{t} = \frac{\hat{V}_{tri}}{T_{s/4}}$$

$$t_1 = \frac{\hat{v}_{control} * T_s}{4}$$

$$T_{on} = 2t_1 + \frac{T_s}{2}$$

$$D = \frac{T_{on}}{T_s} = \frac{2t_1 + \frac{T_s}{2}}{T_s}$$

$$= \frac{2t_1}{T_s} + \frac{1}{2}$$

$$D = \frac{\hat{v}_{control}}{\hat{V}_{tri}} + \frac{1}{2}$$

Three phase inverter


When three single-phase inverters are connected in parallel a three phase inverter is formed.

The gating signal has to be displaced by 120° with respect to each other so as to achieve three phase balanced voltages.

A 3-phase output can be achieved from a configuration of six transistors and six diodes.

Two type of control signal can be applied to transistors, they are such as 180° or 120° conduction.

180-degree conduction

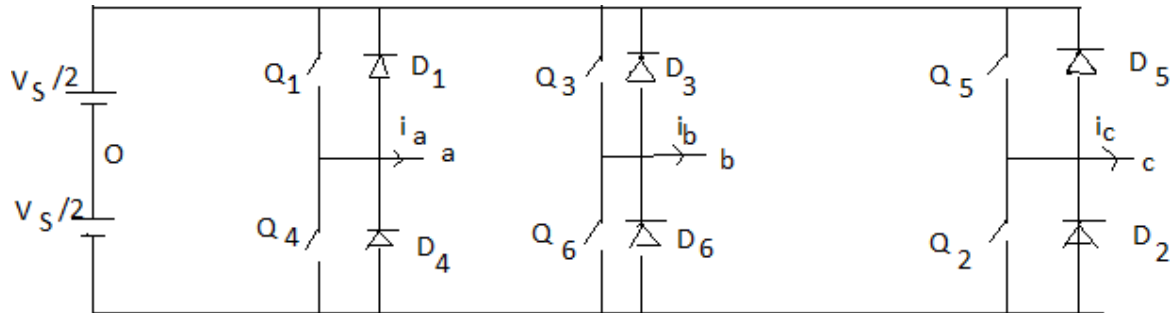

When Q_1 is switched on, terminal a is connected to the positive terminal of dc input voltage.


When Q_4 is switched on terminal a is brought to negative terminal of the dc source.

There are 6 modes of operation in a cycle and the duration of each mode is 60° .


The conduction sequence of transistors is 123,234,345,456,561,612. The gating signals are shifted from each other by 60° to get $3-\phi$ balanced voltages.

Switching states for the three phase voltage inverters

Step I

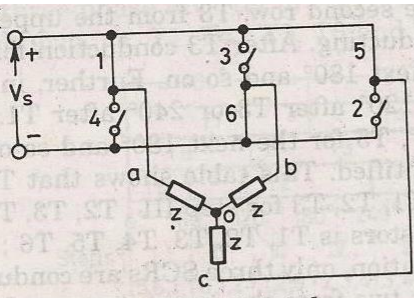


(a) $0-60^\circ$; 5, 6, 1 closed.

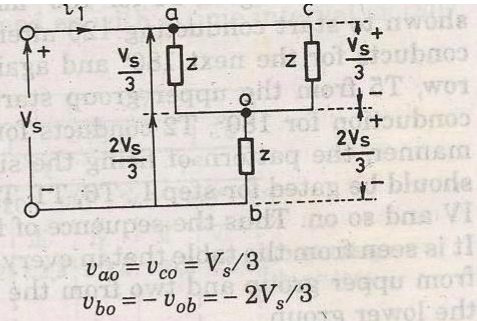


$$v_{ao} = v_{co} = V_s/3$$

$$v_{bo} = -v_{ob} = -2V_s/3$$

Step II

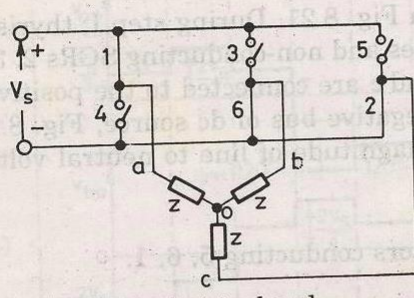


(b) $60-120^\circ$; 6, 1, 2 closed.

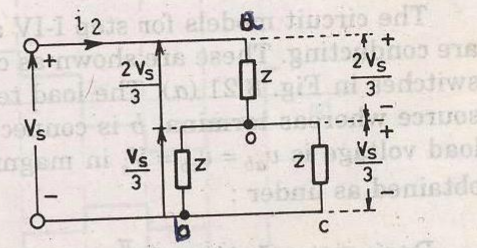


$$v_{ao} = V_s/3$$

$$v_{bo} = v_{co} = -V_s/3$$

Step III

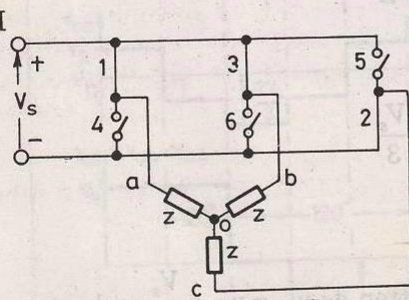


(c) $120-180^\circ$; 1, 2, 3 closed.

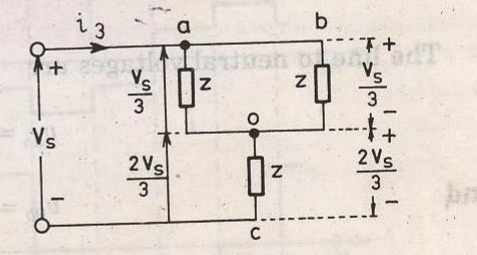


$$v_{ao} = v_{bo} = V_s/3$$

$$v_{co} = -2V_s/3$$

Step IV

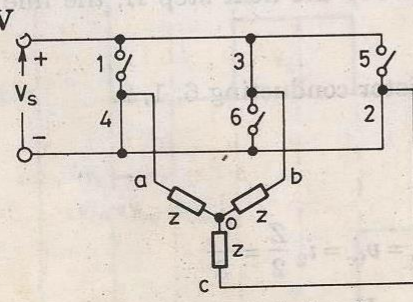


(d) $180-240^\circ$; 2, 3, 4 closed.

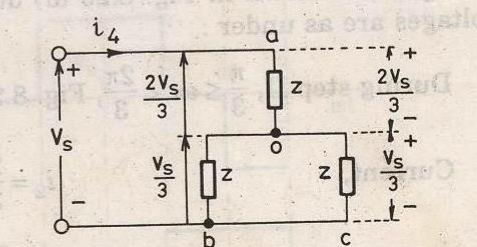


$$v_{bo} = 2V_s/3$$

$$v_{ao} = v_{co} = -V_s/3$$

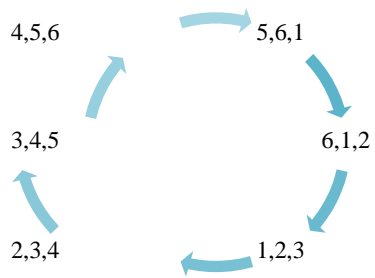

V R N	V Y N	V B N	V R Y	V Y B	V B R	V_1 <u> </u>
$\frac{V}{3}$	<u> </u> - 2 V 3	$\frac{V}{3}$	V a c	- V d c	0	$\frac{V}{2}$ (330 ^o) $\sqrt{3}$
2 $\frac{V}{3}$	<u> </u> $\frac{V}{3}$	<u> </u> $\frac{V}{3}$	V d c	0	- V d c	$\frac{V}{2}$ (30 ^o) $\sqrt{3}$
V 3	$\frac{V}{3}$	<u> </u> 2 $\frac{V}{3}$	0	V	- V	$\frac{V}{2}$ (90 ^o) $\sqrt{3}$
- V 3	2 $\frac{V}{3}$	<u> </u> $\frac{V}{3}$	- V	V	0	$\frac{V}{2}$ (150 ^o) $\sqrt{3}$
- 2 V 3	$\frac{V}{3}$	$\frac{V}{3}$	- V	0	0	$\frac{V}{2}$ (210 ^o) $\sqrt{3}$
- V <u> </u> -3	<u> </u> $\frac{V}{3}$	2 $\frac{V}{3}$	0	- V	0	$\frac{V}{2}$ (270 ^o) $\sqrt{3}$

Fourier analysis

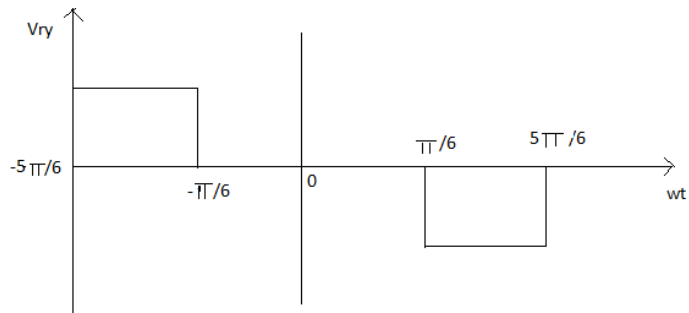

If we go for harmonic analysis $V_{RY} = \sum_{n=1,3,5,\dots}^{\infty} V_n \sin(n\omega t + \phi_n)$

$$\frac{4V}{\pi} \sin \frac{n\pi}{6} \sin(\omega t + \pi/6)$$

$n=1,3,5,\dots,n\pi$ 3

6

—
 —
 —
 —
 —

$$V_{YB} = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_s \sin \frac{n\pi}{3}}{n\pi} \sin(\omega t - \frac{n\pi}{3})$$

$$V_{BR} = \sum_{n=1,3,5,\dots}^{\infty} \frac{4V_s \sin \frac{n\pi}{3}}{n\pi} \sin(\omega t - \frac{n\pi}{6})$$

All even harmonics are zero all triple n harmonics are zero. The rms nth component of the line voltage is

$$= \frac{4V_s}{\sqrt{2n\pi}} \sin \frac{n\pi}{3} = \frac{4V_s}{\sqrt{2\pi}} \sin(60^\circ)$$


For n=1

$$= 0.7797V_s$$


Three phase 120° mode VSI

The circuit diagram is same as that for 180° mode of conduction.

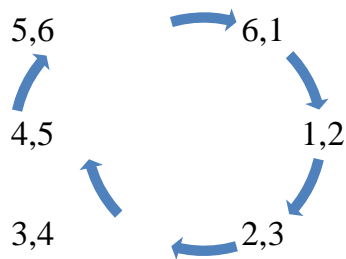
Here each thyristor conducts for 120°. There are 6 steps each of 60° duration, for completing one cycle of ac output voltage.



Step I

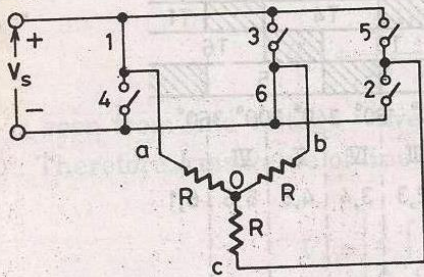


(a) $0-60^\circ$; 6, 1 closed

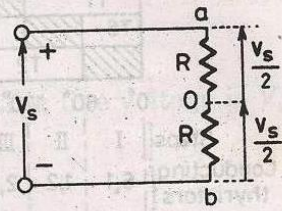


$$v_{ao} = V_s/2$$

$$v_{bo} = -V_s/2 \text{ and } v_{co} = 0$$

Step II

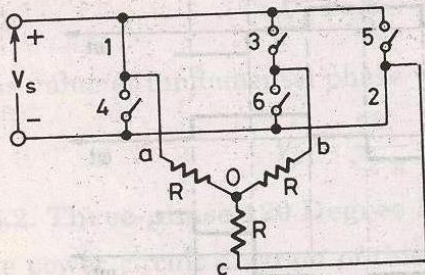


(b) $60-120^\circ$; 1, 2 closed

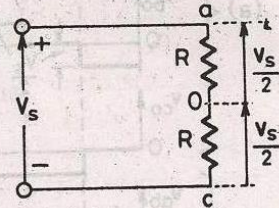


$$v_{ao} = V_s/2$$

$$v_{co} = -V_s/2 \text{ and } v_{bo} = 0$$

Step III

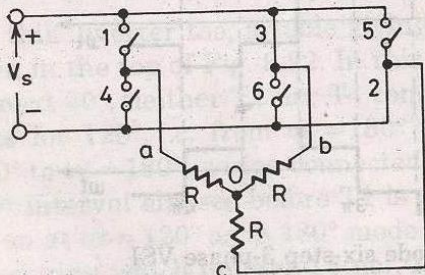


(c) $120-180^\circ$; 2, 3 closed

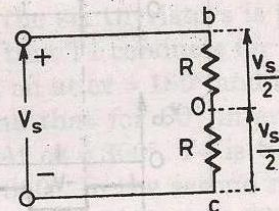


$$v_{bo} = V_s/2$$

$$v_{co} = -V_s/2 \text{ and } v_{ao} = 0$$

Step IV

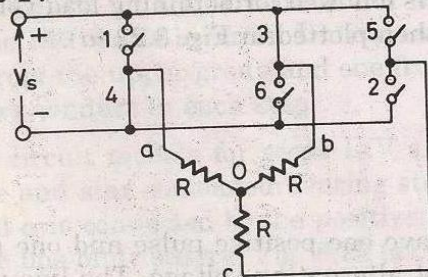

(d) $180-240^\circ$; 3, 4 closed

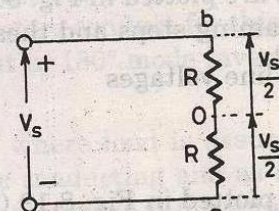

$$v_{bo} = V_s/2$$

$$v_{ao} = -V_s/2 \text{ and } v_{co} = 0$$

Step 1: 6,1 conducting

$$V_{an} = \frac{V_s}{2}, V_{bn} = -\frac{V_s}{2}, V_{cn} = 0$$

Step 2: 1,2 conducting

$$V_{an} = 0, V_{bn} = \frac{V_s}{2}, V_{cn} = -\frac{V_s}{2}$$

Step 3: 2,3 conducting

$$V_{an} = -\frac{V_s}{2}, V_{bn} = \frac{V_s}{2}, V_{cn} = 0$$

Step 4: 3,4 conducting

$$V_{an} = -\frac{V_s}{2}, V_{bn} = 0, V_{cn} = \frac{V_s}{2}$$

Step 5: 4,5 conducting

$$V_{an} = 0, V_{bn} = \frac{V_s}{2}, V_{cn} = -\frac{V_s}{2}$$

Step 6: 5,6 conducting

$$V_{an} = \frac{V_s}{2}, V_{bn} = -\frac{V_s}{2}, V_{cn} = 0$$

120° conduction mode

Step	Thyristor conducting	V_{Rn}	V_{Yn}	V_{Bn}	\vec{v}
1	6,1	$\frac{V_s}{2}$	$-\frac{V_s}{2}$	0	$\frac{\sqrt{3}V_s}{2} (-30^\circ)$
2	1,2	$\frac{V_s}{2}$	0	$-\frac{V_s}{2}$	$\frac{\sqrt{3}V_s}{2} (30^\circ)$
3	2,3	0	$\frac{V_s}{2}$	$-\frac{V_s}{2}$	$\frac{\sqrt{3}V_s}{2} (90^\circ)$
4	3,4	$-\frac{V_s}{2}$	$\frac{V_s}{2}$	0	$\frac{\sqrt{3}V_s}{2} (150^\circ)$
5	4,5	$-\frac{V_s}{2}$	0	$\frac{V_s}{2}$	$\frac{\sqrt{3}V_s}{2} (210^\circ)$
6	5,6	0	$-\frac{V_s}{2}$	$\frac{V_s}{2}$	$\frac{\sqrt{3}V_s}{2} (-30^\circ)$

